

# **Electromechanical devices MM2EMD**

## **Lecture 3 - Digital design and race times**

**Dr. Roderick MacKenzie**

**roderick.mackenzie@nottingham.ac.uk**

**Summer 2015**



**@rcimackenzie**

Released under  **creative  
commons**




- **Recap of last lecture**
- Using JK flip flops to run motors
- Digital design
  - What is digital design?
  - How to do it.
  - Where you might meet digital design
  - FPGAs
- Race times
 
# Recap: Understanding more complex digital circuits



- If we have a circuit comprising of multiple gates we can analyze it by first writing out the truth table containing all possible input combinations.
- With the output column left blank.




A	B	Q
0	0	
0	1	
1	0	
1	1	
 
# Recap: Understanding more complex digital circuits




- Then one line at a time, we propagate the values through the circuit.




A	B	Q
0	0	
0	1	
1	0	
1	1	
 
# Recap: Understanding more complex digital circuits



A	B	Q
0	0	
0	1	
1	0	
1	1	
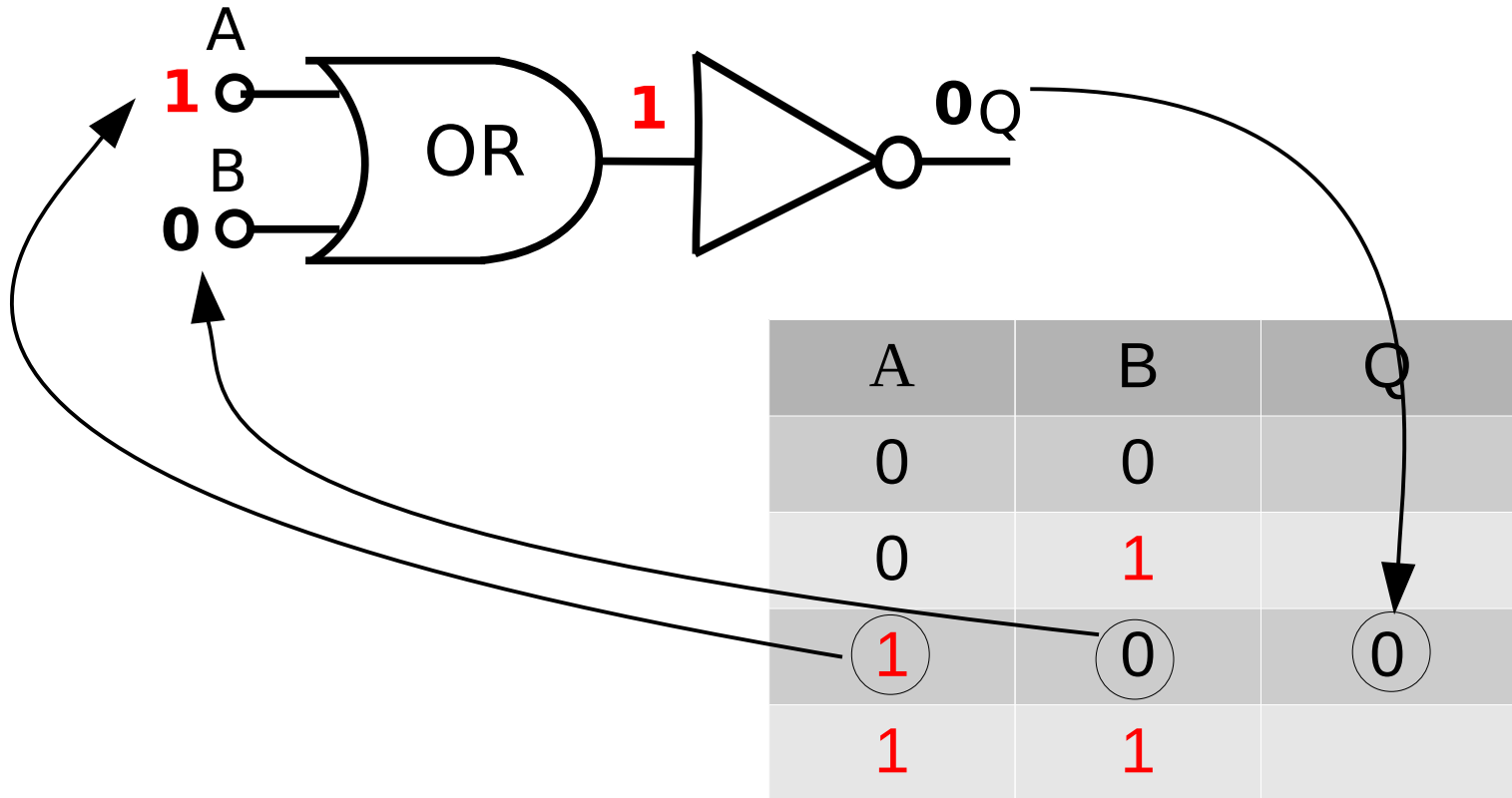
# Recap: Understanding more complex digital circuits




Then write the table in the output column.
 
# Recap: Understanding more complex digital circuits




If we do this with all inputs we can figure out what the circuit does




A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0
 
# Recap: We did this with the more complex XOR gate circuit:




A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

 




# Recap: Basic latches

 


- I introduced the principle of a latch.
- Latches are used to remember past electronic events.
- A latch always has some type of feed back element, here is an example....

## Recap: Basic latches

 


- If initially A, B and Q are zero

## Recap: Basic latches

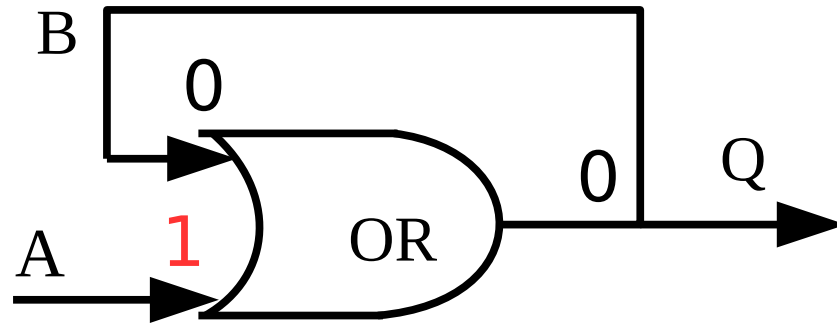


- If initially A, B and Q are zero
- Then you make input A=1

# Recap: Basic latches

 


- This will make the output=1

## Recap: Basic latches

 


- It will also make the input B, 1

## Recap: Basic latches

 

- Now if we again make input A 0
- No matter what we do to A the output will always remain 1 because of the feedback.
- The OR gate latch has remembered it was turned on due to the feedback - **it has latched.**

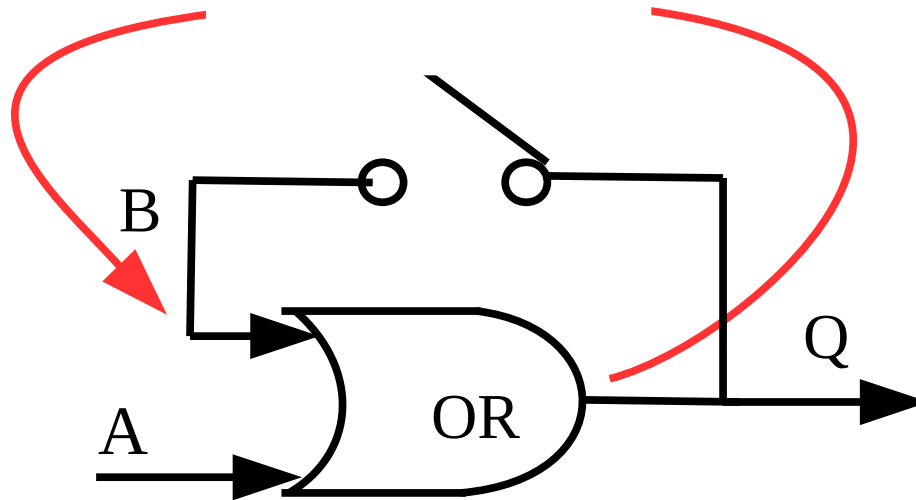- However the problem with a latch is that the only way to turn it off is by breaking the feedback loop.




- We found that JK flip-flops are a more flexible latch which don't have this problem.
 
# Recap: We use a circuit called a JK flip-flop – it looks like this:



- This is a real memory circuit that you would find in a computer. It can store a **1** or a **0**.




- It looks a bit complicated.



Dejđer / Digga - Flickr




# Recap: The JK flipflop

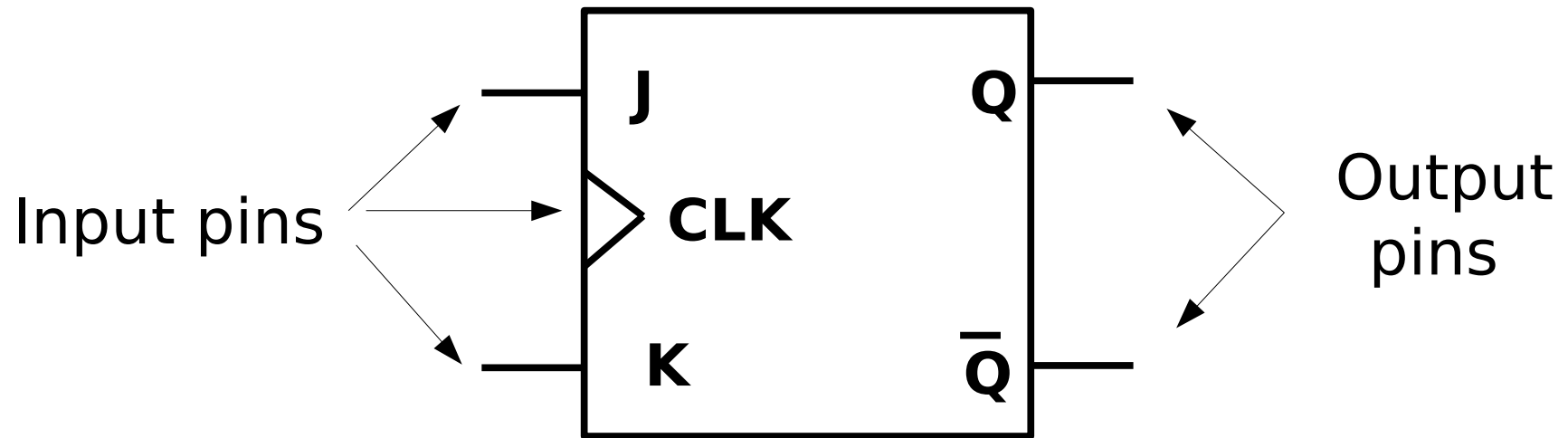

 
## Recap: The JK flipflop

The value the flip flop is currently remembering appears on pin Q and the inverse appears on pin  $\bar{Q}$ .




# Recap: The JK flip flop

 

- This is the most basic electronic memory element used to store 1's or 0's.
  - It is therefore important to remember what it does and how you would use it.
- You will meet this all the time as soon as you start working with electronic circuits. Used in **memory, counters, processors** etc...

 
## Recap: Storing a 1

- The basic idea is that you put what you want to remember on the J input - in this case a 1.



 
## Recap: Storing a 1

- At the same time you put the inverse of what you want to store on the K input:



 
# Recap: Storing a 1

- You then change the CLK (clock) pin from a 0 to a 1.



# Recap: Storing a 1

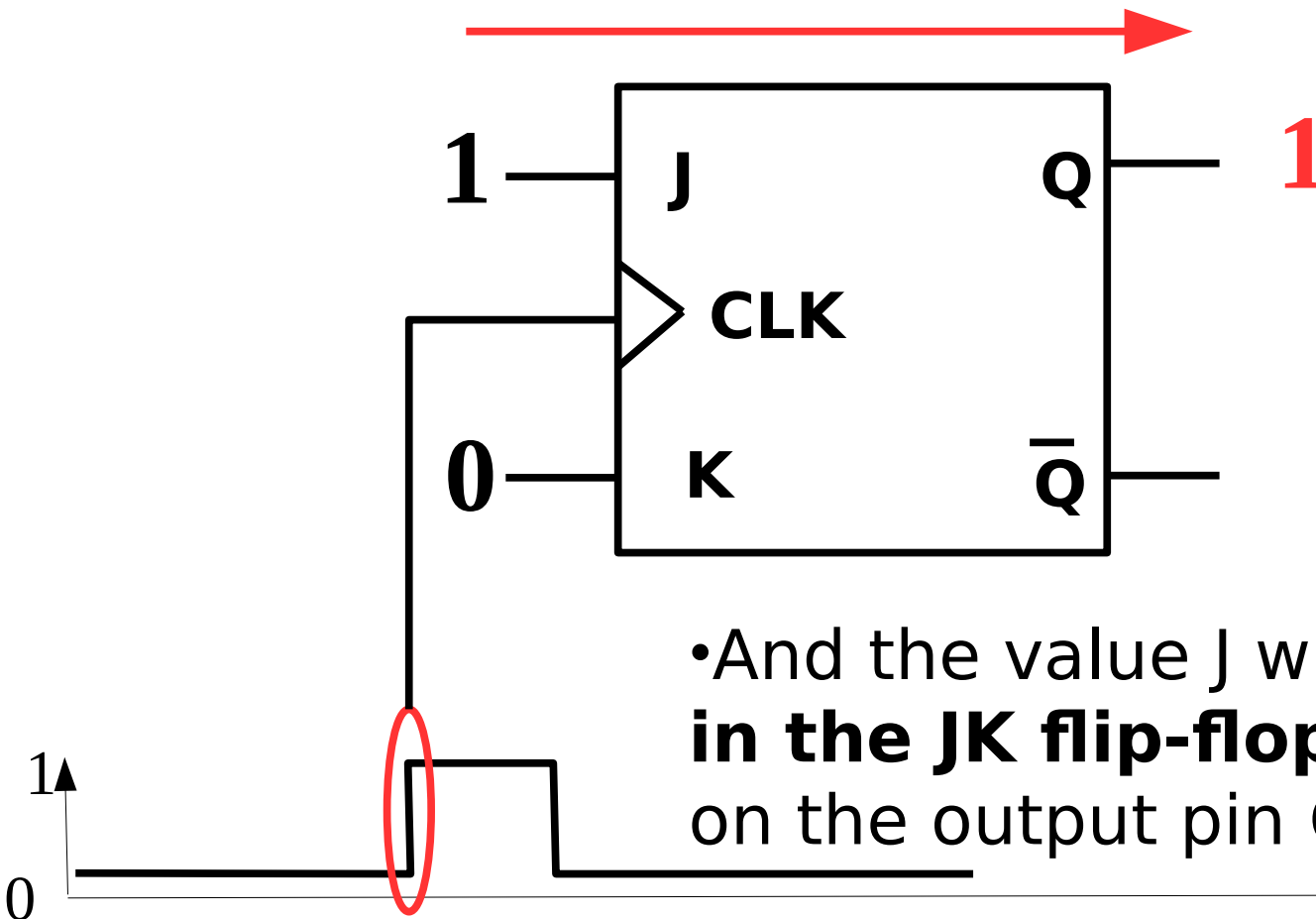


•And the value J will be **stored in the JK flip-flop** and appear on the output pin **Q**.

Recap: We need a clock pulse to remember things.




 - Then no matter what you do the **J** or **K** pins the **output will remain unchanged**







# Recap: Storing a zero

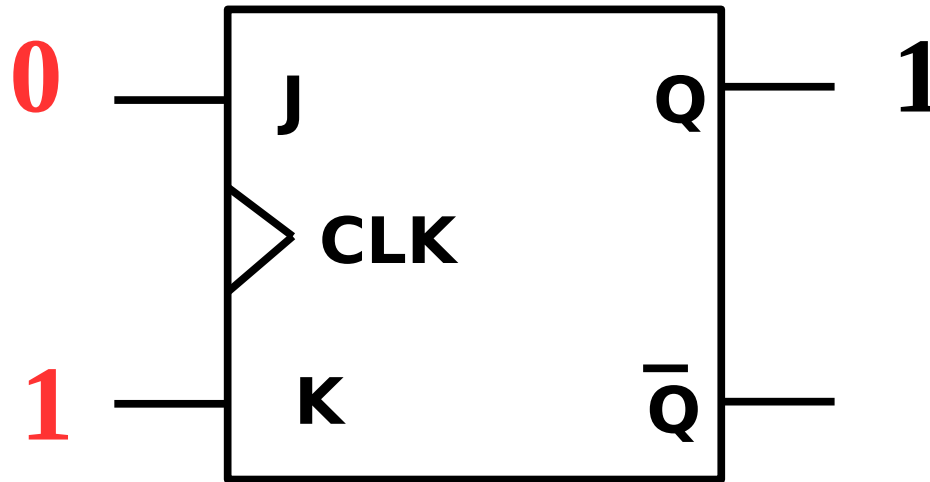

# Recap: Storing a zero

 


# Recap: Storing a zero

 


Recap: Nothing happens without a clock pulse.



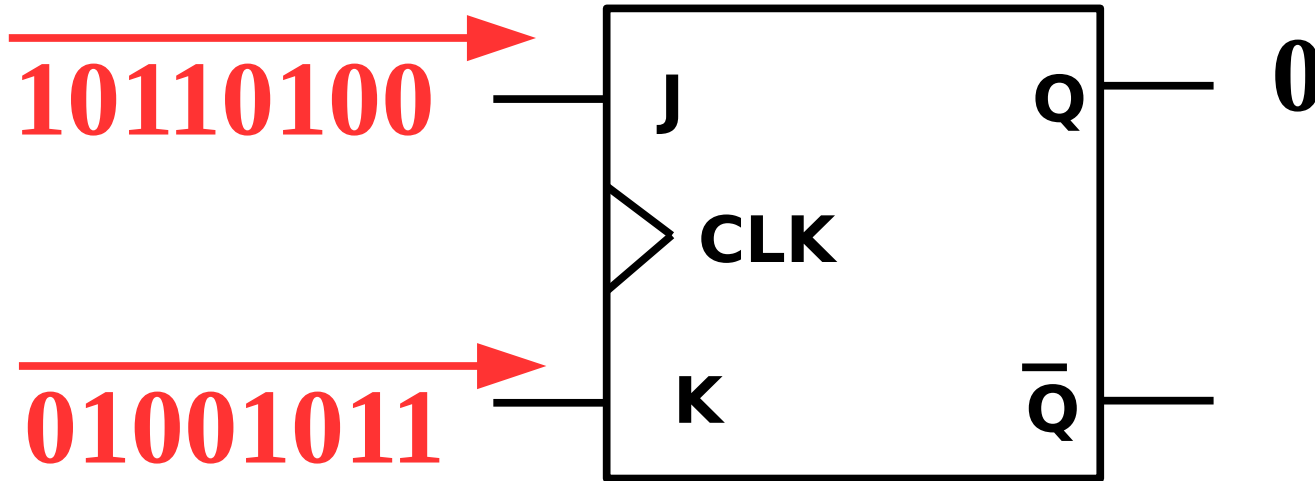- Then no matter what you do the **J** or **K** pins the **output will remain unchanged**



# Recap: The JK flipflop truth table

 


J	K	Q	Comment
0	0	Q	No change
1	0	1	Set Q to 1
0	1	0	Set Q to 0
1	1	flip	Flip

# Summary of today's lecture




- Recap of last lecture
- Using JK flip flops to run motors**
- Digital design
  - What is digital design?
  - How to do it.
  - Where you might meet digital design
  - FPGAs
- Race times

# Switch reluctance (SR) motor

 


- An SR motor is a motor which has an iron bar at it's center.
- You can move the bar by turning on and off the field in the different electromagnets.
- It's like the stepper motor Arthur has been teaching you about but a bit more simple

# Green electromagnet on

 





# Blue electromagnet on

 


# Red electromagnet on

 


# Green electromagnet on

 


# Blue electromagnet on

 


# Red electromagnet on

 

# Green electromagnet on

 


# Blue electromagnet on

 

- By switching on and off the magnetic field you can move the motor.


- Good, but what has this got to do with digital electronics?

# Serial to parallel converter

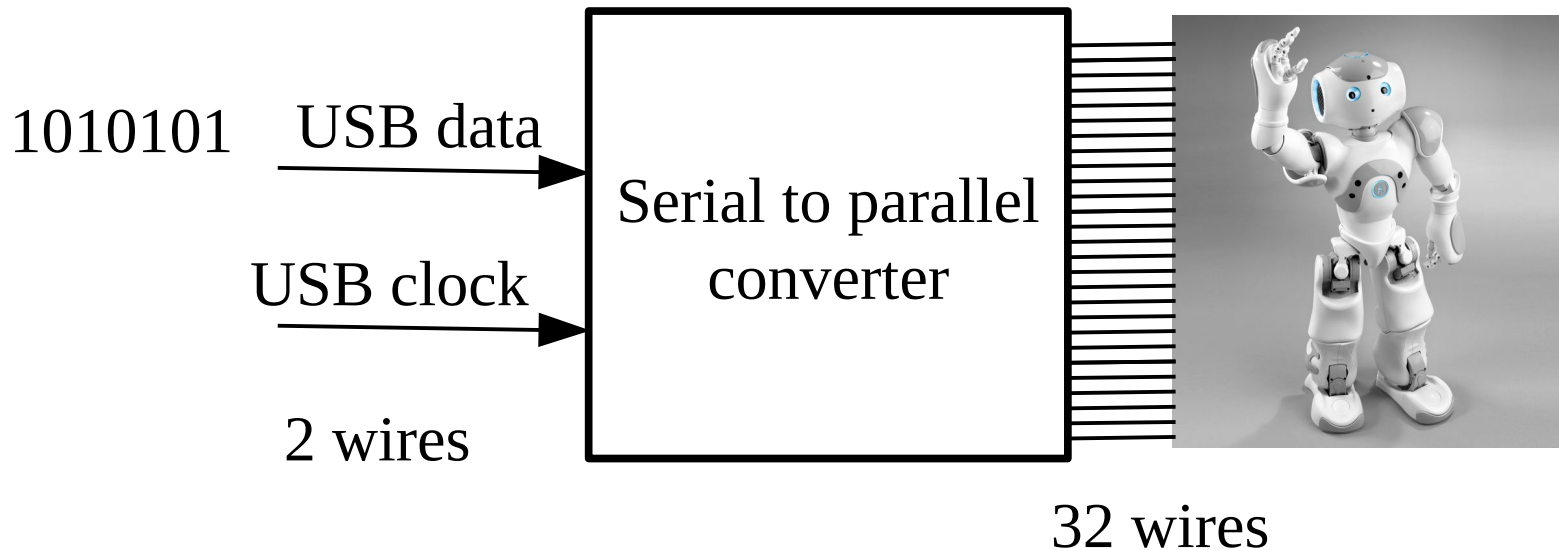





# Serial to parallel converter

 


# Serial to parallel converter

 


# Serial to parallel converter

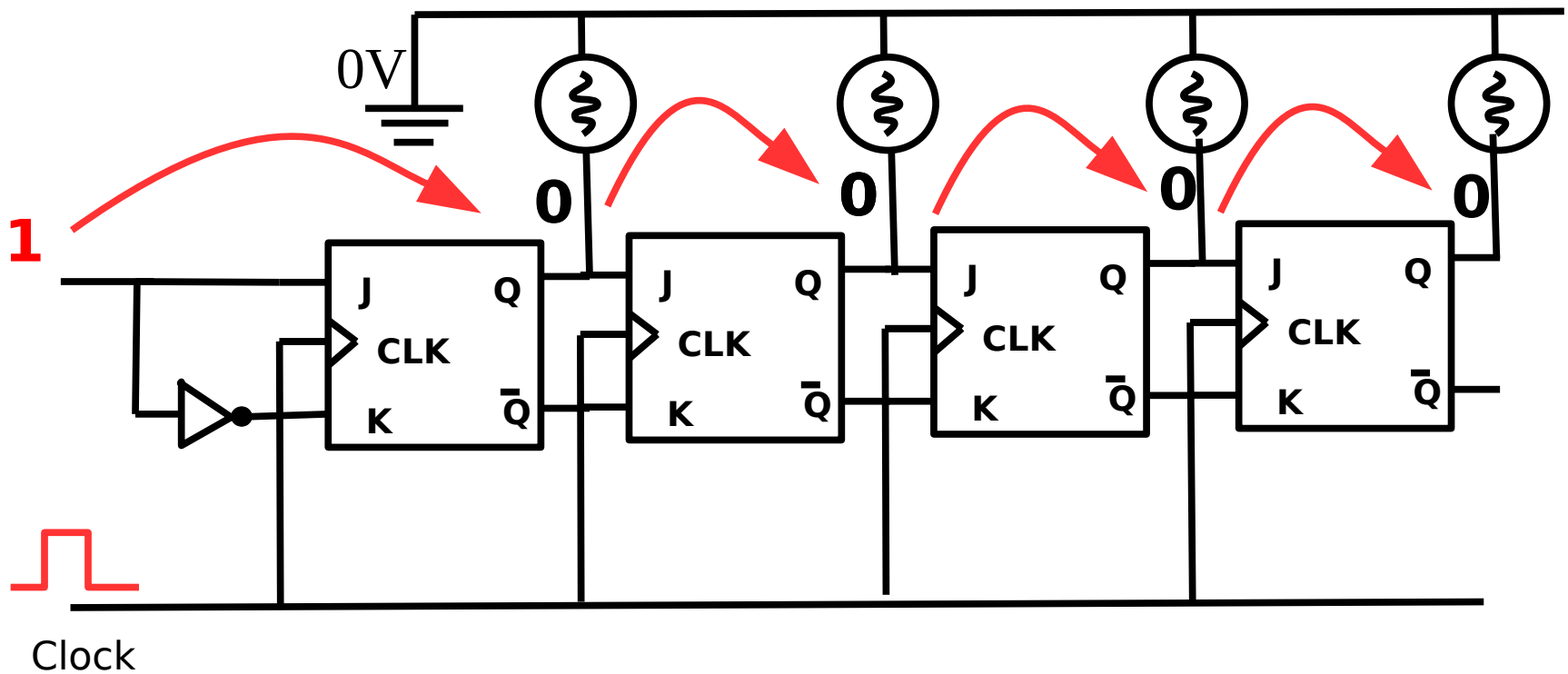


# Serial to parallel converter

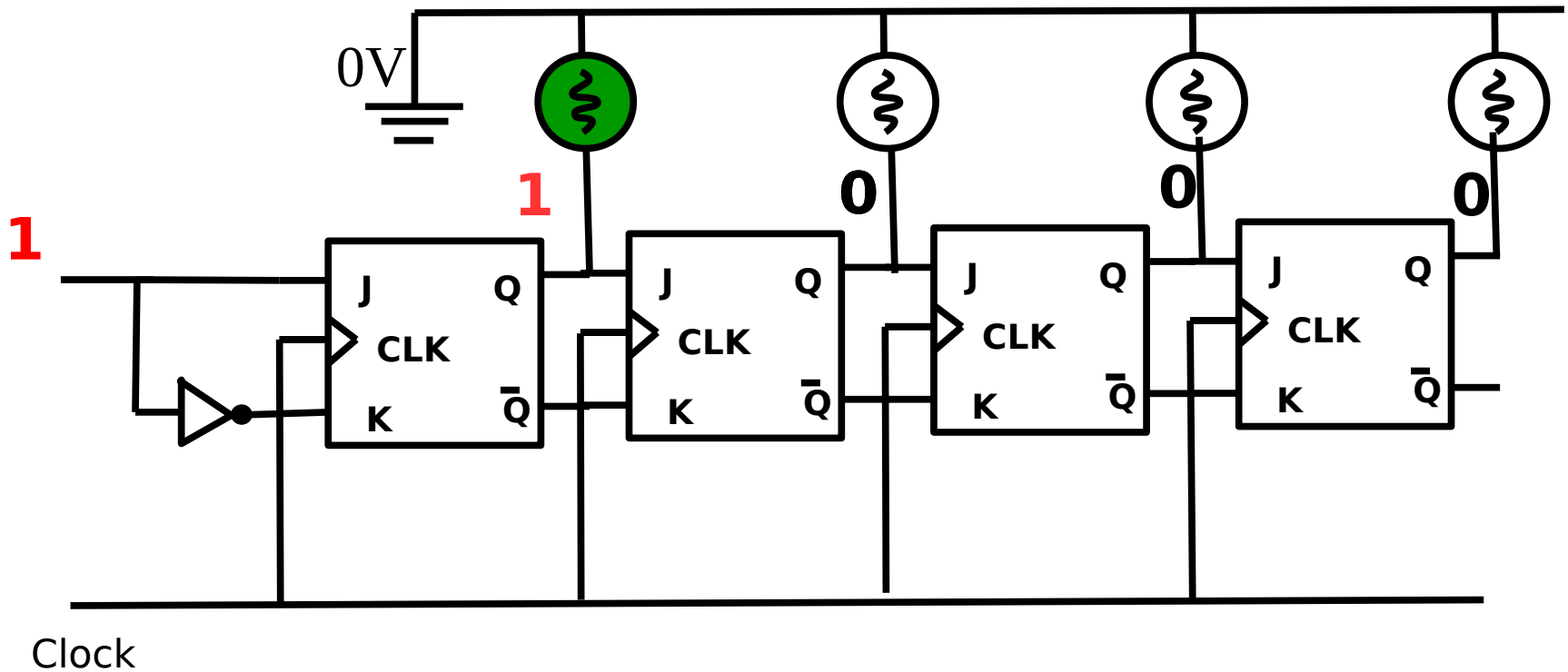


# Serial to parallel converter

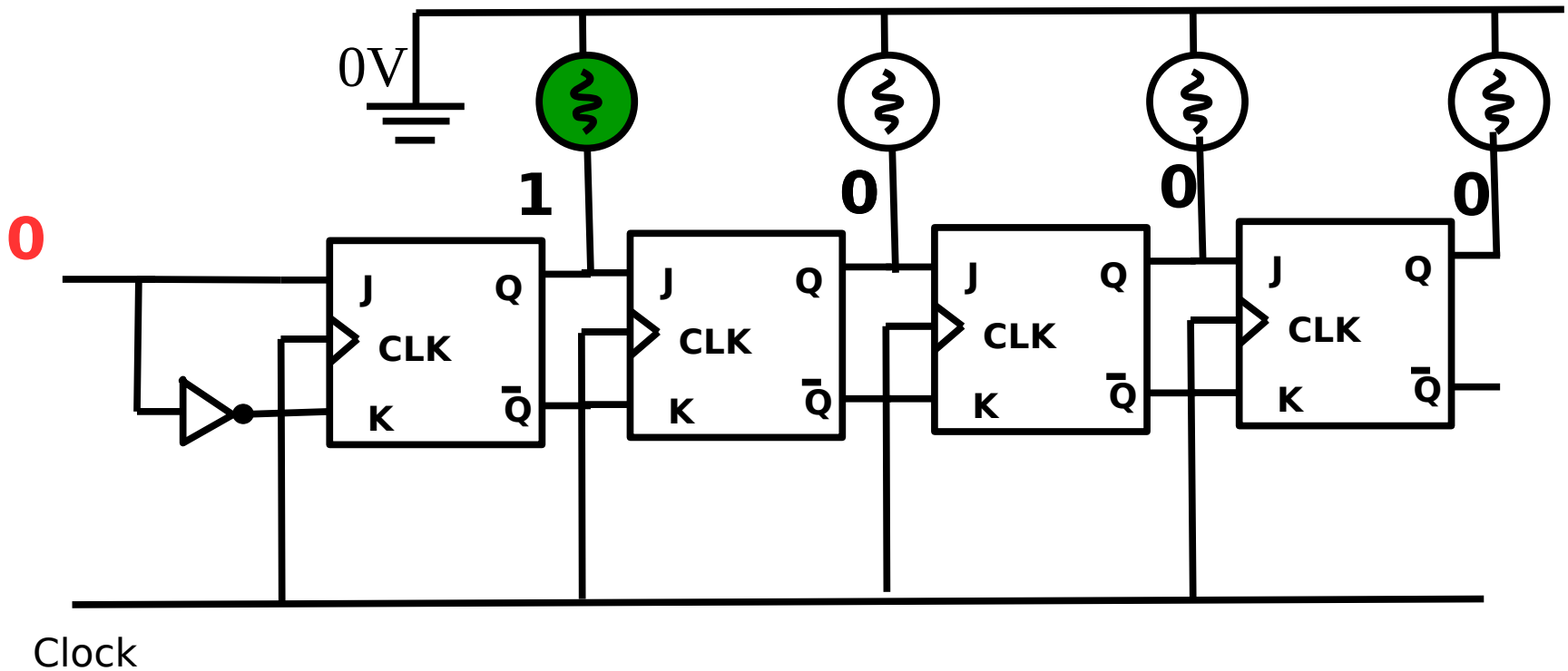


# Serial to parallel converter

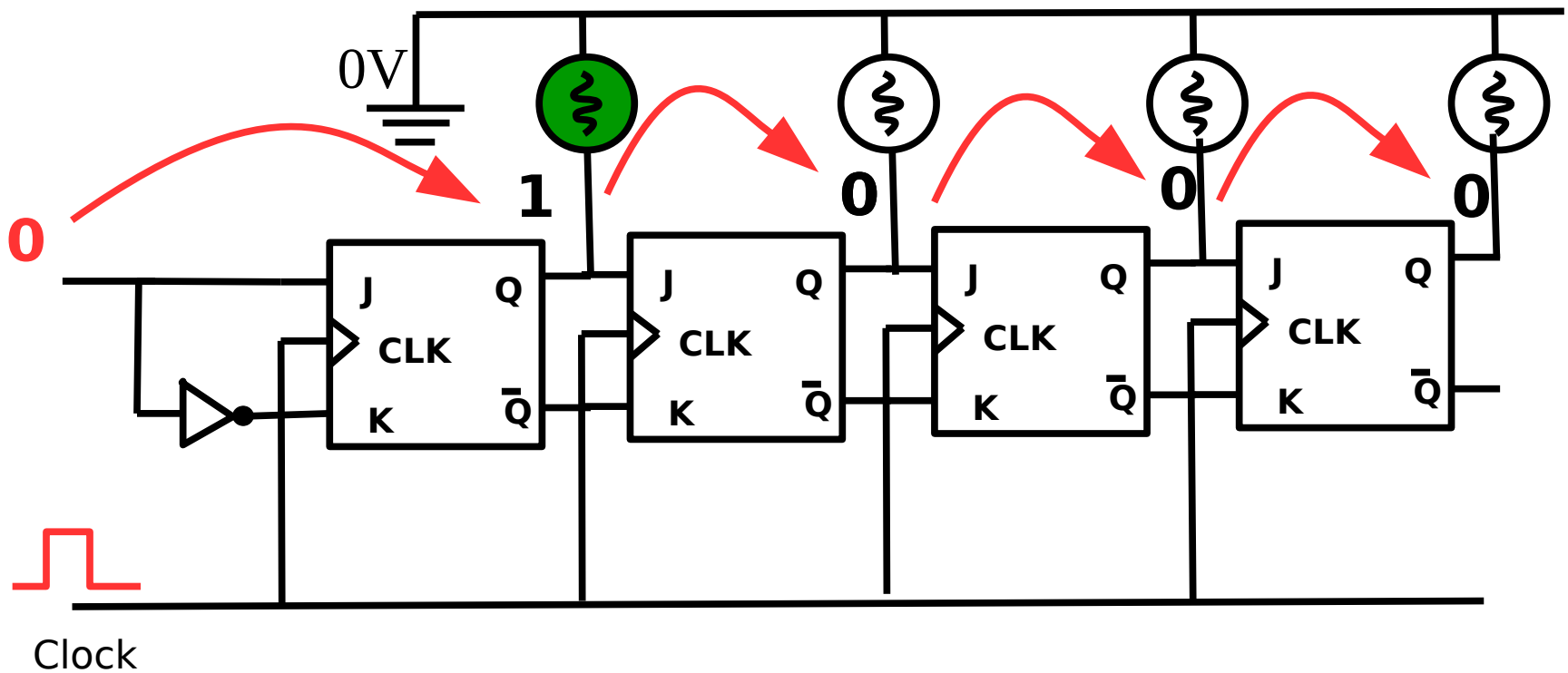

# Serial to parallel converter

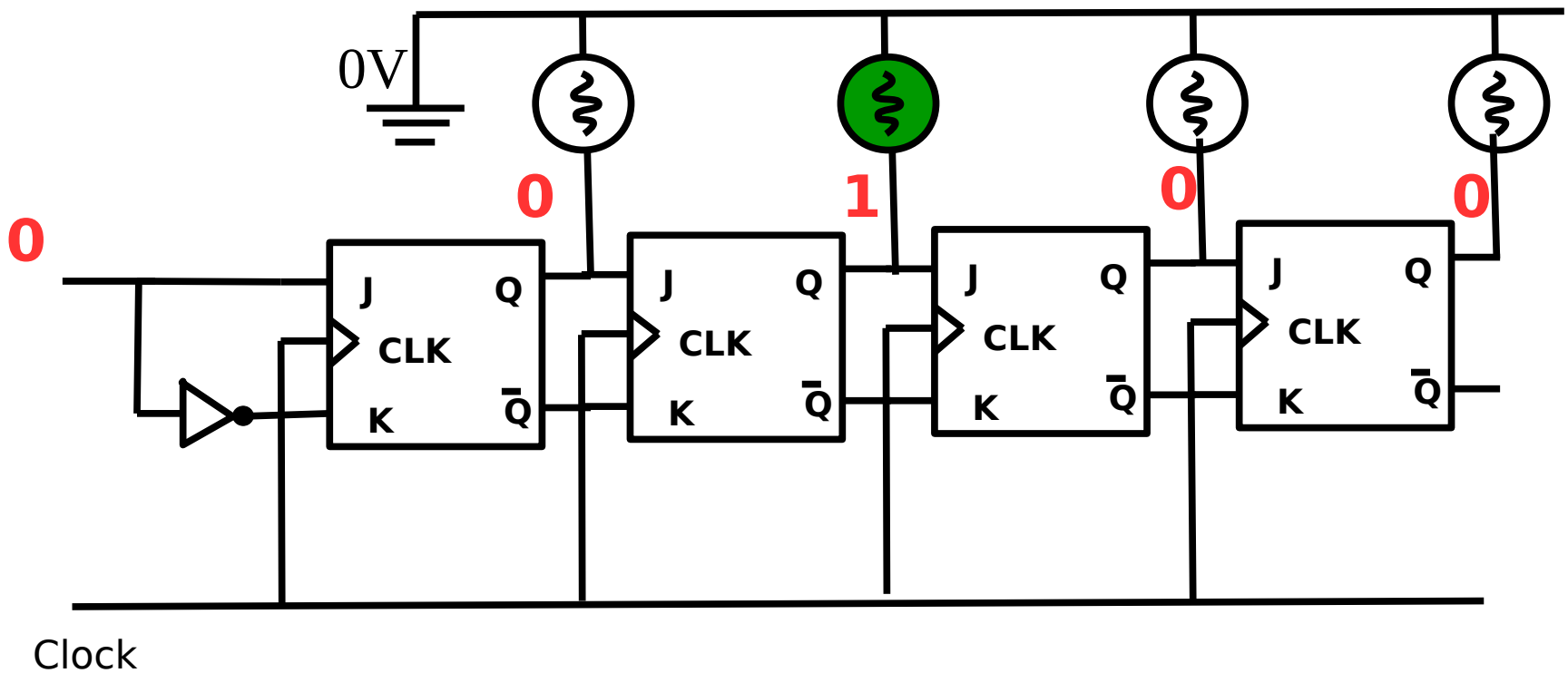


# Serial to parallel converter

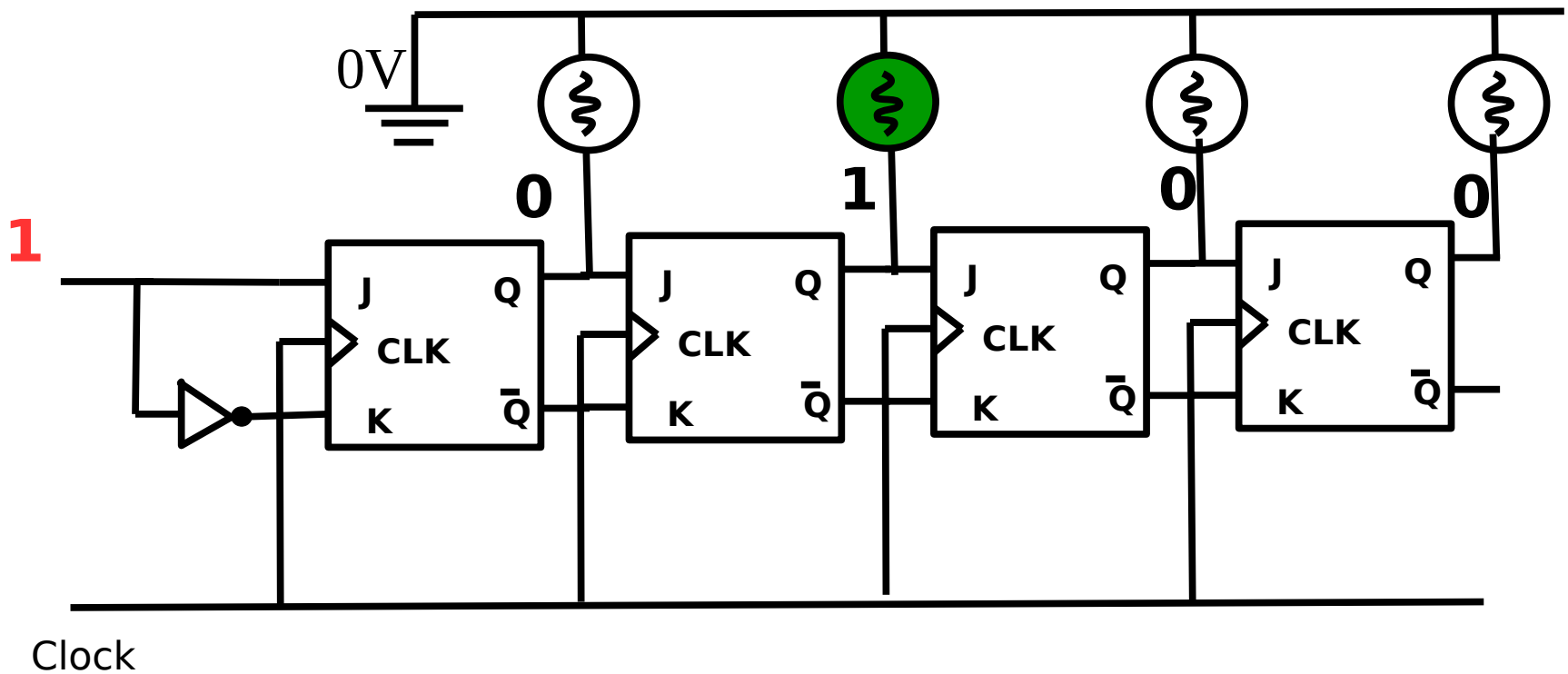





# Serial to parallel converter

 


# Serial to parallel converter

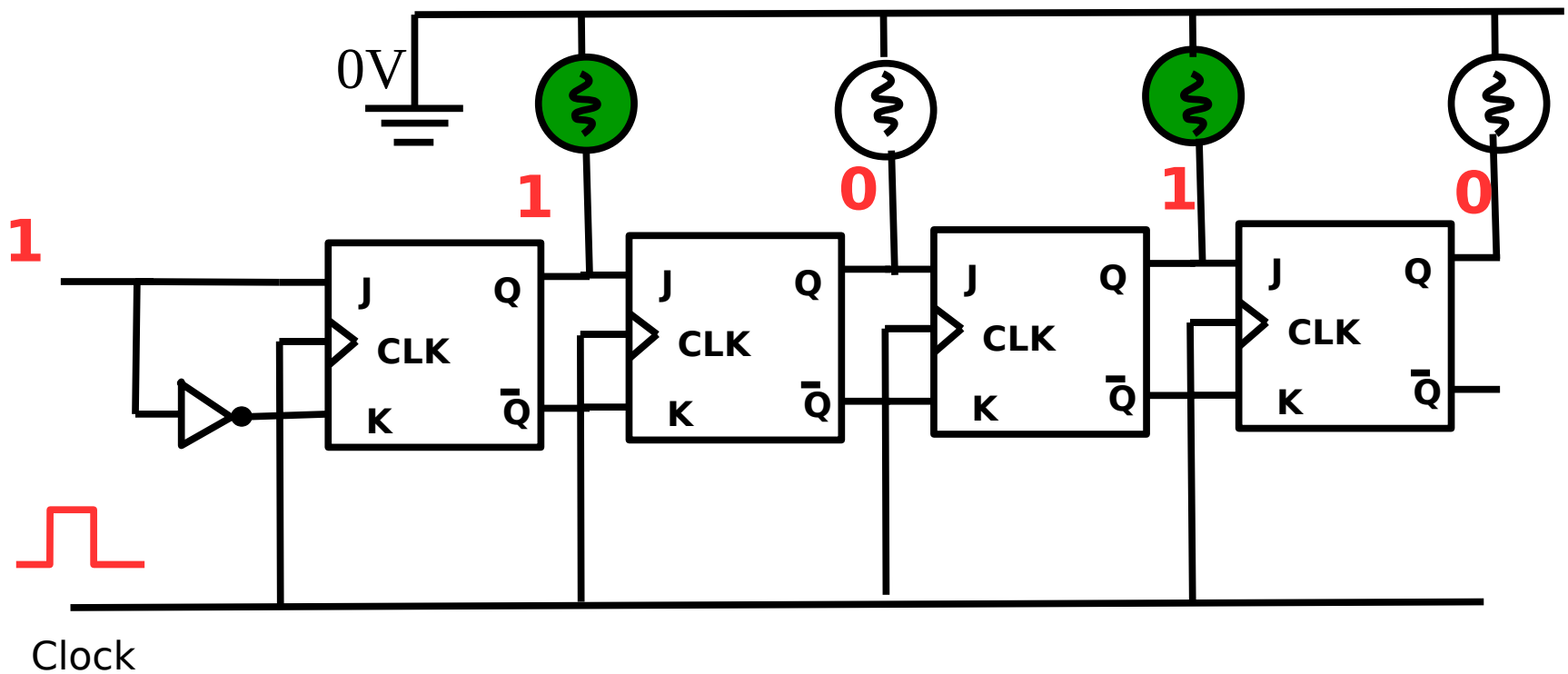


# Serial to parallel converter

 



# Serial to parallel converter

 

# Serial to parallel converter

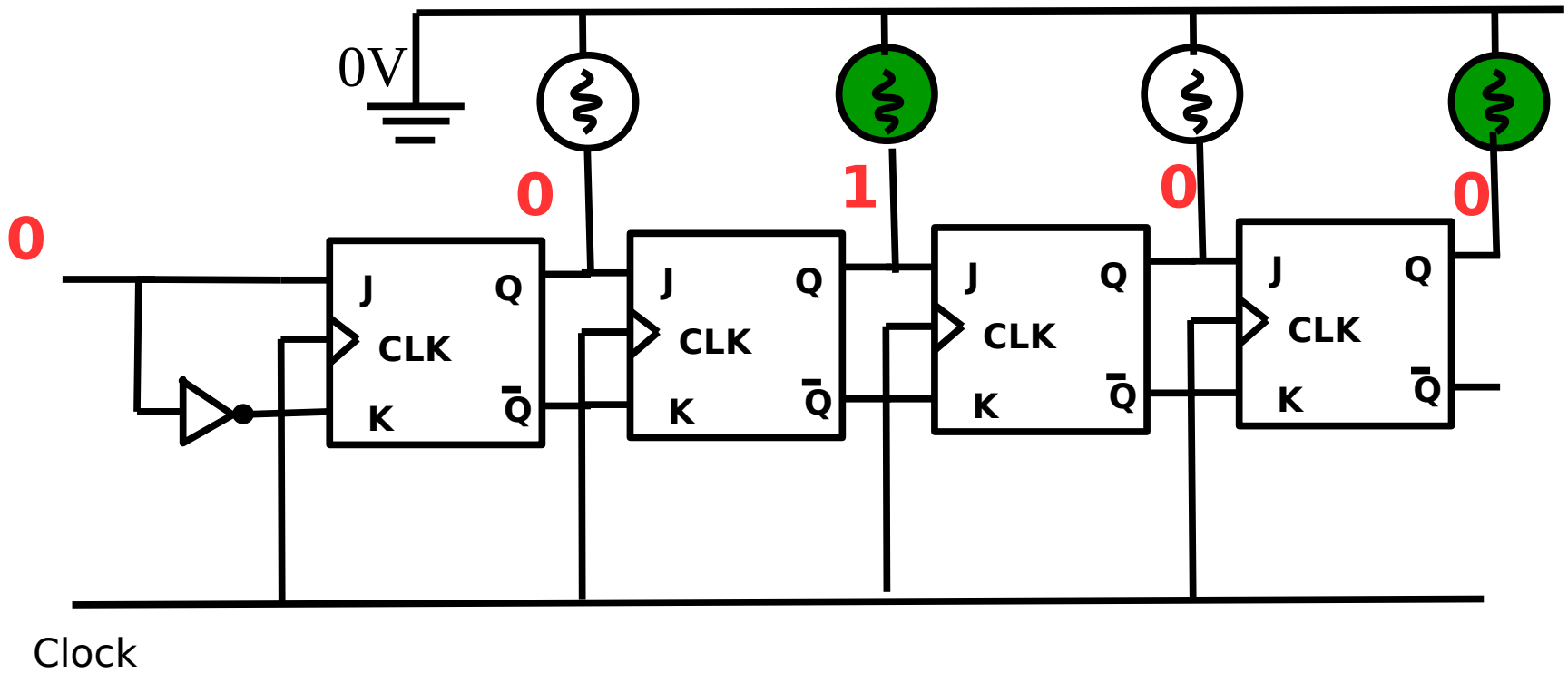

 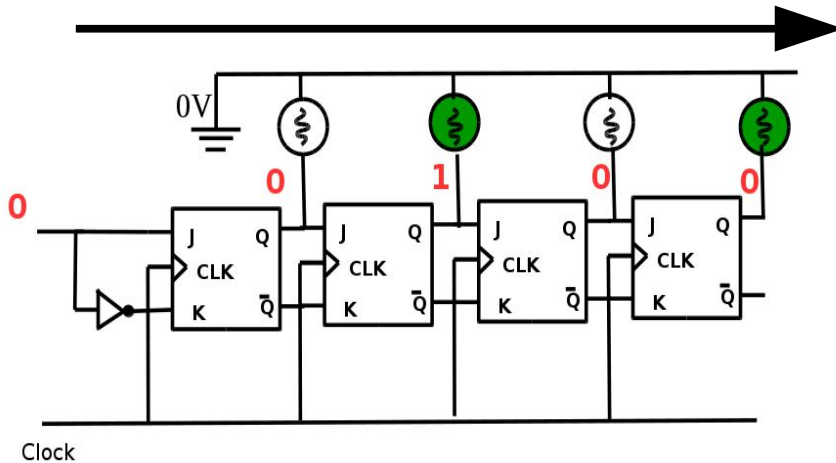
# Are there any similarities between the motor and the serial to parallel converter?



We can actually convert the serial to parallel converter circuit to a motor driver circuit.

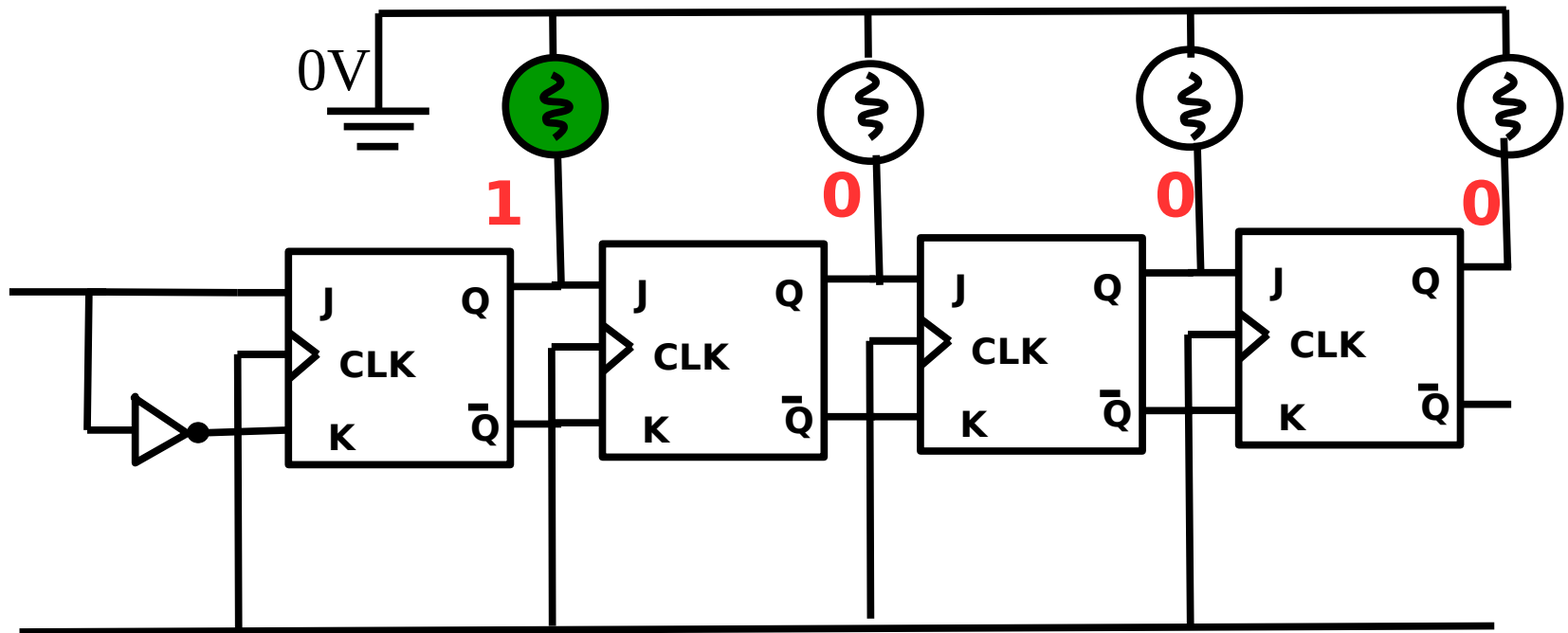
# Let's modify it

- Firstly let's only switch on one JK flipflop



- And get rid of one flipflop


# Let's get rid of one flipflop

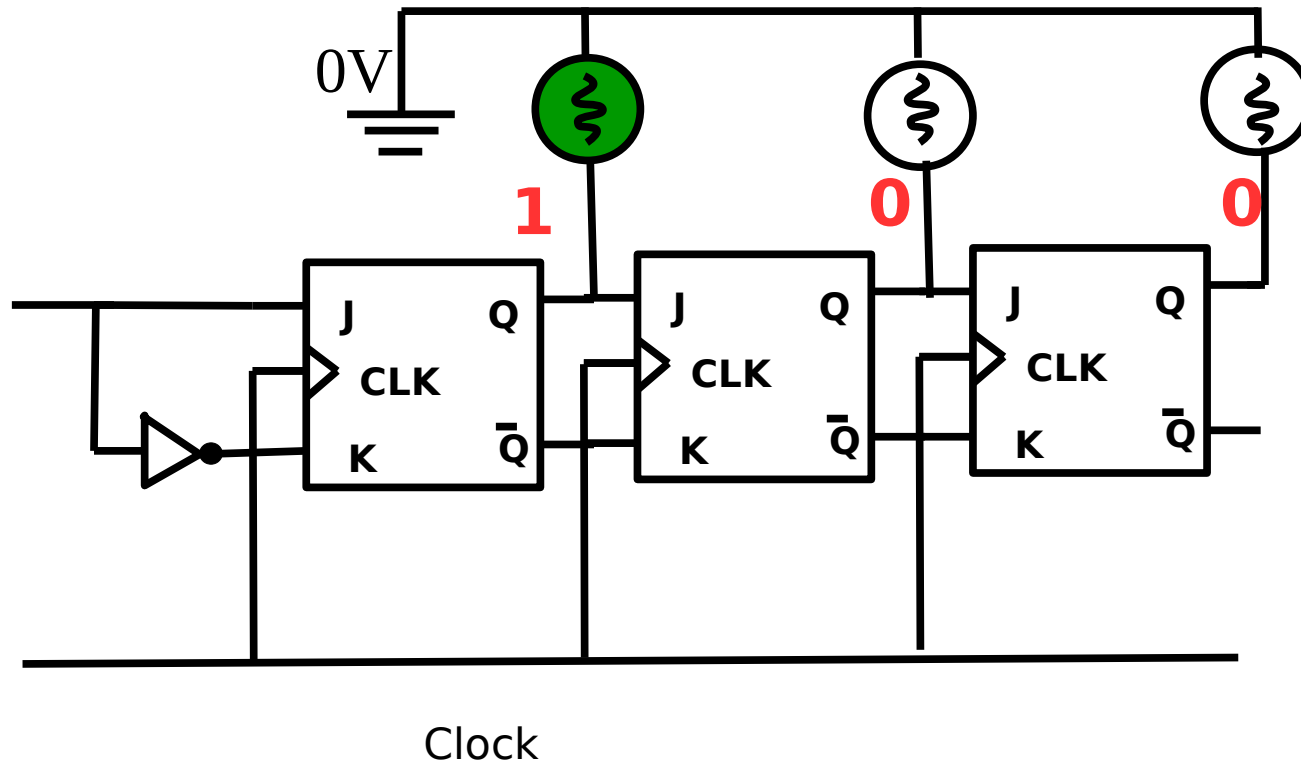

- Let's connect the input to the output.....





Now let's join the input to the output


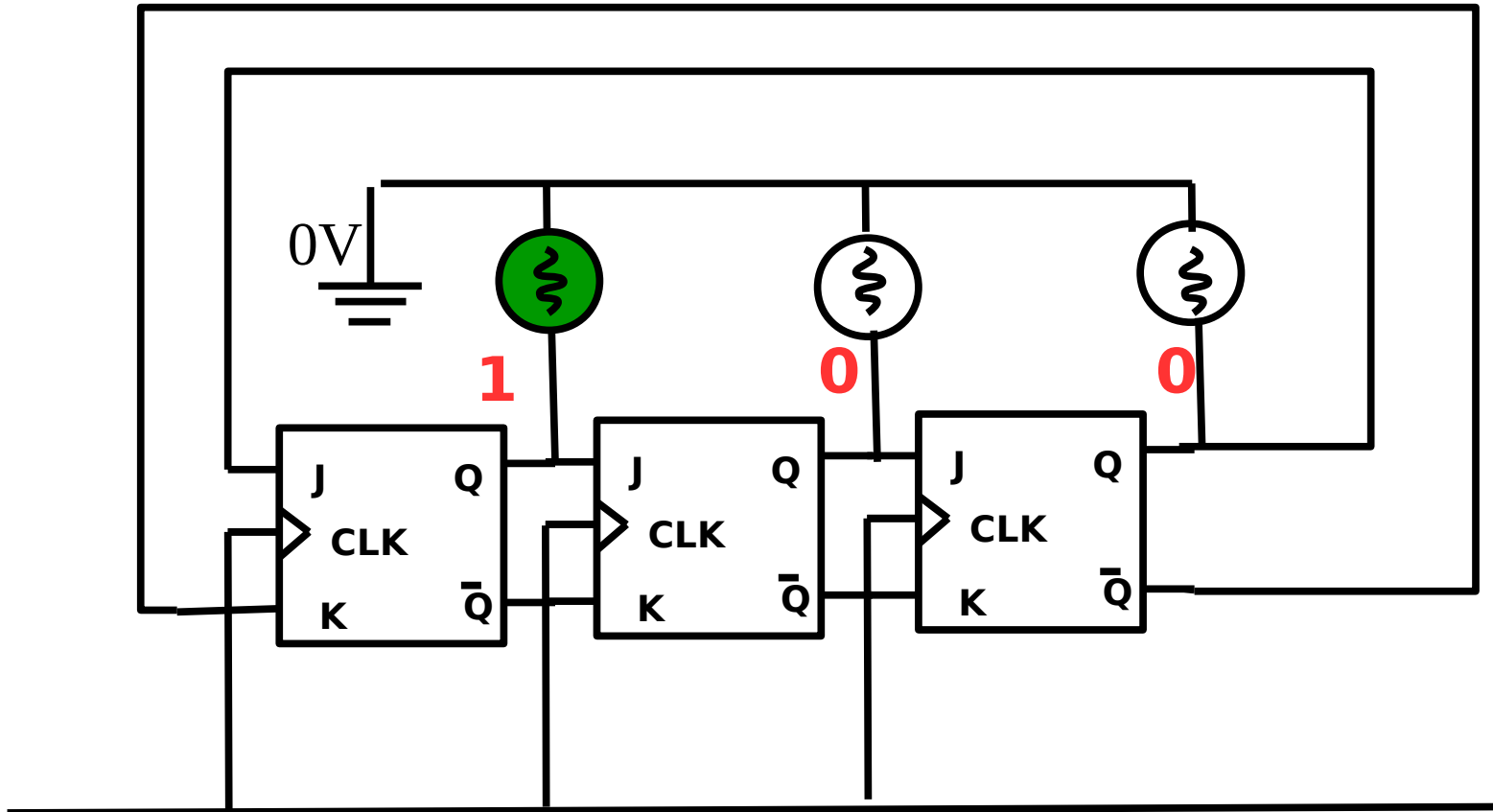


- And replace the bulbs with the coils of the motor....

  Replace the bulbs with the coils of the motor.





And apply a clock pulse...

 
 




Now let's join the input to the output

 
 


# Now let's join the input to the output

  

- Now apply another clock pulse.



# Now let's join the input to the output

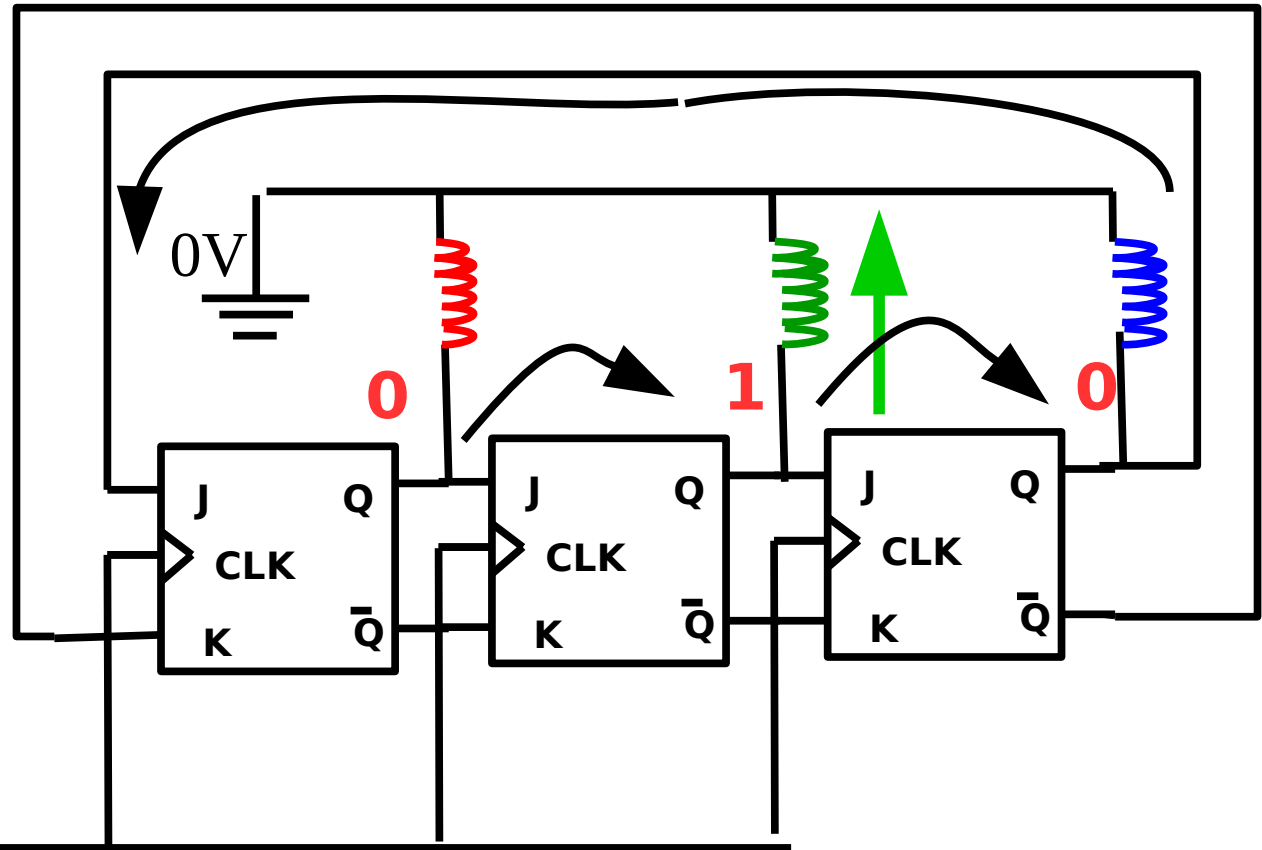 



Clock

- Now apply another clock pulse.

# Now let's join the input to the output

  

# Now let's join the input to the output

 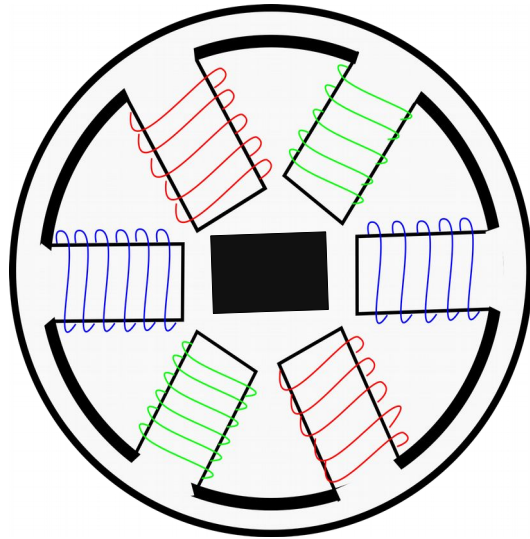



Clock

- Now apply another clock pulse.







# Now let's join the input to the output

 
 




# Now let's join the input to the output

  

# Now let's join the input to the output

  

- Now apply another clock pulse.



# Outline of the lecture

- Recap of last lecture
- Using JK flip flops to run motors
- Digital design**
  - What is digital design?
  - How to do it.
  - Where you might meet digital design
  - FPGAs
- Race times



# What is digital design?

- In the first couple of lectures we learnt about:
  - AND gates
  - OR gates
  - NOT gates
  - XOR gates
- We also made some simple circuits involving AND gates and OR gates.
- However there are often times when you need to design much more complex circuits as an engineer.


# Examples of slightly complex digital circuits



- Imagine you were designing a circuit to monitor a digital thermometer embedded in a nuclear reactor.



Atomic Energy of Canada Limited

 


Rama

 
# Examples of slightly complex digital circuits



- You wanted to automatically shut off the reactor when the cooling fluid (water) got higher than 50 degrees.



Rama

 

Argonne National Laboratory

# Examples of slightly complex digital circuits



- They did not have one of these circuits in Chernobyl...
- Quite a useful type of circuit to learn about(!)





 
# Examples of slightly complex digital circuits



- Your digital thermometer gives it's output using a three digit binary number.




$O_1$	$O_2$	$O_3$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

# Examples of slightly complex digital circuits



- In normal numbers that is.....

 


$O_1$	$O_2$	$O_3$	Number
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7
 
# Examples of slightly complex digital circuits



- Each number corresponds to a 10 degree step in temperature...




$O_1$	$O_2$	$O_3$	Number	Temperature
0	0	0	0	0
0	0	1	1	10
0	1	0	2	20
0	1	1	3	30
1	0	0	4	40
1	0	1	5	50
1	1	0	6	60
1	1	1	7	70

- We want to design a circuit that shuts off the reactor if the temperature is above 50 degrees.
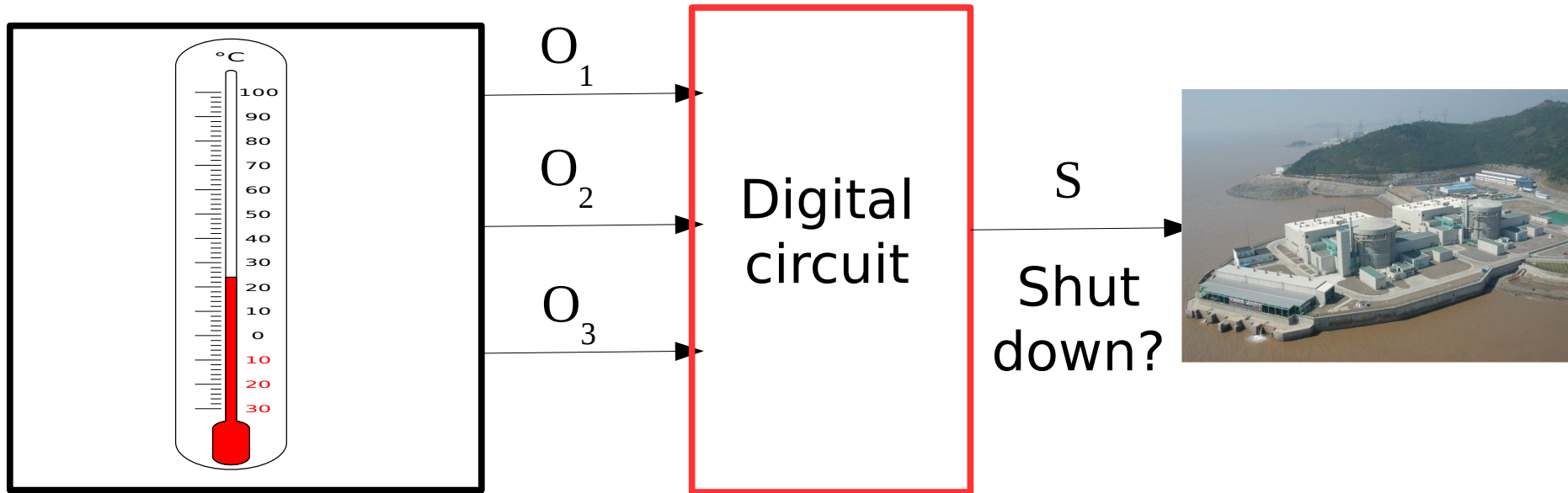
# Examples of slightly complex digital circuits



- We want to design a circuit that shuts off the reactor if the temperature is above 50 degrees.



If  $S=1$  the reactor will shutdown and if  $S=0$  the reactor will continue working.

# Draw a truth table for the circuit we want to design



$O_1$	$O_2$	$O_3$	Number	Temperature	S
0	0	0	0	0	0
0	0	1	1	10	0
0	1	0	2	20	0
0	1	1	3	30	0
1	0	0	4	40	0
1	0	1	5	50	0
1	1	0	6	60	1
1	1	1	7	70	1

- Remember
  - S=0 means stay on
  - S=1 shutdown

# Truth table




$O_1$	$O_2$	$O_3$	Number	Temperature	S
0	0	0	0	0	0
0	0	1	1	10	0
0	1	0	2	20	0
0	1	1	3	30	0
1	0	0	4	40	0
1	0	1	5	50	0
1	1	0	6	60	1
1	1	1	7	70	1

- We need to construct two logic circuits that give a 1 when the inputs are 110 and 111.
- Let's look at the 111 case first because it's easy
 
# Let's draw a logic table

- We want a circuit that will produce a 1 when all inputs are 1

- Let's just use an AND gate with three inputs.



$O_1$	$O_2$	$O_3$	$S$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

# Now let's make a circuit for the 60 degree case



$O_1$	$O_2$	$O_3$	Number	Temperature	S
0	0	0	0	0	0
0	0	1	1	10	0
0	1	0	2	20	0
0	1	1	3	30	0
1	0	0	4	40	0
1	0	1	5	50	0
1	1	0	6	60	1
1	1	1	7	70	1


- We want a circuit that will produce a 1 when all inputs are 1 except  $O_3$ .


 
# Let's draw a logic table

• We want a circuit that will produce a 1 when all inputs are 1 except  $O_3$ .

• Let's just make an and gate with input  $O_3$  inverted.



$O_1$	$O_2$	$O_3$	$S$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

# One more example



• Presumably it would also be bad if our coolant froze so let's make a circuit to shut down the reactor if the temperature is freezing

$O_1$	$O_2$	$O_3$	Number	Temperature	S
0	0	0	0	0	1
0	0	1	1	10	0
0	1	0	2	20	0
0	1	1	3	30	0
1	0	0	4	40	0
1	0	1	5	50	0
1	1	0	6	60	1
1	1	1	7	70	1


Ian Mackenzie


 
## Let's draw a logic table

- So now we want our circuit to produce a 1 when  $O_1$ ,  $O_2$  and  $O_3$  are all set to 0.


So let's just invert all the inputs.  
So the AND gate only turns on  
when all inputs are 0.



$O_1$	$O_2$	$O_3$	$S$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0


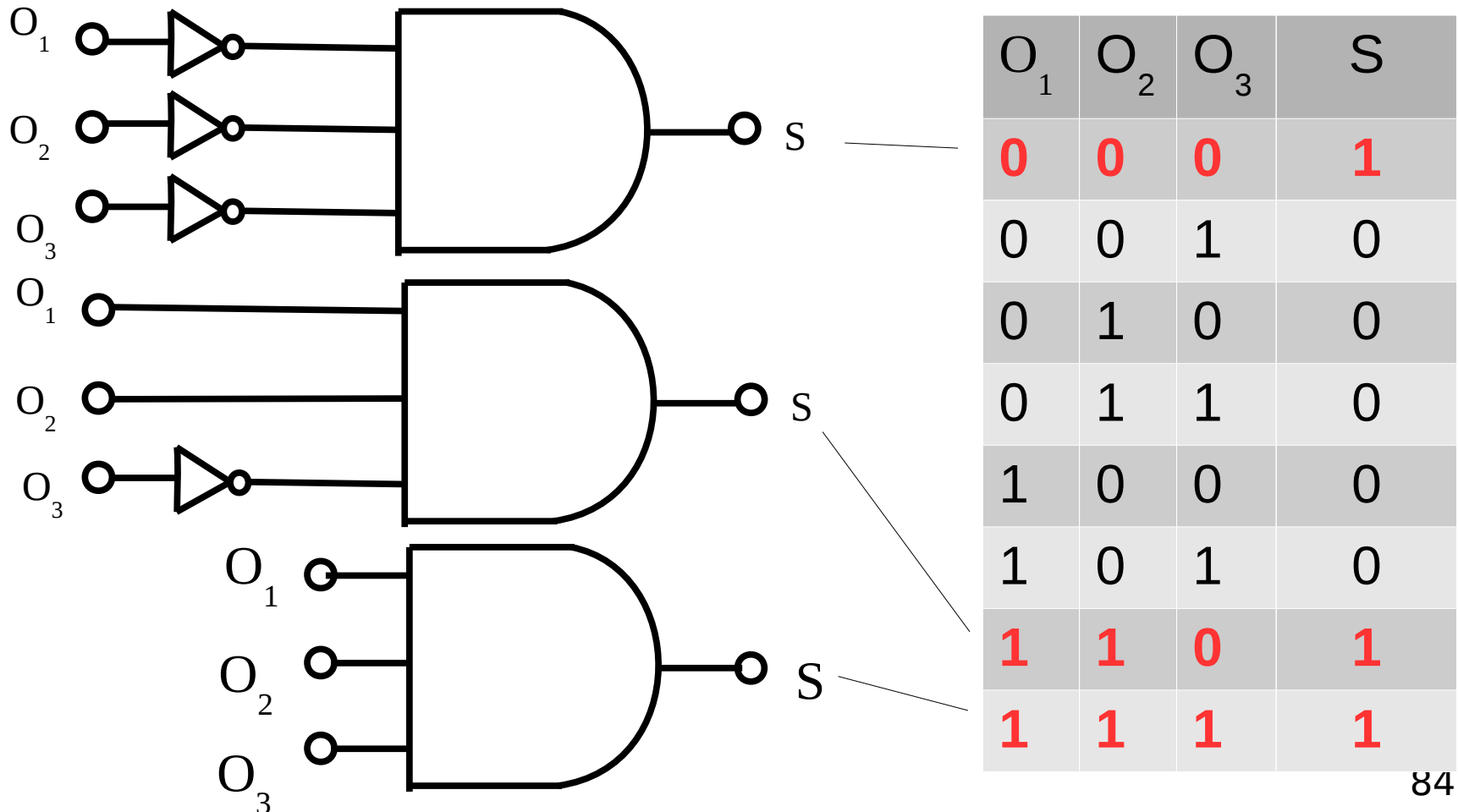
# The final circuit (sort of)

- We now have three circuits which all give one when our criteria to shut down the reactor are met.




• But we need to make this into one circuit.....

# Join together the inputs

  


• Looking good, now let's join the outputs together with an OR gate.

# Join together the inputs

 

•Finished!!!

# Join together the inputs

 

•This circuit will produce this truth table.


$O_1$	$O_2$	$O_3$	$S$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

•Finished!!!
 
# Examples of slightly complex digital circuits



- And we have correctly interfaced our thermometer to the nuclear power plant shut down circuit.



- And our nuclear power plant can no longer blow up!



# Recap – how to design digital circuits 1




- Write out the truth table

$O_1$	$O_2$	$O_3$	S
<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>
 
# Recap – how to design digital circuits 2



- Use AND and NOT gates that produce circuits that only give a 1 when a set of desired inputs is met




$O_1$	$O_2$	$O_3$	$S$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1
 
# Recap – how to design digital circuits 3



- Stitch the inputs together and join the outputs with an OR gate.




•And that is it!

# Summary digital design


- You can now design any digital circuit that is thrown at you if you follow those simple steps.
- You can now even design the circuits that go into computer chips using this method




Processor

 

# Adding unit

 

Adding unit

 

The electronics inside a processor

- Simply draw out the truth tables and you would get the answer.

# Now' its your turn

•However that's a bit complex to do in the lecture. So you will now design a circuit to detect if a number is odd:


•Hint you need four AND gates, one OR gate, and a collection of NOT gates.

$O_1$	$O_2$	$O_3$	S
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>

# The answer



## •The answer

 

$O_1$	$O_2$	$O_3$	S
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# However



- Do you notice something about this truth table??


Value	$O_1$	$O_2$	$O_3$	S
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

- When ever  $O_3$  is one we have an odd number


 
## A much simpler circuit

- We could actually replace this whole circuit with a wire!! (in this case):




- The method I have just taught you will work 100% of the time without any problems.
- However, it will not try to simplify the circuit at all and you may end up using far more gates than you really need.

# A much simpler circuit

- There are programs which will take a truth table and convert it into a minimized circuit which uses the least number of gates that are possible.

Dec	Hex	A	B	C	D	F1
0	0	0	0	0	0	
1	1	0	0	0	1	
2	2	0	0	1	0	
3	3	0	0	1	1	
4	4	0	1	0	0	1
5	5	0	1	0	1	
6	6	0	1	1	0	
7	7	0	1	1	1	
8	8	1	0	0	0	1
9	9	1	0	0	1	
10	A	1	0	1	0	
11	B	1	0	1	1	
12	C	1	1	0	0	1
13	D	1	1	0	1	
14	E	1	1	1	0	
15	F	1	1	1	1	


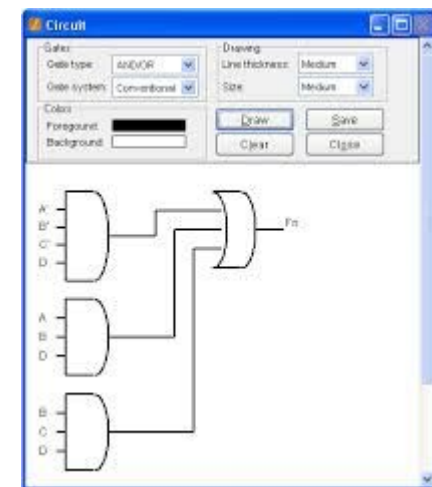


- If you start doing this seriously in industry I suggest you take a look at some of this software..
  
# Field programmable gate array



- Final tip, I have introduced you to logic chips that look like this, they have contain 8 gates.



# Field programmable gate array

- Although these chips are still used (especially in glue logic).
- It is very common today to use something called an (Field programmable gate array) FPGA.
- This single chip can contain **half a million gates** and the connections between each gate are programmable.
- This means you can actually 'rewire' your circuit with a computer while your machine is running.
- You will meet these in industry.




Cost <10 pounds

100
 
# Last tip on digital electronics **race times**



- Think about this circuit, if you changed the inputs from 11 to 00 the outputs would not change.




Slooby from Chicago

- Let's draw this out in detail
 
# Last tip on digital electronics **race times**



- Think about this circuit, if you changed the inputs from 11 to 00 the outputs would not change.





Slooby from Chicago

- Let's draw this out in detail

# Last tip on digital electronics **race times**



- The ideal case:

 
 


Slooby from Chicago
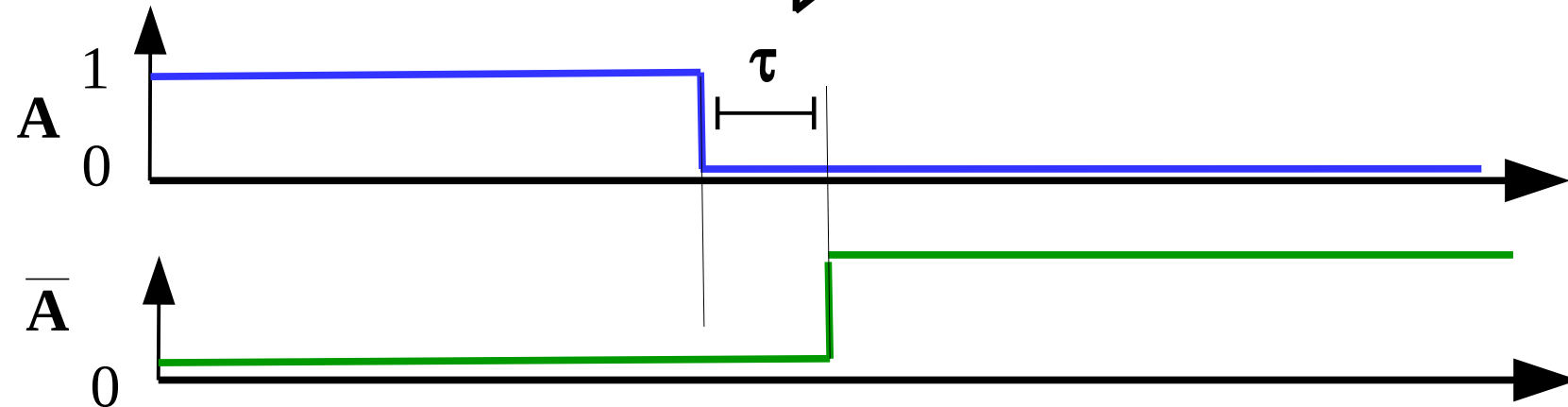 
# However, you should know that....



- All gates have a 'turn on' and 'turn off' time.
- This is in effect a time it takes the gate to react to an input -  $\tau$ .






  
# Last tip on digital electronics **race times**




• However every gate takes a finite time to respond (micro seconds).


 
# Last tip on digital electronics **race times**



- Gates take microseconds to respond.
- This means your output can be wrong for up to a microsecond.
- The more gates you have the longer these effects will last for.
- Often glitches don't matter, but if you are designing sensitive (fast) circuits, they can be really really important.



# Summary of today's lecture



- Recap of last lecture
- Using JK flip flops to run motors
- Digital design
  - What is digital design?
  - How to do it.
  - Where you might meet digital design
  - FPGAs
- Race times