

# **Electromechanical devices MM2EMD**

## **Lecture 5 - Using Operational Amplifiers (opamps) in the real world**

**Dr. Roderick MacKenzie**

**roderick.mackenzie@nottingham.ac.uk**

**Summer 2015**



**@rcimackenzie**


Released under  **creative  
commons**





- **Recap of last lecture**
- Mini Quiz
- Books and resources
- Op-amps used in the real world
  - Measuring acceleration
  - Measuring stress and strain.
- Summary
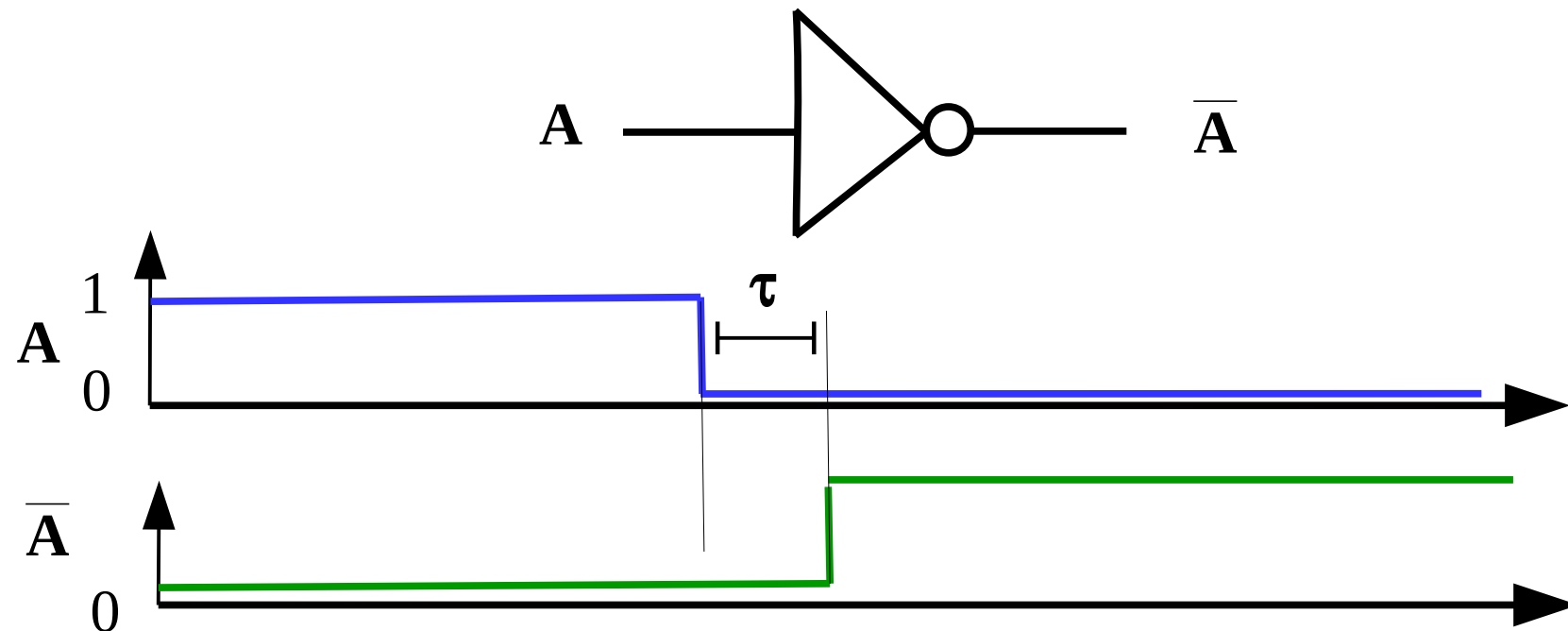
## Recap: Race times

- All gates have a 'turn on' and 'turn off' time.
- This is in effect a time it takes the gate to react to an input -  $\tau$ .




# Recap: Race times

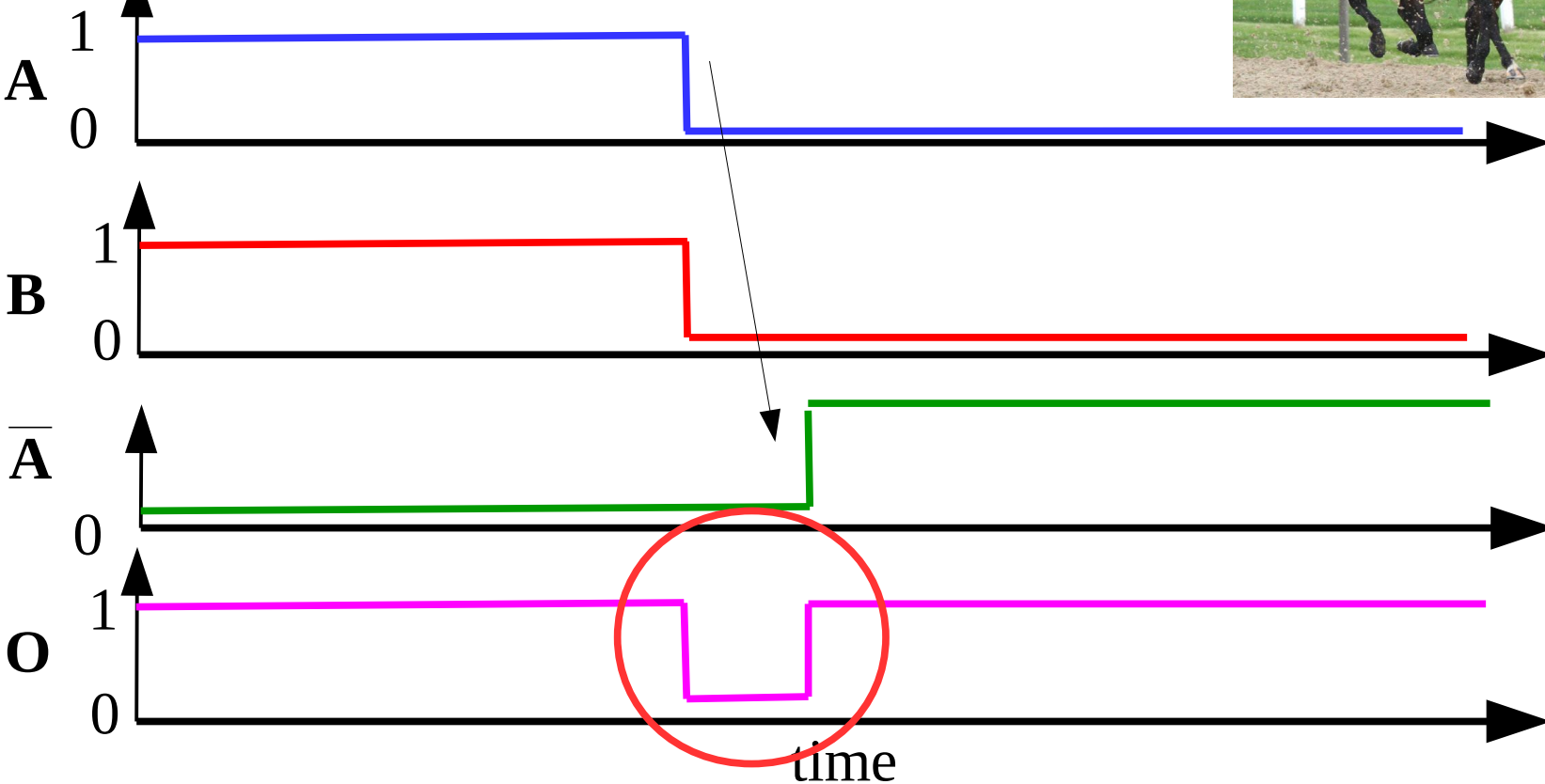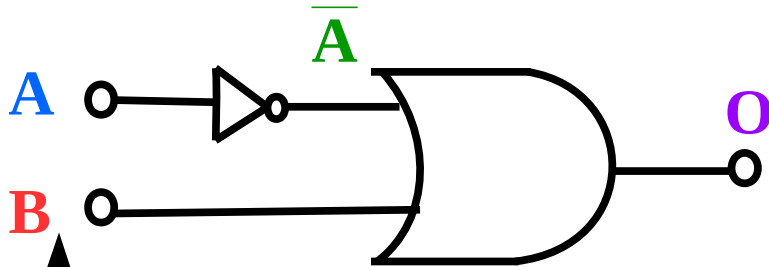

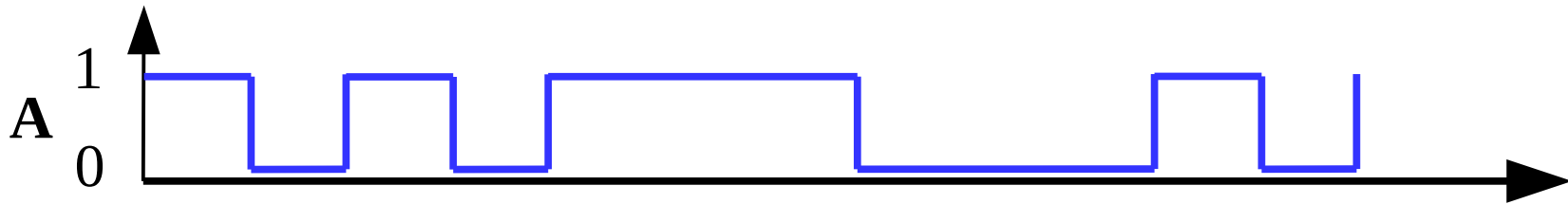
# Recap: digital v.s. analog signals



- Digital signal can only have two values on and off.



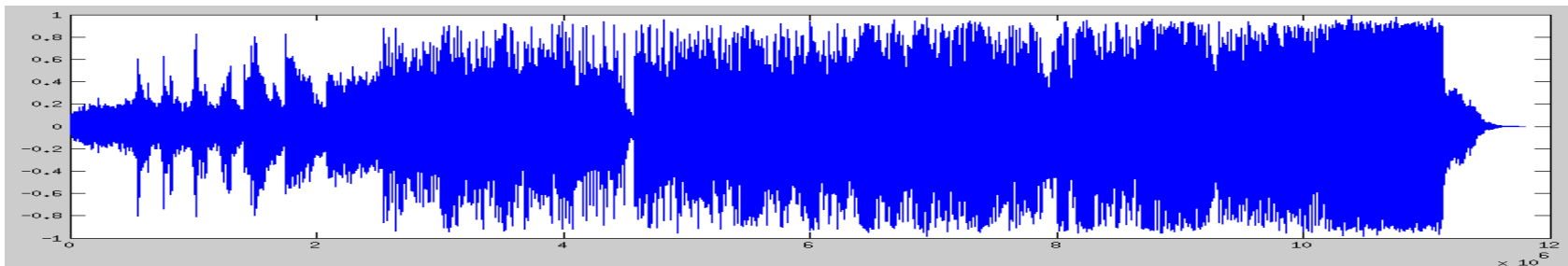
- Analog signals can take any value.
- You find analog signals in the real world, think of sound or vibration signals.




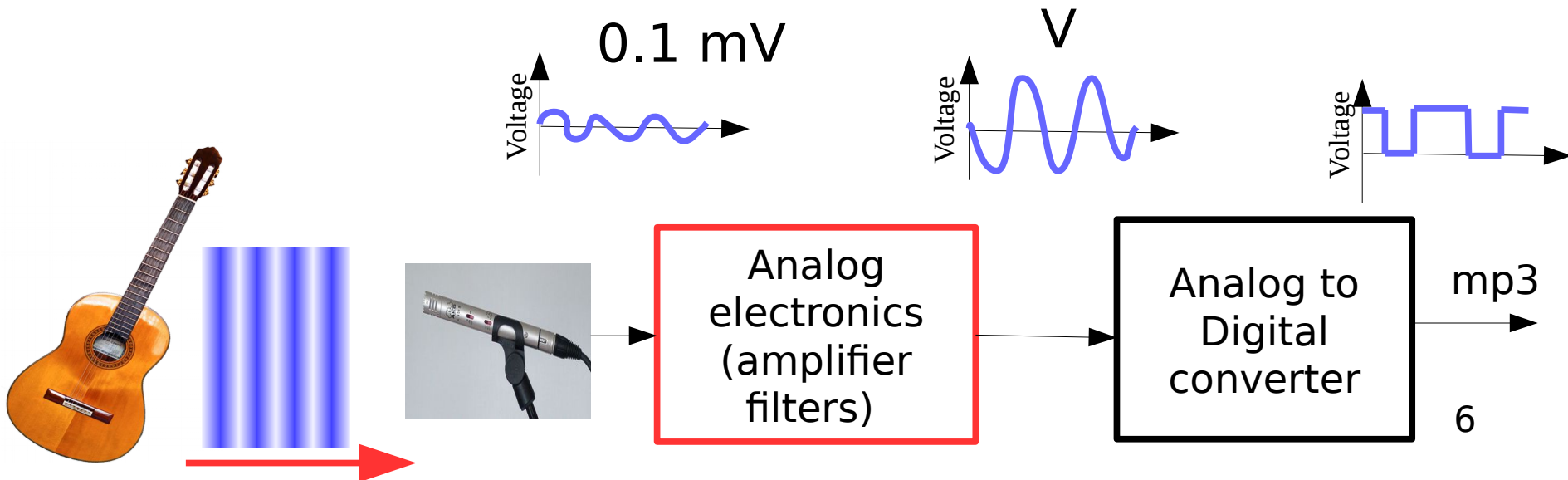
# Recap: Modern analog systems an mp3 recorder.



- Many modern digital systems have analog electronic preprocessing of data.



# Recap: The op-amp (Bob Widlar)

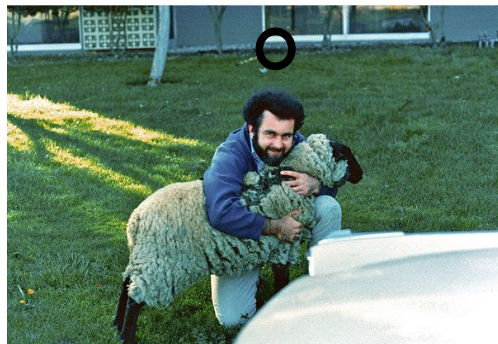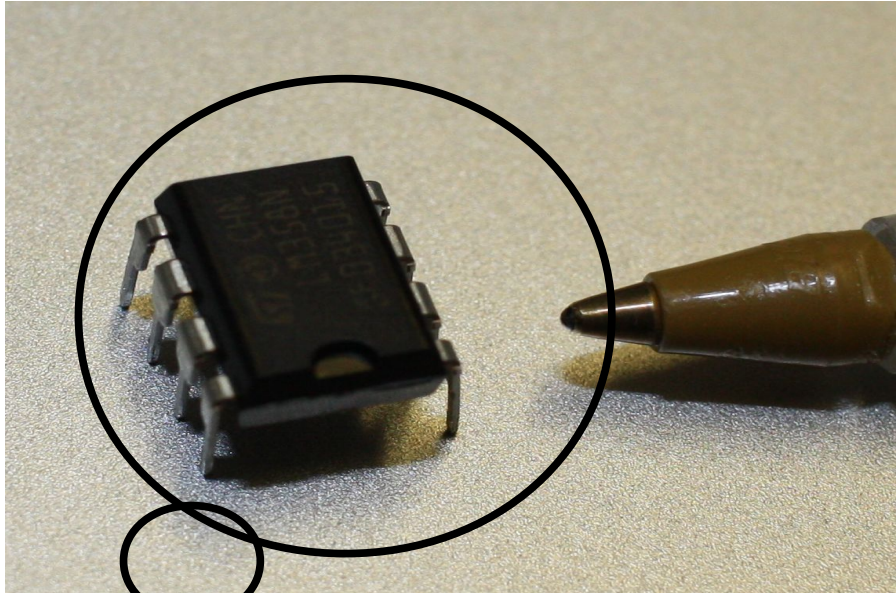


## Operational amplifier

And 'operation', think of a mathematical operation.


An amplifier i.e. something that makes a signal bigger.

# Recap: What's inside... ahhh..

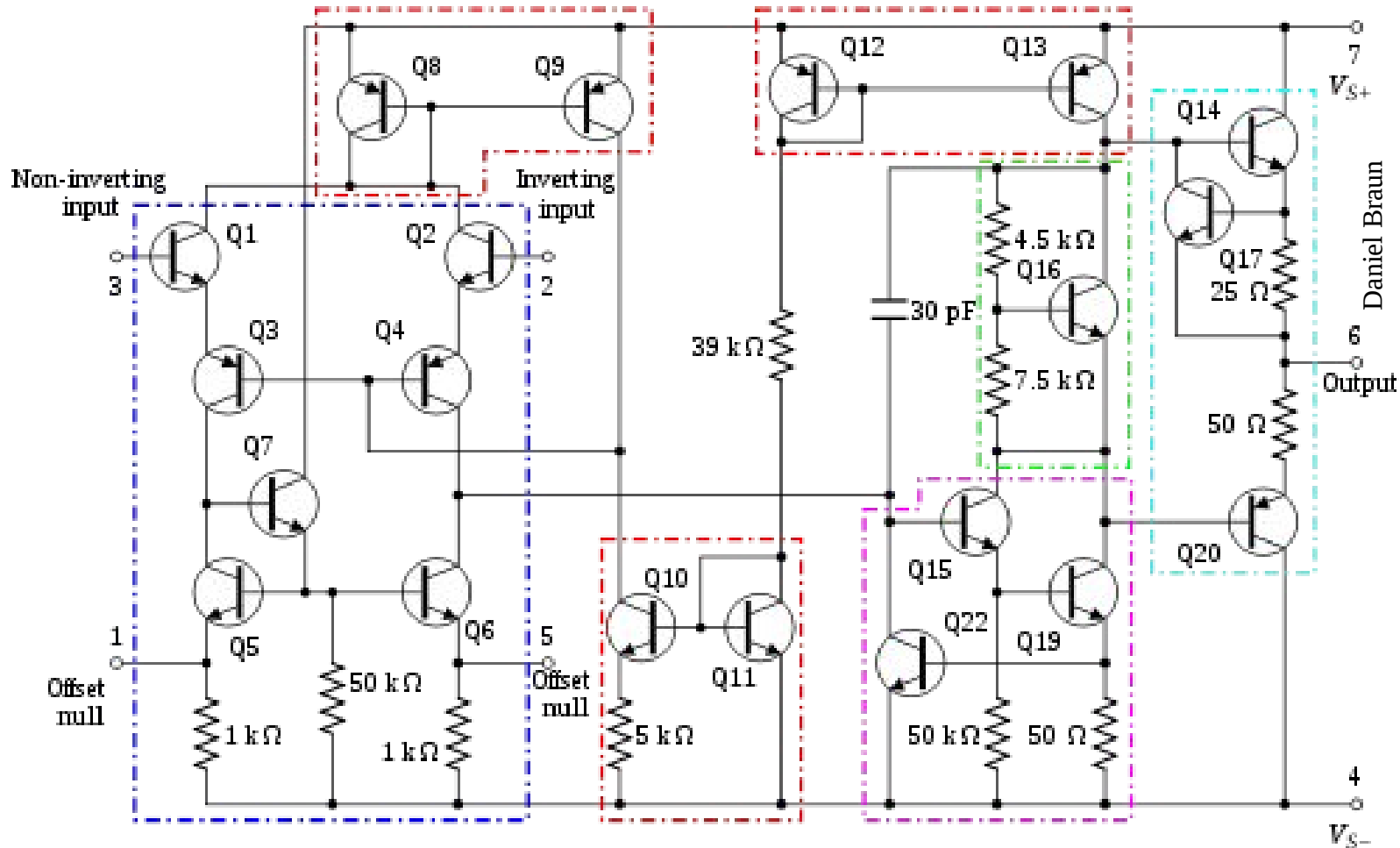




# Recap: op-amp equivalent circuit

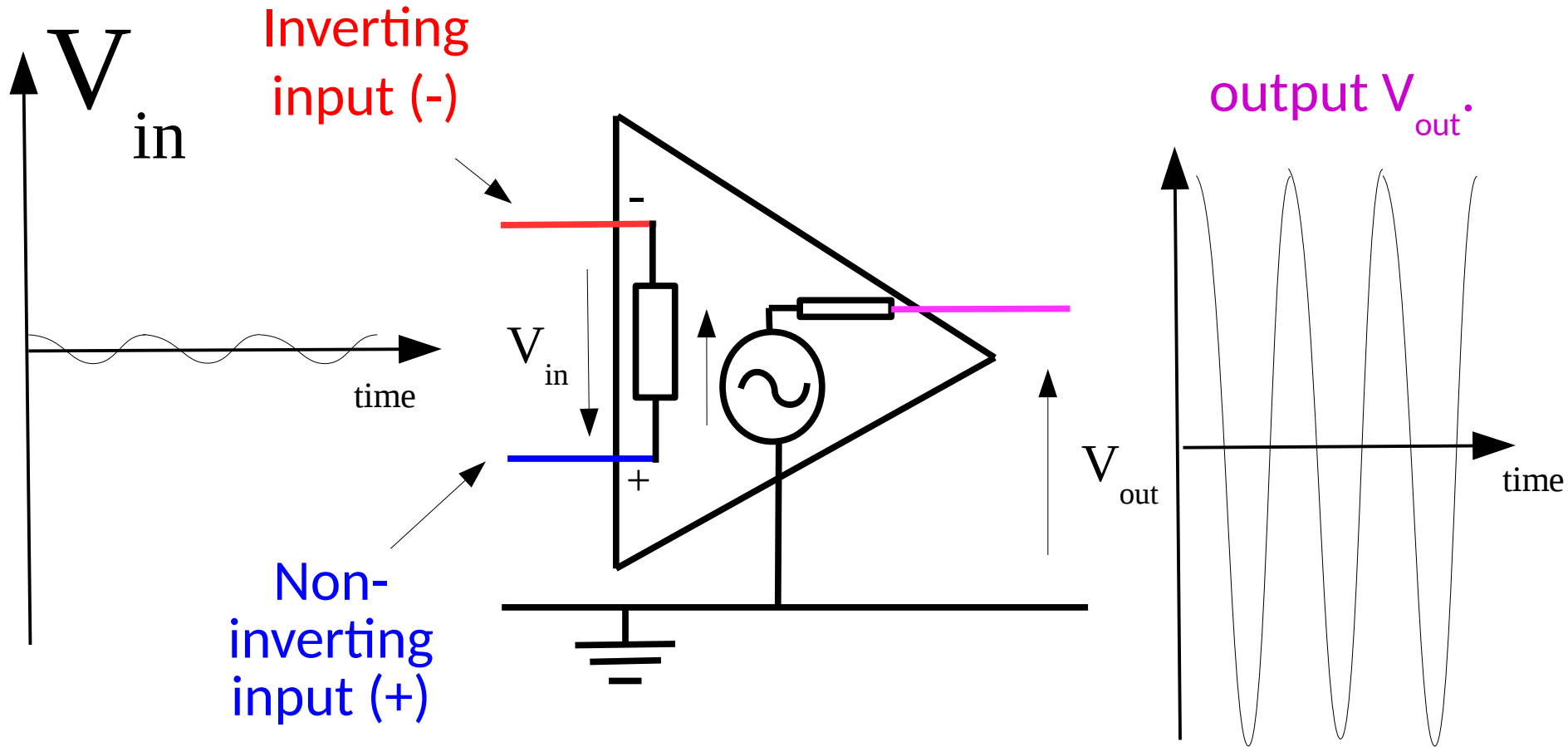

$$V_{in} \quad A = V_{out}$$

# Recap: It contains two resistors

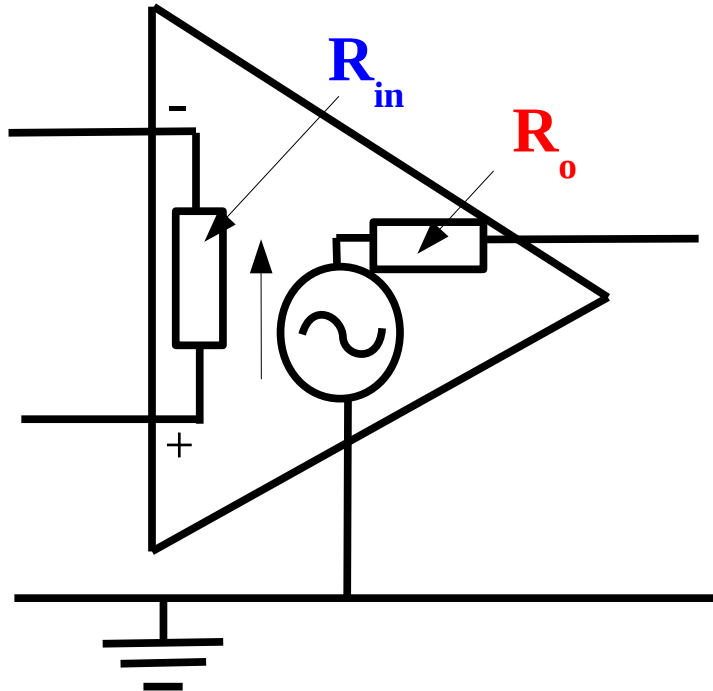


$R_{in}$  = an input resistance - very high - we can assume this is infinite.


$R_o$  = output resistance - very low - we can assume this is zero (i.e. a short circuit)

So let's further simplify our circuit taking into account the high  $R_{in}$  and the low  $R_o$ .

# Recap: A simple op-amp circuit

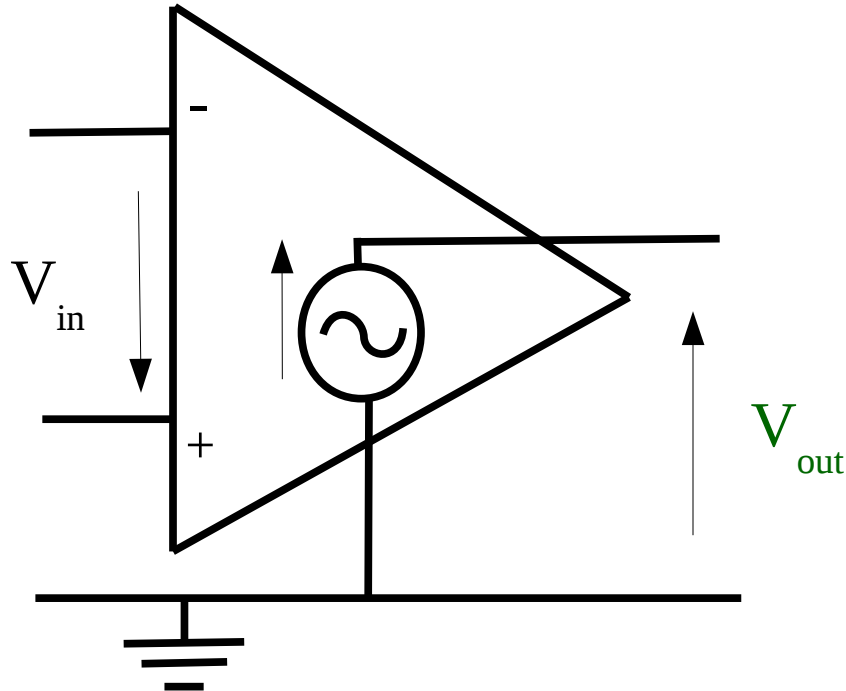


# Recap: Problems with the op-amp..

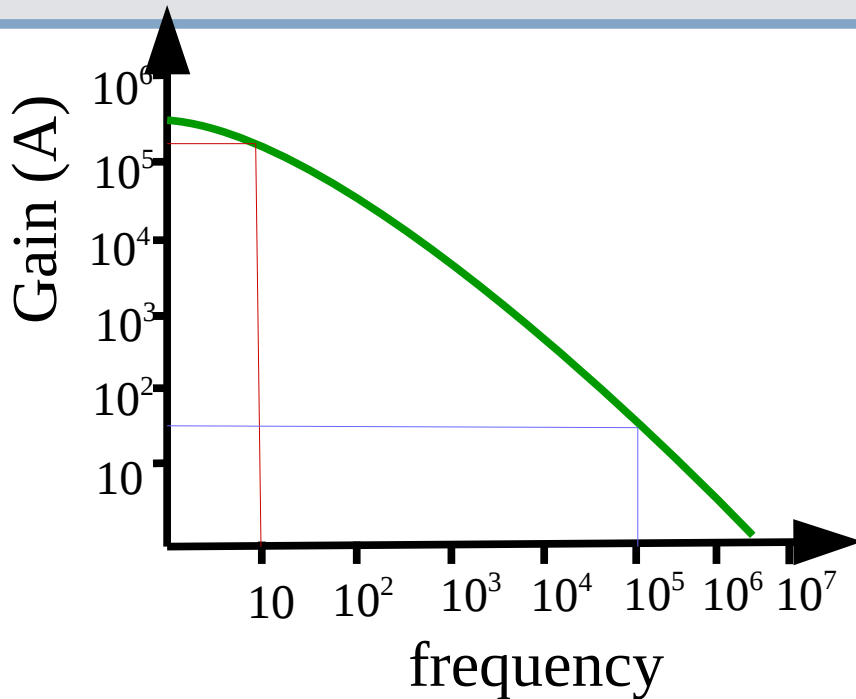


- Non linear gain



- Output clipping


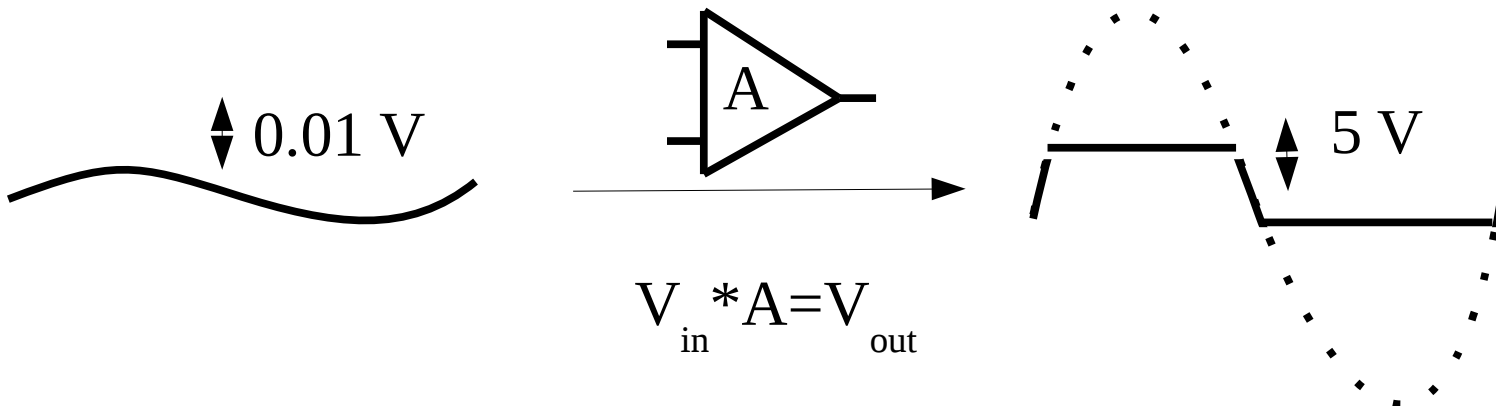

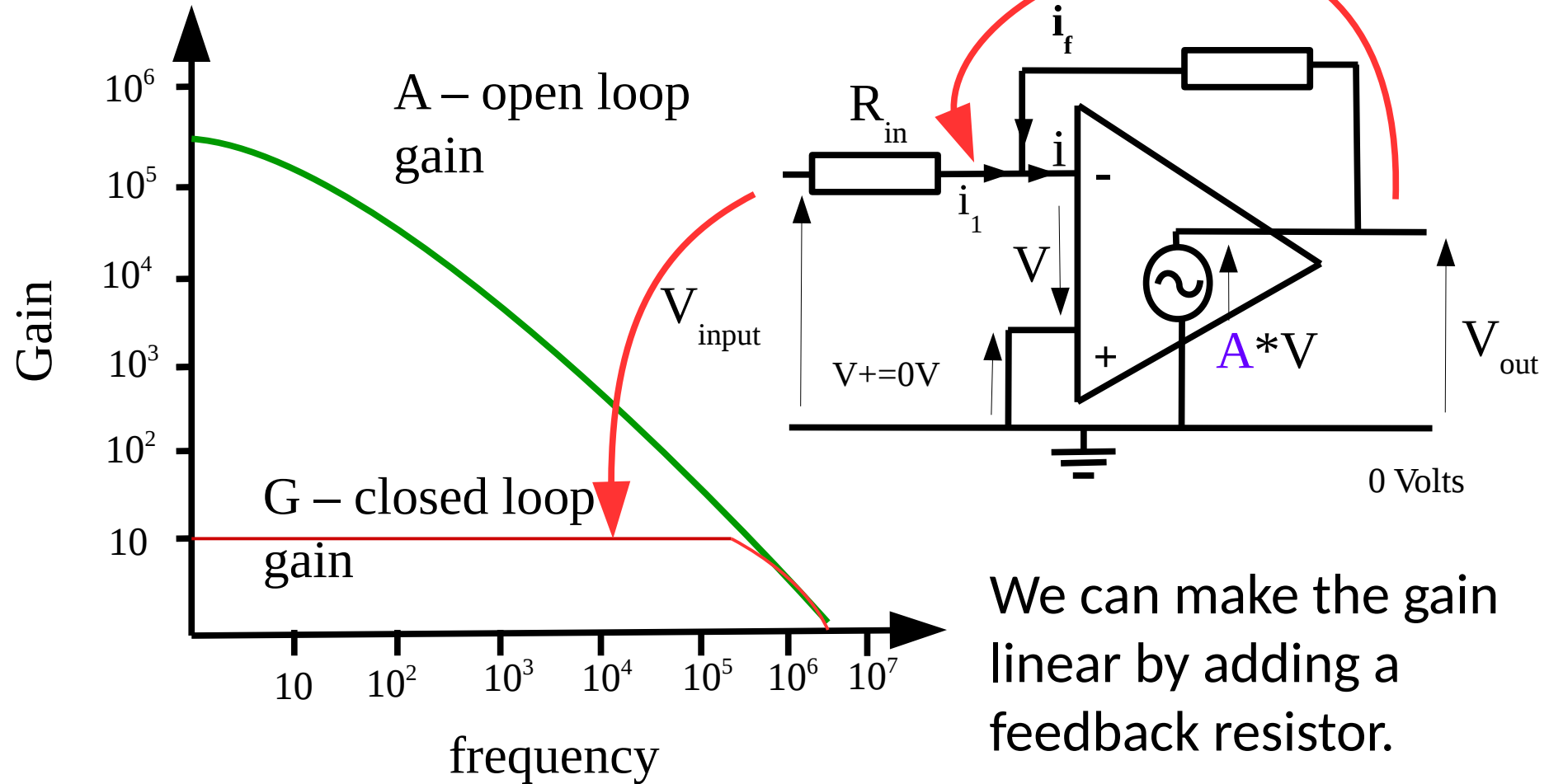
# Recap: Op-amps give a lot of non-linear gain.



We can make the gain linear by adding a feedback resistor.
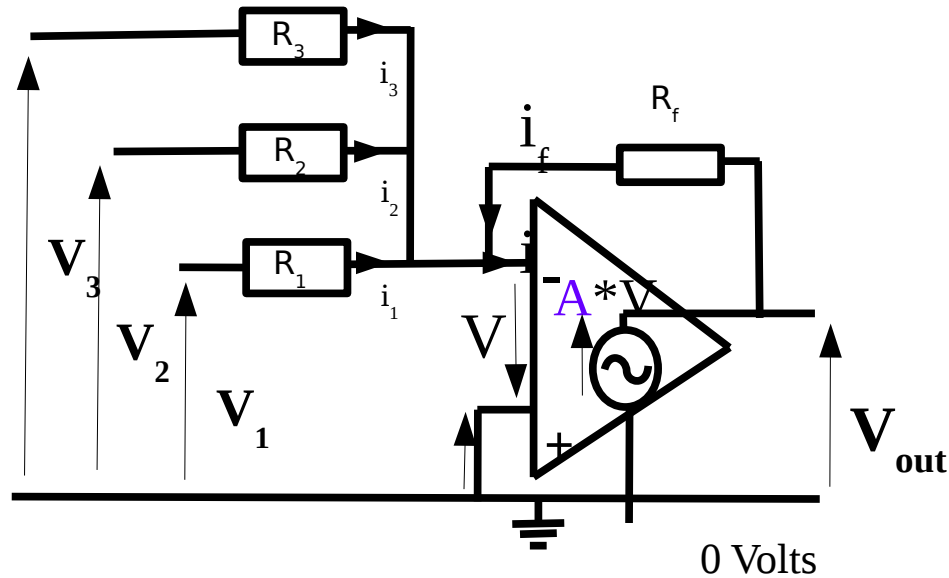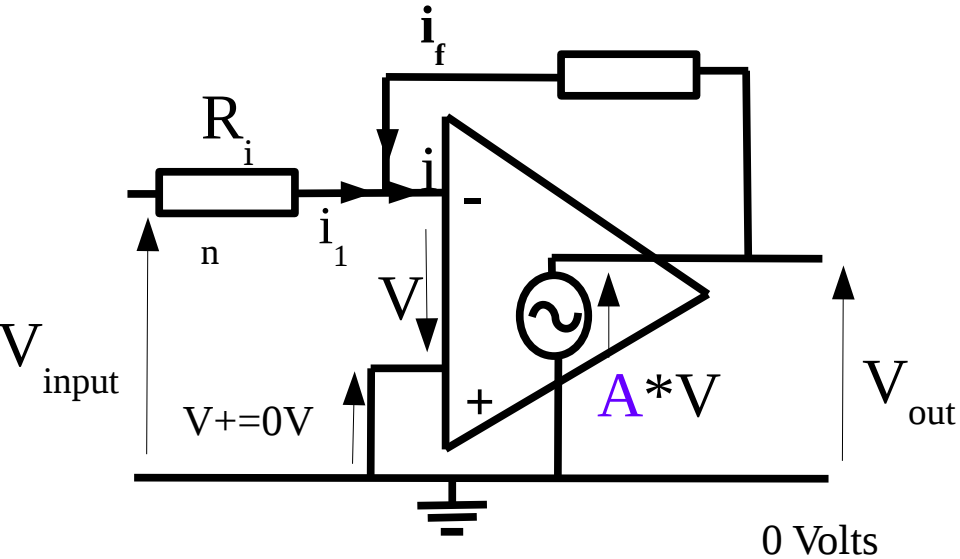
# Recap: Inverting amplifier and adding amplifier



$$\frac{V_0}{V_i} = \frac{-R_f A}{[R_r (A+1) + R_f]}$$

$$V_{out} = -[V_1 + V_2 + V_3]$$

$$G = \frac{V_0}{V_i} = -\frac{R_f}{R_1}$$




# Outline of the lecture

- Recap of last lecture
- Mini Quiz**
- Books and resources
- Op-amps used in the real world
  - Measuring acceleration
  - Measuring stress and strain.
- Summary
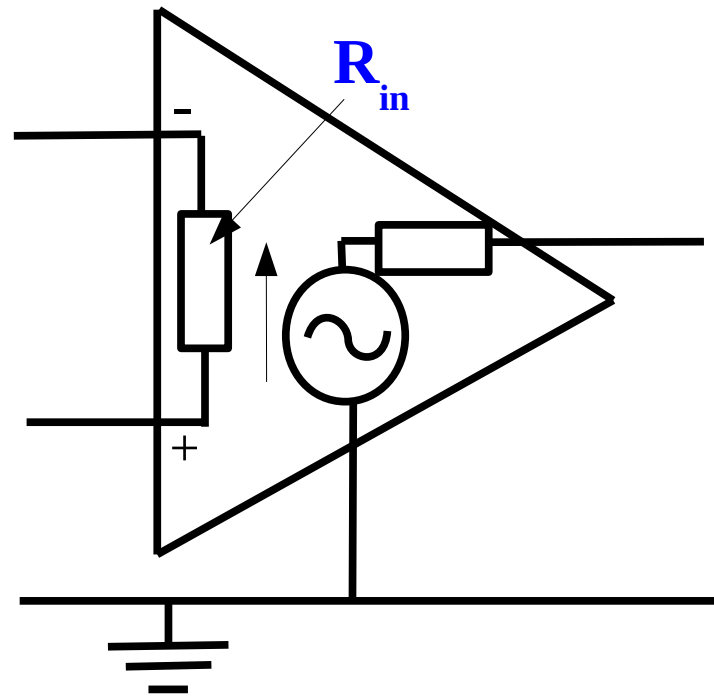
# Quiz Q1:


Q: What can we assume the input resistance of an op-amp is?




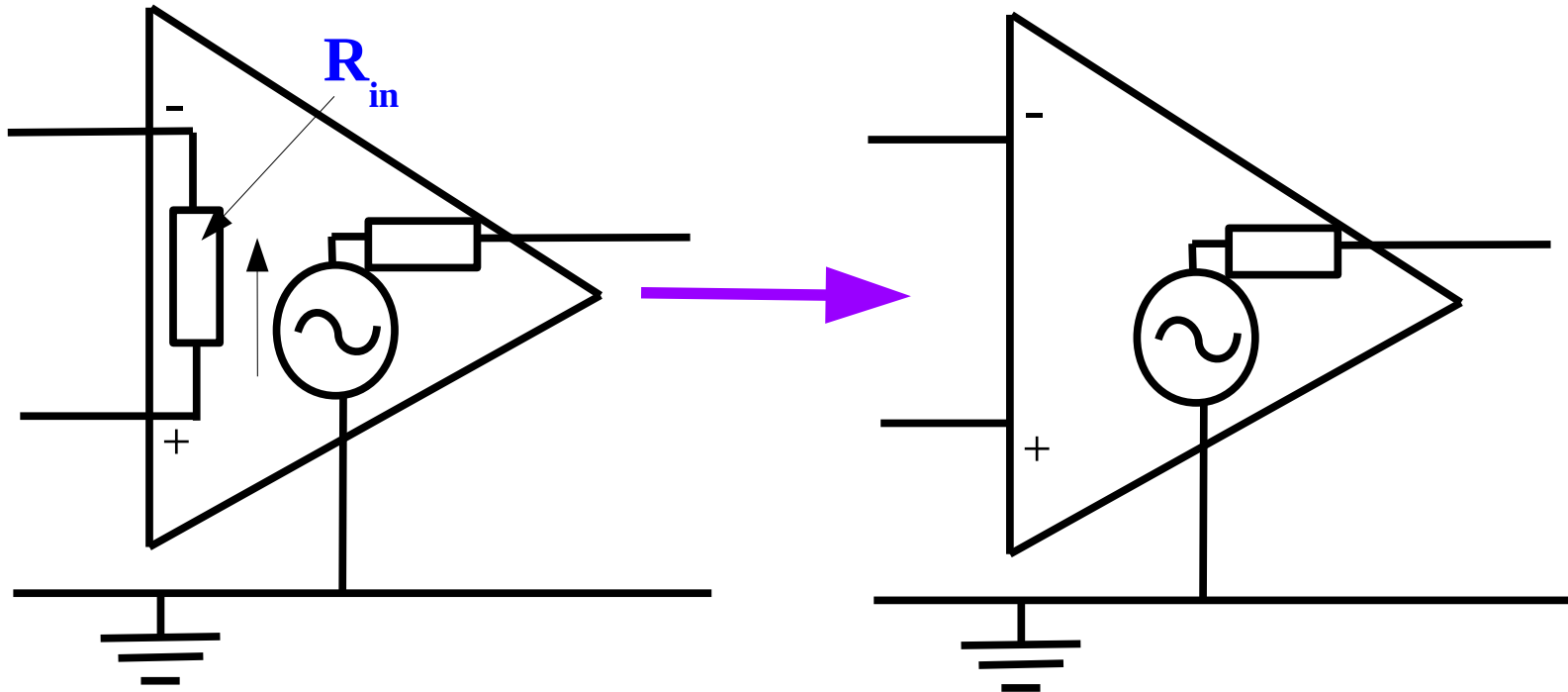
# Quiz A1:


- Q: What can we assume the input resistance of an op-amp is? **Infinite**



In fact it's so big we can assume it's not there!

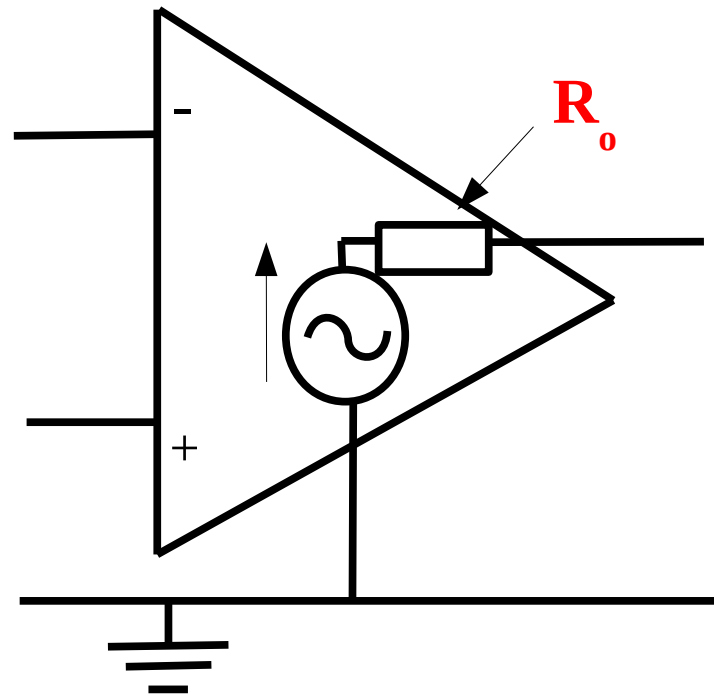
## Quiz Q2:

Q: What can we assume the output resistance of an op-amp is?


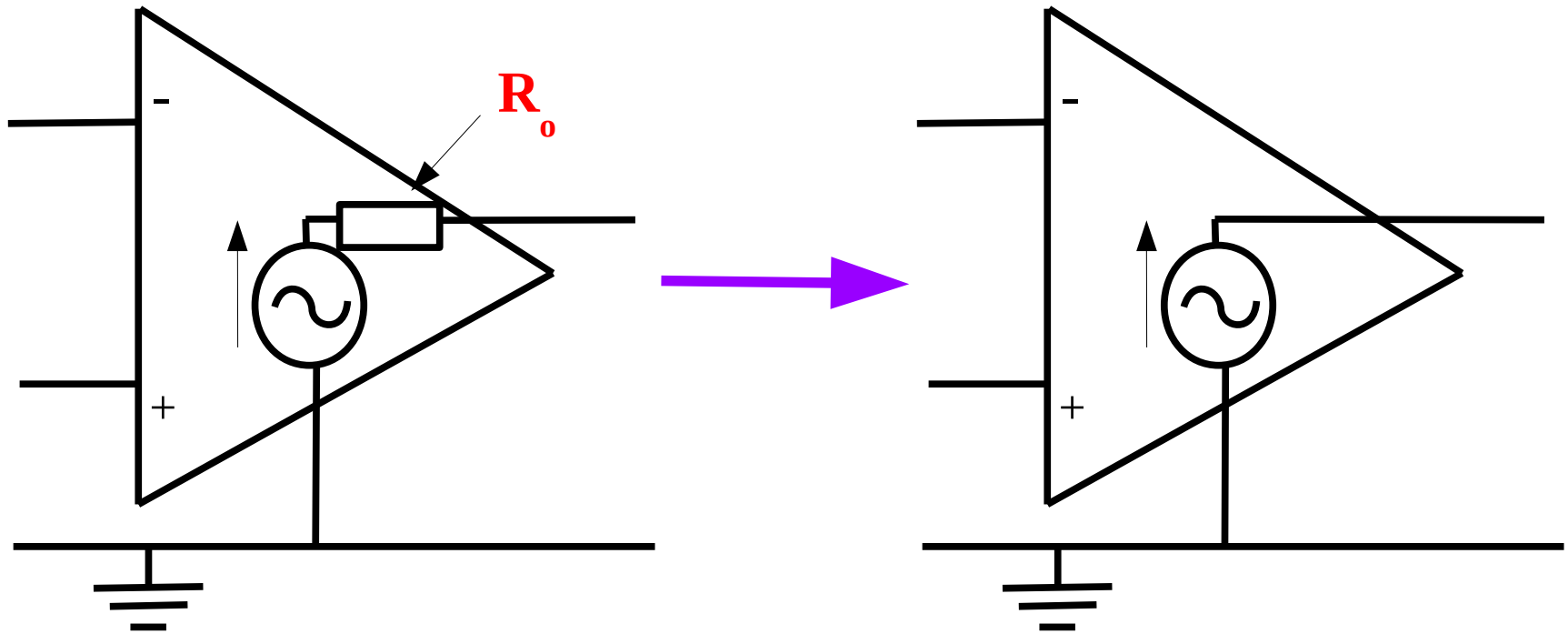
# Quiz A2:


Q: What can we assume the output resistance of an op-amp is? **zero**



In fact it's so small we can assume it's not there!
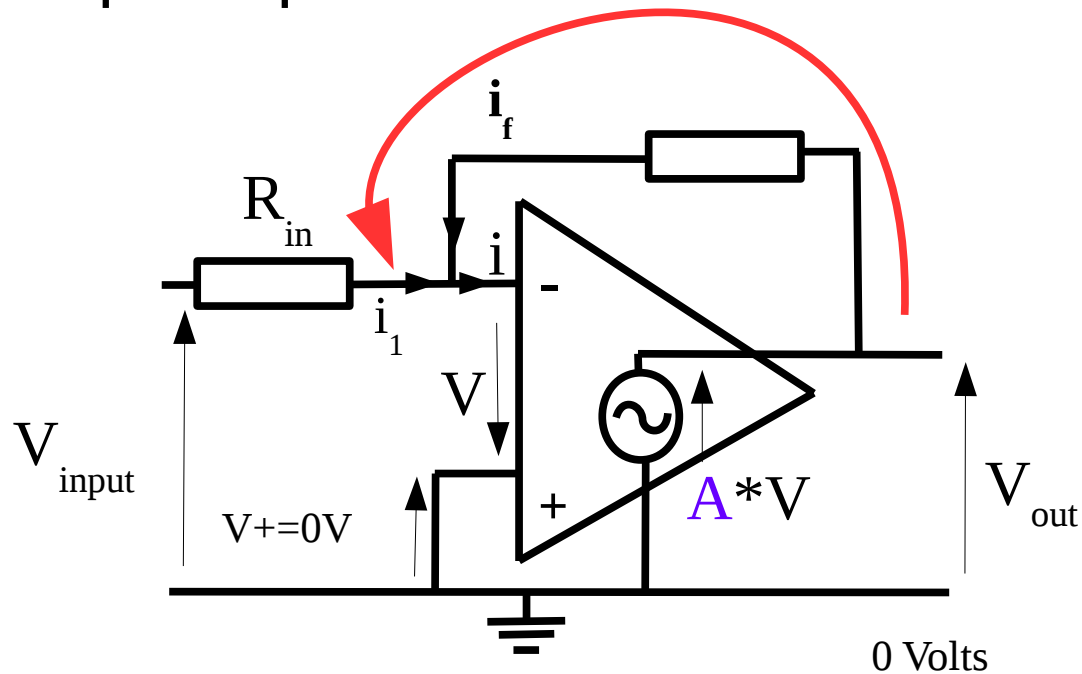
# Quiz Q3:

Q: Why do we need to use a feedback resistor in an op-amp circuit?




# Quiz A3:



Q: Why do we need a feedback resistor to use an op-amp?

A1) The gain is too high to be useful

A2) The gain is non-linear.

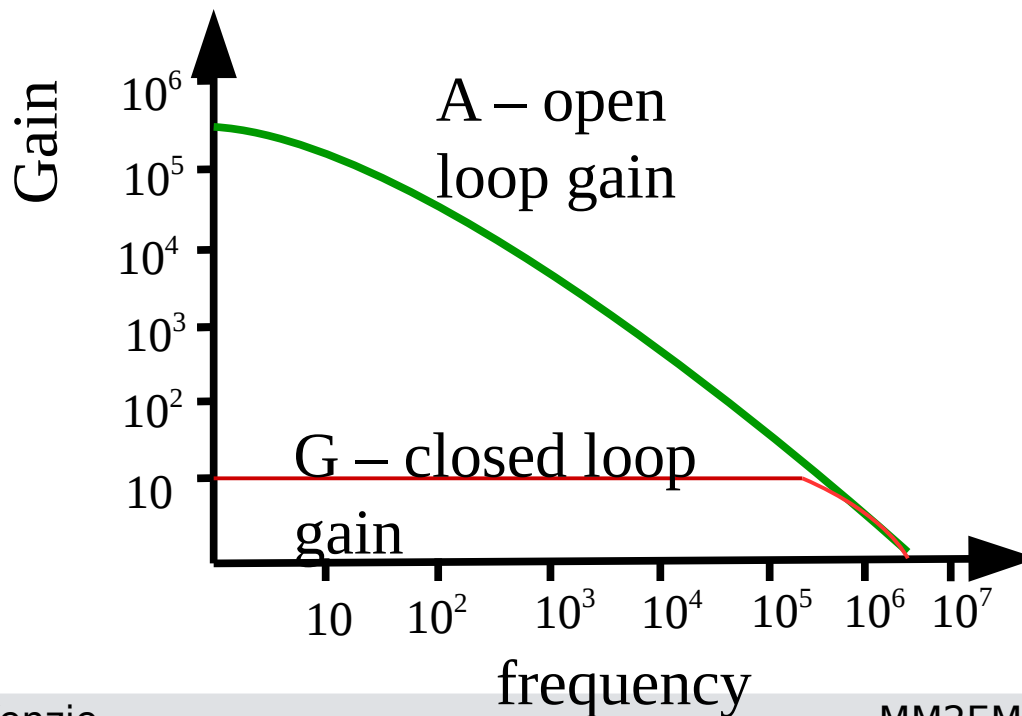

# Outline of the lecture




- Recap of last lecture
- Mini Quiz
- Books and resources**
- Op-amps used in the real world
  - Measuring acceleration
  - Measuring stress and strain.
- Summary
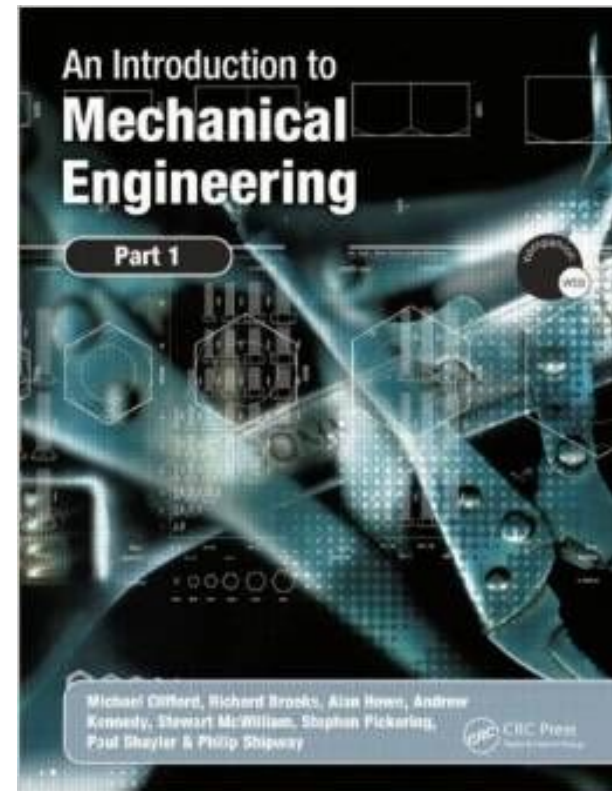
# Recommended reading: A general text book



If you feel you need a text book and only want to buy one – get this one:

An introduction  
to Mechanical  
Engineering, Part  
1 pp. 365-371




£42

23




Recommended reading: Useful for later in industry or now if you are interested

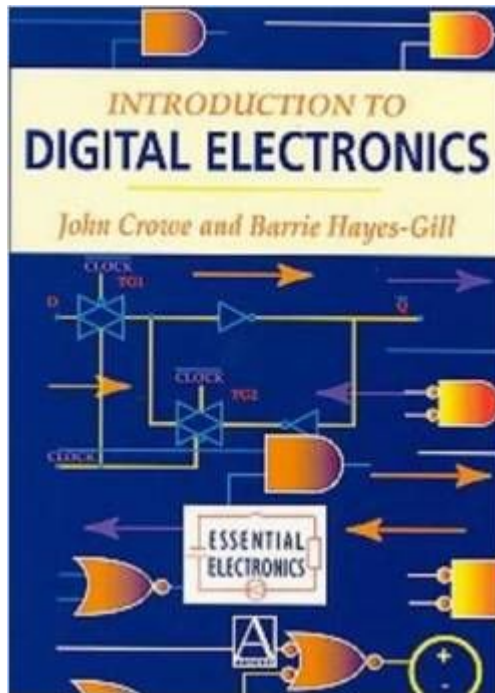A little more in depth on digital electronics:



£29-£42

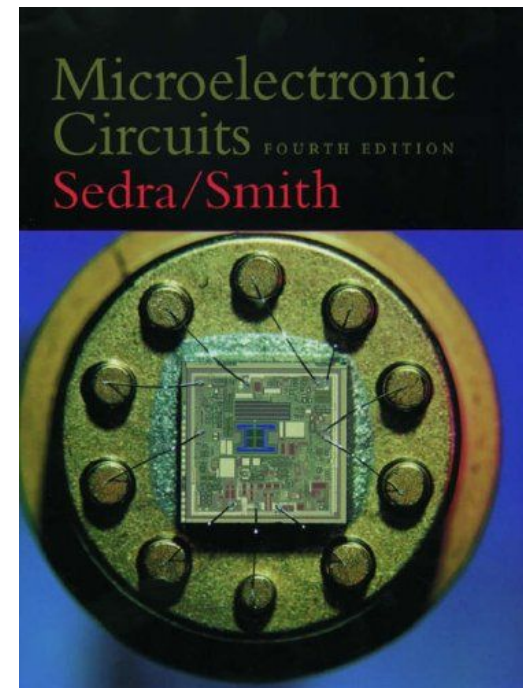Lots of in depth stuff on analog circuits – classic text book.



£30-£60



Recommended reading: Useful for later in industry or now if you are interested



- This is the classical ***practical*** electronics book.
- Every electronic engineer has this on his shelf.

£28-60



# Outline of the lecture

- Recap of last lecture
- Mini Quiz
- Books and resources
- Op-amps used in the real world**
  - Measuring acceleration**
  - Measuring stress and strain.
- Summary

# Let's think about measuring acceleration



- Often we need to measure acceleration



- Because acceleration can tell us a lot about our environment

$$\int \text{acceleration } dt = \text{velocity}$$

$$\int \text{velocity } dt = \text{position}$$

# Now let's think about the crystal quartz



Quartz



AlaskaMining


# The pizoelectric effect in quartz



- Normally quartz has a regular arrangement of positive and negative ions:




JJ Harrison

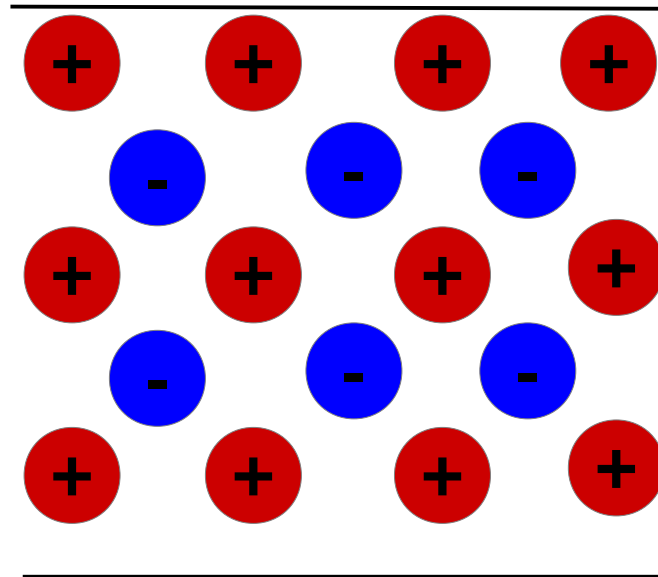

quartz

# The pizoelectric effect in quartz

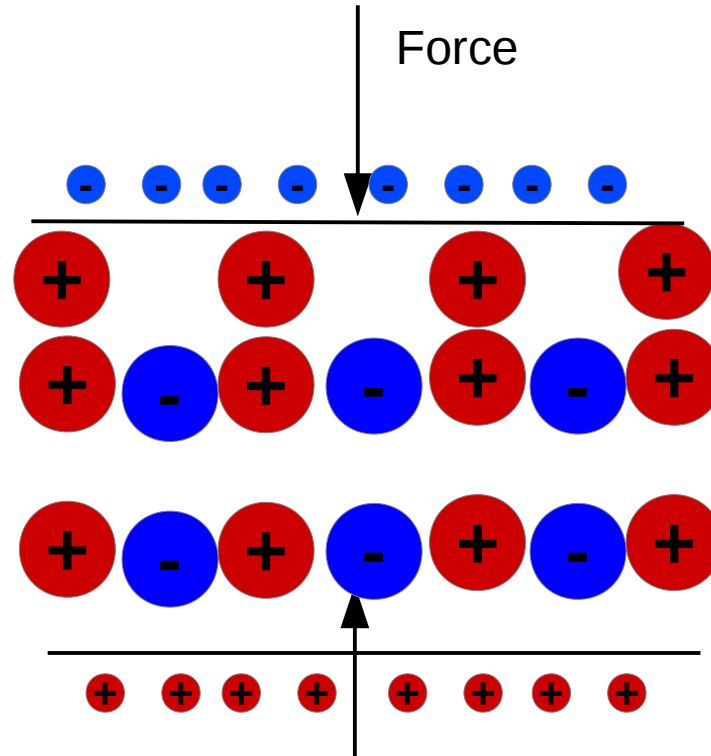


But what has this got to do with measuring acceleration?

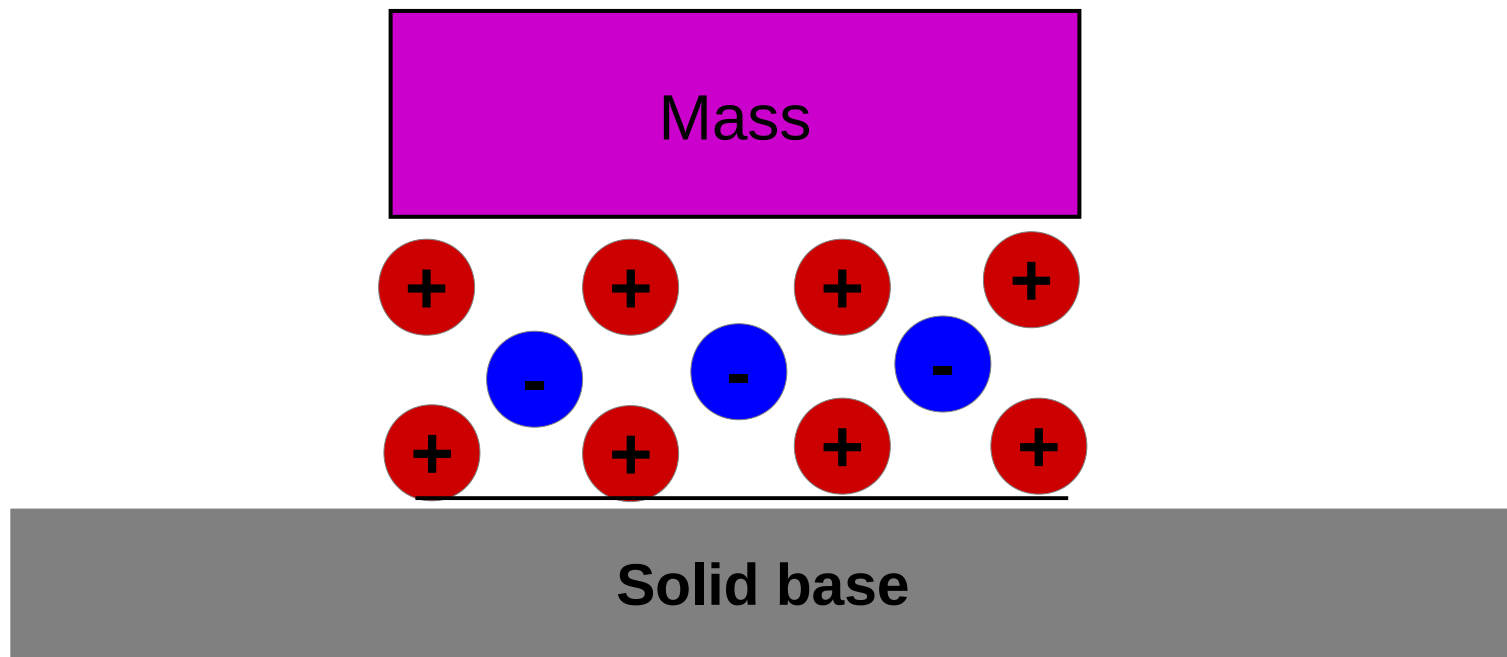
# Detecting acceleration with quartz crystal



Let's put a mass on top of the quartz crystal




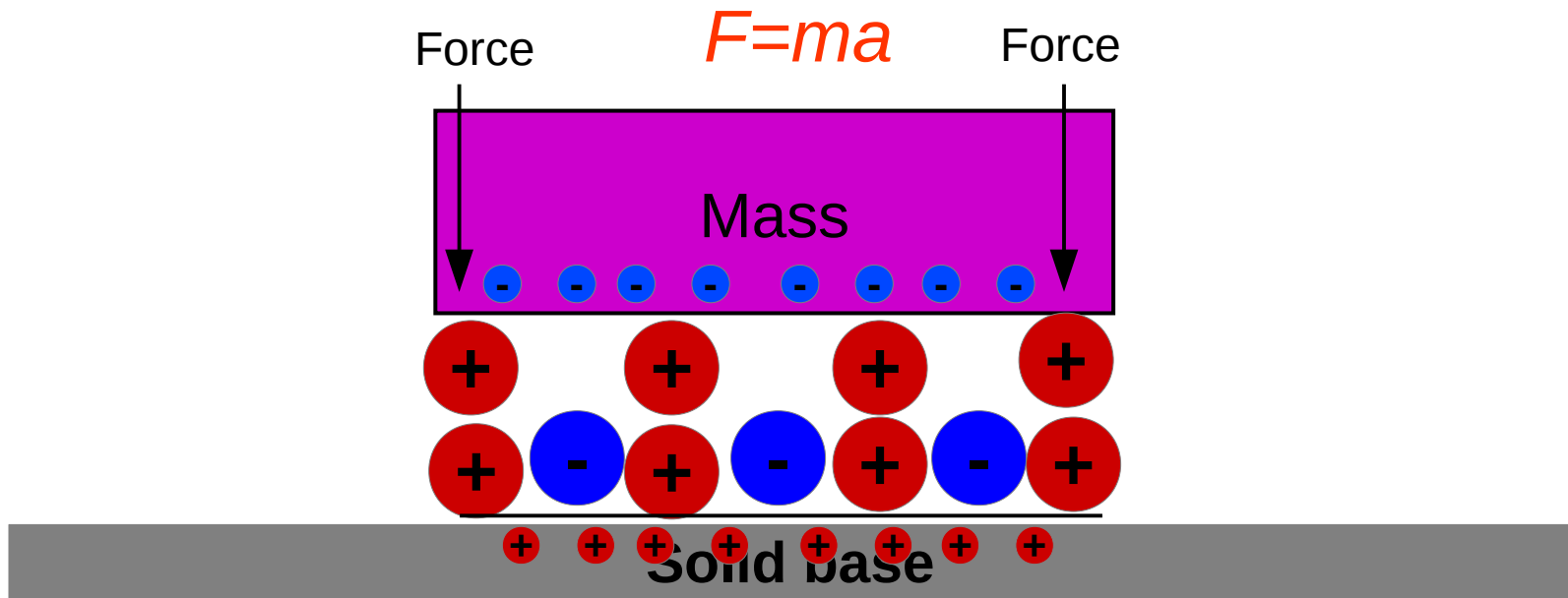
Acceleration *a* produces force ( $F=ma$ )



The movement causes the output charge from the piezoelectric crystal to change producing a current.




# This is how you make an accelerometer

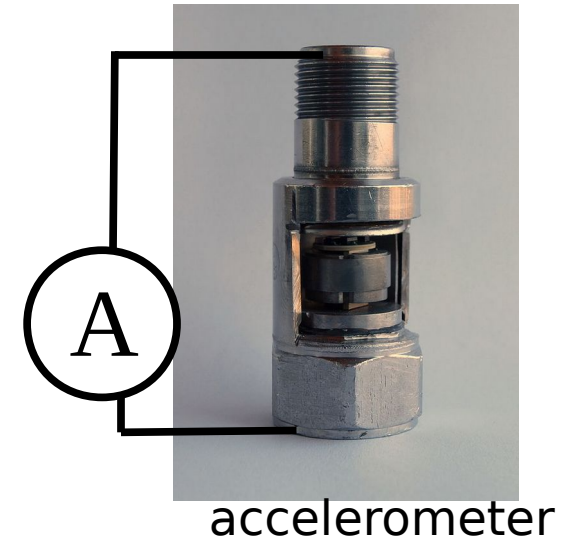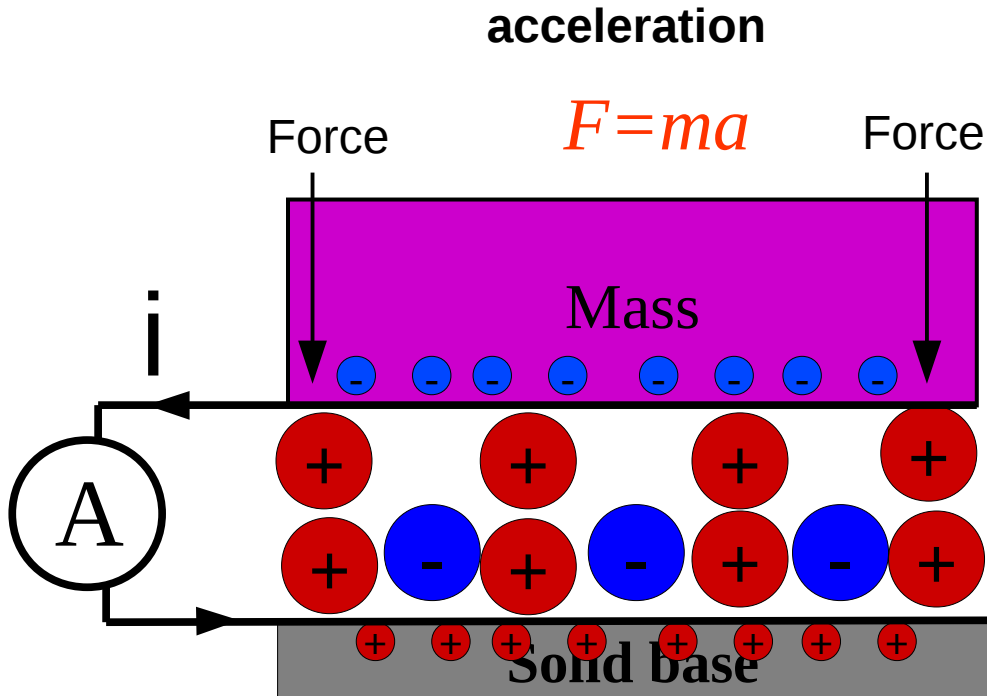


- The current changes when the sensor experiences acceleration
- Let's have a look at this effect in more detail....

# We have two problems....

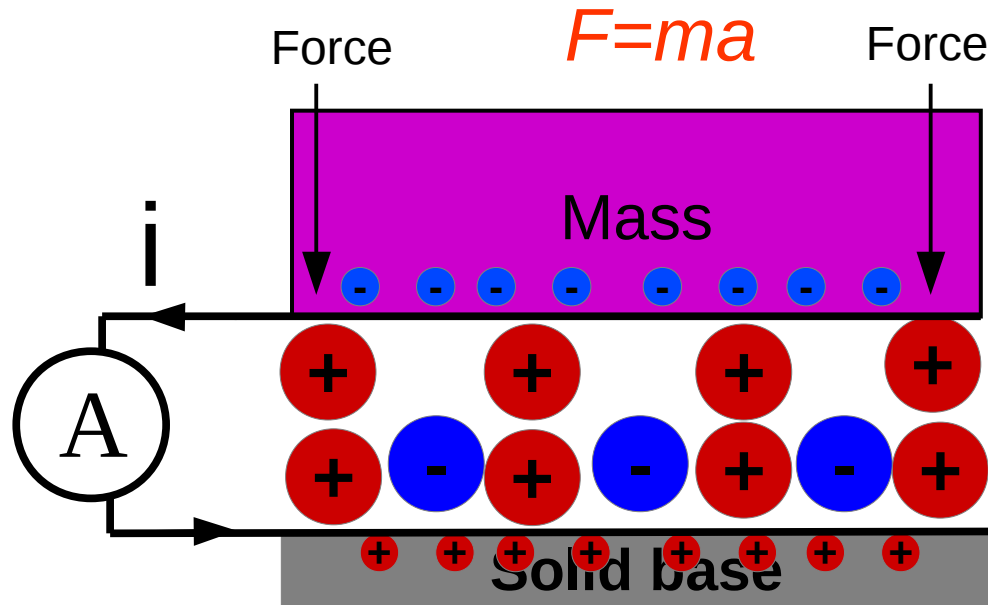


- **Problem 1:**  $i$  is very small.. too small to be used.... how might we fix that??
- **Problem 2:**  $i$  is not proportional to the acceleration, it's actually a bit more complex.. let's have have a look at this first...


# Simplification of accelerometer

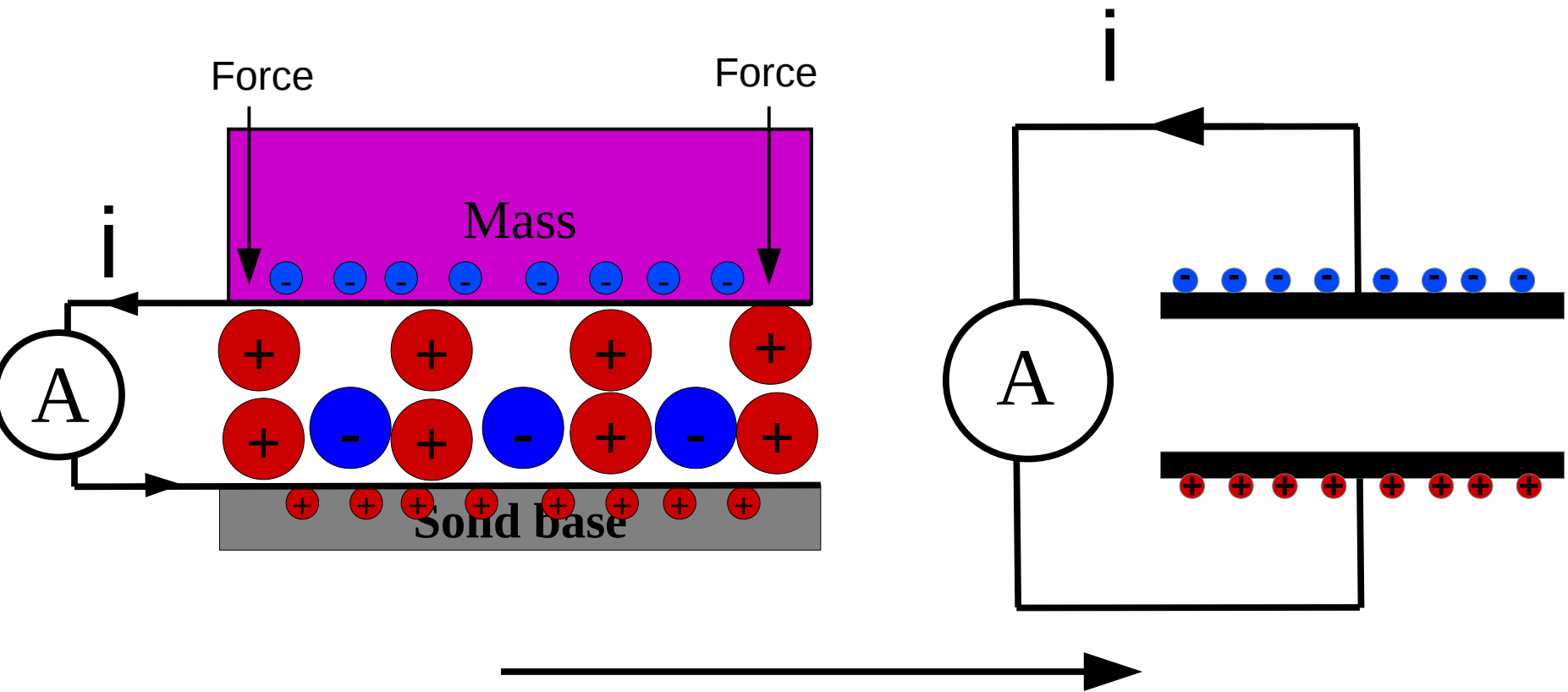

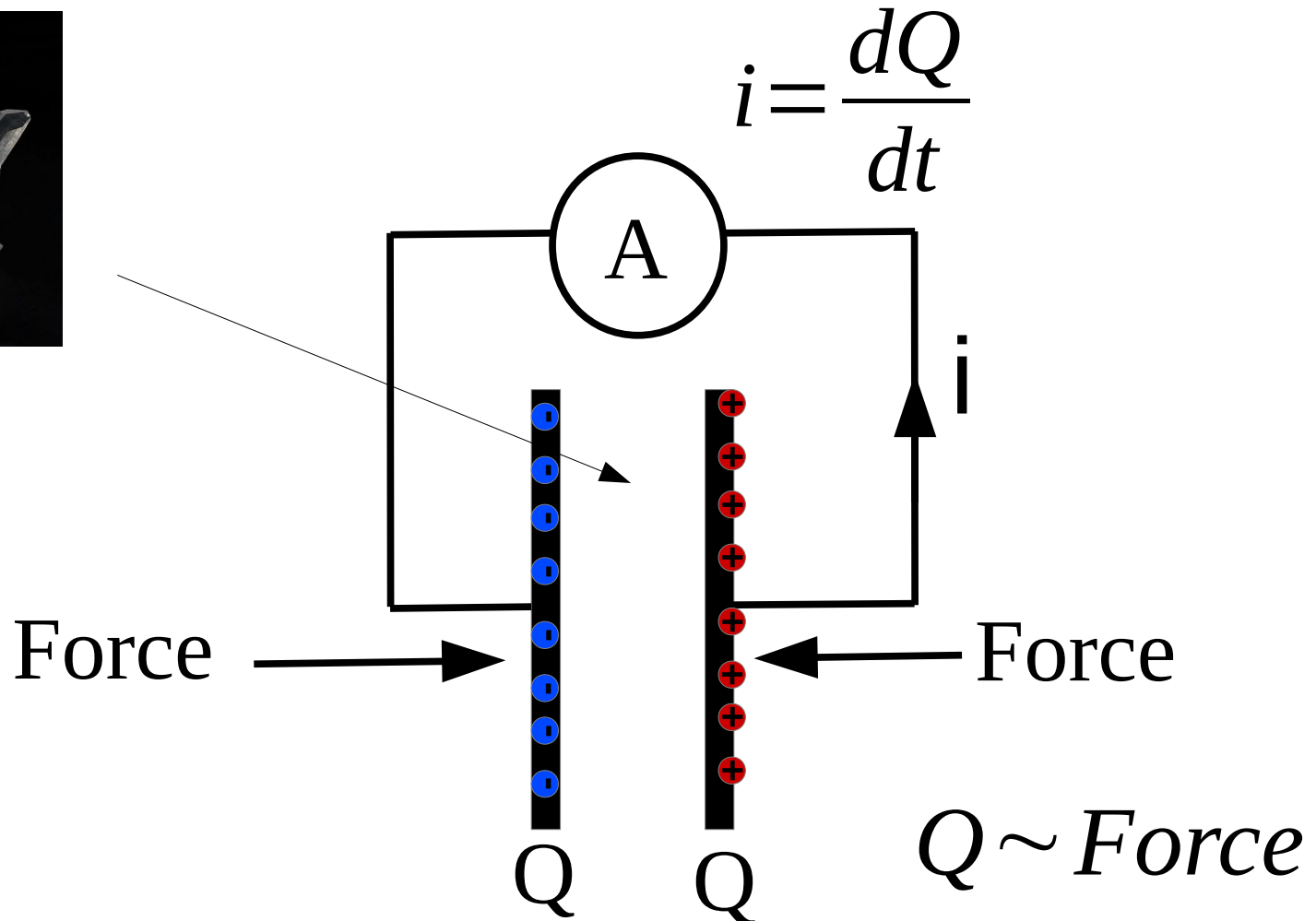
# You can think of a piezoelectric crystal as a capacitor



We can therefore we can write...

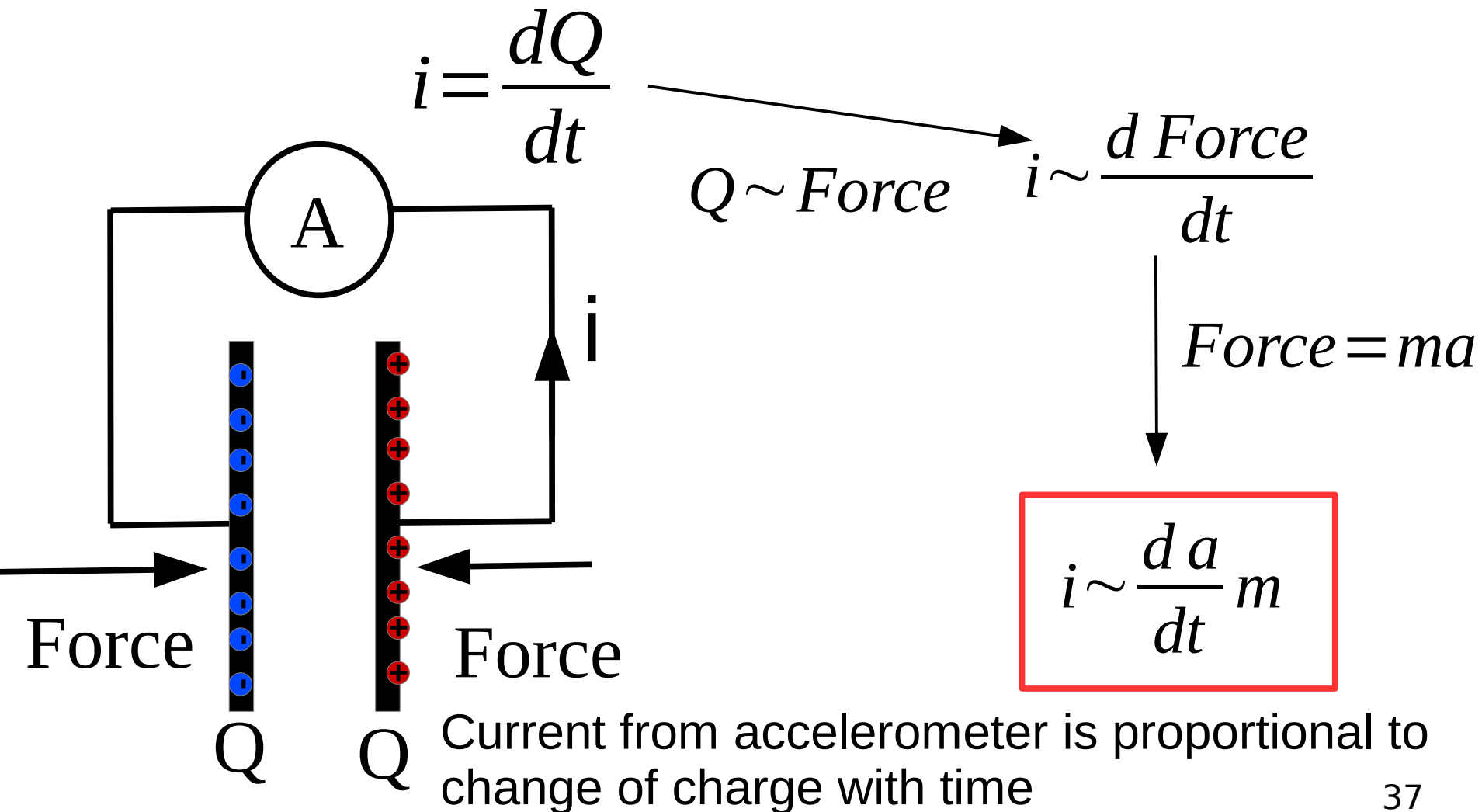

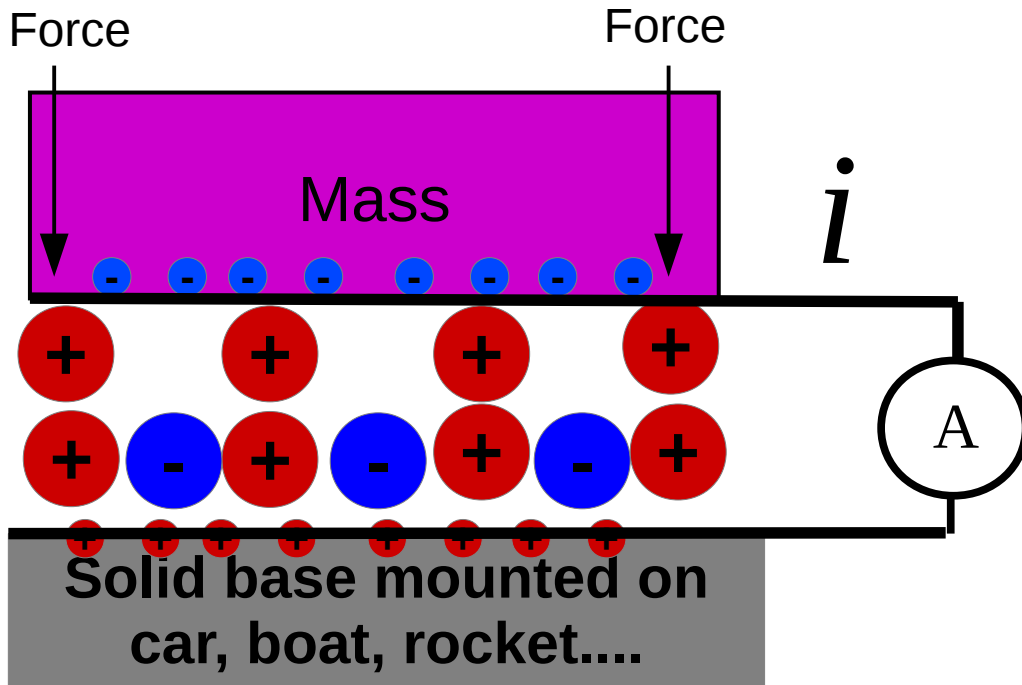
# How would you solve this equation for 'a'?



$$i \sim \frac{d \boxed{a}}{dt} m$$

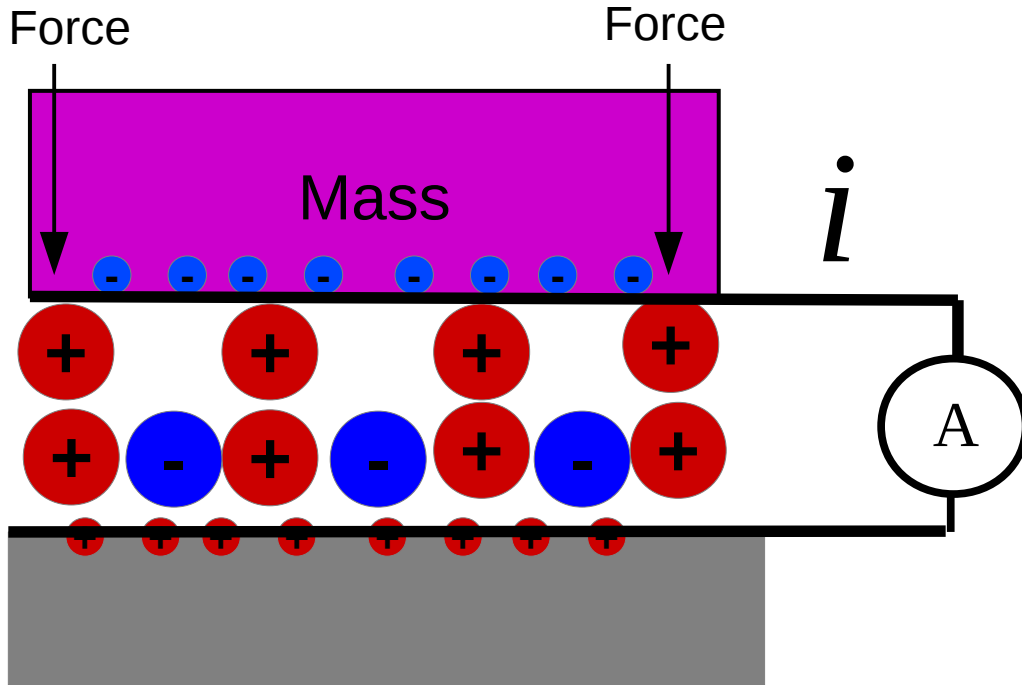To solve this equation we need to integrate...




$$i \sim \frac{d a}{d t} m$$



$$\frac{1}{m} \int i dt \sim a$$

- To calculate the acceleration we need to integrate the current.
- To do this we need an integrator circuit.....

# An op-amp based integrator circuit

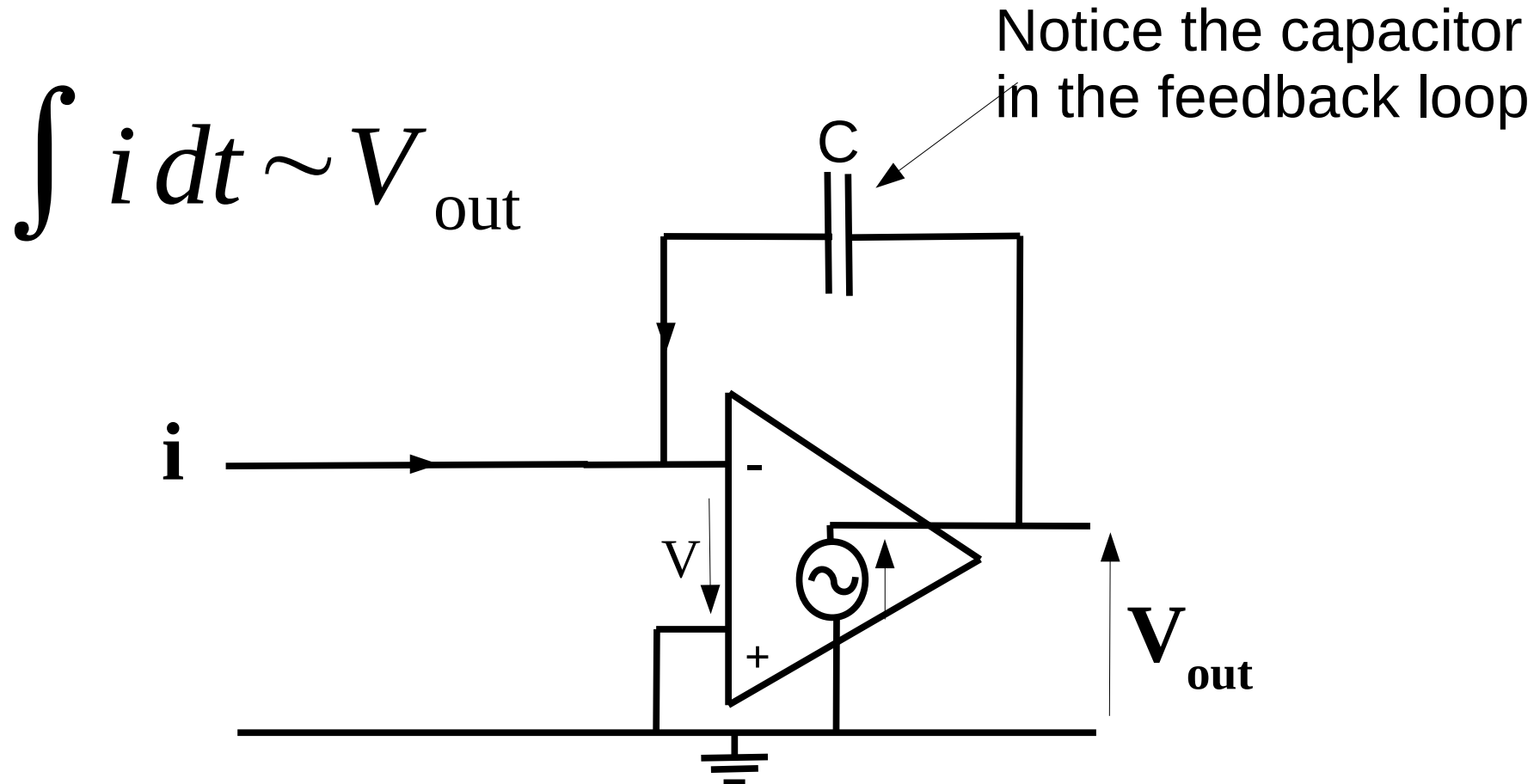


This will integrate current  $i$ , and  $V_{out}$  will be proportional to the sum of the integration.


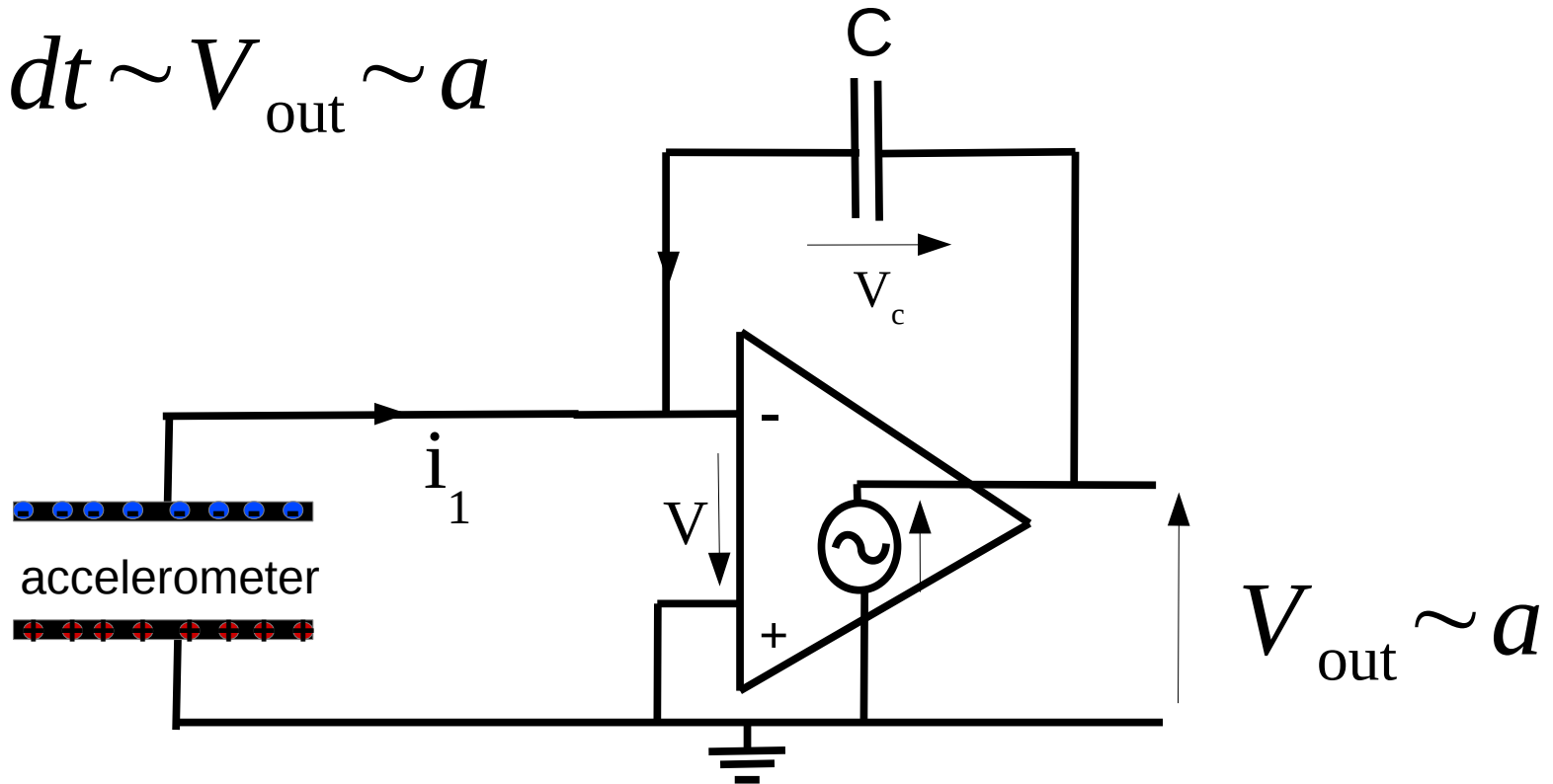
# An integrator circuit




$$\int i_1 dt \sim V_{\text{out}} \sim a$$


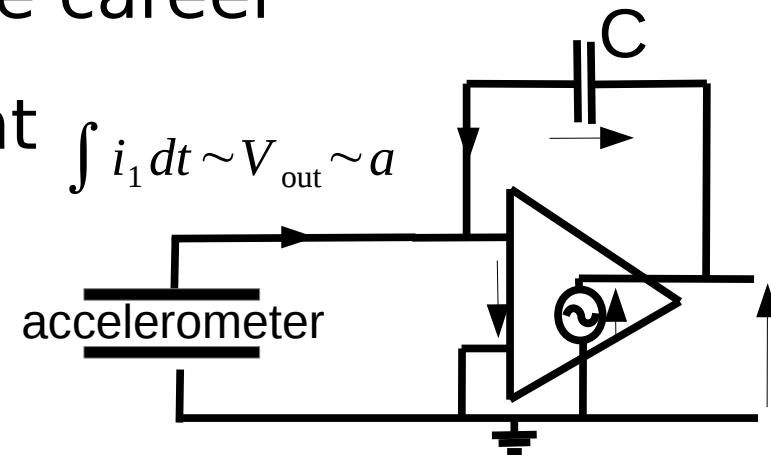
## Question

- How many people think understanding the accelerometer/integrator circuit is:
  - Boring and pointless
  - Important to my future career
  - Very important to my future career
  - Possibly the most important thing I will learn at university!!




# An example of an accelerometer and integrator circuit in action.



An example is in this Russian proton M rocket.




Pavel Kolotilov




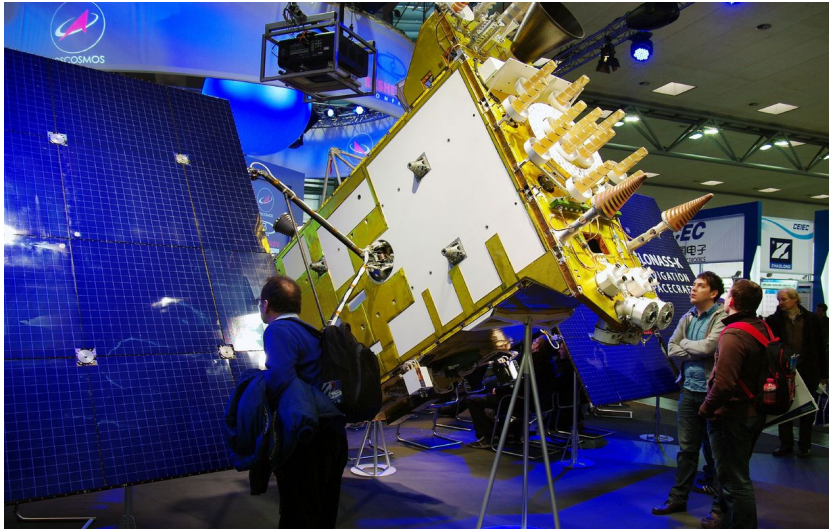


- GLONASS satellite (Russian GPS)
- On the 1<sup>st</sup> July 2013 it was put on top of a Proton M rocket - combined cost costs 4.4 billion rubles.

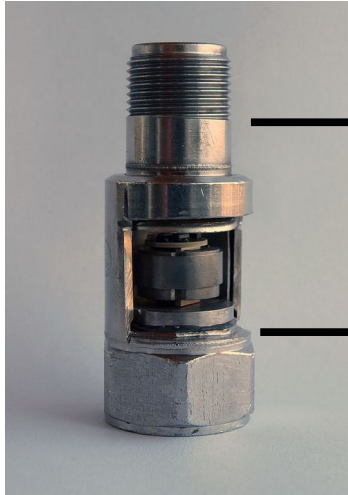An engineer coupled the accelerometer the wrong way around to the op-amp.



accelerometer

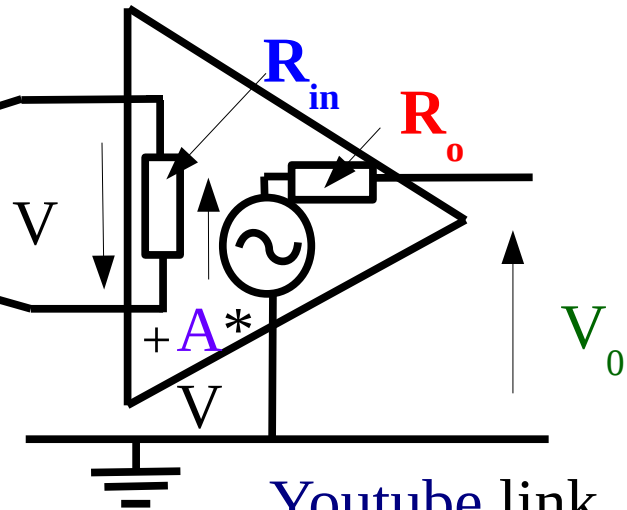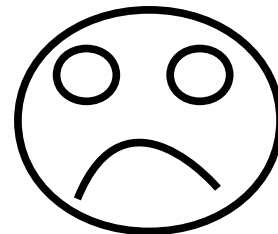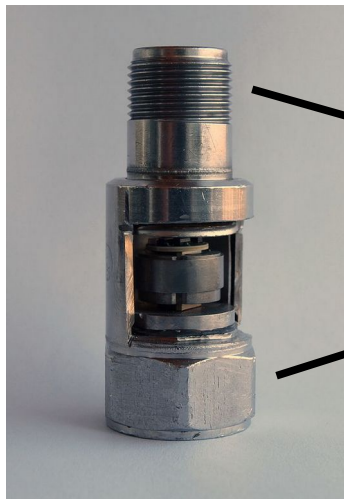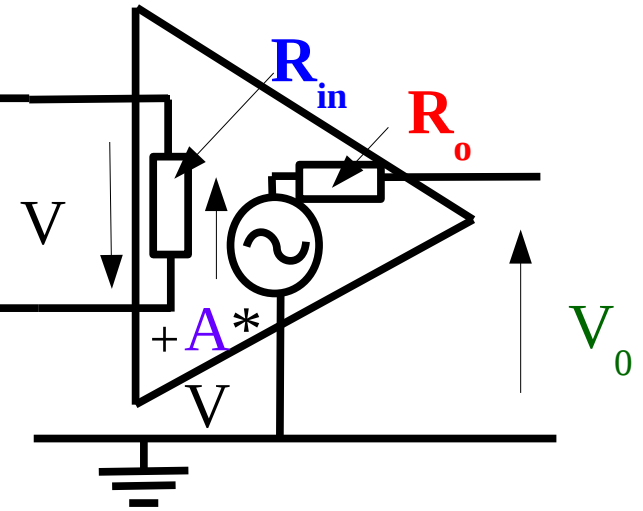

[Youtube link](#)

So..




- Op-amps in general are very important to know about and get correct.
- It's too important to just leave everything up to the electronic engineer.
- With this in mind we are going to spend a little time deriving the equation describing this circuit and linking acceleration to  $V_{out}$ .
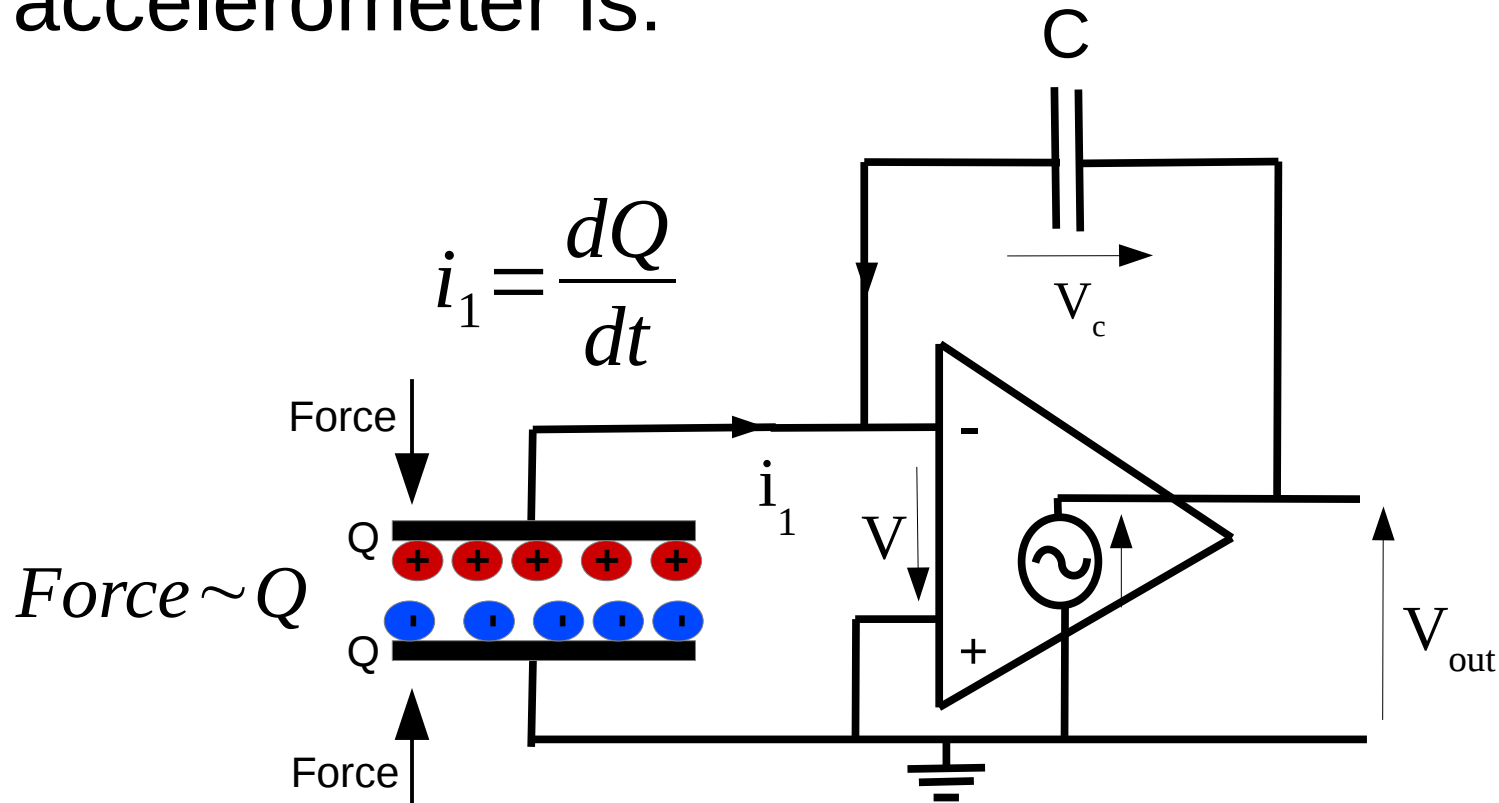
# An integrator circuit



Input current from the  
accelerometer is:



# Examine the current node at the inverting input



The amplifier has infinite input resistance so...  
 $i=0$ , therefore:


$$i_f = -i_1$$

But we already know..

$$i_1 = \frac{dQ}{dt}$$

Therefore,
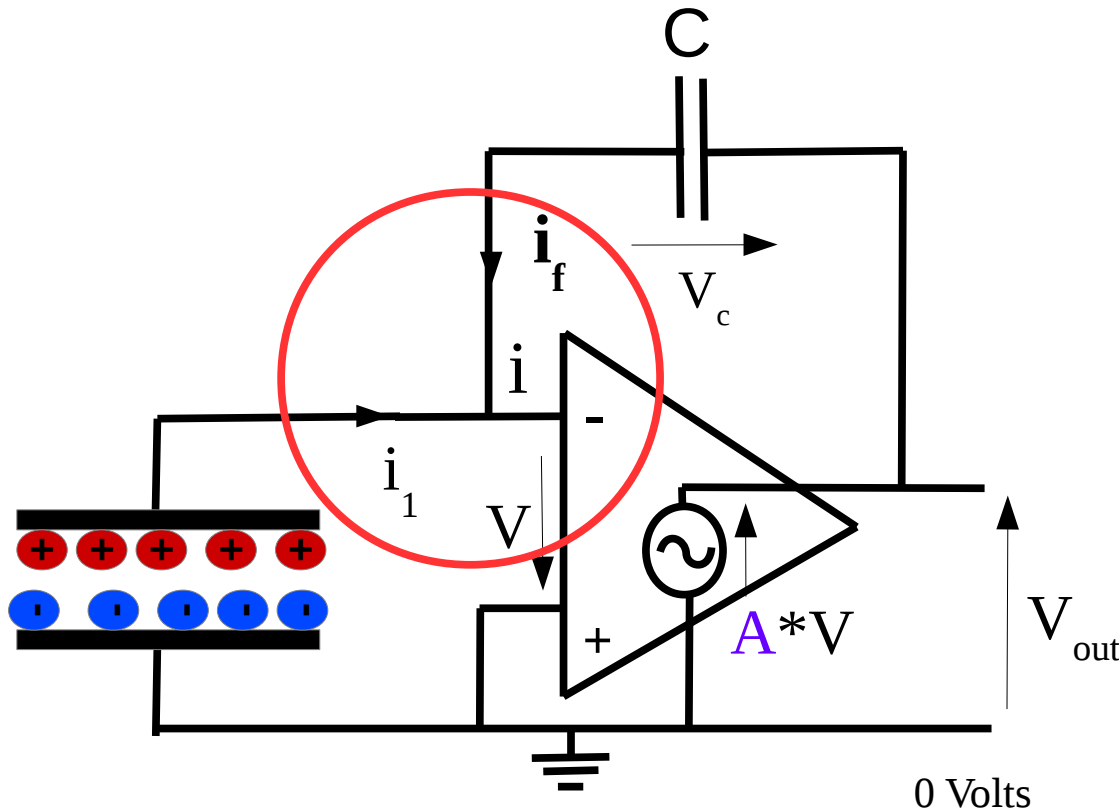
$$\textcircled{1} \quad i_f = -\frac{dQ}{dt}$$




# Examine the capacitor...

From your notes on capacitance:

$$i_f = C \frac{dV_c}{dt}$$

②

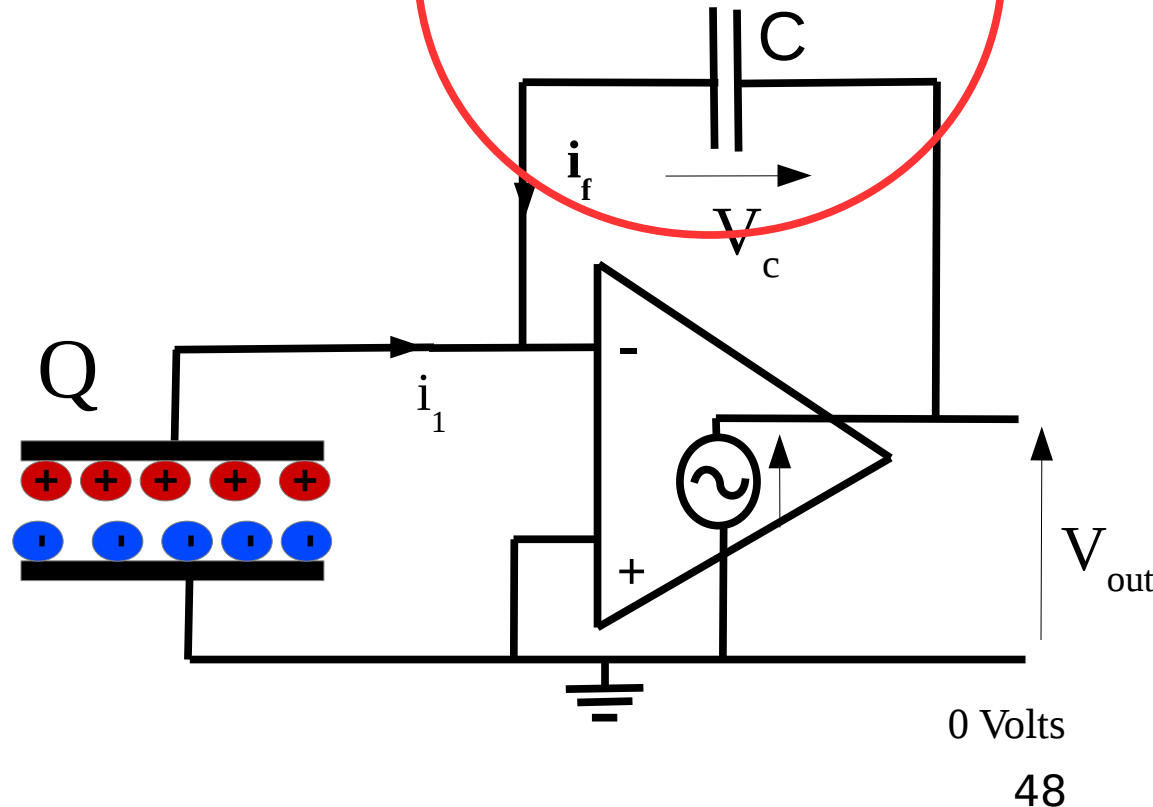



# Examine the capacitor...



From your notes on capacitance:

But we already know


$$\textcircled{1} \quad i_f = -\frac{dQ}{dt}$$

Equate equations 1 and 2

$$\frac{dQ}{dt} = -C \frac{dV_c}{dt}$$

$$\frac{dV_c}{dt} = -\frac{1}{C} \frac{dQ}{dt}$$

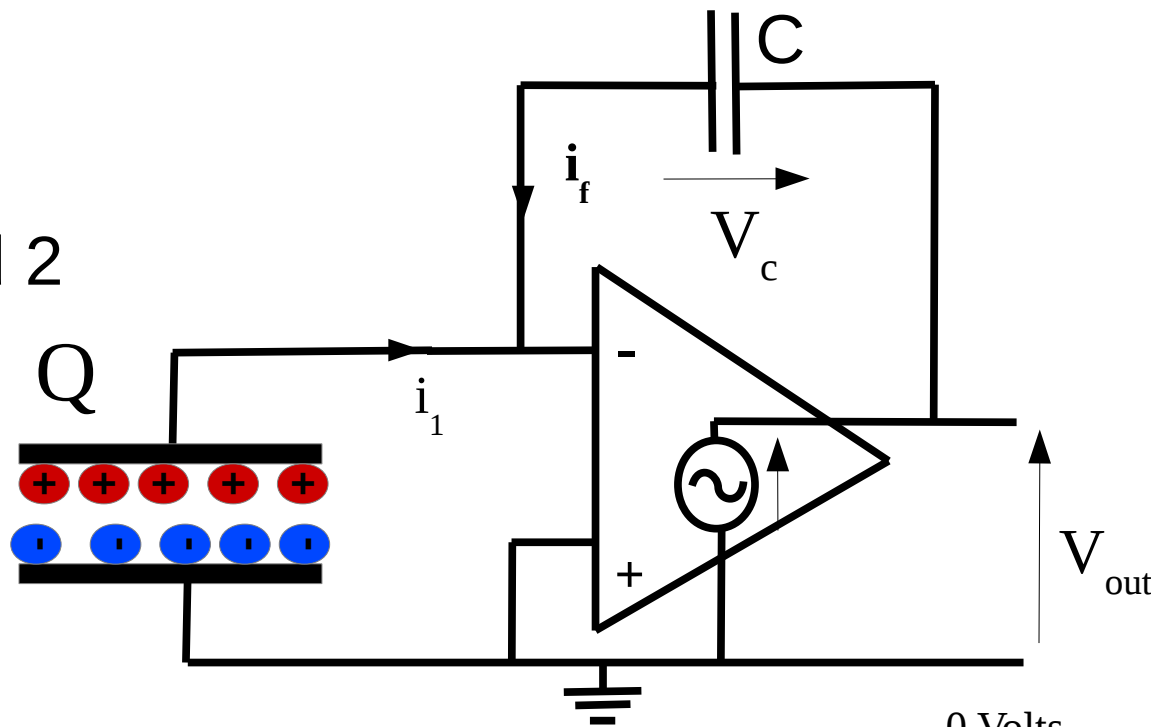
$$i_f = C \frac{dV_c}{dt} \quad \textcircled{2}$$


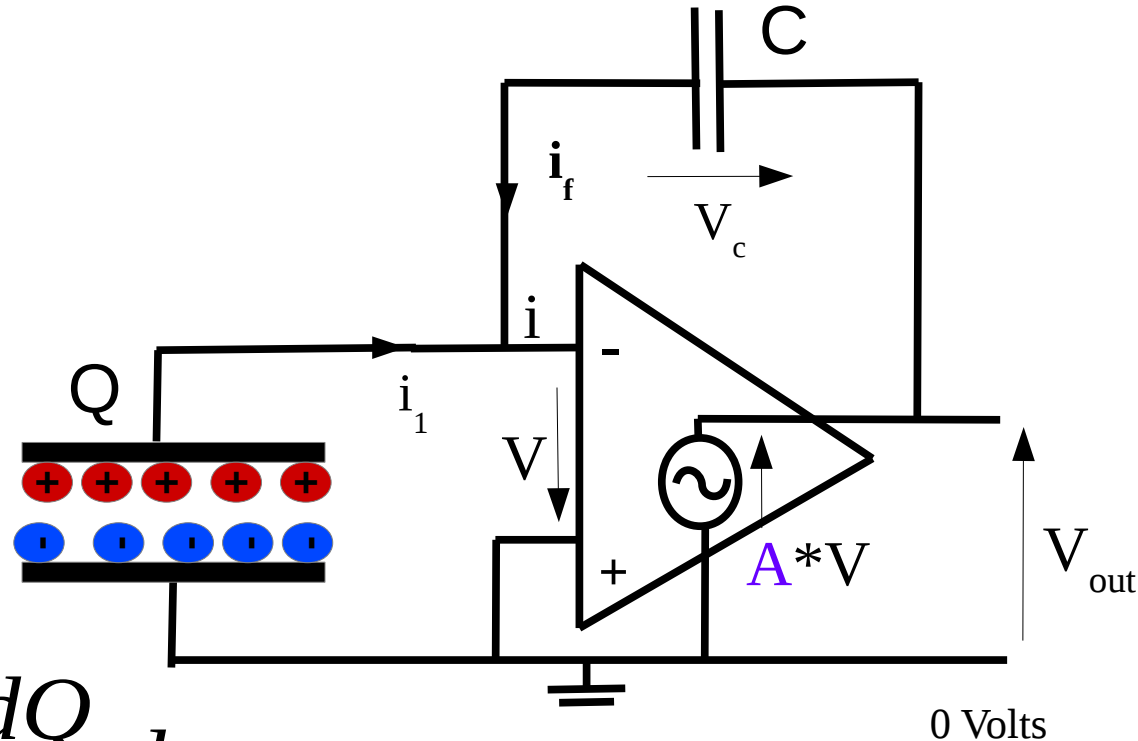
# Integrate both sides



$$\frac{dV_c}{dt} = -\frac{1}{C} \frac{dQ}{dt}$$



$$\int \frac{dV_c}{dt} dt = -\int \frac{1}{C} \frac{dQ}{dt} dt$$

$$V_c = -\frac{1}{C} Q$$

# Integrate both sides


$$V_c = -\frac{1}{C} Q$$

We also know that

$$V_c - V = V_{out}$$

and

$$V_{out} = AV$$

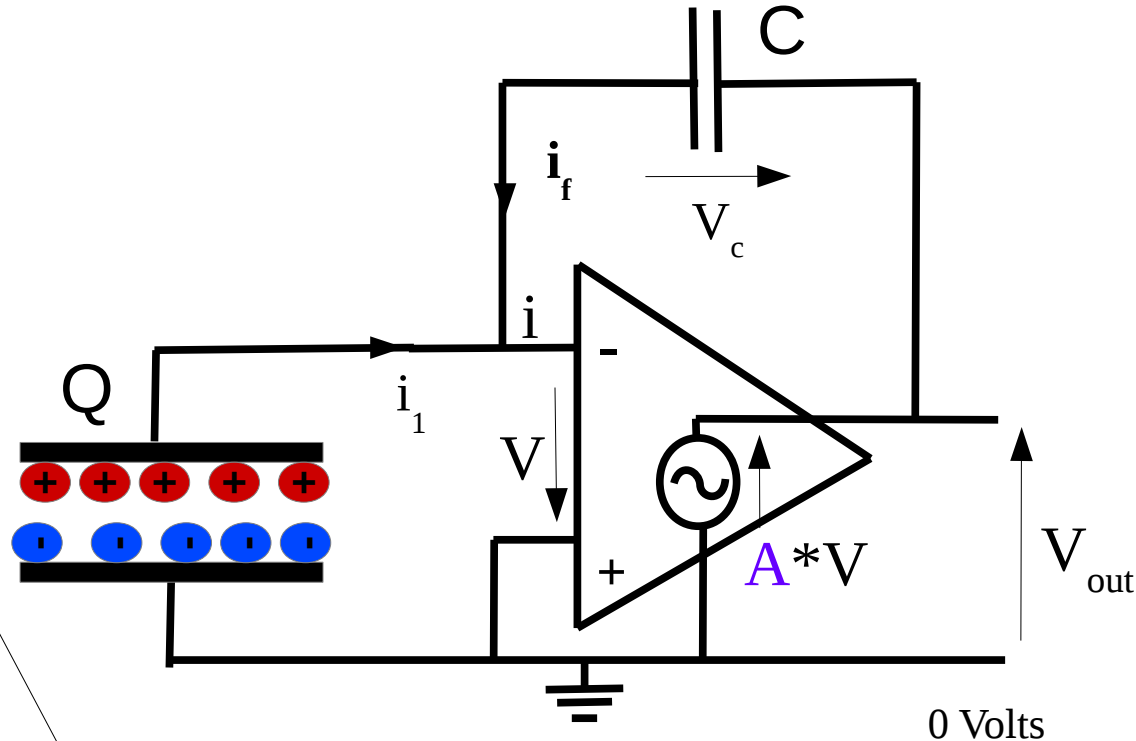

$$-\frac{1}{C} Q - \frac{V_{out}}{A} = V_{out}$$

# The final step...



$$-\frac{1}{C} Q - \frac{V_{out}}{A} = V_{out} \quad V = \frac{V_{out}}{A} \rightarrow 0$$


However, A is very large so we can write

Therefore,

$$V_{out} = -\frac{1}{C} Q$$

Amplifier output voltage

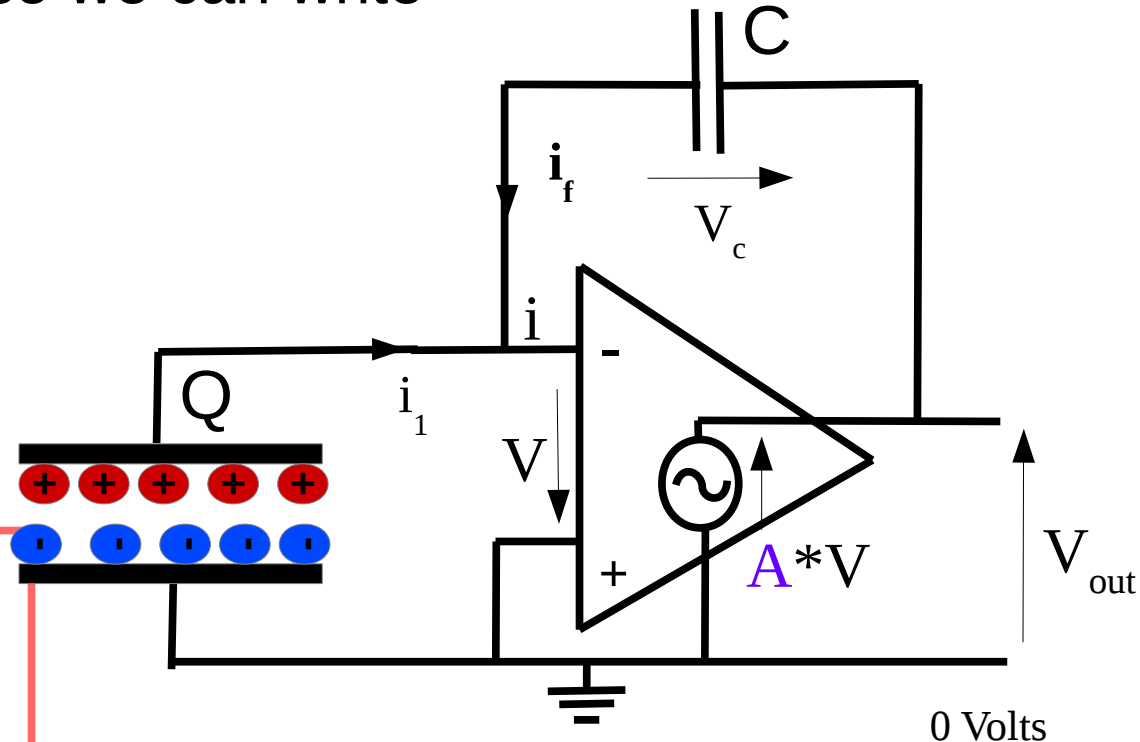
$$V_{out} = -\frac{Q}{C} \sim \frac{F}{C} \sim \frac{a}{C}$$






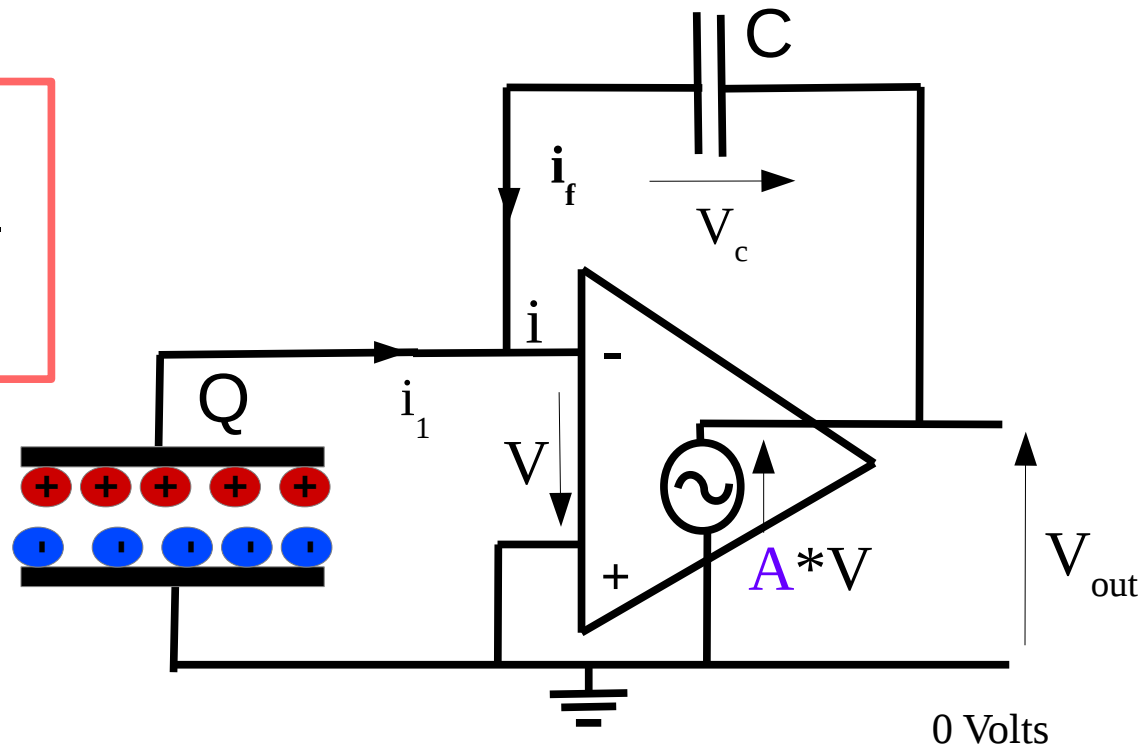
# Question:

If you wanted to make your circuit more sensitive to small changes in acceleration (or  $Q$ ) what would you change?

$$V_{\text{out}} = -\frac{Q}{C} \sim \frac{F}{C} \sim \frac{a}{C}$$


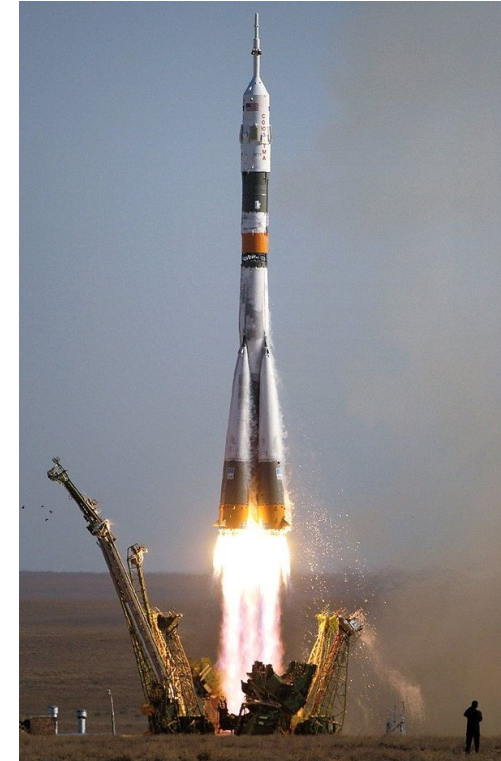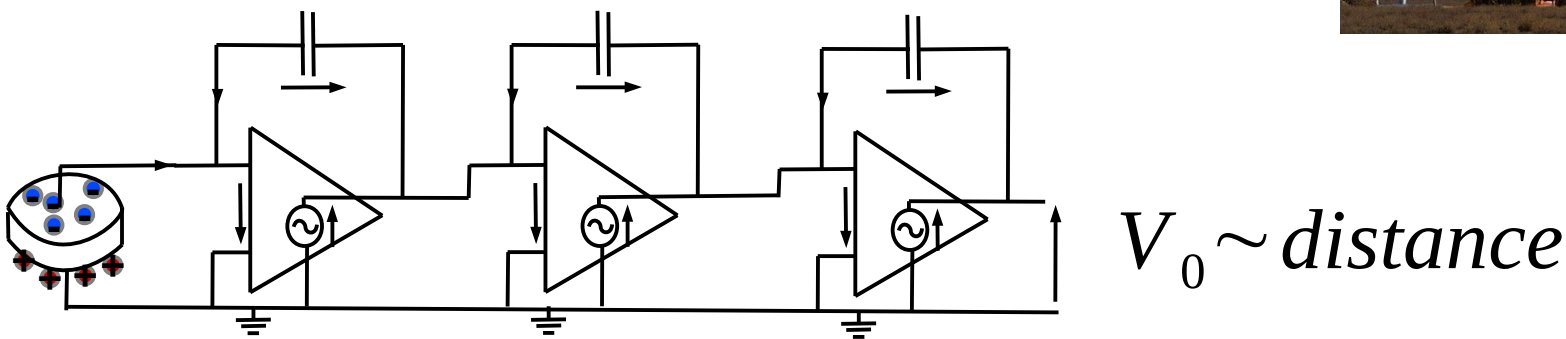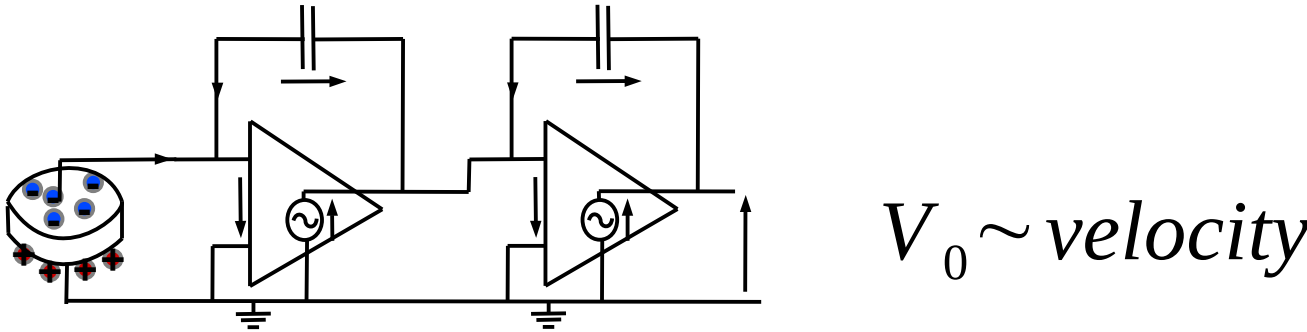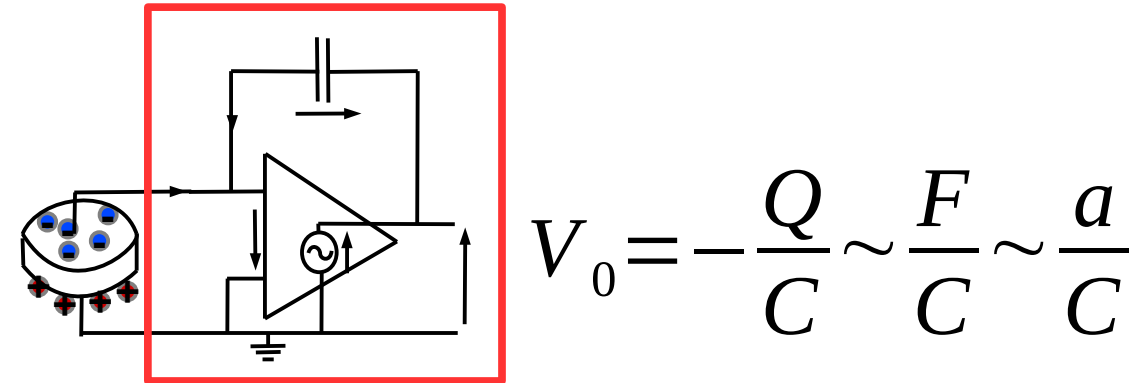
# We can cascade these integrator elements






# Outline of the lecture




- Recap of last lecture
- Mini Quiz
- Books and resources
- Op-amps used in the real world**
  - Measuring acceleration
  - Measuring stress and strain.**
- Summary

# A strain gauge

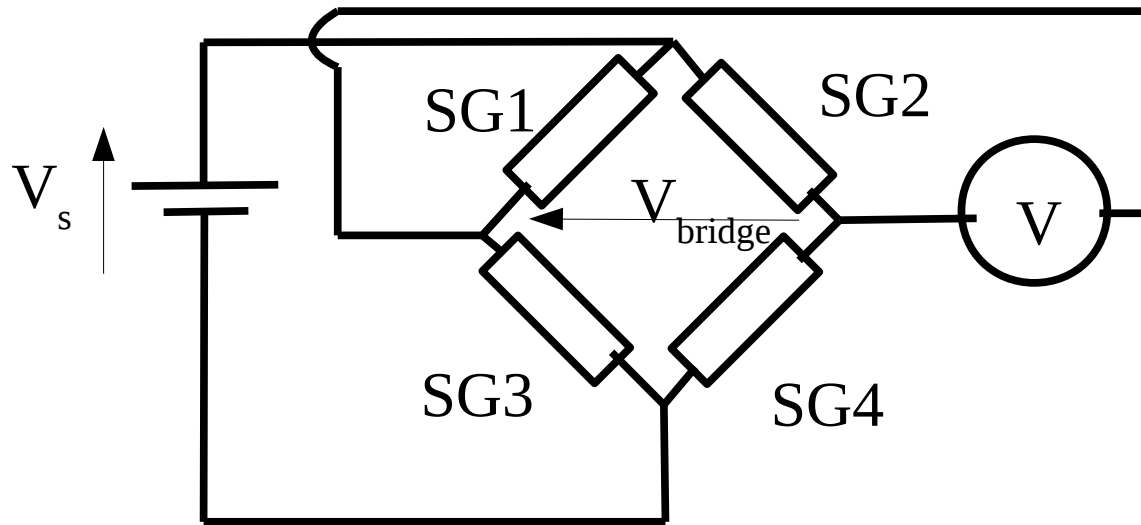


•The voltage  $V_{bridge}$  is very small...  
so we need to amplify it..

•And what do we use to amplify  
it?????

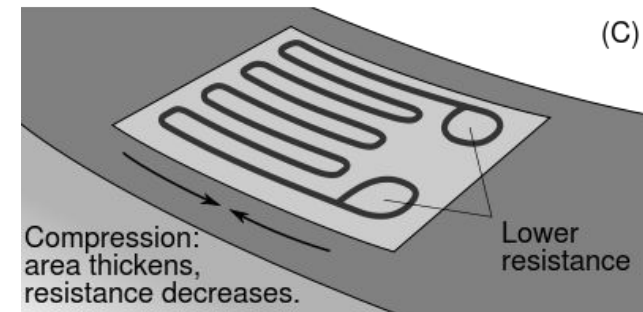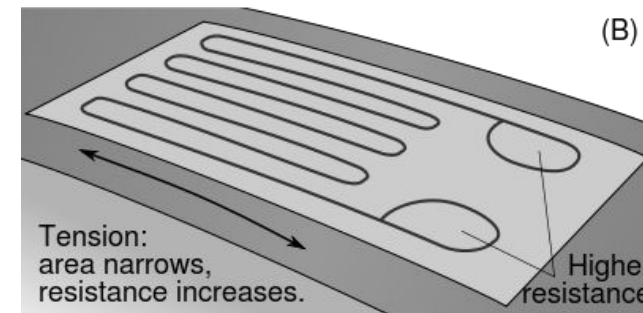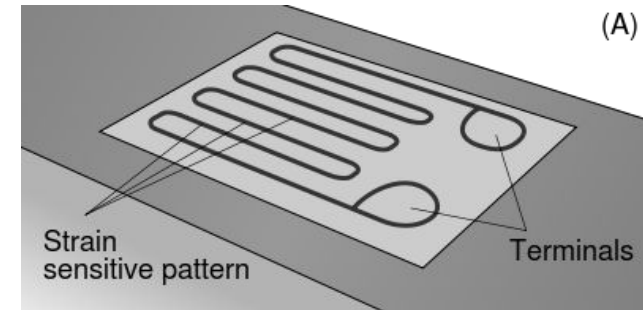


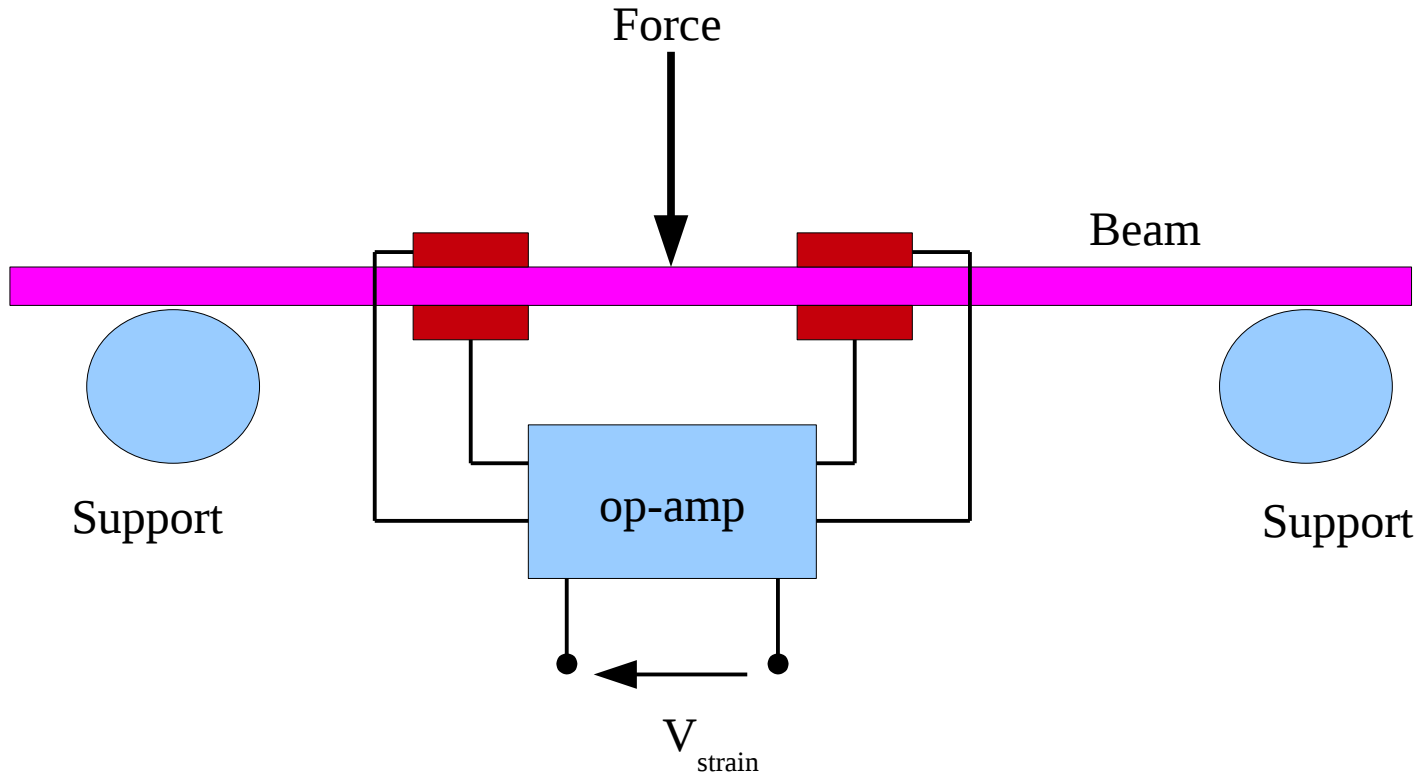
# Application of op-amps to strain gauges..




Practical applications could be measuring strain on an aeroplane wing.

Video of lab....


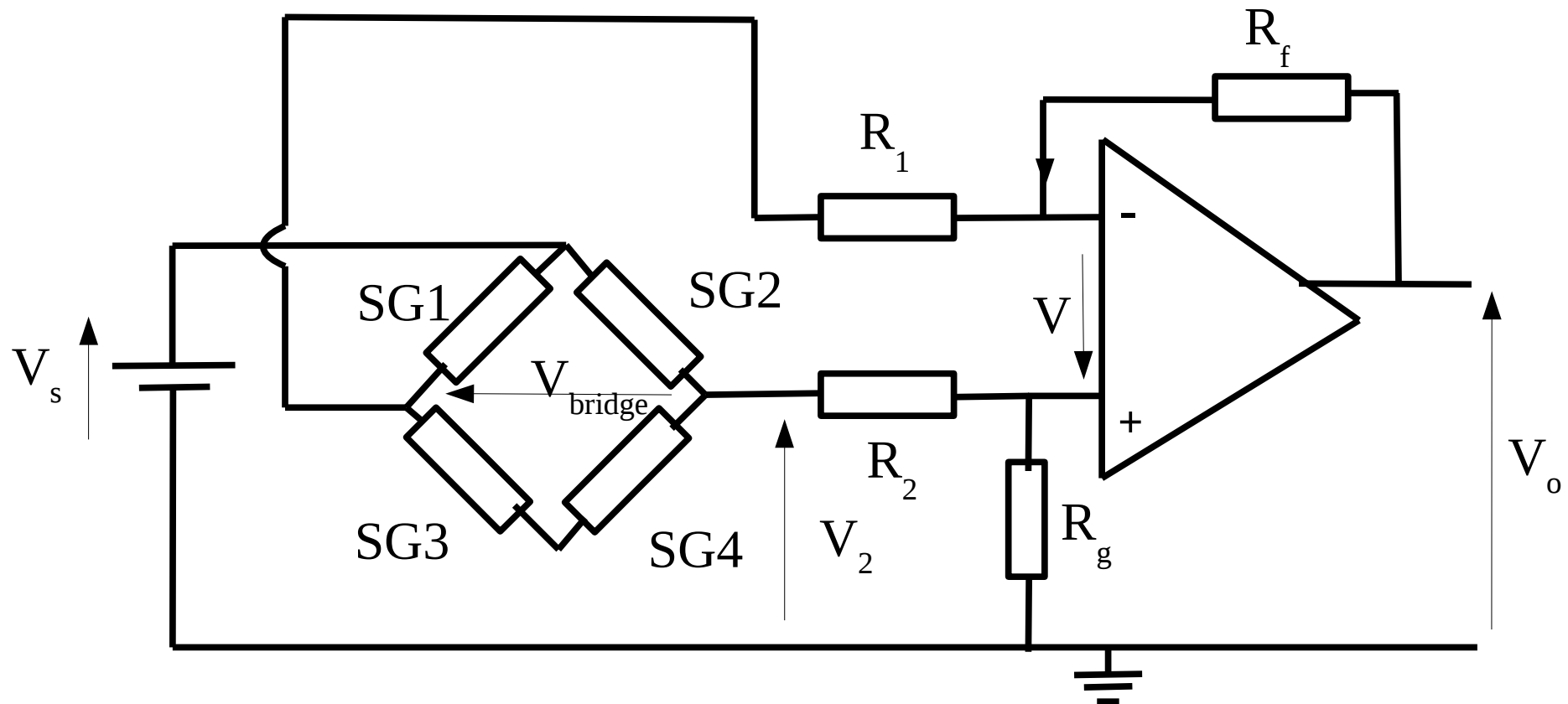
# Using an op-amp to amplify the output of a strain gauge



We need to derive an expression relating  $V_{\text{bridge}}$  to  $V_{\text{out}}$ .

# Relate the inputs to the outputs




The general idea is to write expressions **relating the input terminals to the inputs of the op-amp.**

Then to write an expression relating the **input terminals of the op-amp to the output of the op-amp.**


Let's have a go..
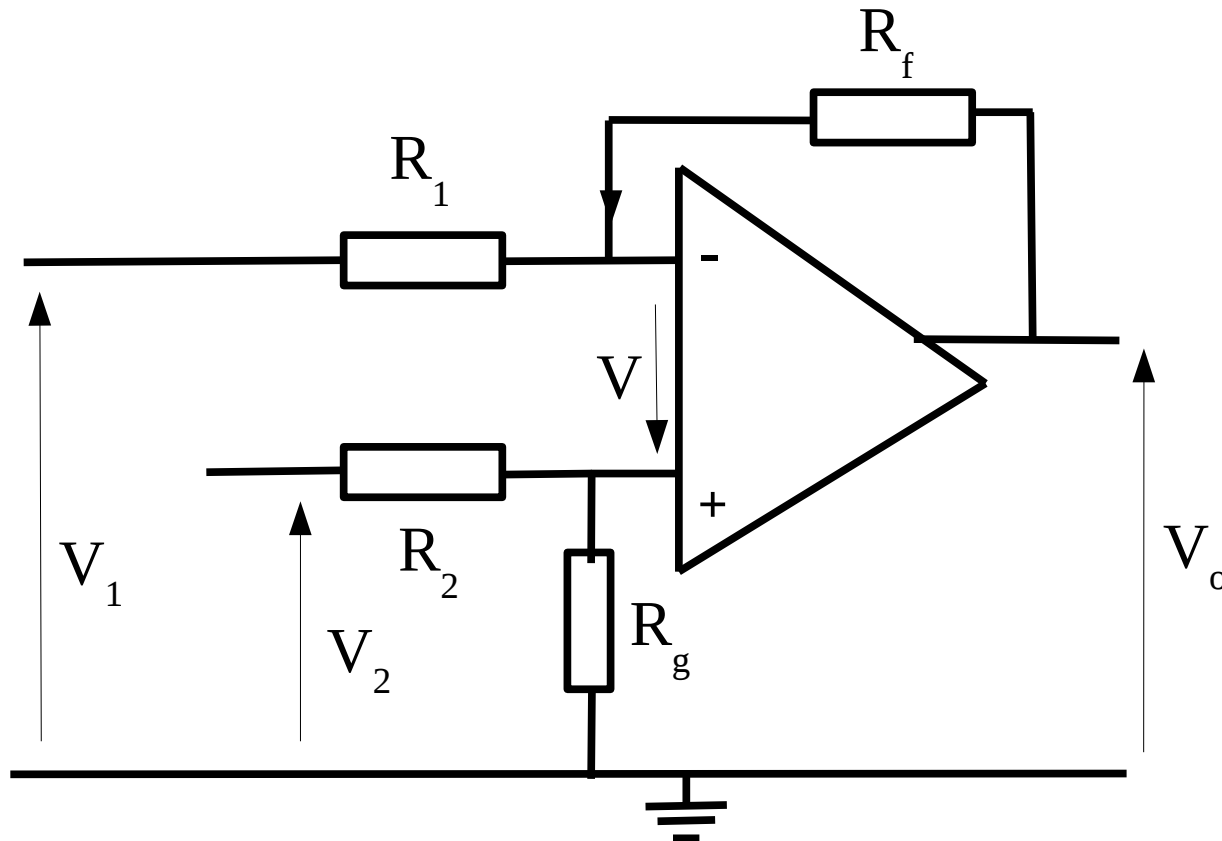
# Let's just start off by looking at the op-amp.



Write on all current and voltage arrows.
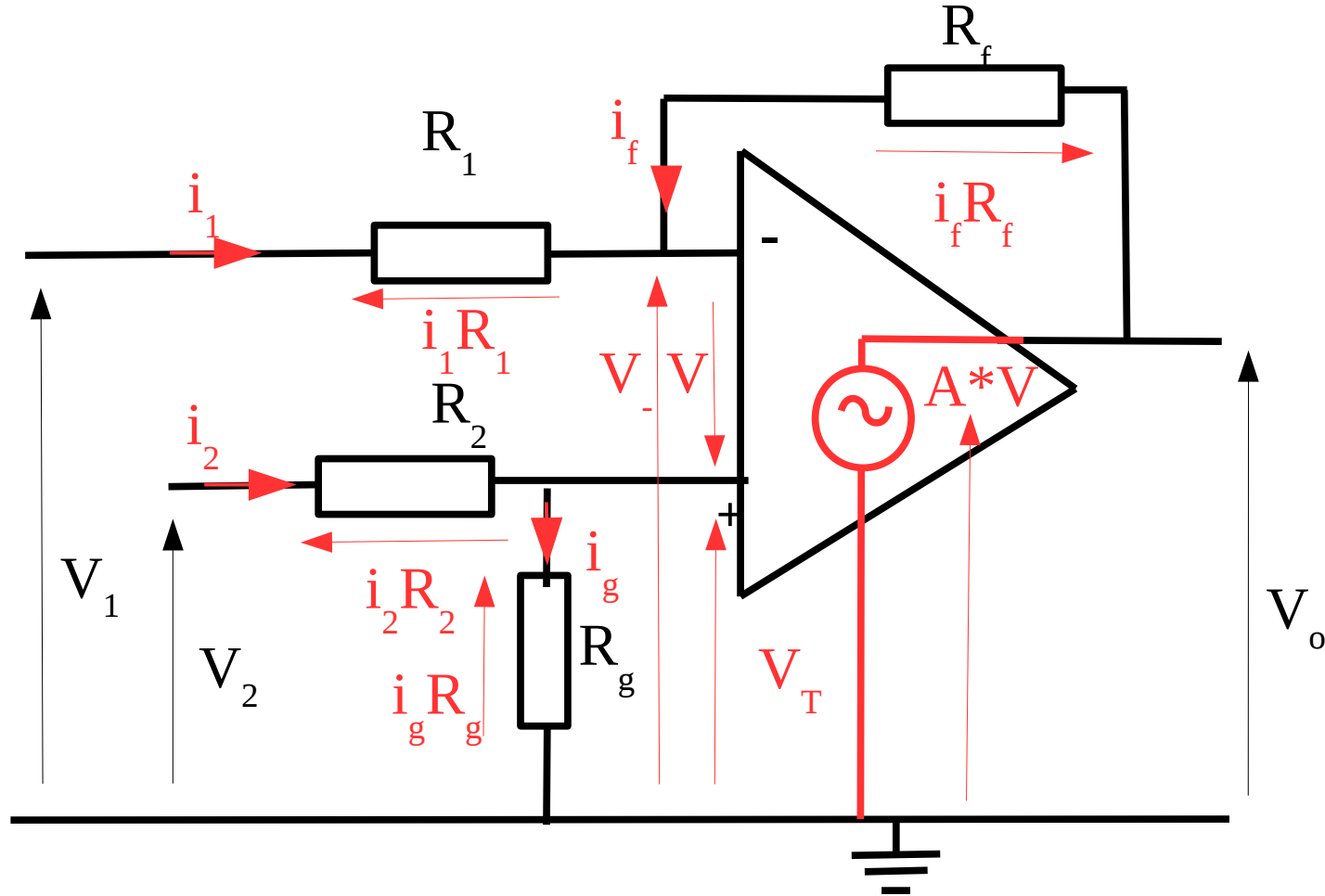
# Annotate the diagram with arrows, currents and voltages



**First write an expression relating  $V_1$  of the circuit to the inverting input of the op-amp.**

$$V_- = V_1 - i_1 R_1$$

$$i_1 = \frac{V_1 - V_-}{R_1} \quad 1$$


$$V_- = V_0 - i_f R_f$$

$$i_f = \frac{V_0 - V_-}{R_f} \quad 2$$

Equating equation 1 and 2

$$i_f = -i_1$$
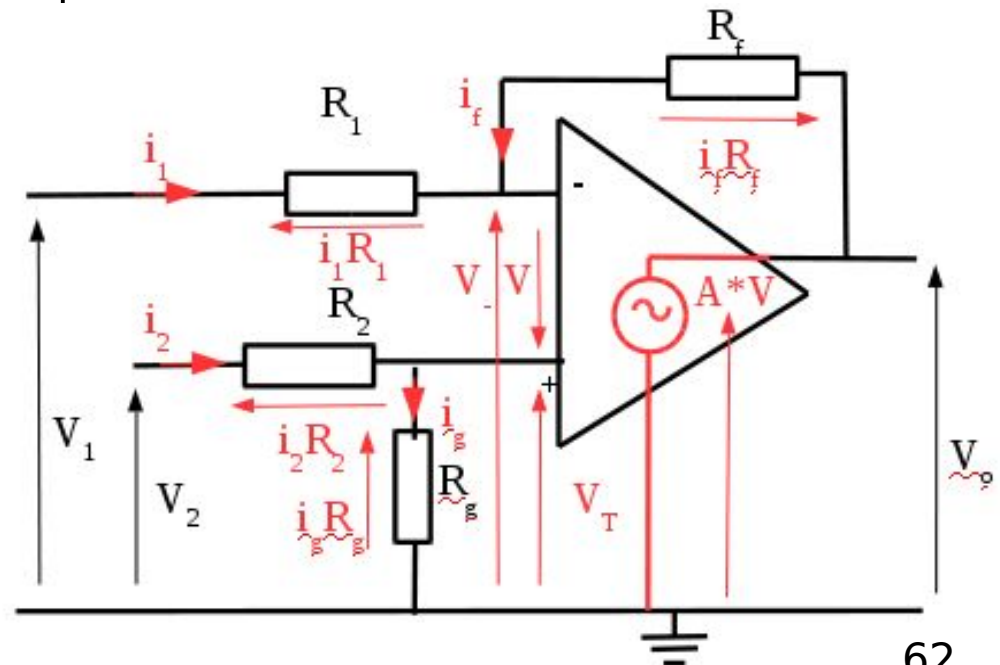
$$\frac{V_1 - V_-}{R_1} = \frac{V_1 - V_0}{R_f}$$



Rearrange the equations to get the voltage  $V_-$

$$\frac{V_1 - V_-}{R_1} = \frac{V_1 - V_0}{R_f}$$

$$V_1 R_f - V_- R_f = V_1 R_1 - V_0 R_1$$

$$V_1 R_f + V_0 R_1 = V_- [R_1 + R_f]$$

$$V_- = \frac{V_1 R_f + V_0 R_1}{R_1 + R_f}$$


**Then write an expression relating input  $V_2$  to the non-inverting input of the op-amp.**

As the input resistance of the op-amp  $R_{in} = \infty$

$$i_g = i_2$$

And  $R_2$  and  $R_g$  from a potential divider

$$V_+ = \frac{R_g}{R_2 + R_g} V_2$$

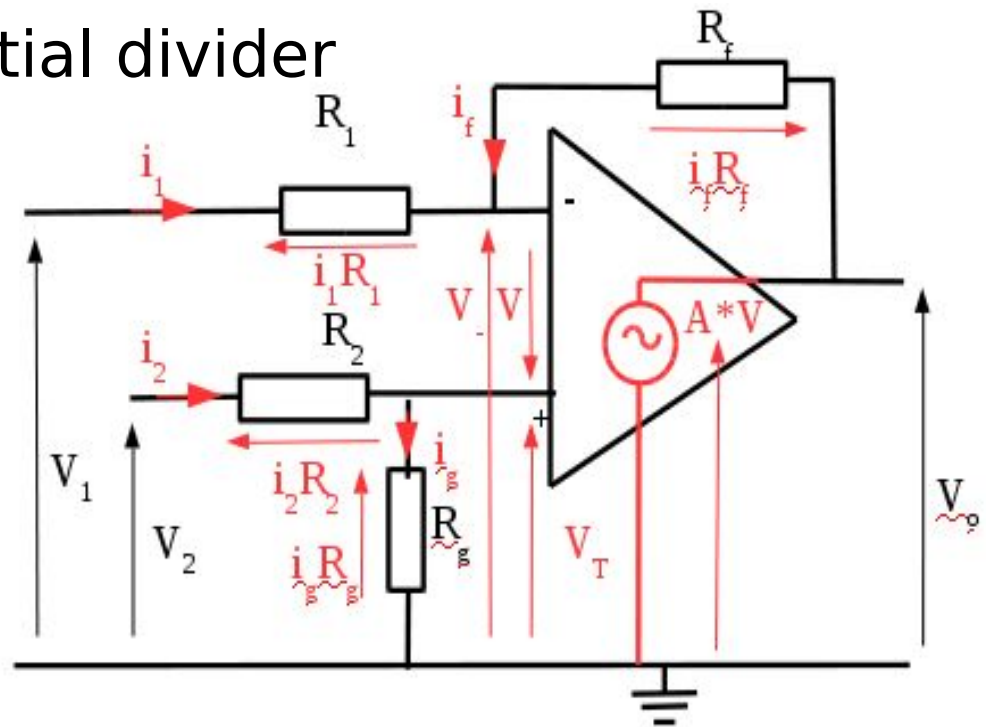




# Now write an expression relating the inputs of the op-amp to the output of the circuit

We know that,  $V_0 = VA$  5

We also know,  $V = V_+ - V_-$  4

Therefore  $\frac{V_0}{A} = V_+ - V_-$

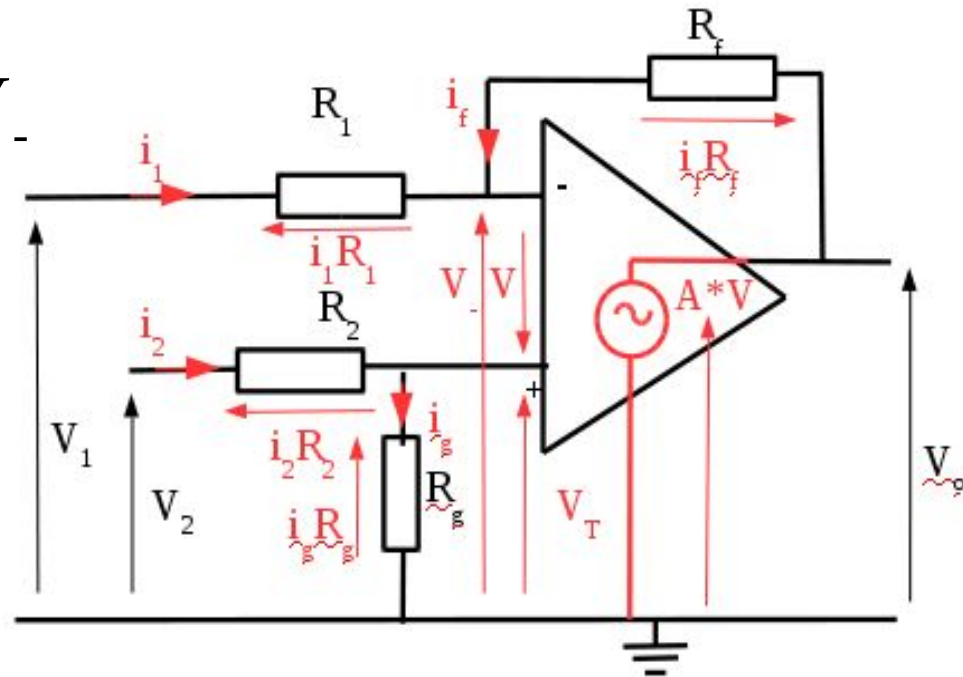We now have an expression **relating the inputs of the op-amp to the output** and we have **expressions relating the input terminals to the inputs of the op-amp.**



# Recap and rearranging our equations.....

$$\frac{V_0}{A} = V_+ - V_- \quad V_- = \frac{V_1 R_f + V_0 R_1}{R_1 + R_f} \quad V_+ = \frac{R_g}{R_2 + R_g} V_2$$

Substituting 3,4 and 6 in 5 we get

$$\frac{V_0}{A} = \left[ \frac{R_g}{R_2 + R_g} \right] V_2 - \left[ \frac{V_1 R_f + V_0 R_1}{R_1 + R_f} \right]$$

$$V_0 \left[ \frac{1}{A} + \frac{R_1}{R_1 + R_f} \right] = V_2 \left[ \frac{R_g}{R_2 + R_g} \right] - V_1 \left[ \frac{R_f}{R_1 + R_f} \right] \quad 7$$

# Let's make a few assumptions..



$$V_0 \left[ \frac{1}{A} + \frac{R_1}{R_1 + R_f} \right] = V_2 \left[ \frac{R_g}{R_2 + R_g} \right] - V_1 \left[ \frac{R_f}{R_1 + R_f} \right]$$

If  $A \gg 0$ ,  $R_2 = R_1$  and  $R_g = R_f$


Which is generally true for difference amplifiers

$$V_0 \left[ \frac{R_1}{R_1 + R_f} \right] = V_2 \left[ \frac{R_g}{R_2 + R_g} \right] - V_1 \left[ \frac{R_f}{R_1 + R_f} \right]$$

$$V_0 [R_1] = V_2 [R_f] - V_1 [R_f]$$

$$V_0 = [V_2 - V_1] \frac{R_f}{R_1}$$

# Questions

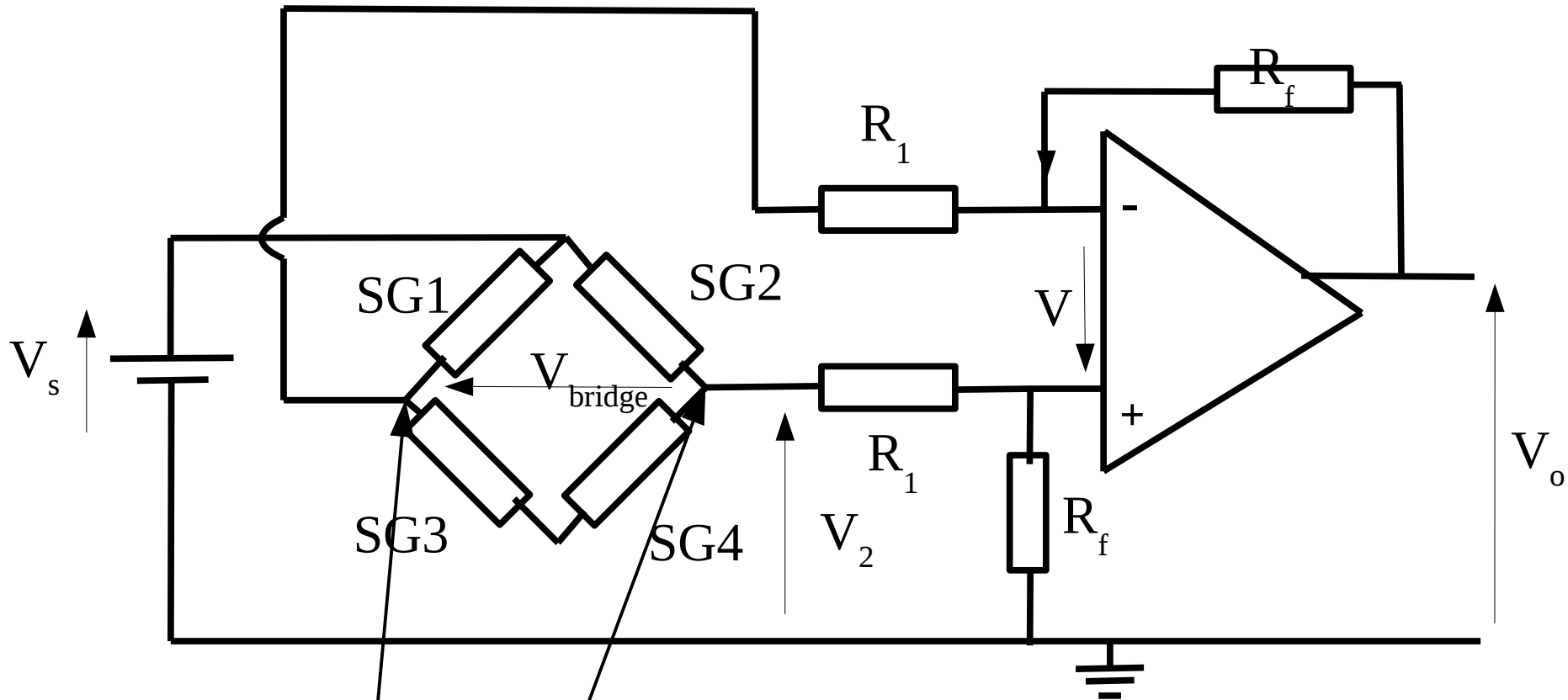

$$V_o = [V_2 - V_1] \frac{R_f}{R_1}$$



## Typical exam question:

- a) Explain why you would need to use an operational amplifier when using a strain gauge?
- b) Your strain gauge is attached to an operational amplifier with  $R_1=R_2=10\text{ k}\Omega$  and  $R_g=R_f=1\text{ M}\Omega$  calculate the output voltage when the wheatstone bridge produces  $0.1\text{ V}$  across it.

$$V_0 = [V_2 - V_1] \frac{R_f}{R_1}$$

a) Strain gauges produces very small voltages which need to be amplified.

b)  $R_1 = R_2 = 10 \text{ k}\Omega$                        $R_1 = R_2 = 1 \text{ M}\Omega$


Therefore

$$V_0 = [V_2 - V_1] \frac{1 \times 10^6}{1 \times 10^4}$$


$$V_0 = 100 [V_2 - V_1]$$

# Summary

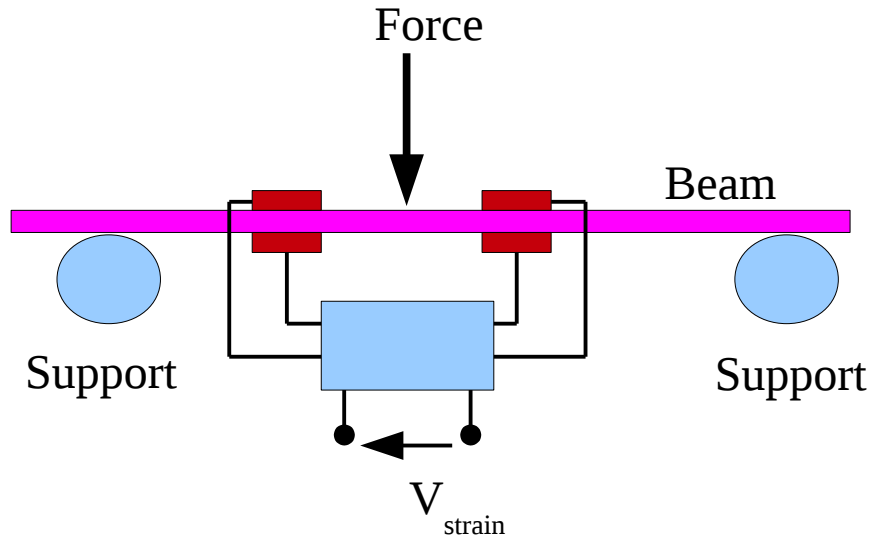**We can now analyse the circuit for strain gauges and accelerometers**



**Strain gauge**

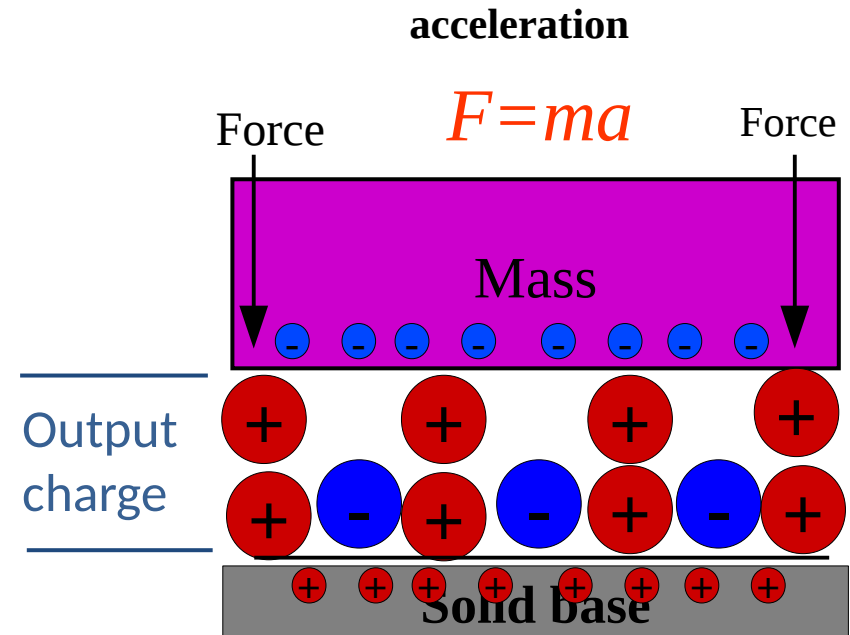

**Accelerometer**