

# **Electromechanical devices MM2EMD**

## **Lecture 6 - Diodes (How to power my device I have just designed).**

**Dr. Roderick MacKenzie**

**roderick.mackenzie@nottingham.ac.uk**

**Summer 2015**



**@rcimackenzie**

Released under  **creative  
commons**

- **Recap of last lecture**
- Introduction to diodes
- Power diodes – the basics.
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode
- Other kinds of diodes including Solar cells
- Summary

# Recap: Being able to measure acceleration is important



$$\int \text{acceleration } dt = \text{velocity}$$

$$\int \text{velocity } dt = \text{position}$$

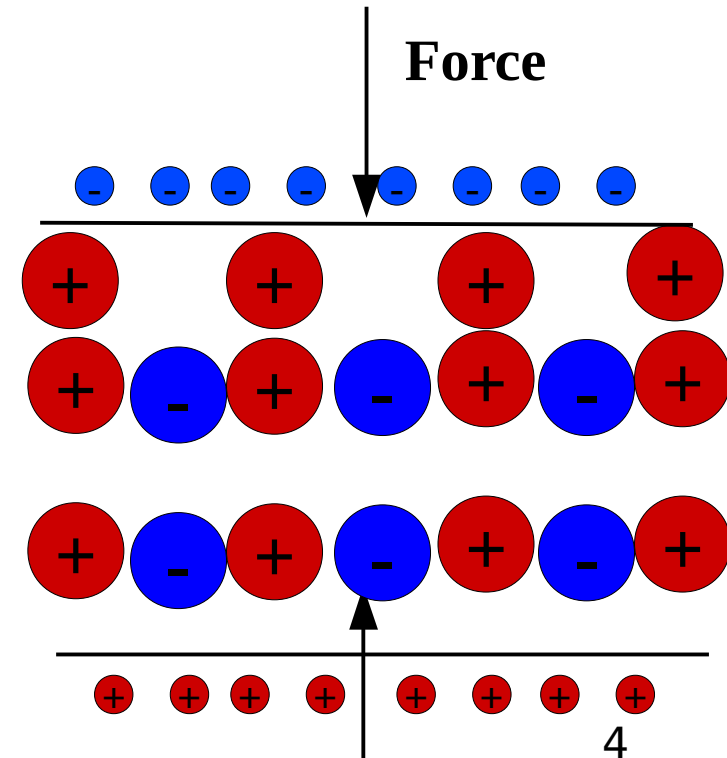
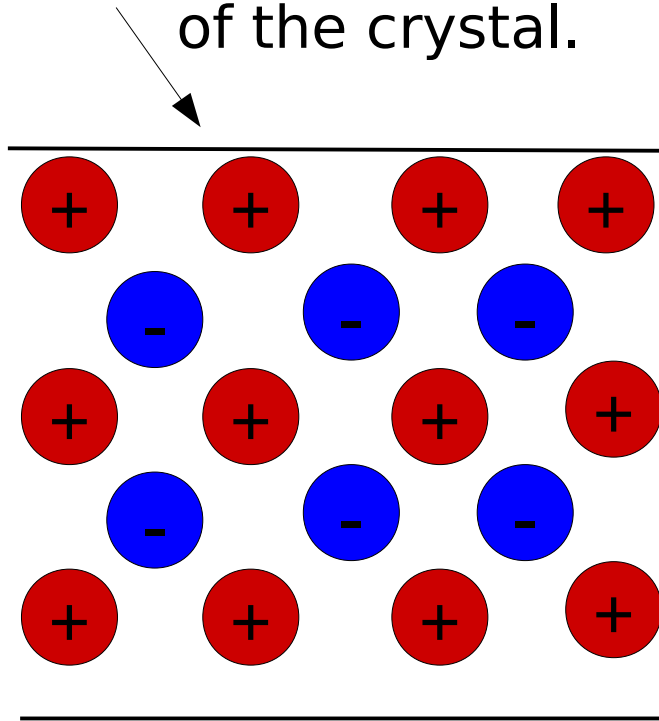
# Recap: Quartz for measuring acceleration





JJ Harrison



- Normally quartz has a regular arrangement of positive and negative ions
- However, when a force is applied, the lattice is distorted and charge forms on the surface of the crystal.


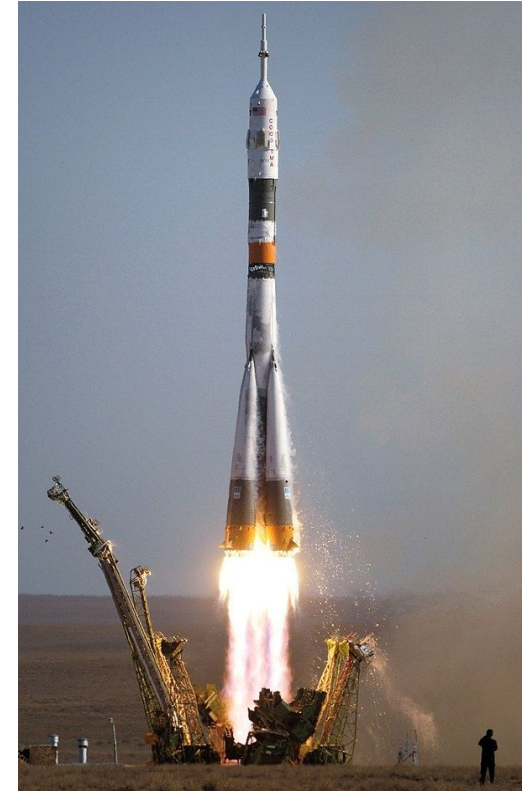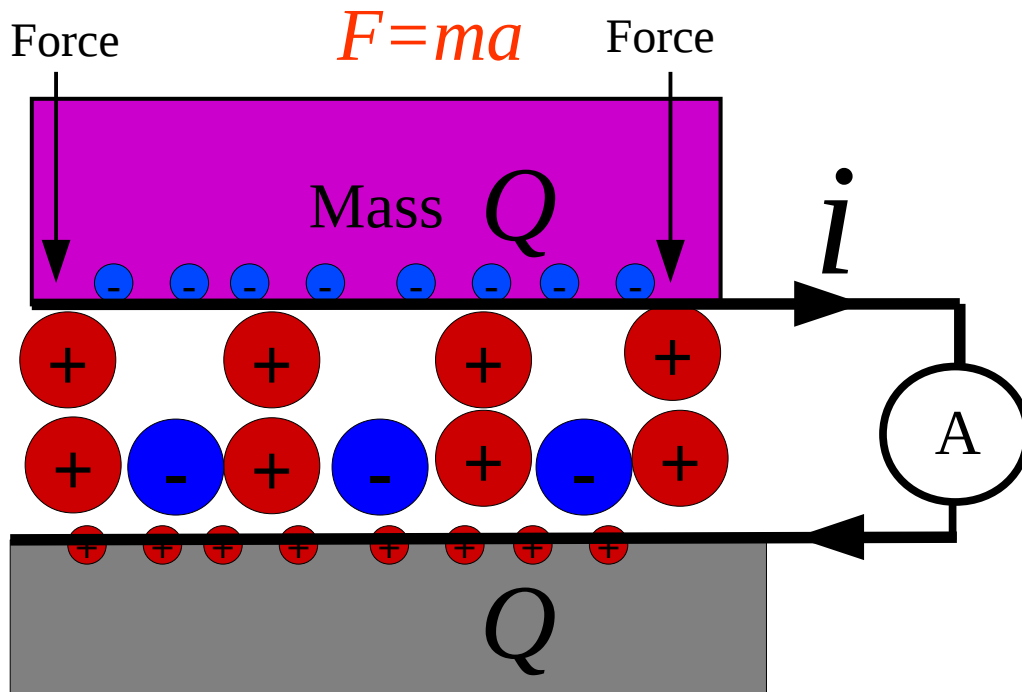
# Recap: Accelerometers and piezoelectric crystals




$$Q \sim F \sim a \longrightarrow i \sim \frac{d\boxed{a}}{dt} m \longrightarrow \boxed{\frac{1}{m} \int i dt \sim a}$$
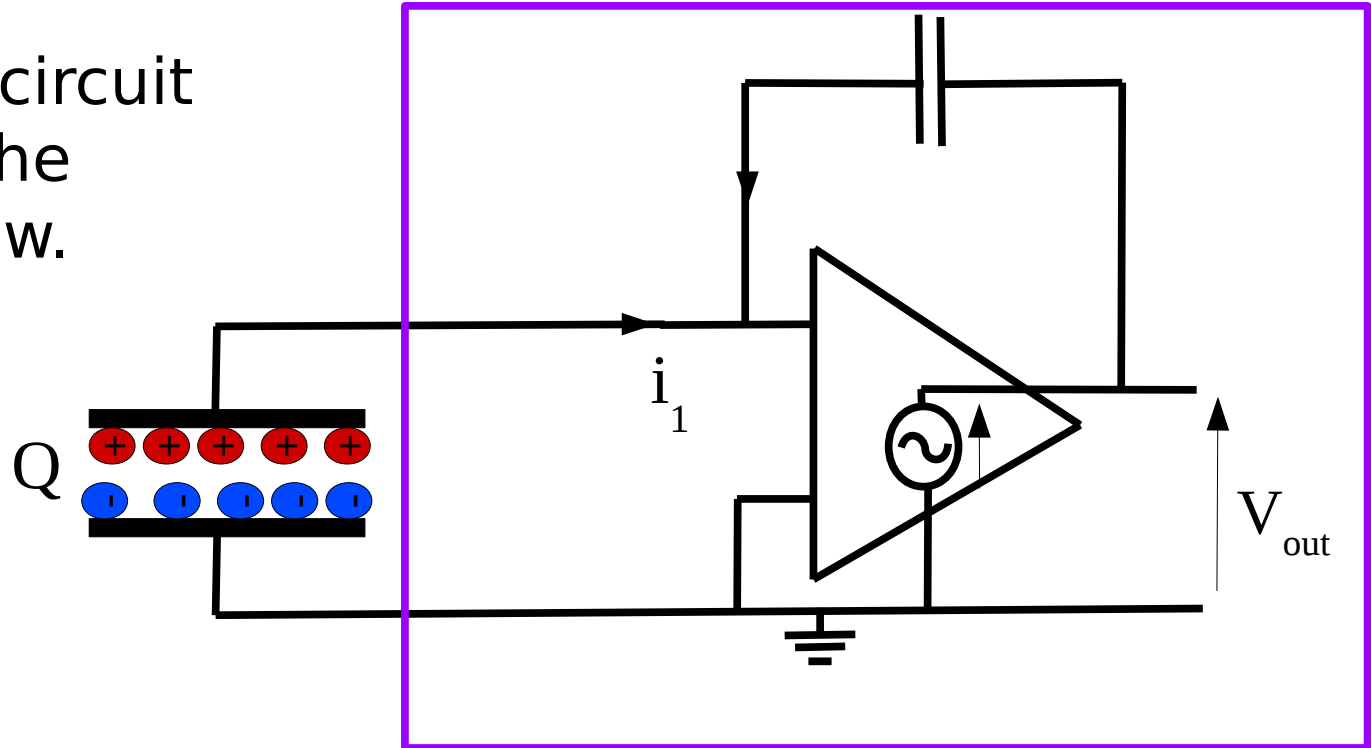
# Recap: To do the integration we need an integrator circuit






We drew this circuit and derived the equation below.



Integrator circuit

$$V_0 = -\frac{Q}{C} \sim \frac{F}{C} \sim \frac{a}{C}$$
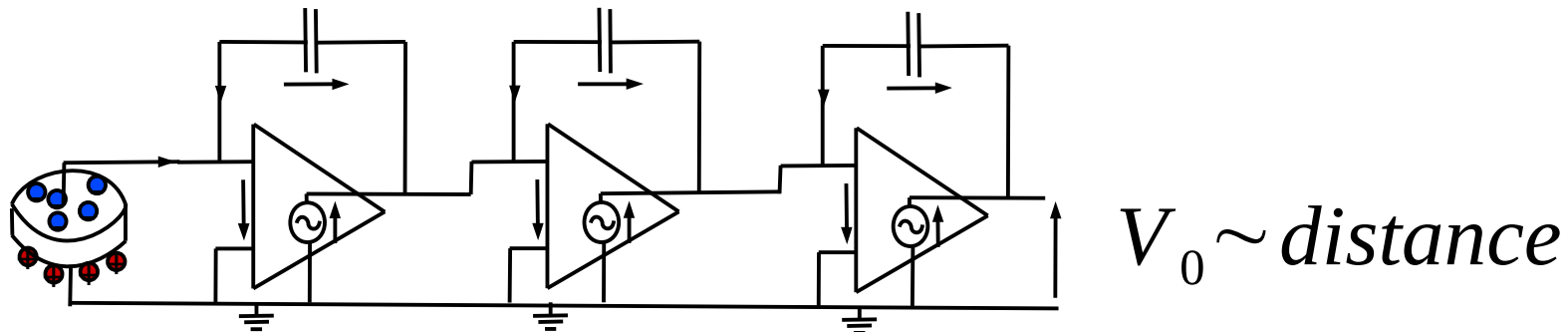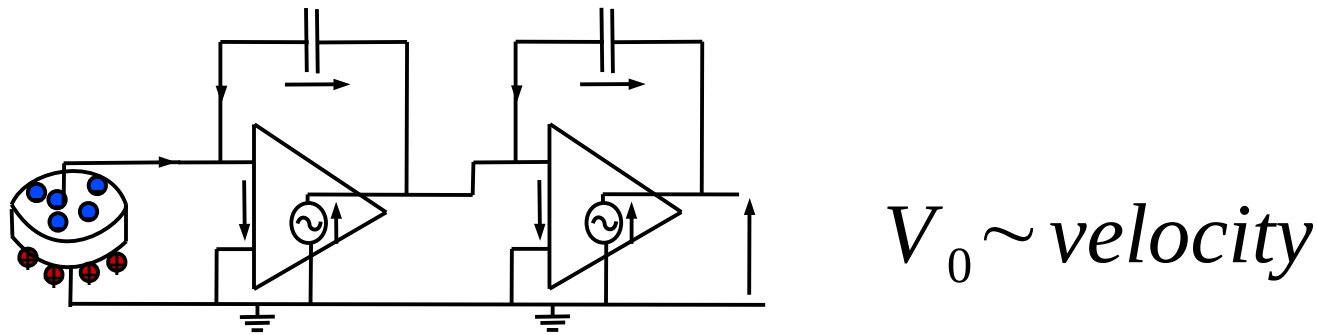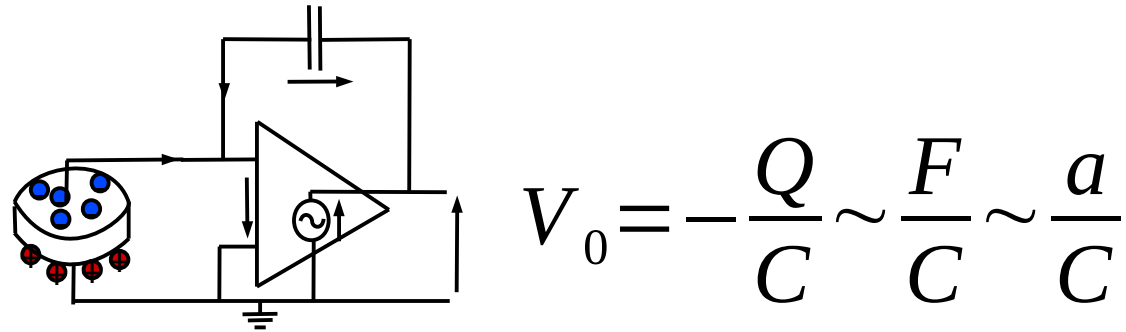
# Recap: We can cascade these integrator elements to get







# Recap: All engineers must know about op-amps and accelerometers :)







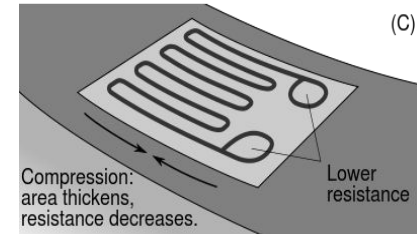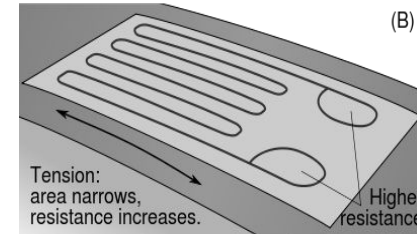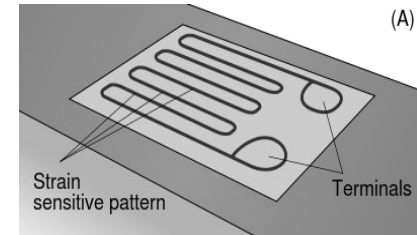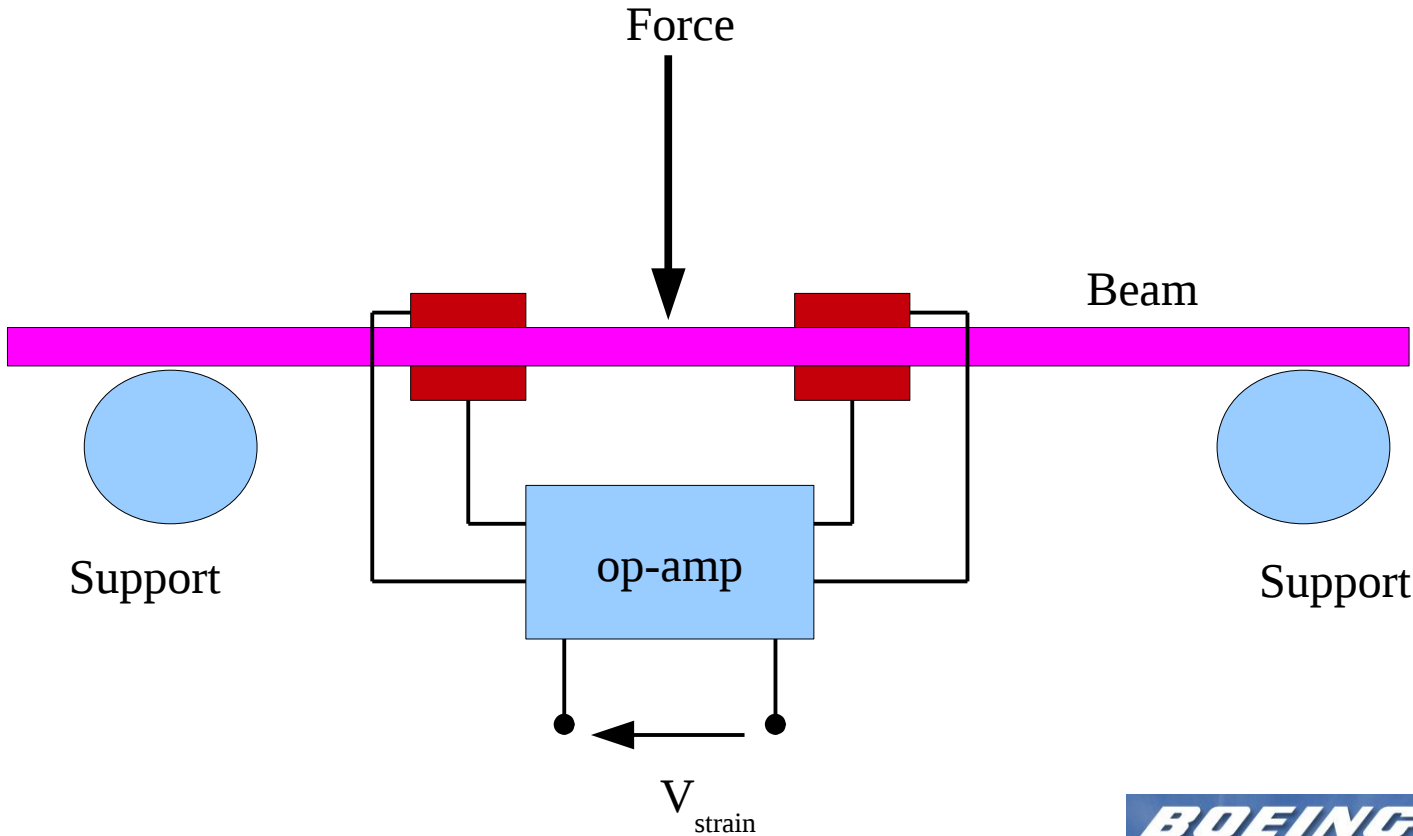
# Recap: Application of op-amps to strain gauges..



The signal that comes out of a strain gauge is very small so it needs amplifying...

# Recap: With this op-amp circuit

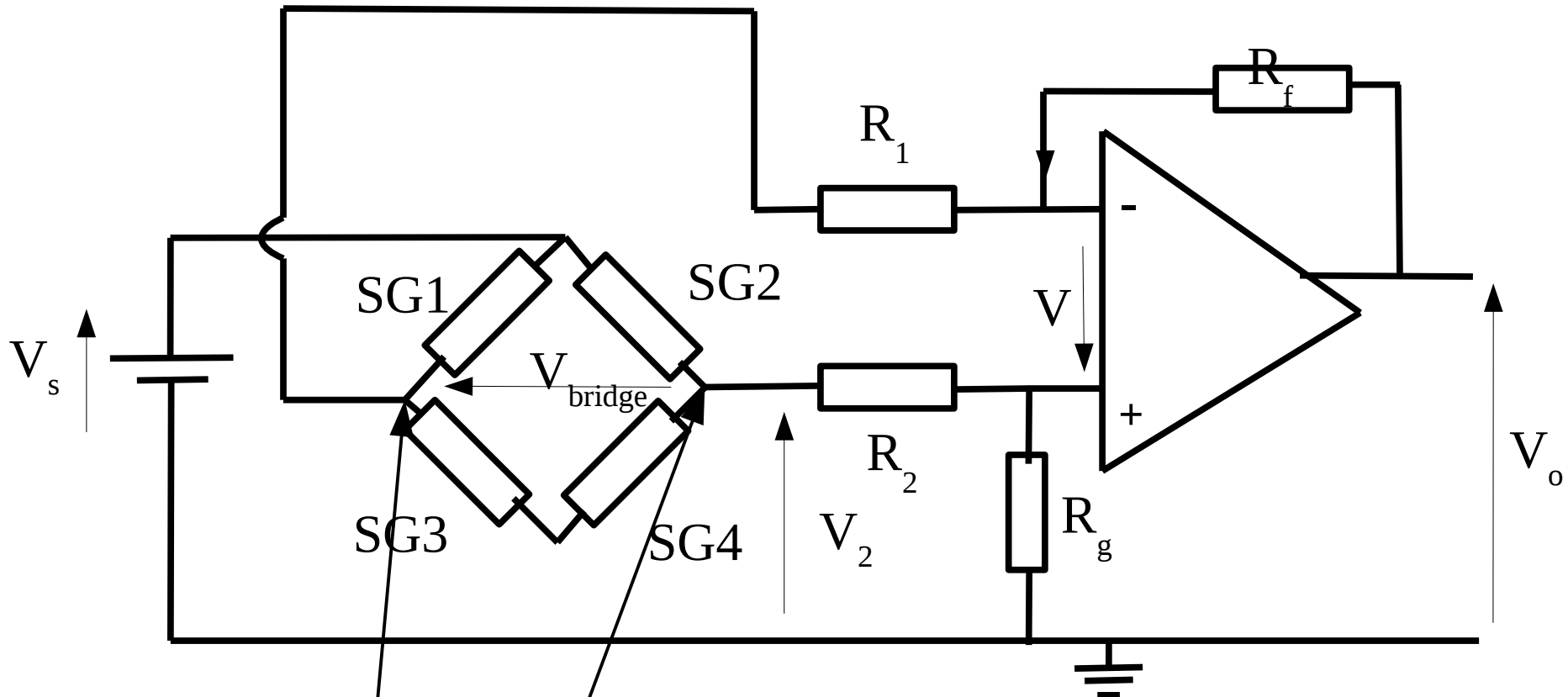

$$V_o = [V_2 - V_1] \frac{R_f}{R_1}$$

And we derived this equation

- Recap of last lecture
- Introduction to diodes.**
- Power diodes – the basics.
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode
- Other kinds of diodes including Solar cells
- Summary



## Book chapters


- All material you will need for the exam is in this lecture and the example sheets, but if you want to do more reading you can look in:

An Introduction to Mechanical  
Engineering: Part 1, pages  
348-360

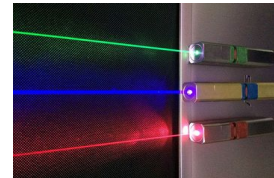
# This lecture is about diodes!

•Diodes are a huge **exciting** topic which encompasses:

- Laser diodes
- Light emitting diodes
- Power diodes
- Solar cells



彭家杰

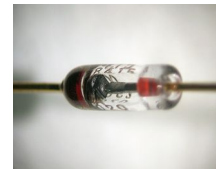

Morcheeba



•I've spent the last ten years of my life researching on light harvesting diodes (solar cells.)

# Diodes




- The focus of this lecture will be on using diodes to power electronic devices.
- This is because whenever you make/design an electronic device you will need to power it.

Mains



Sun

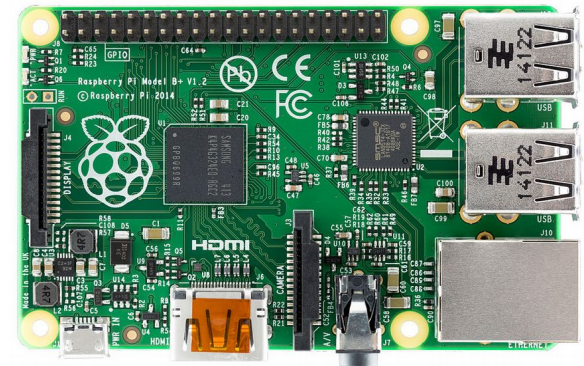

Lucasbosch




# Outline of the lecture

- Recap of last lecture
- Introduction to diodes
- Power diodes - the basics.**
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode
- Other kinds of diodes including Solar cells
- Summary


 
# Diode basics: Diodes for power electronics – what do they look like?



- Diodes you find in high power electronics look like this




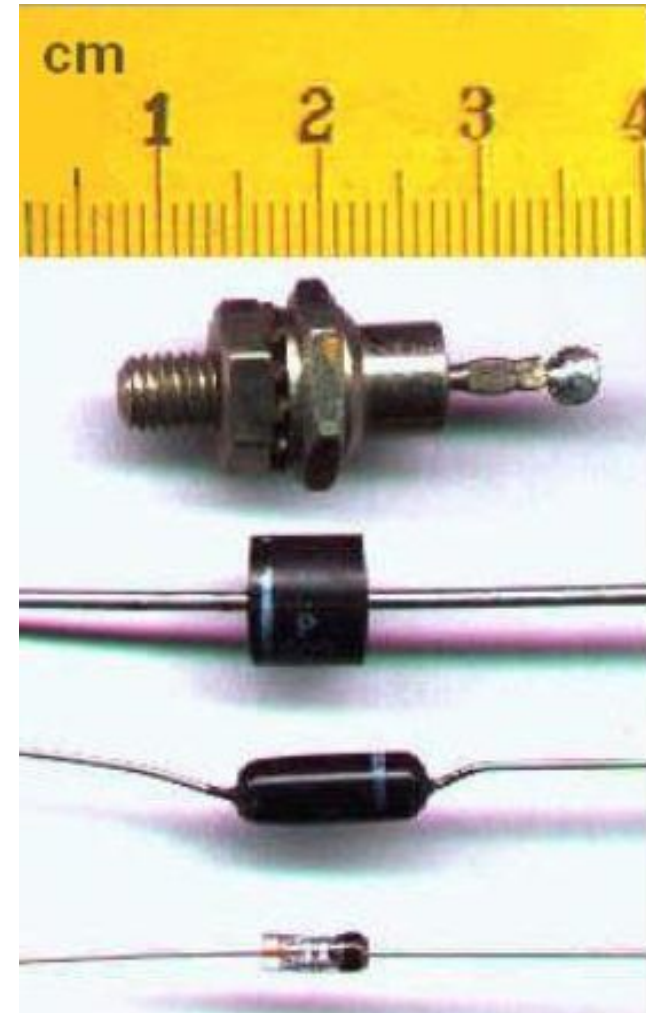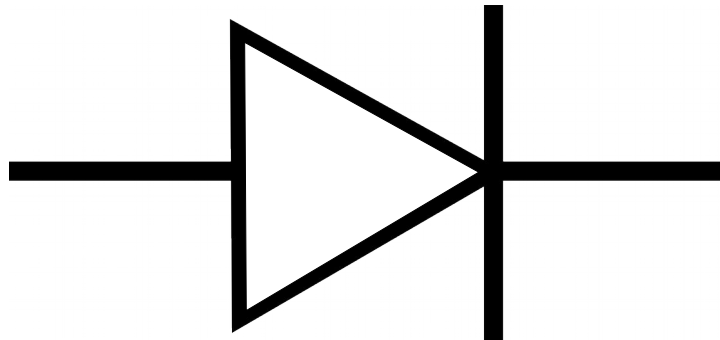- Little black beads with two wires sticking out.






# Diode basics: Notice...

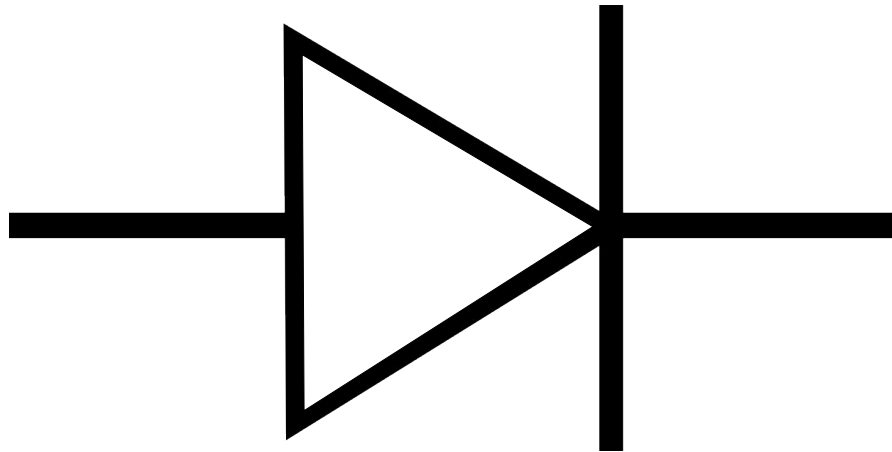

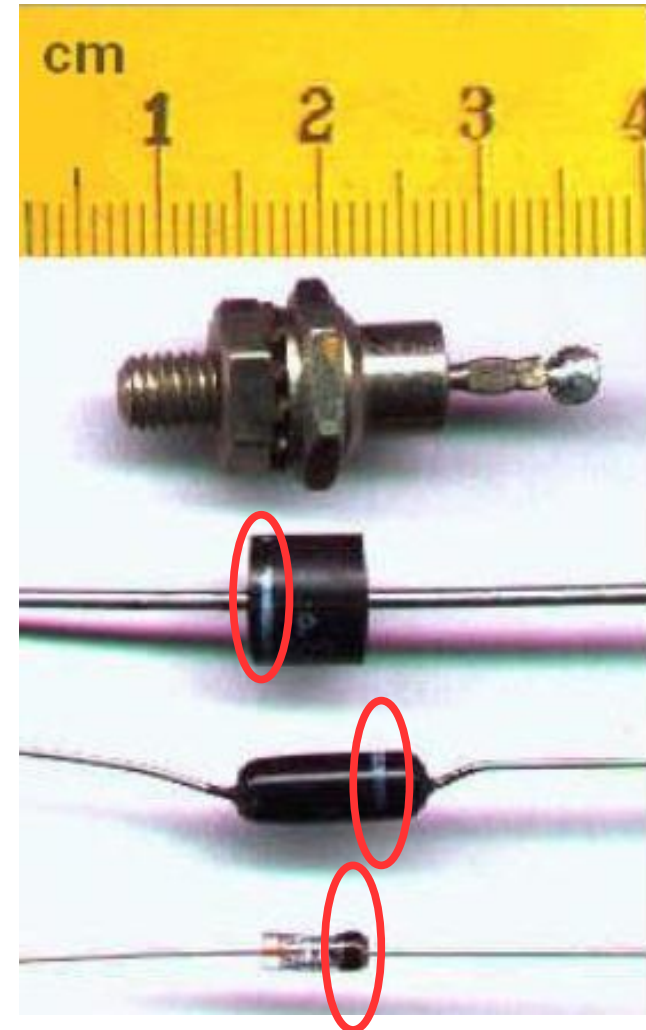
- Notice the silver bar on the end, this is the same as the bar in the diagram.



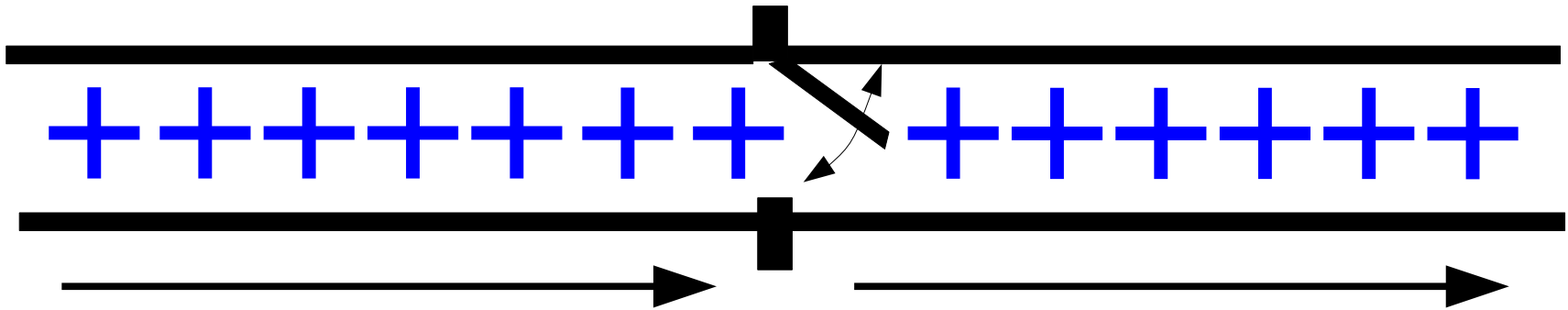
# Diode basics: What do they do?





You can think of a diode as a one way valve for electrons



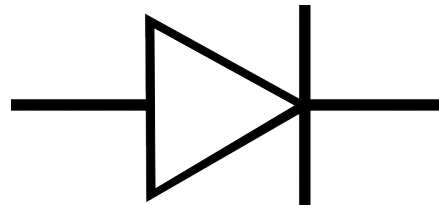If current flows in one direction the diode will allow it to pass.



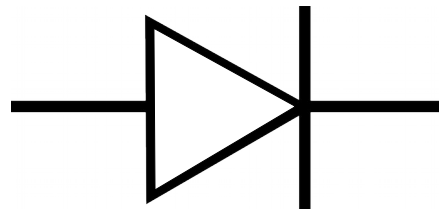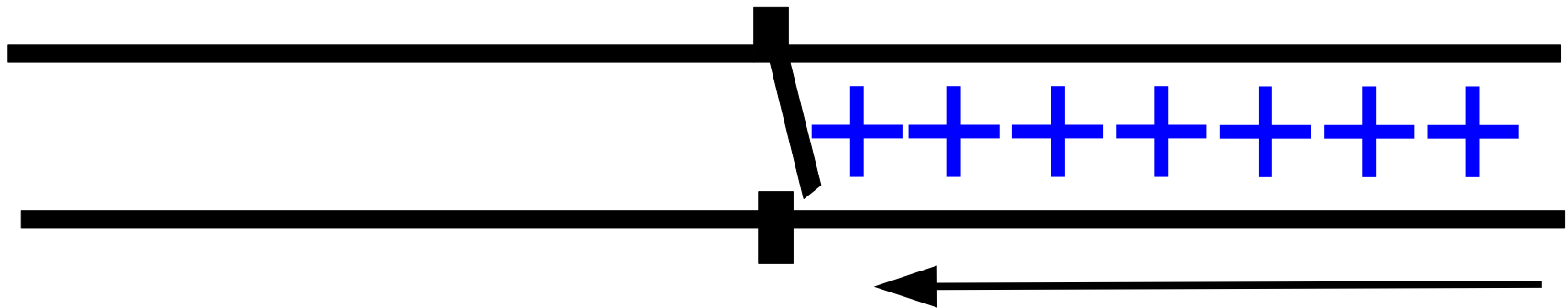If current tries to flow in the **other direction** it will not be allowed to pass.



# Diode basics: A one way cat flap....




You can also think of a diode as a one way cat flap for electrons.

- Electrons (or the cat) are only allowed to go through one way but not the other.




Andrew Dunn
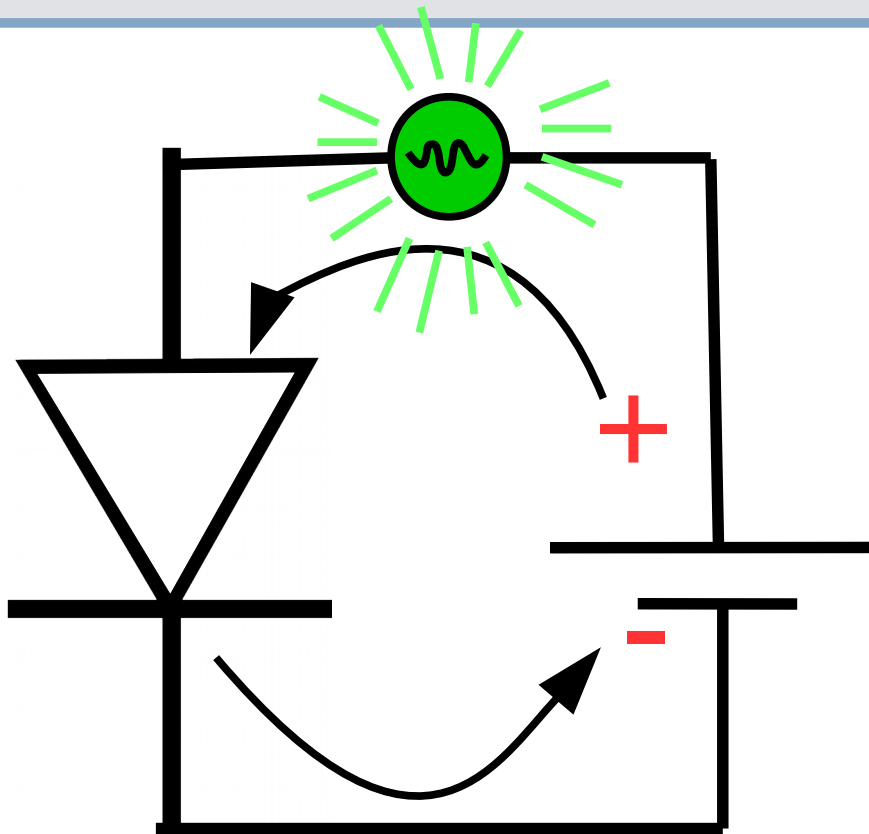
# Diode basics: A diode as a one way trap door for current




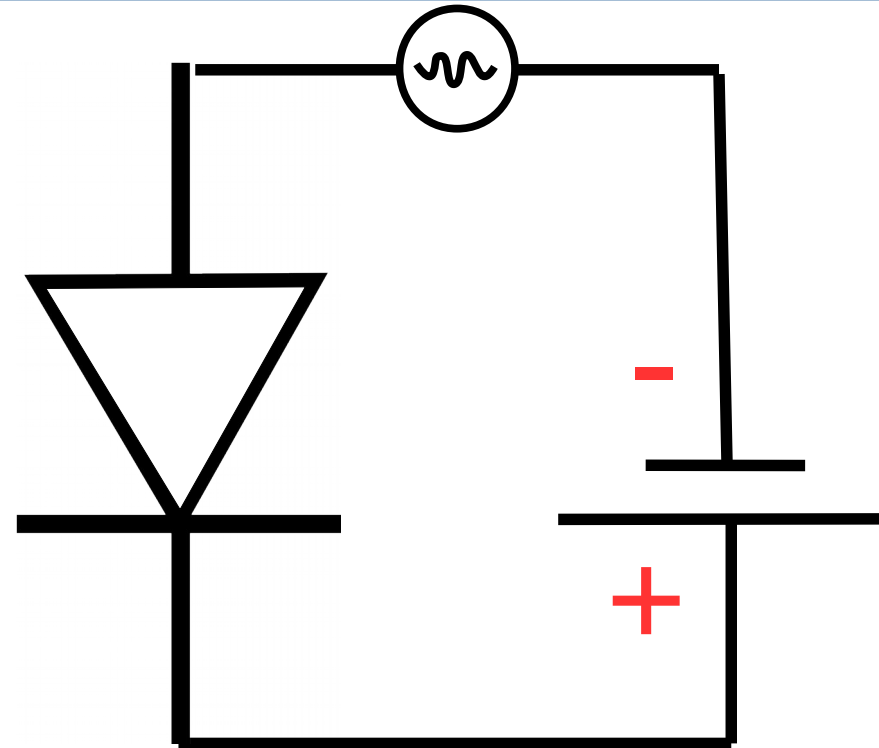With **positive**  
applied voltage  
current flows



With **negative**  
applied voltage  
no current flows
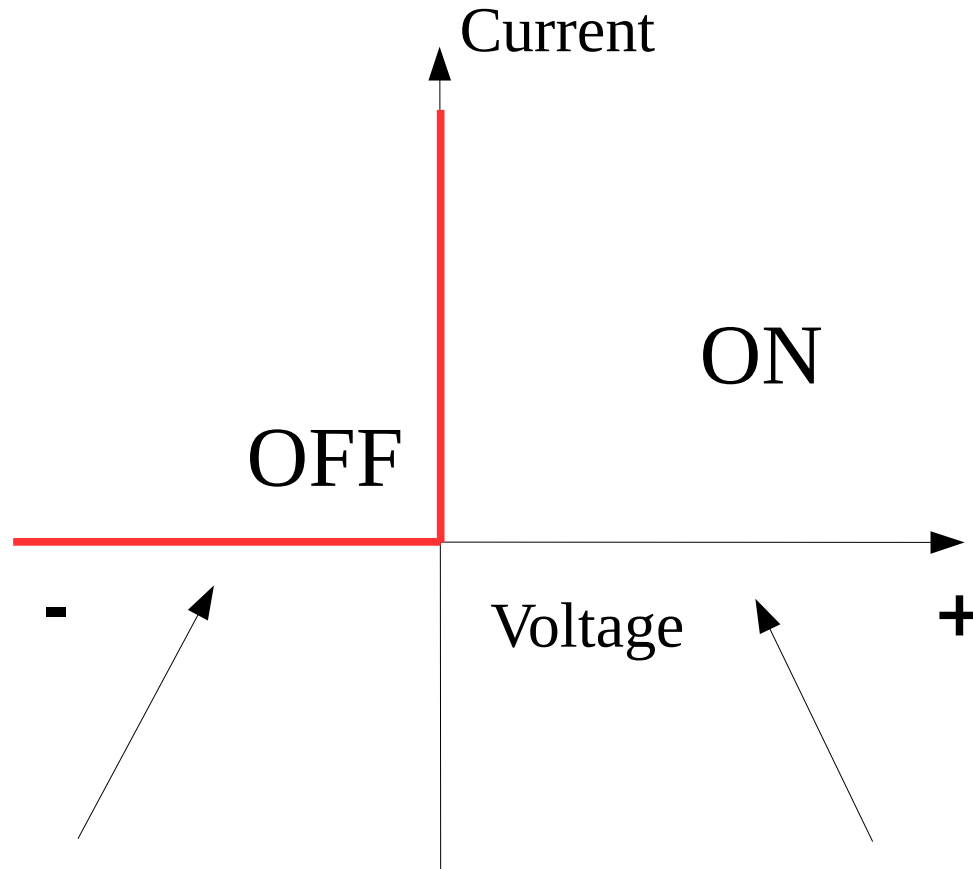
# Diode basics: What does the ideal current voltage curve look like?



At negative voltages it blocks current

At positive voltages any amount of current can flow


- Recap of last lecture
- Introduction to diodes.
- Power diodes – the basics.
- Designing a power supply**
  - Diodes - the bridge between AC and DC**
- The less ideal diode
- Other kinds of diodes including Solar cells
- Summary

# Power supplies, the interface between electrical and electronic engineering

- Think about **digital devices** like your **phone**, **mp3 player** or **tablet**, they run on no more than **5 volts**.
- However, mains gives us **230 V**.
- If we want to power digital electronic circuits off the mains we must convert **230 V to 5V**.



**230 V**

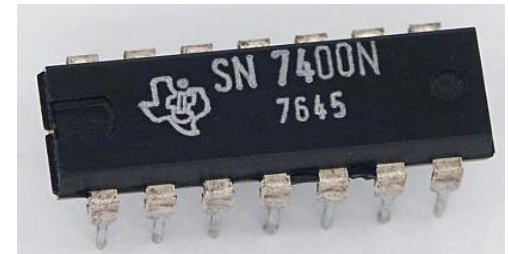


**5 V**






# A transformer...

Last lecture Arthur taught you about transformers, which can convert **high voltages to low voltages**.

Transformer

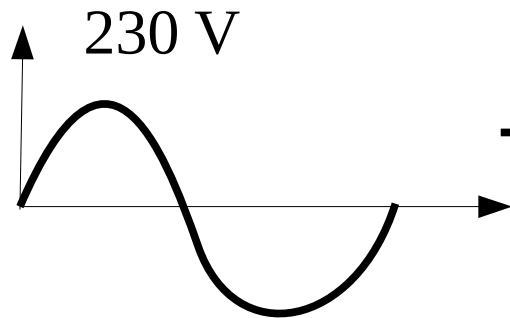

**230 V**

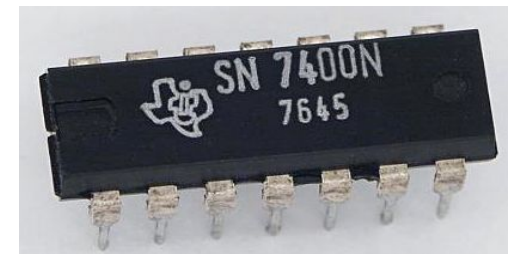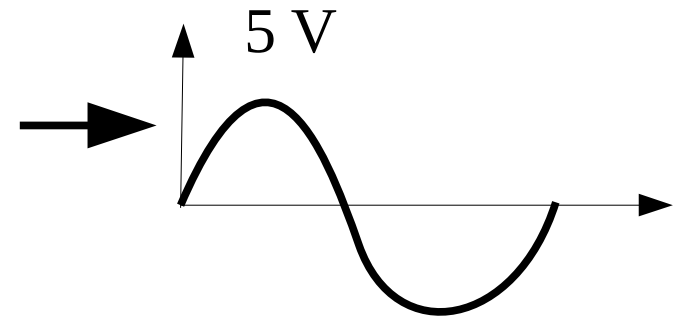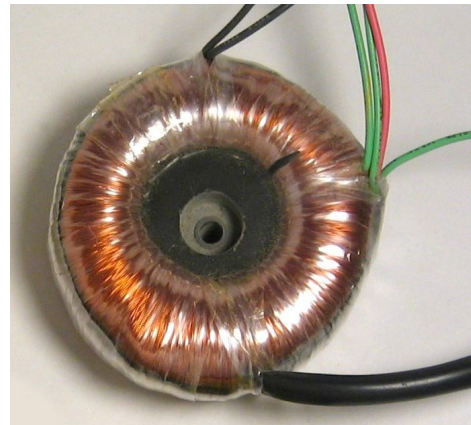




**5 V** 25

So we could use a transformer to get our **5 Volt** supply.....




So to summarize we have this situation...




Input  
230V

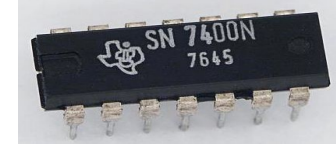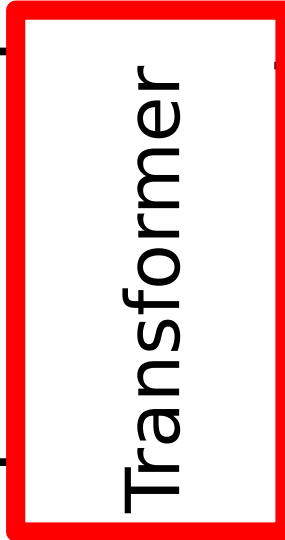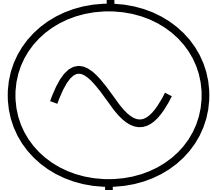

Output  
5V

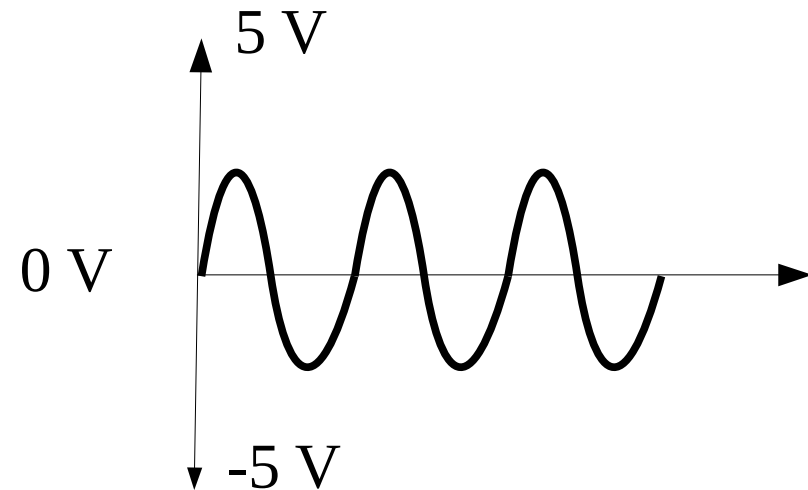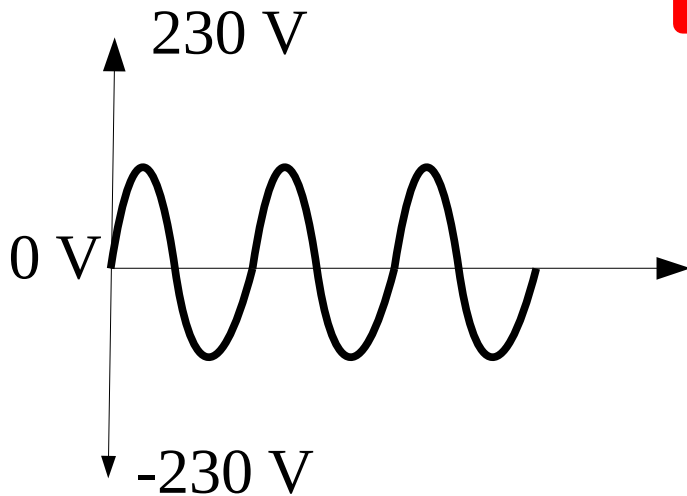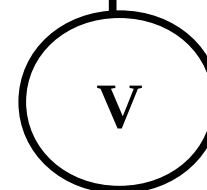


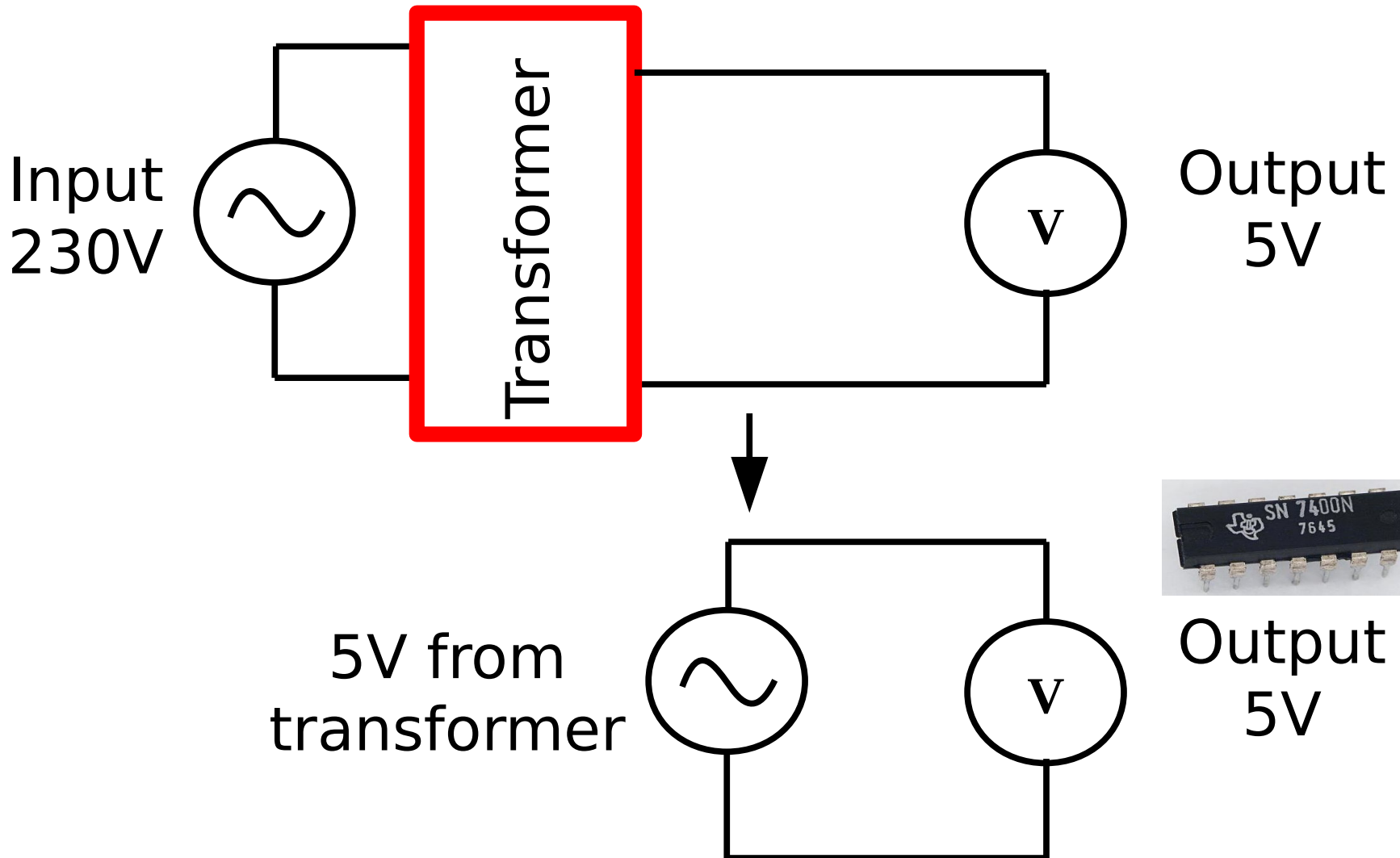From now on I will not draw the transformer and we will only look at the low voltage side....



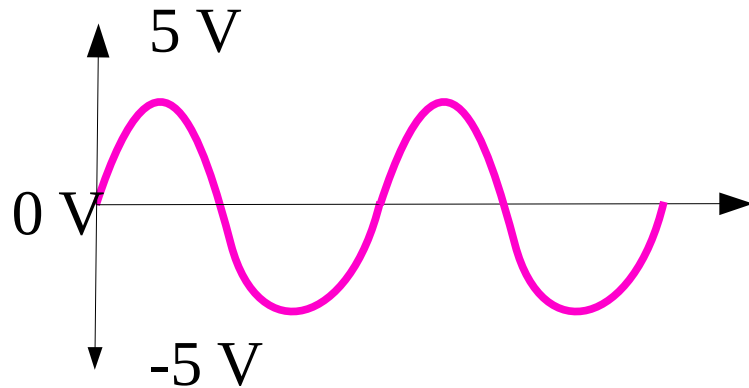
# However.....

- AC switches **ON** and **OFF** again 100 times a second (50 Hz).






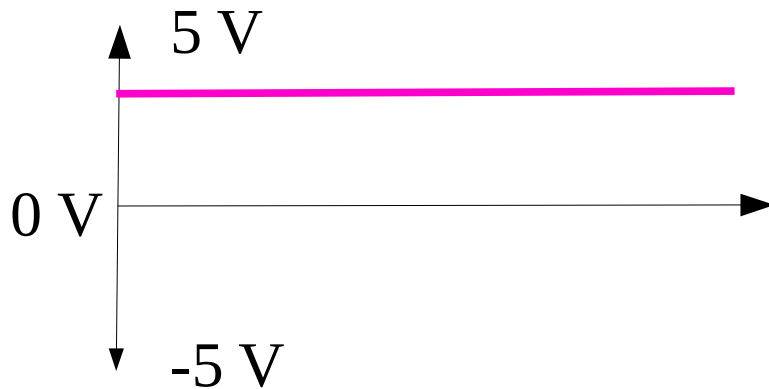- But most chips need a steady **DC 5V** supply to run.





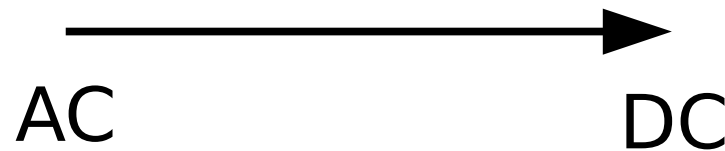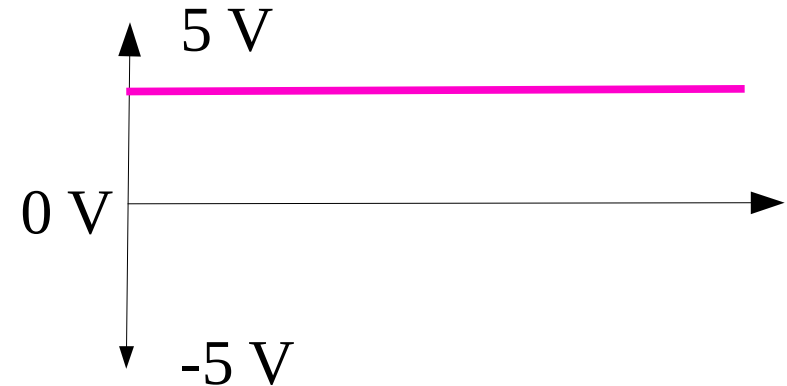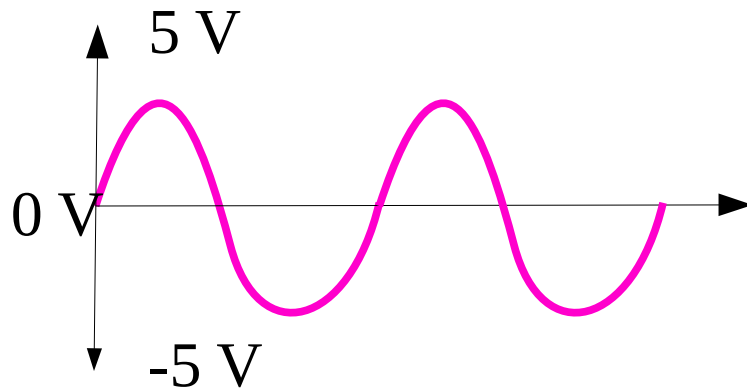
# Question?

Can anybody guess what we might use to turn an AC voltage into a DC voltage?



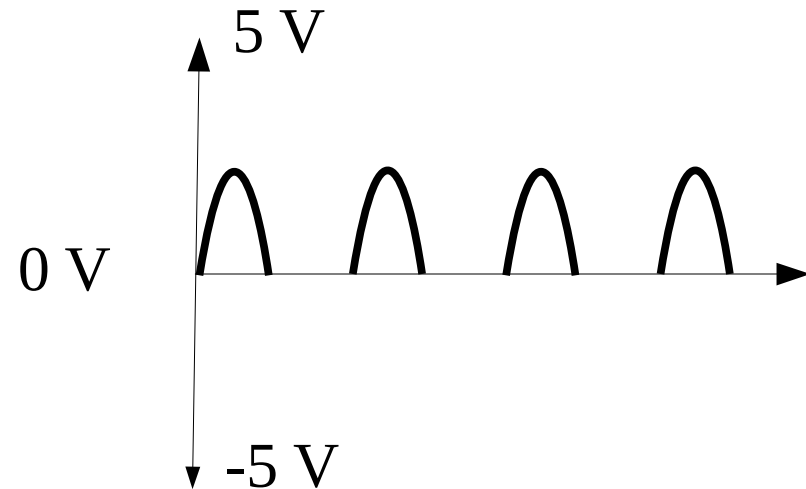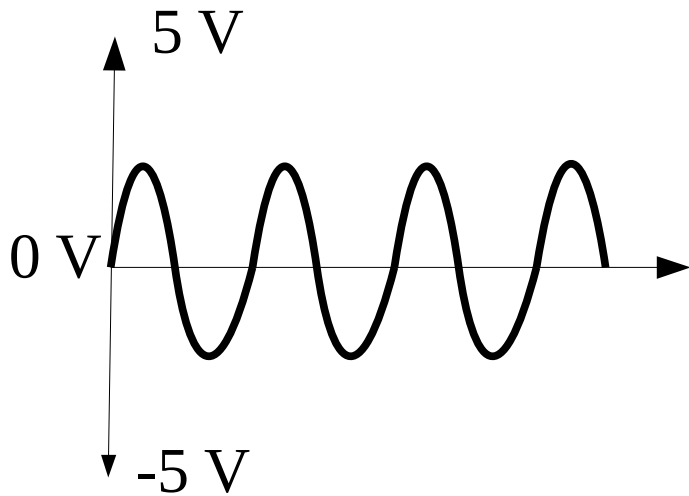
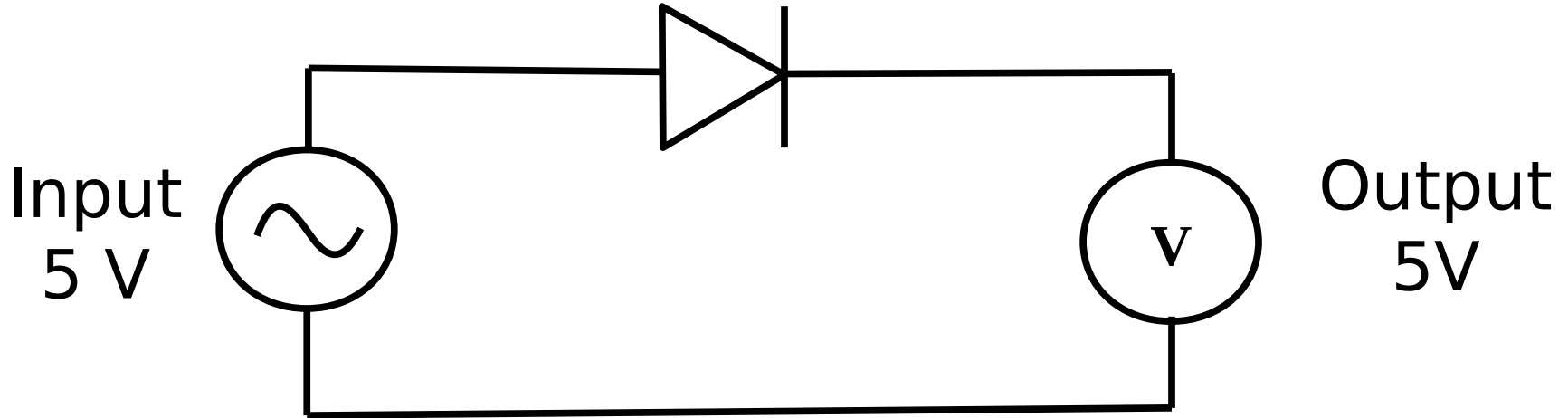
# A diode!! - the diode only lets through the positive voltage



•That's not really DC is it....

This is better, because we no longer get negative voltages...

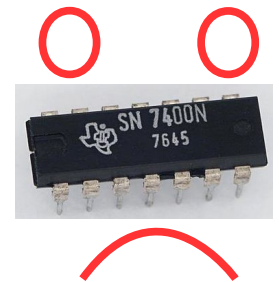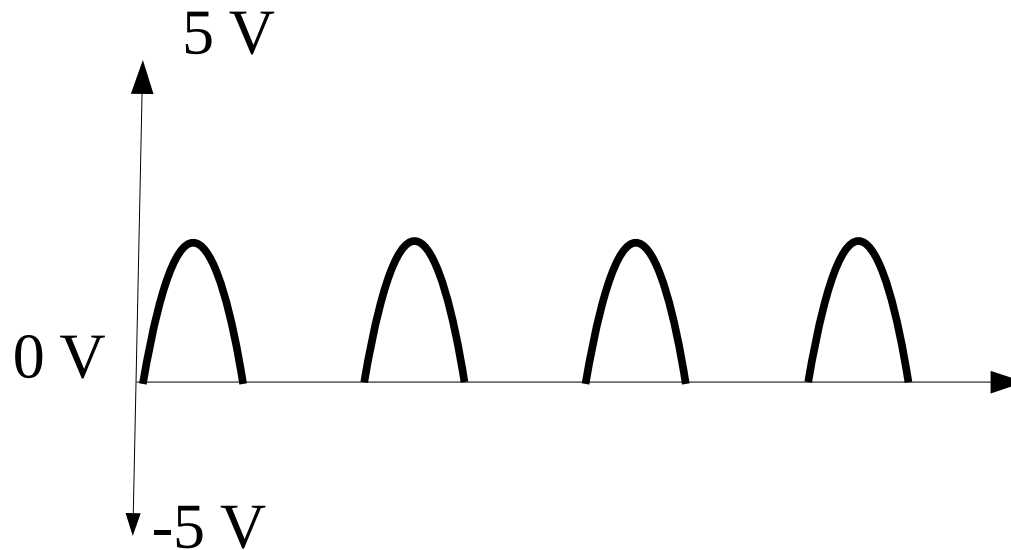- But our circuit will still have its power turned **on** and **off** 50 times a second.
- Again imagine a computer being turned on and off 50 times a second - not good.



• So what we do is the following....

We use four diodes in a square, this is called a **bridge rectifier**.



Input



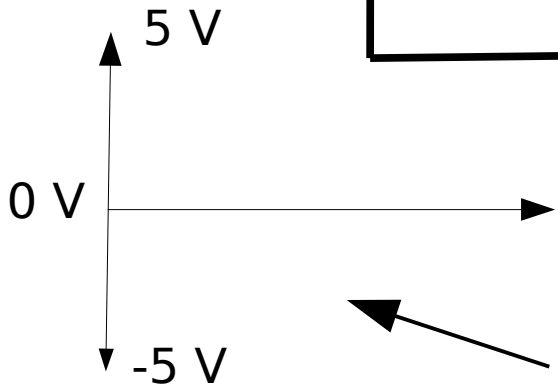
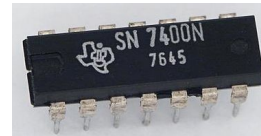


Diagram of voltage wave form


And it works like this.....

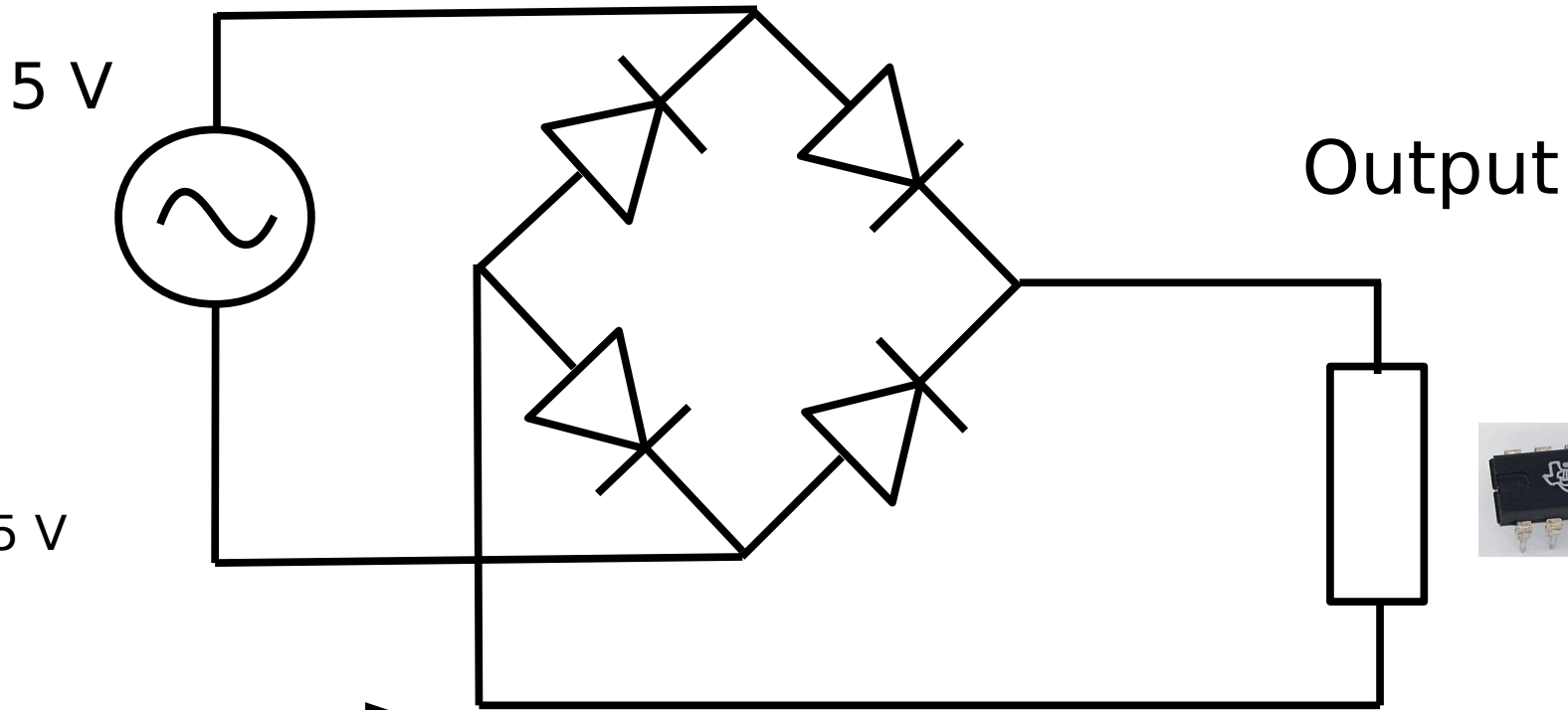


# When the voltage is positive..

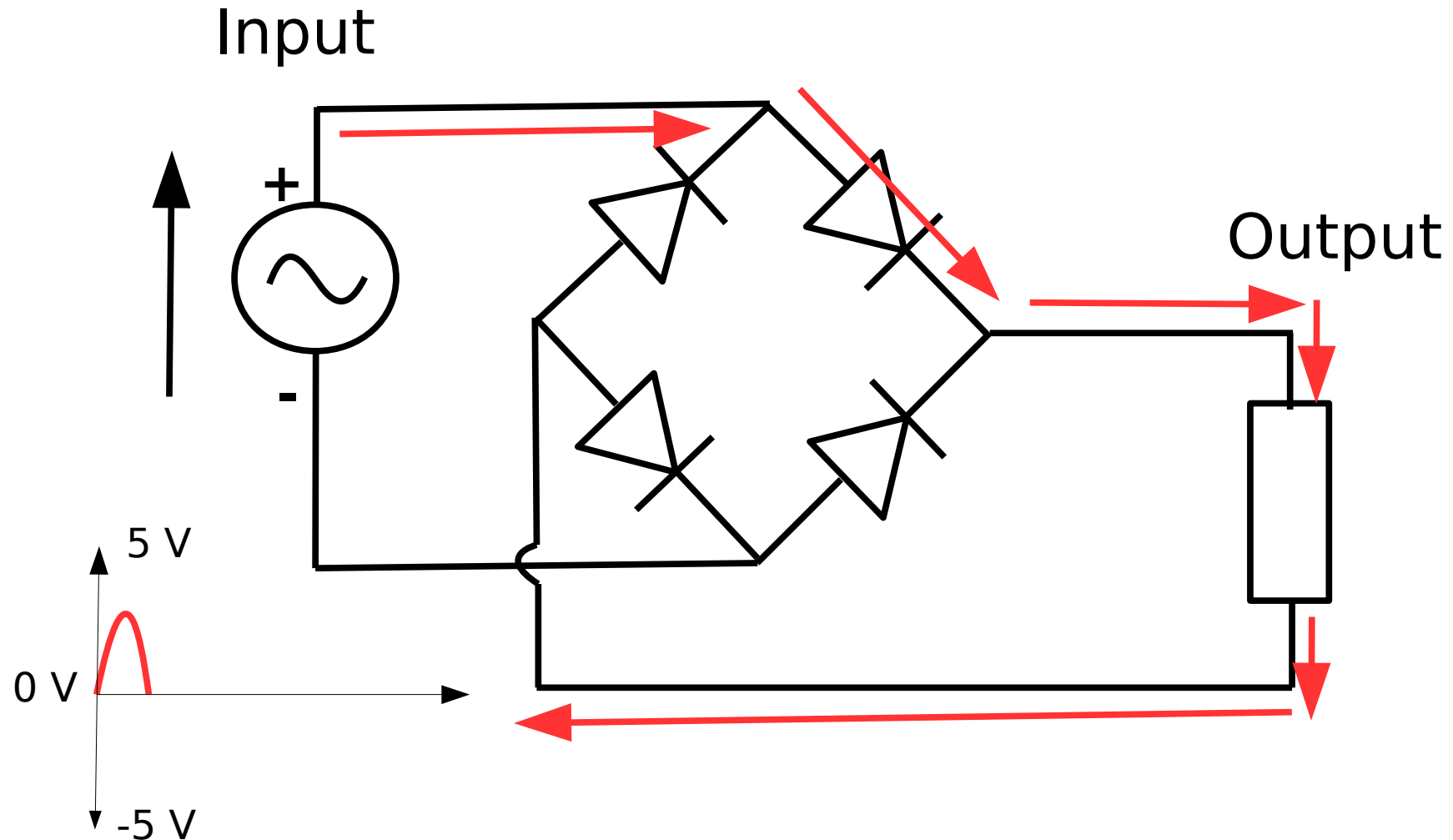


# When the voltage is positive..

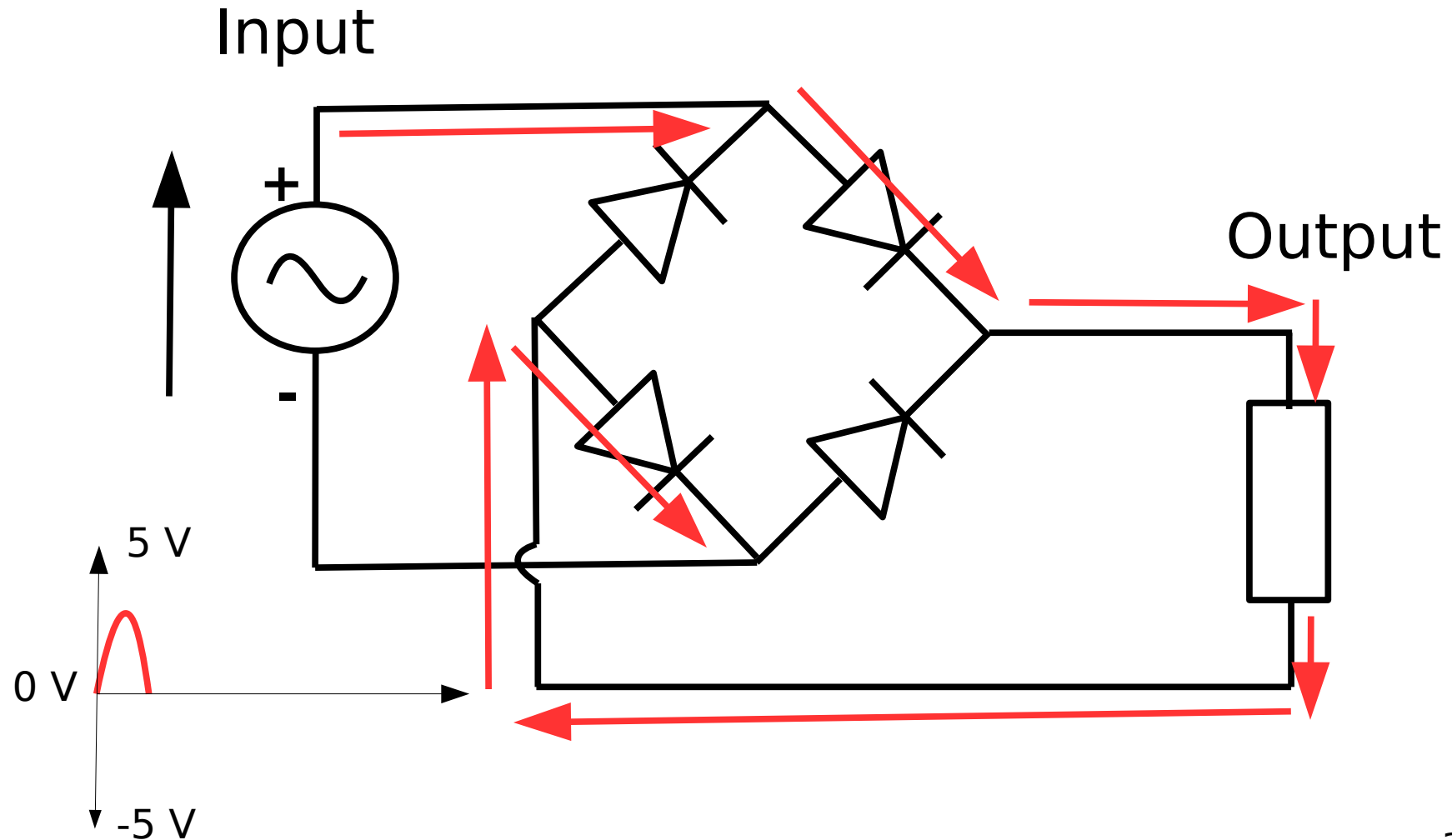


When the voltage is positive..

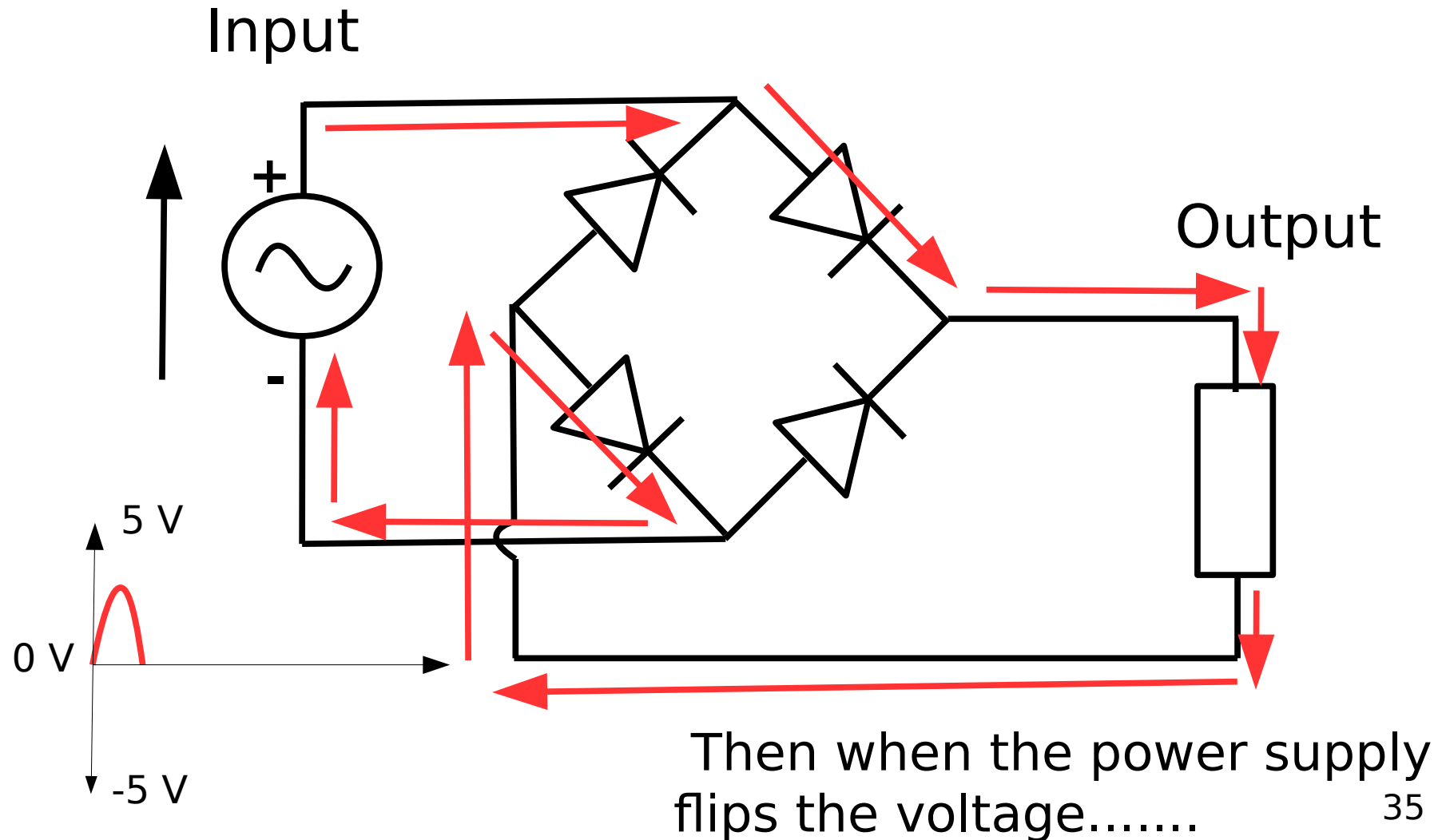

# When the voltage is negative..

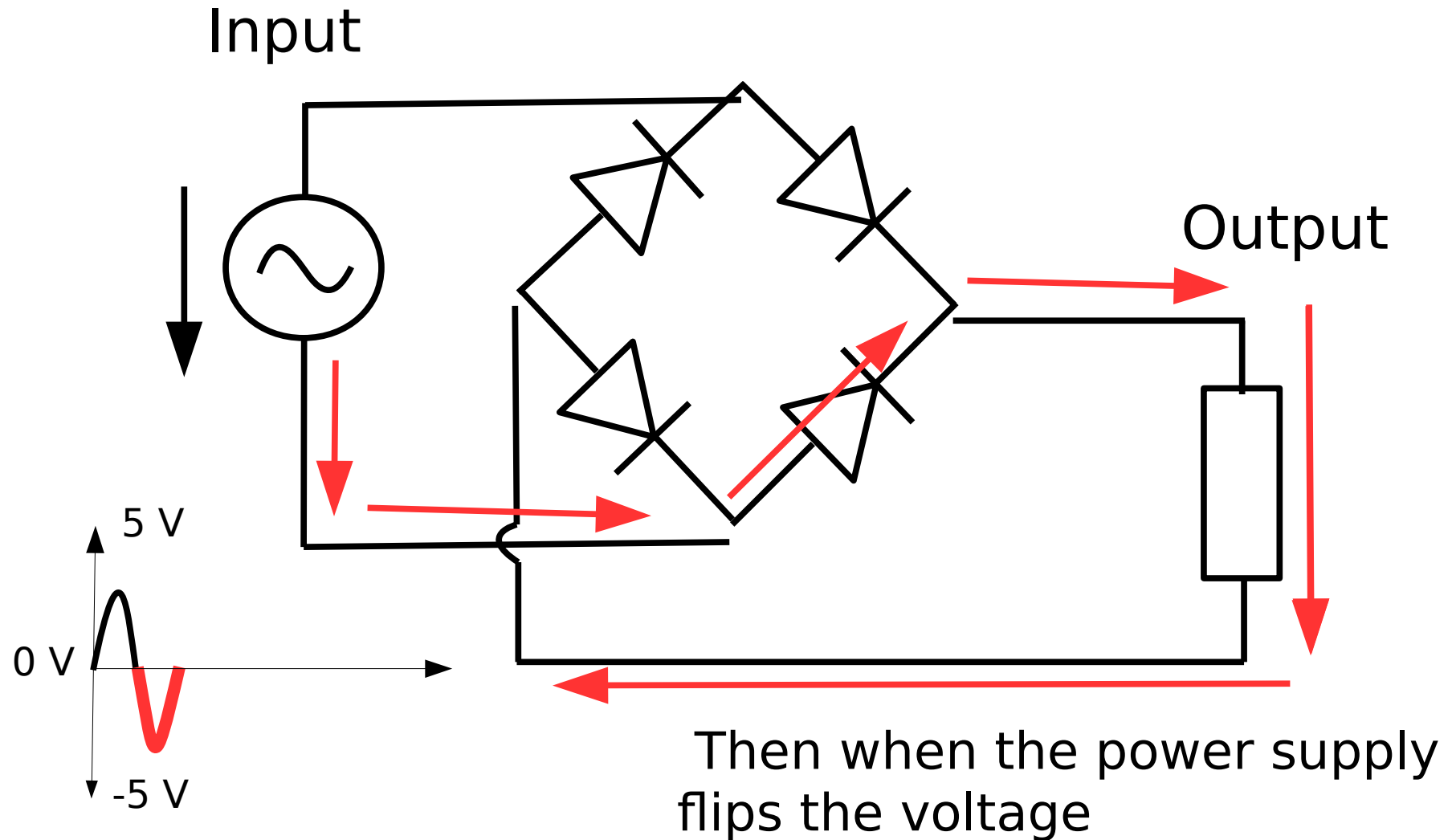


# When the voltage is negative..

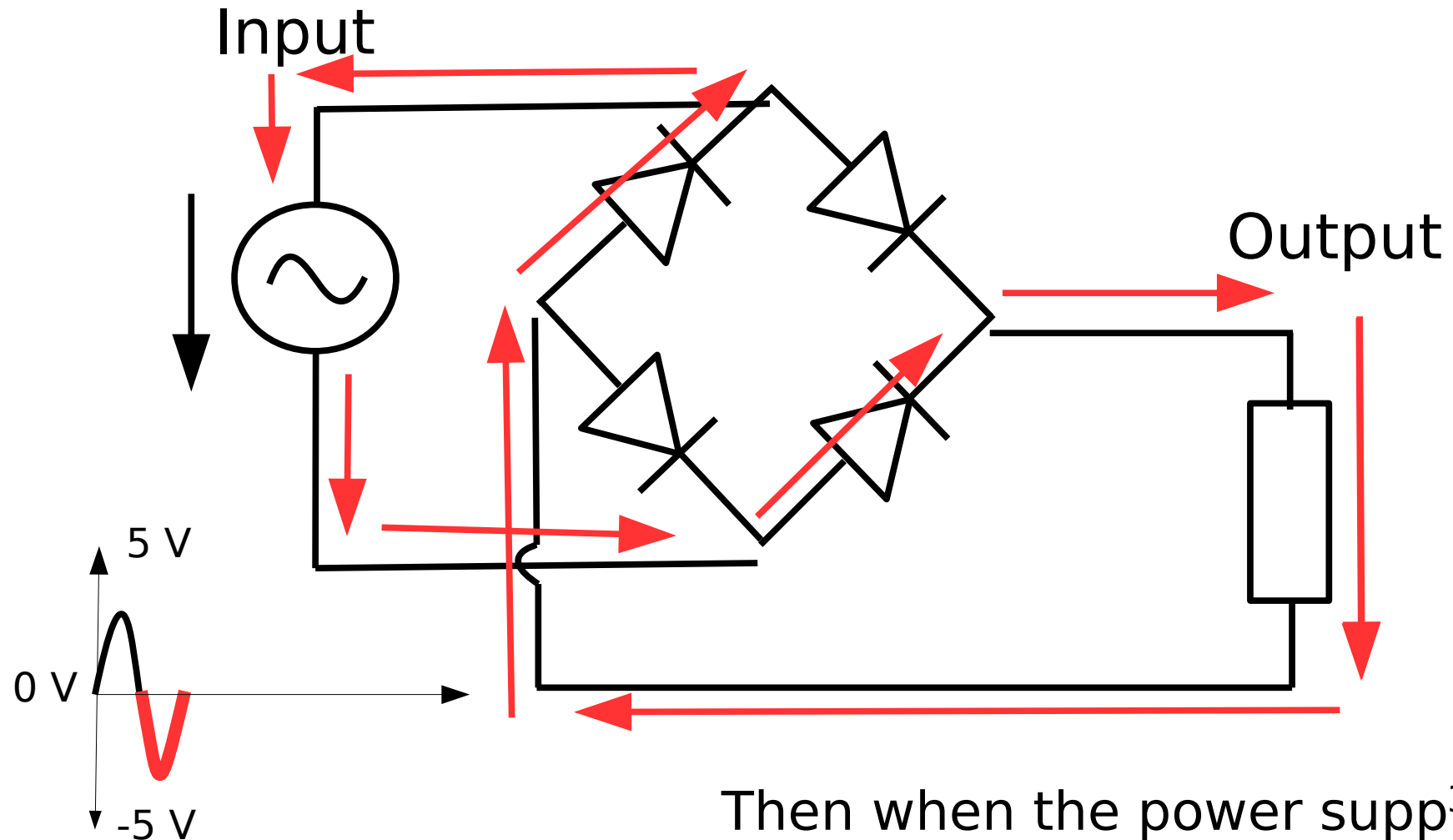


Then when the power supply<sup>B7</sup>  
flips the voltage

# When the voltage is positive...

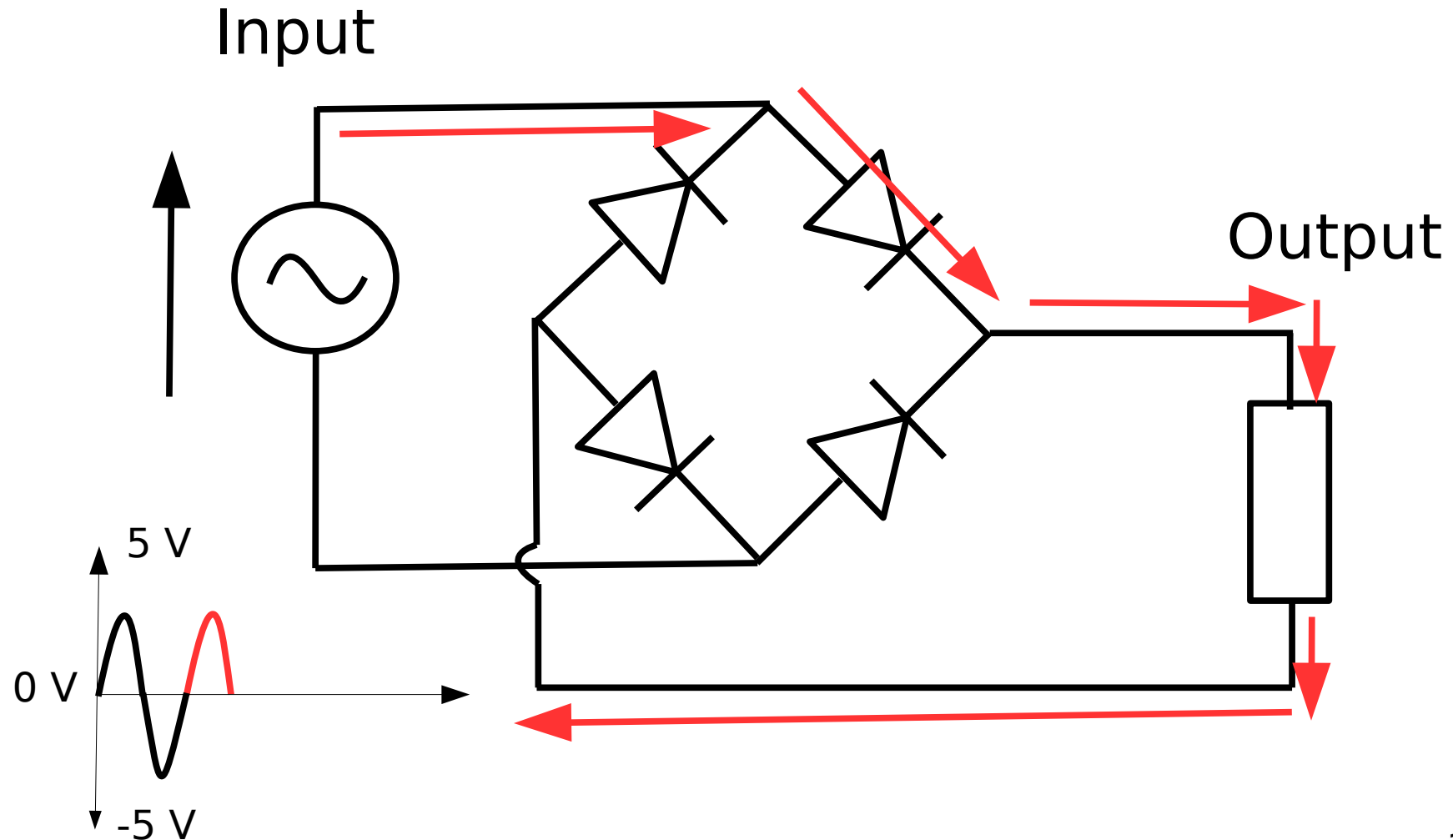


# When the voltage is positive...

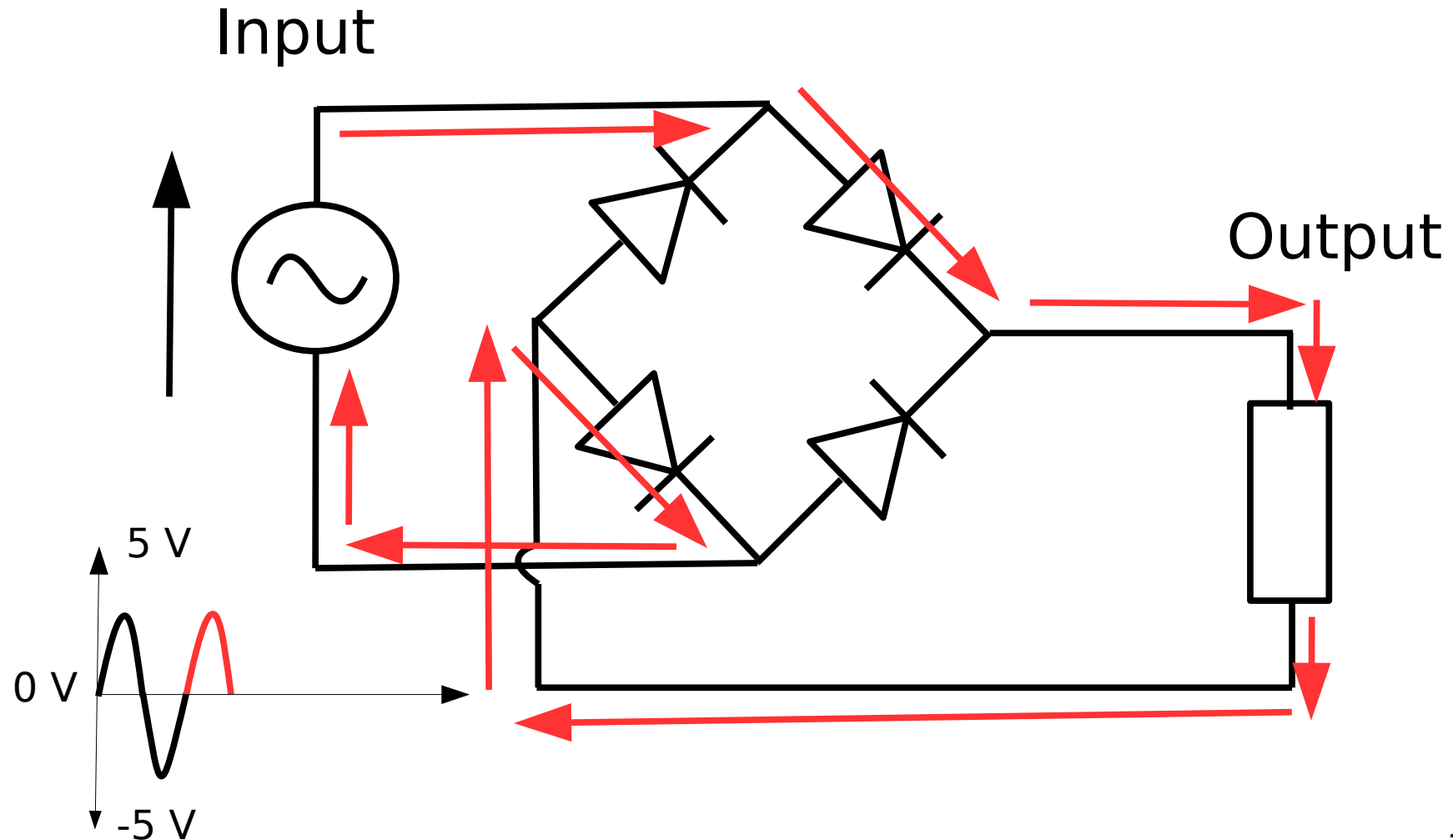


# When the voltage is negative..



Input

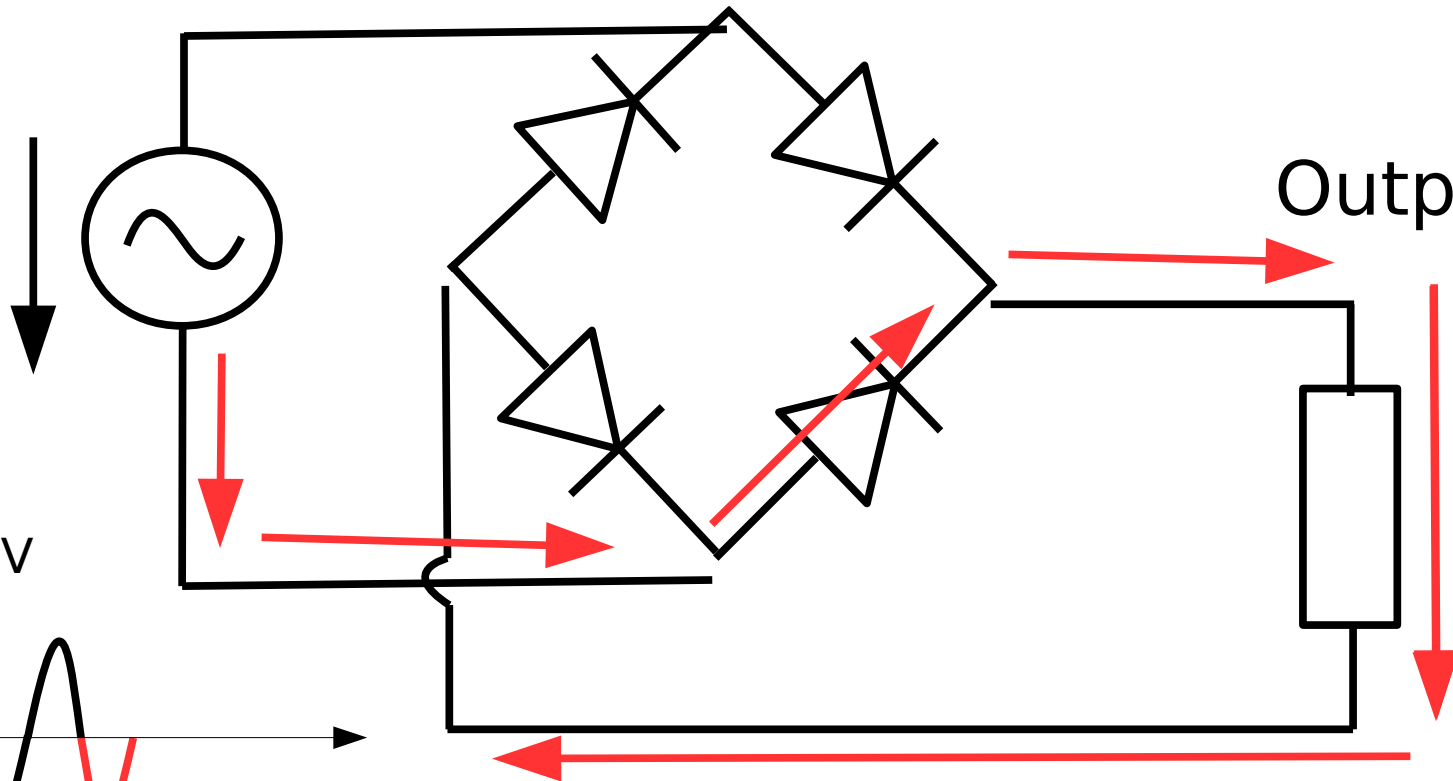


Output

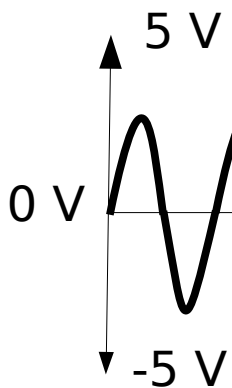




# When the voltage is negative..



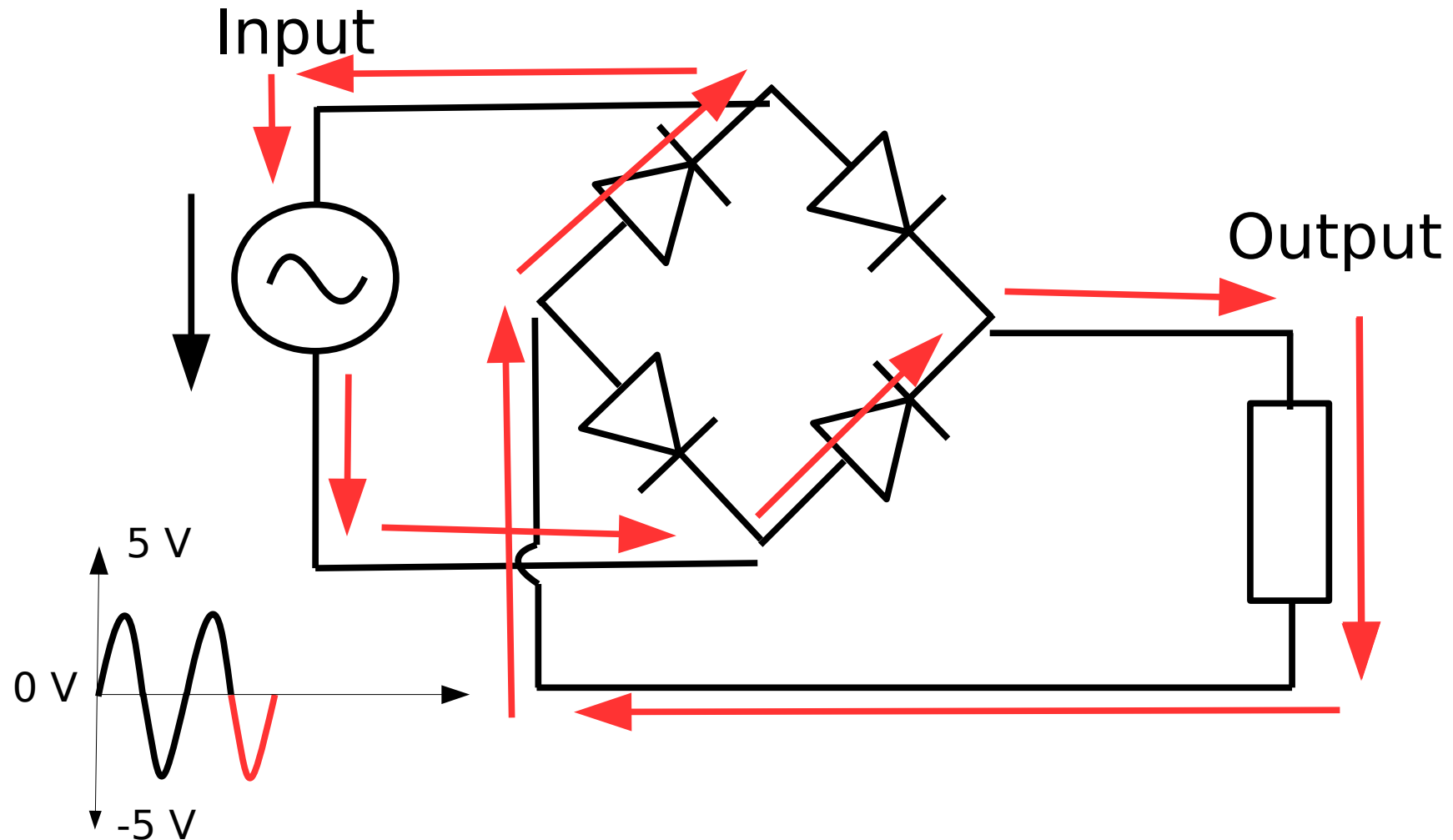


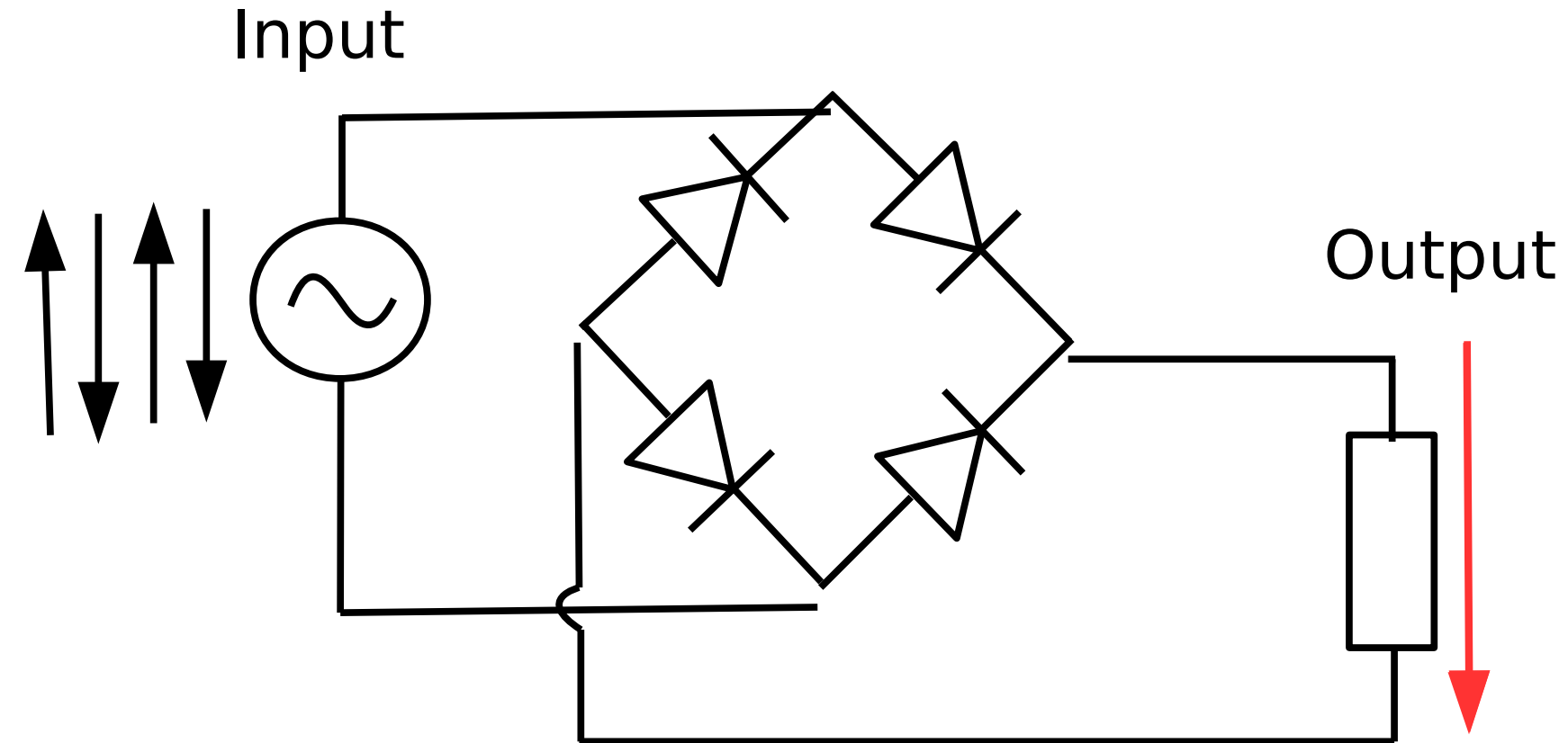Notice, what ever happens to the input voltage the output voltage is always in the same direction







Let's look at the wave forms... 42

# And the result....

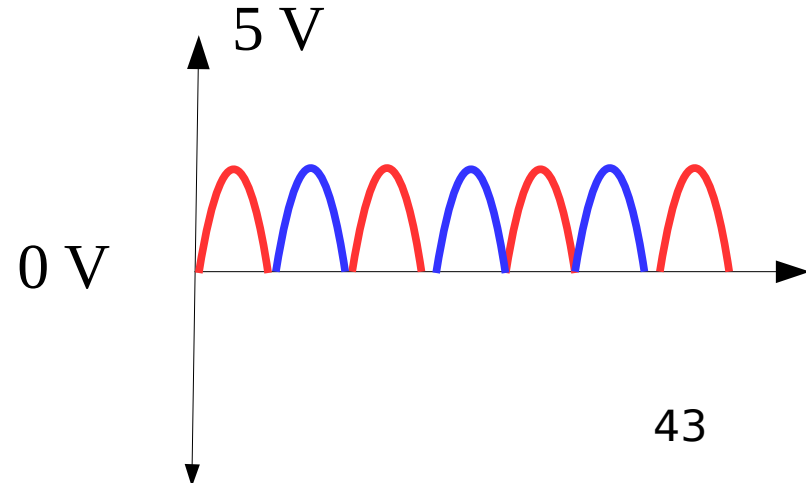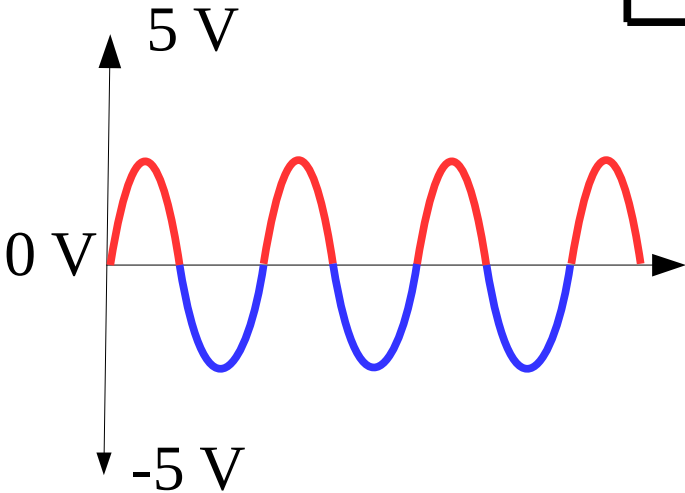
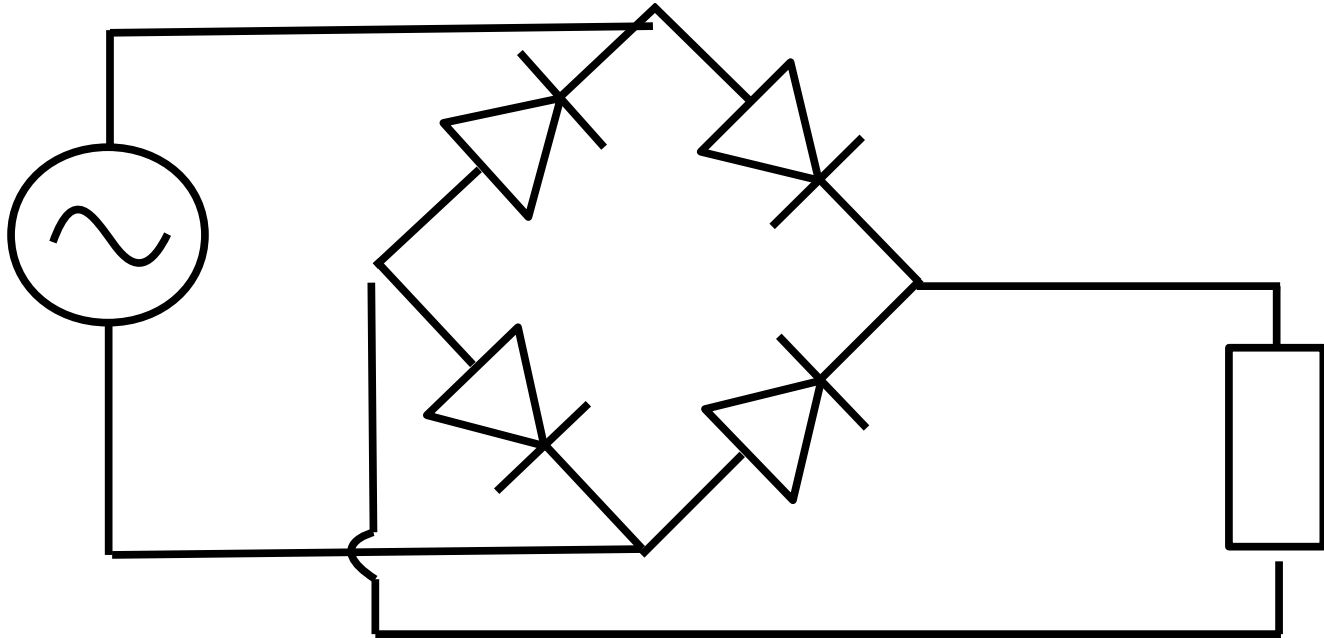


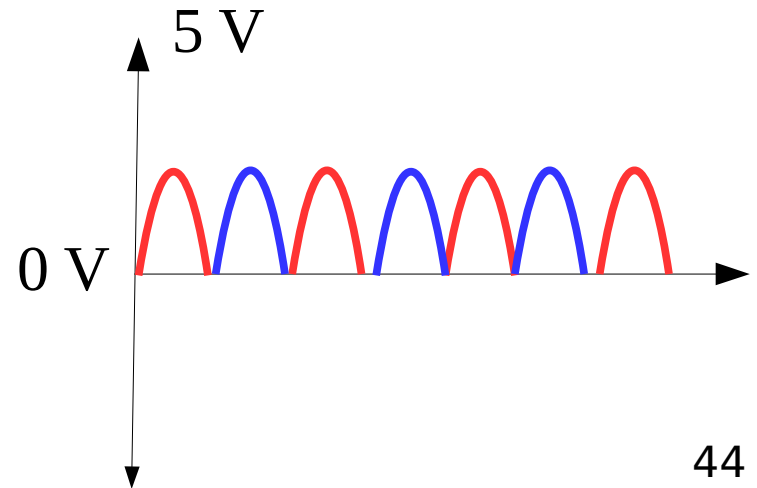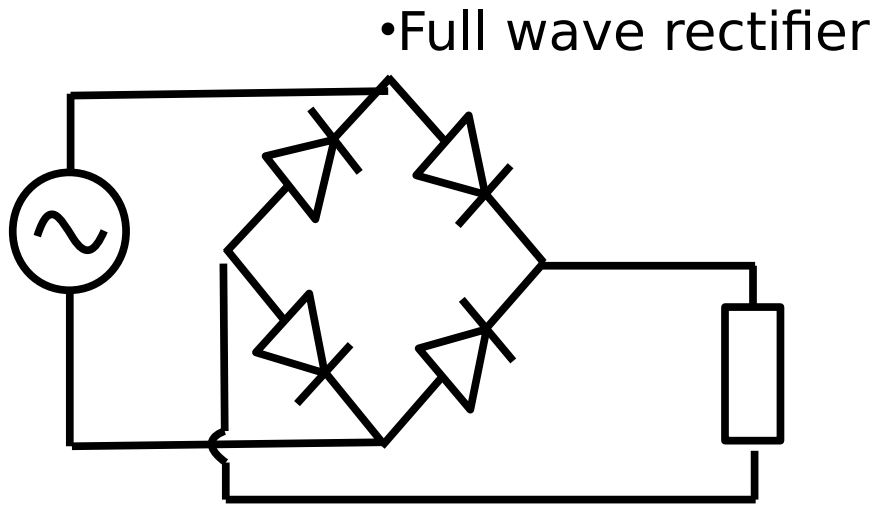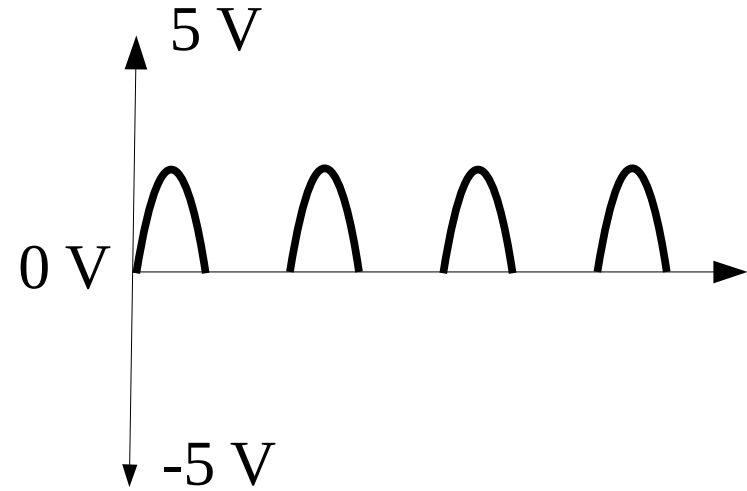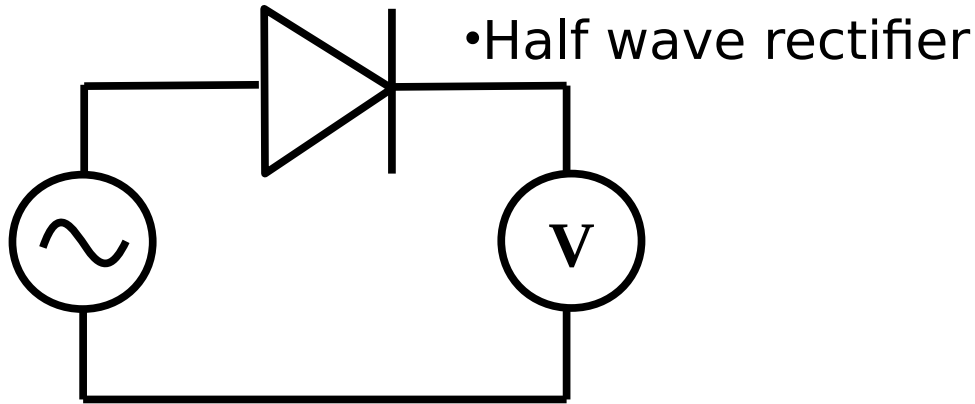We now have positive voltage more of the time.



•Looks useful, but our circuit is still off 100 times a second.



# Add a smoothing capacitor....

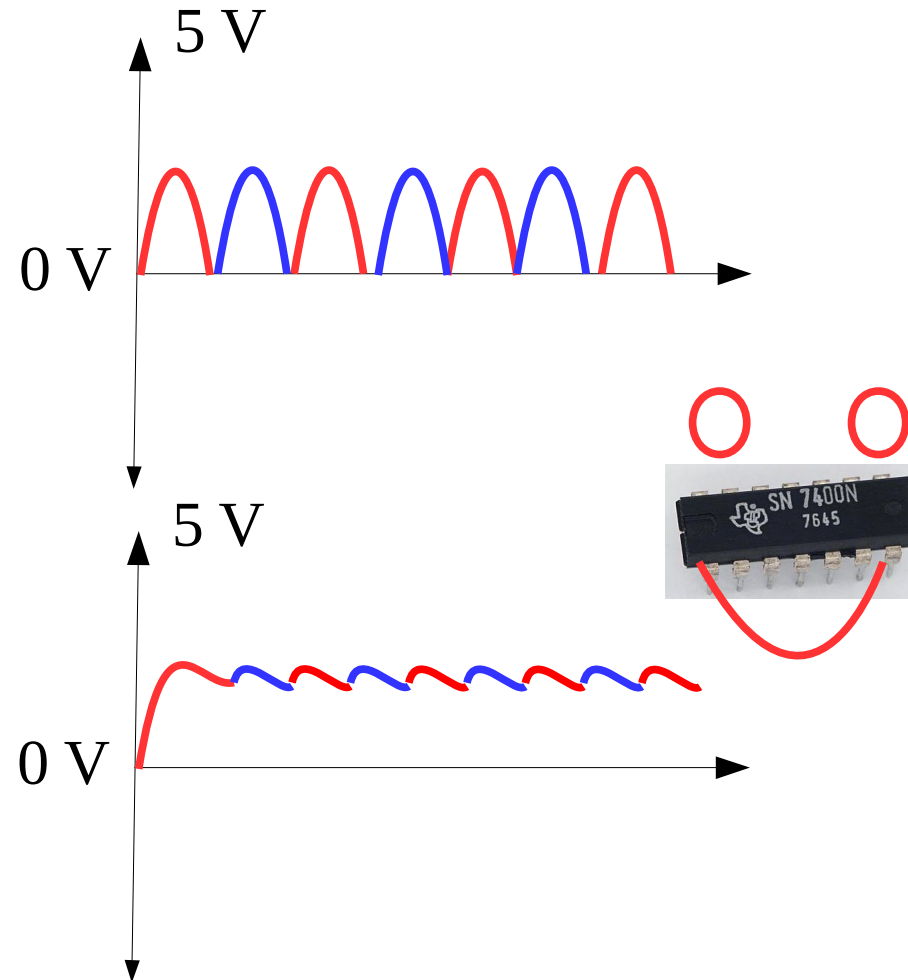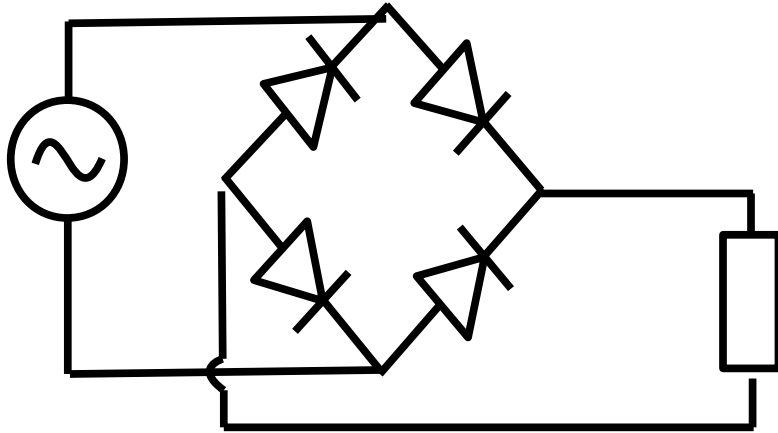

• And we sort of get nice DC, but what is this capacitor doing?

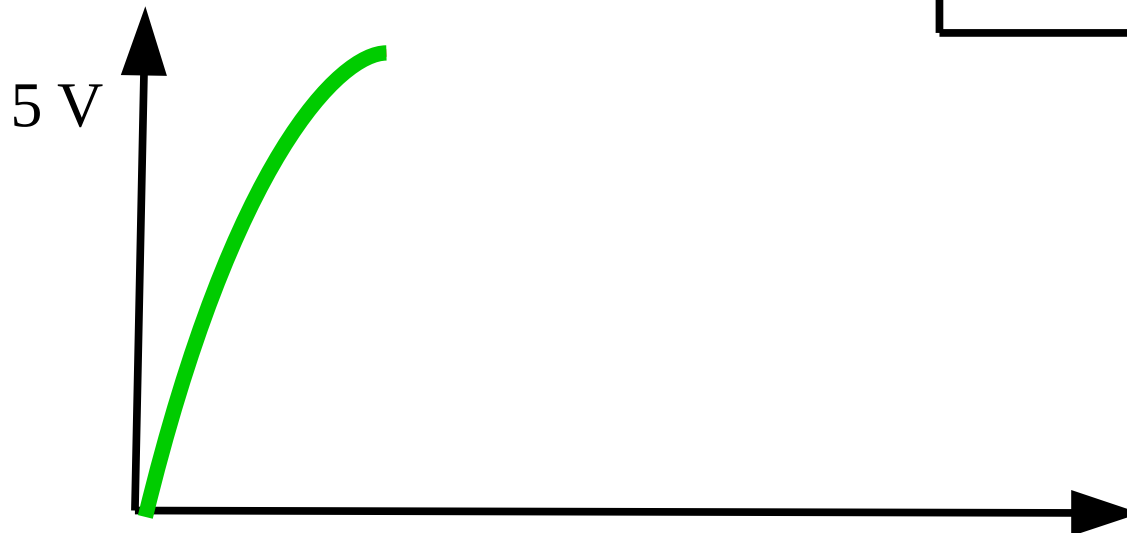
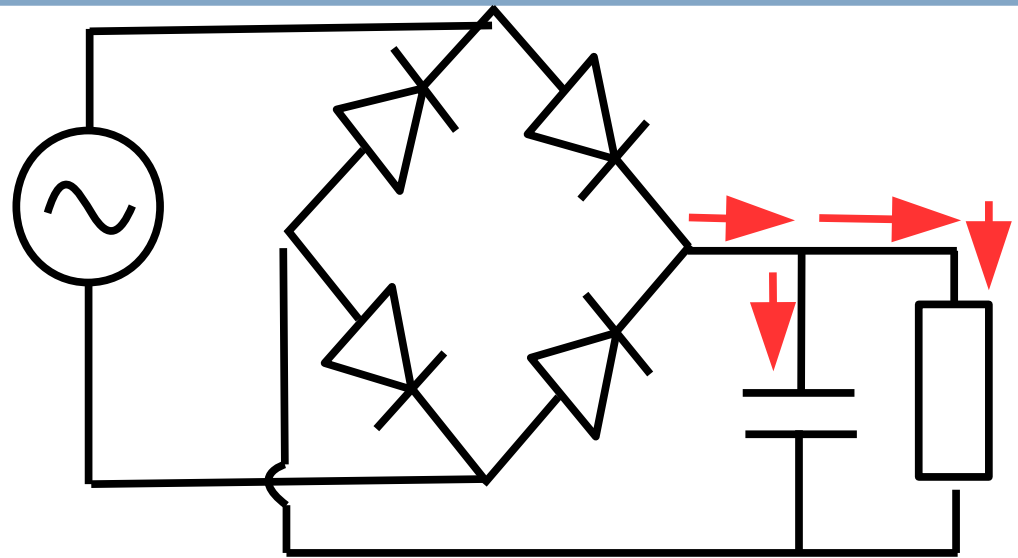
## But why is this?

When the supply is first switched on the rising supply voltage will charge the capacitor.



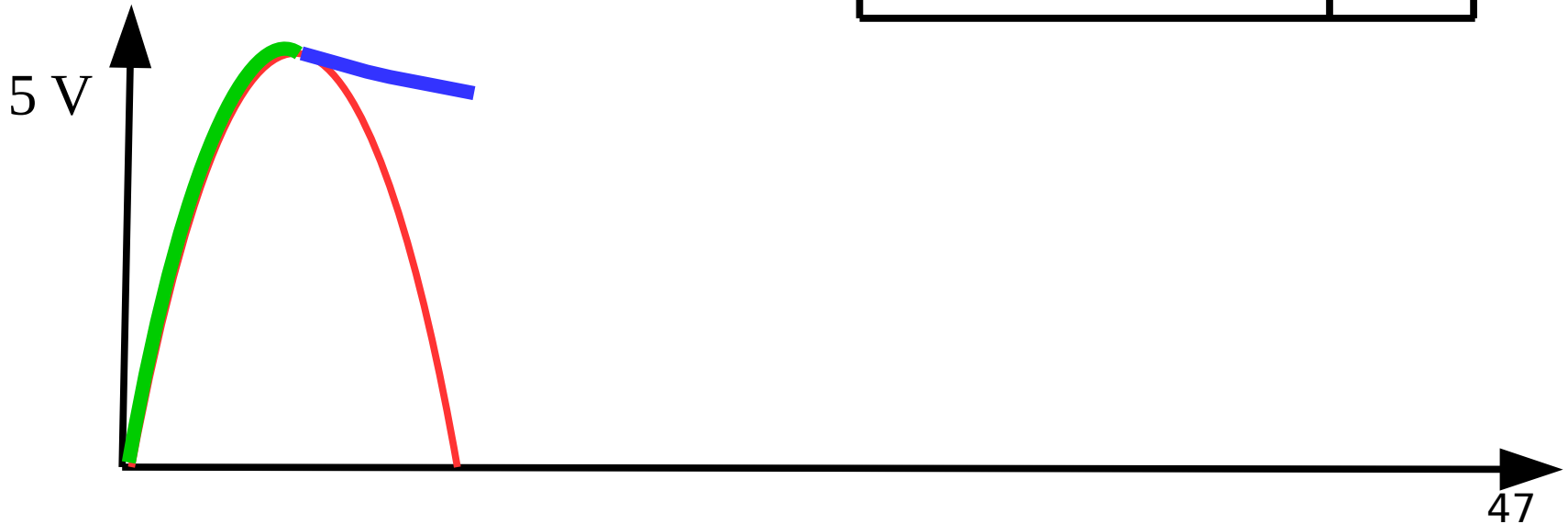
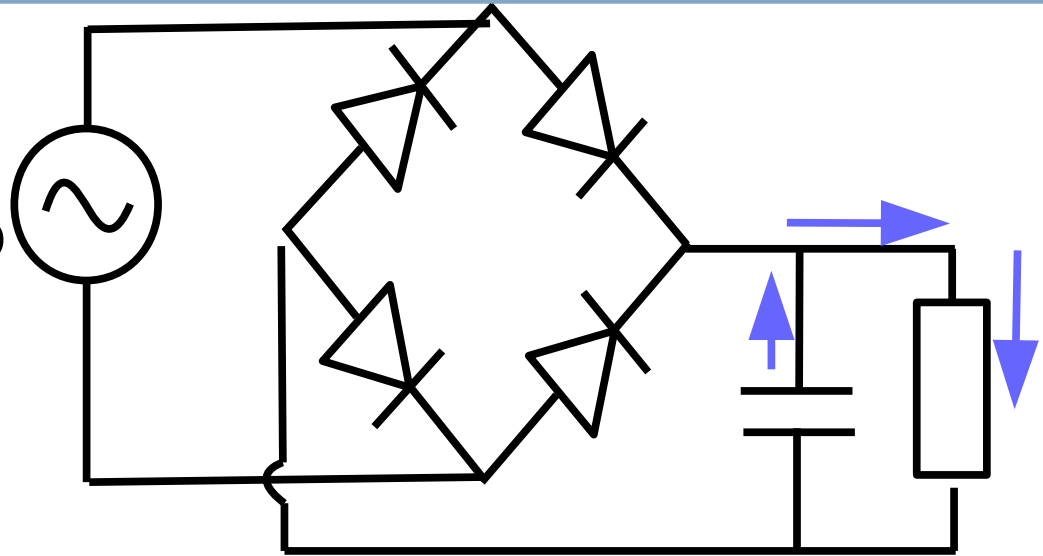
## But why is this?

When the supply voltage starts to dip the capacitor will keep the voltage high and supply the circuit with voltage/charge.


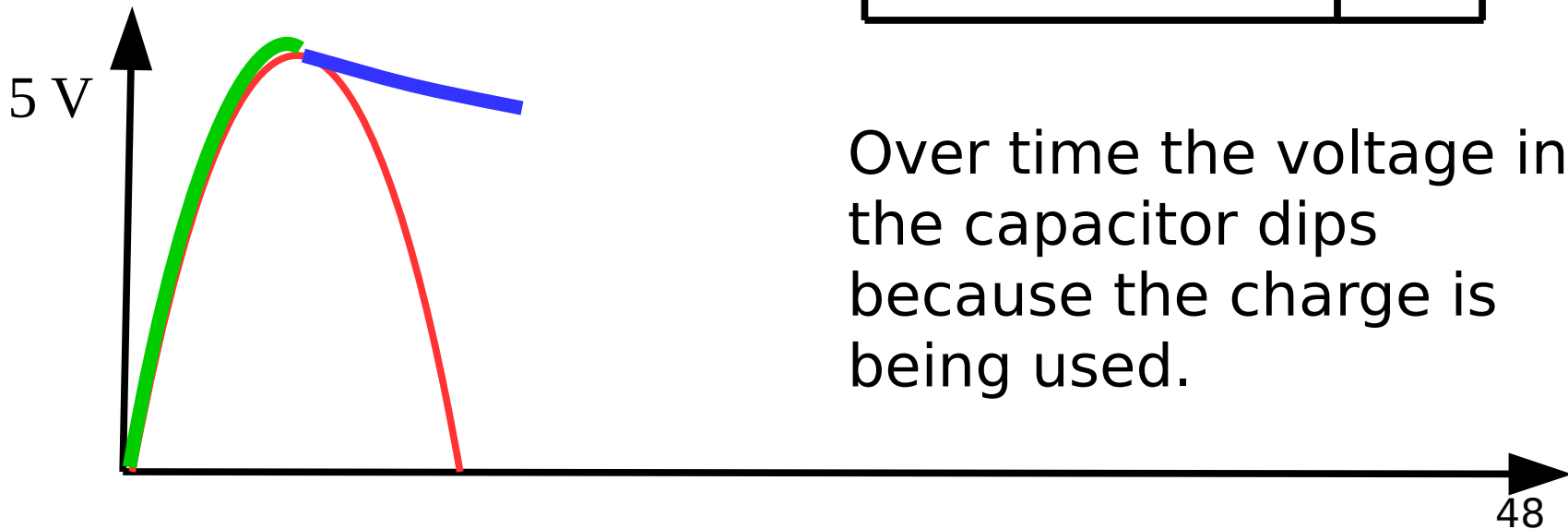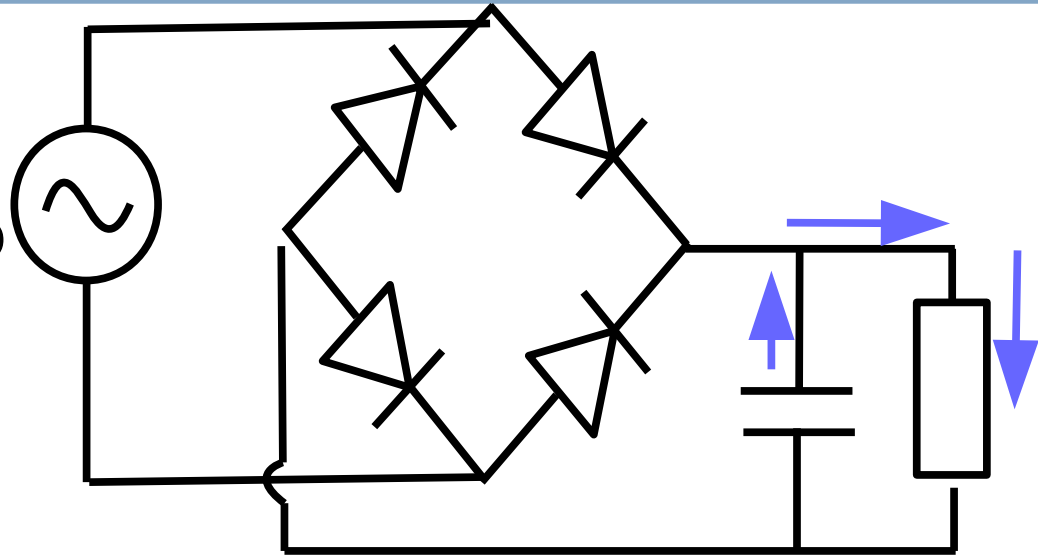
## But why is this?

When the supply voltage starts to dip the capacitor will keep the voltage high and supply the circuit with voltage/charge.





Over time the voltage in the capacitor dips because the charge is being used.



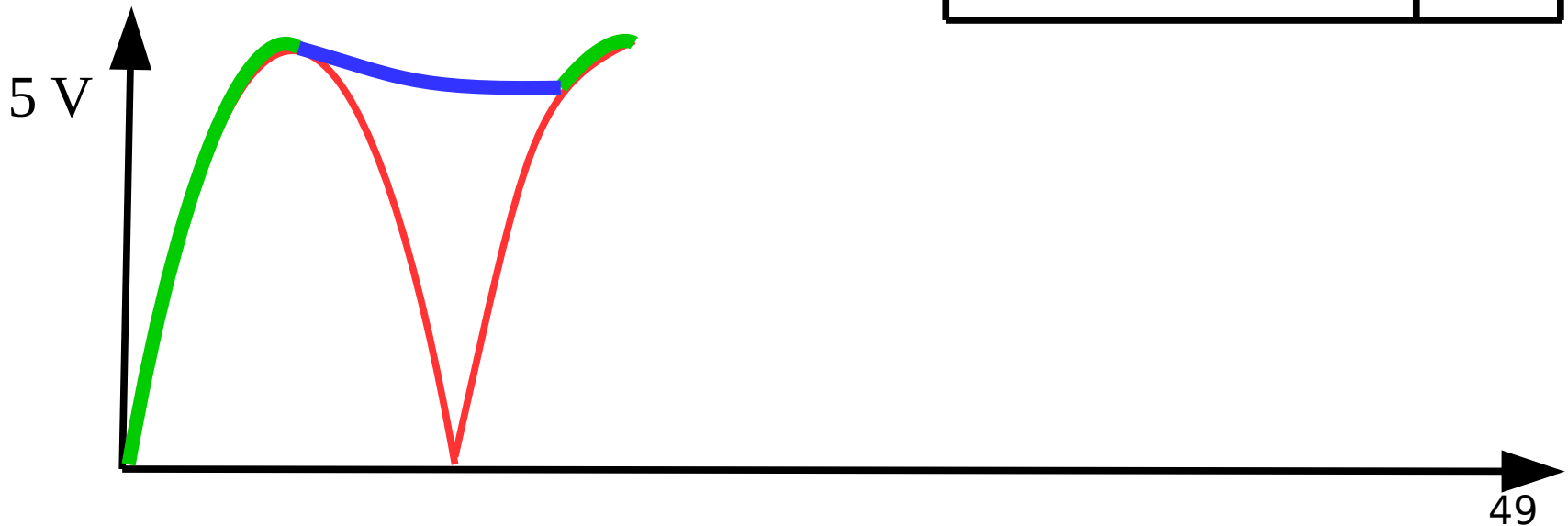
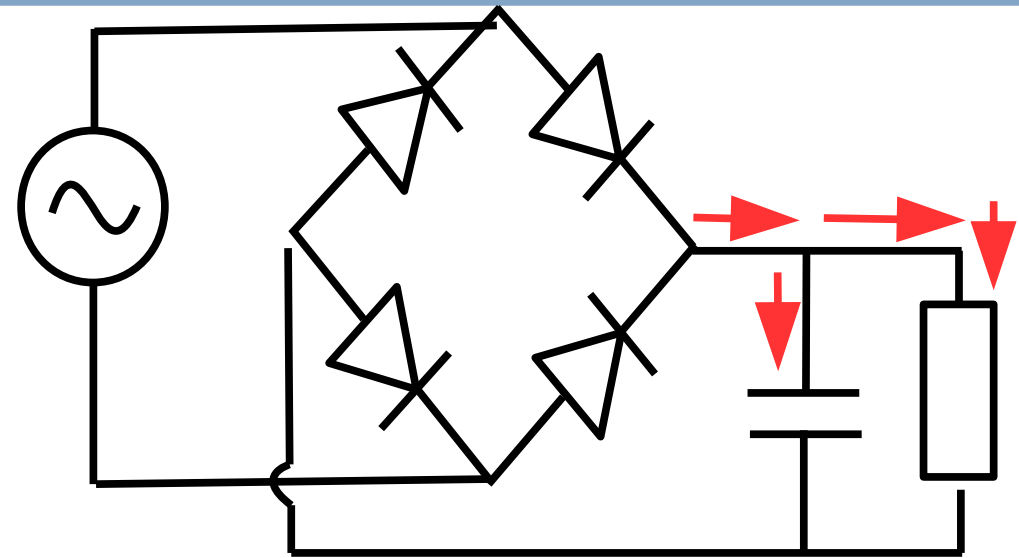
## But why is this?

On the next cycle the capacitor will charge and power will be supplied to the circuit.



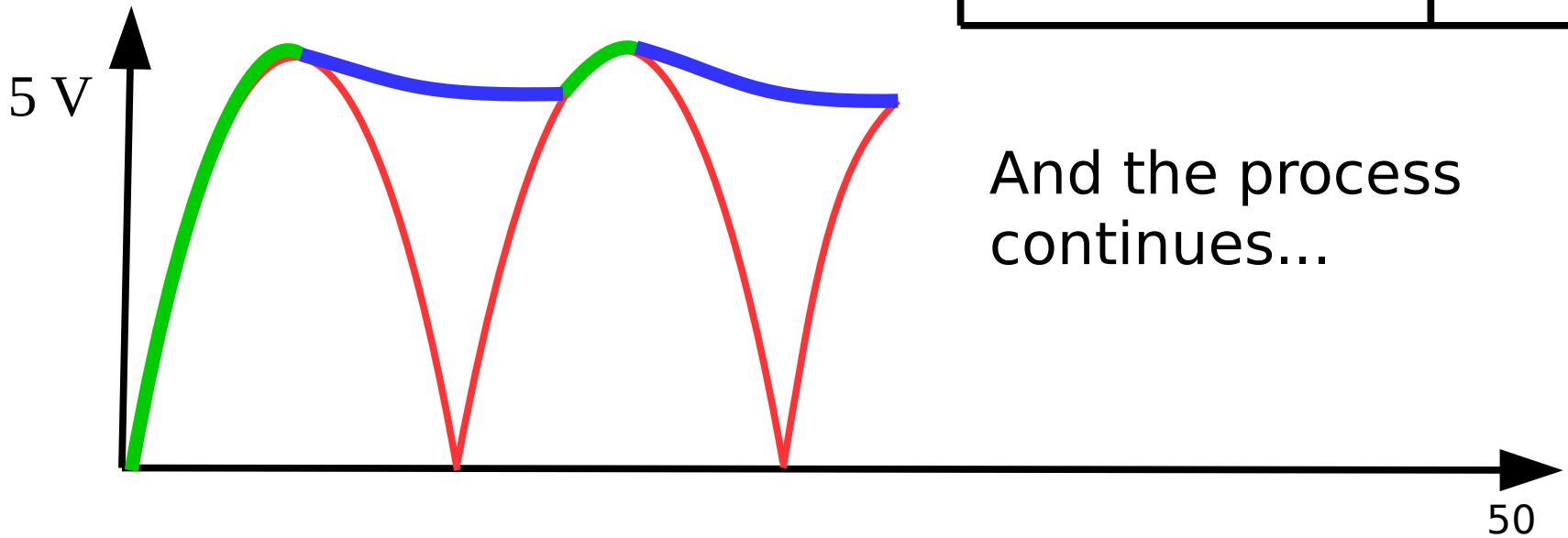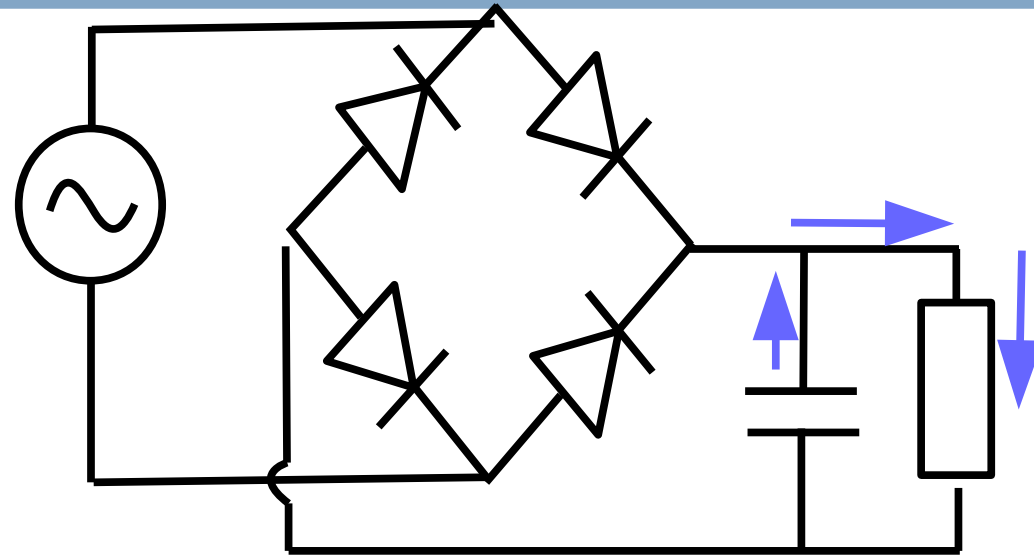
# But why is this?



Over time the voltage in the capacitor dips because the charge is being used.



# A non perfect DC supply

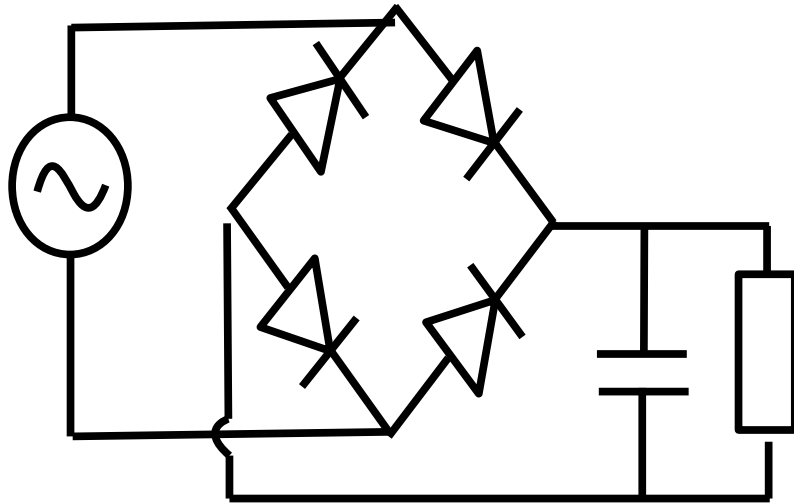

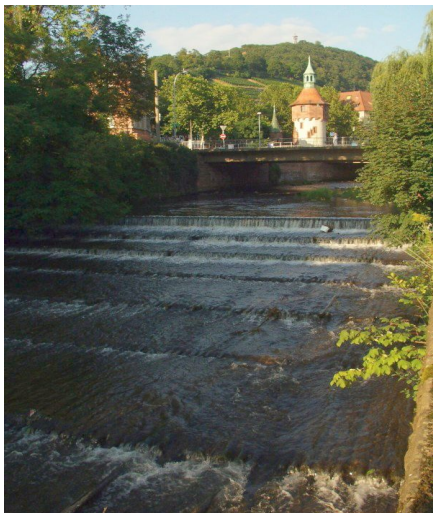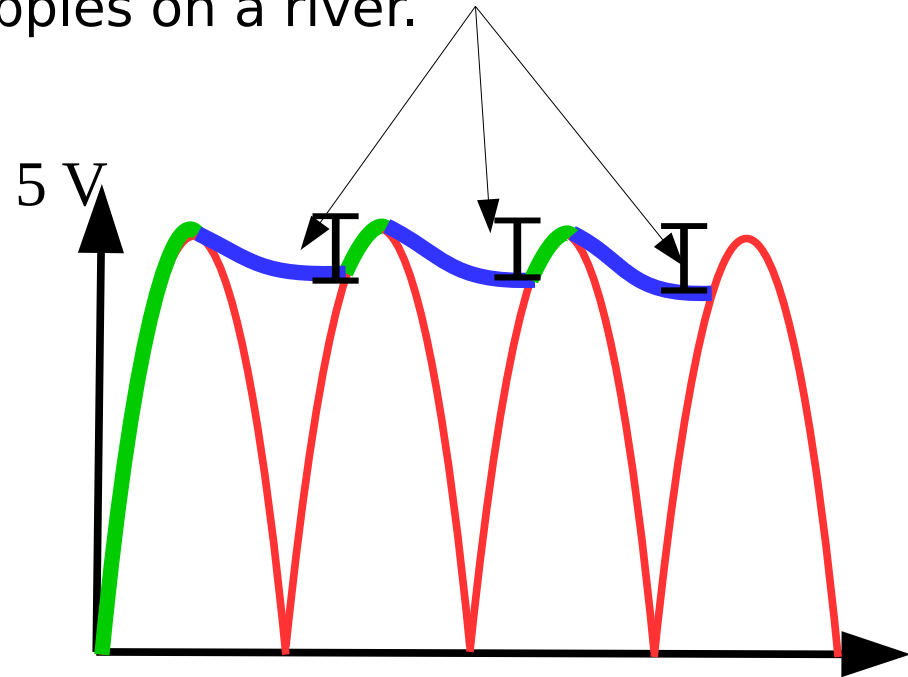
This voltage here is called the ripple voltage - think of it as the ripples on a river.



Philipp Hertzog


How might you make this ripple voltage smaller?

# Ripple voltage

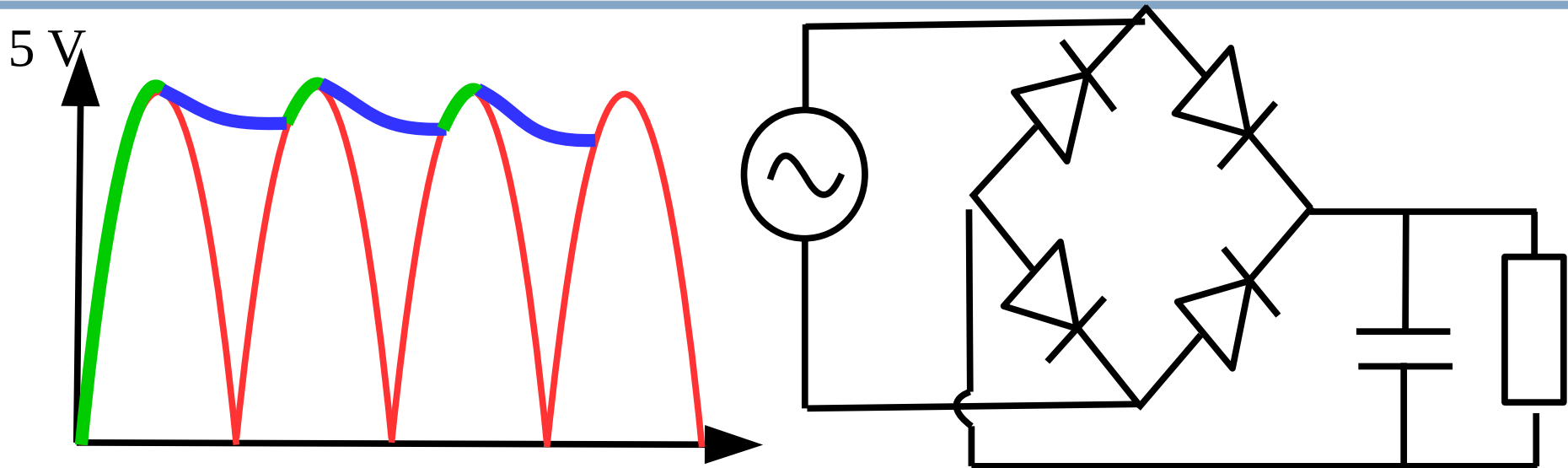

- Increase the size of the capacitor so it can supply more charge for longer.
- Make your device uses less charge.

# Calculating the ripple voltage

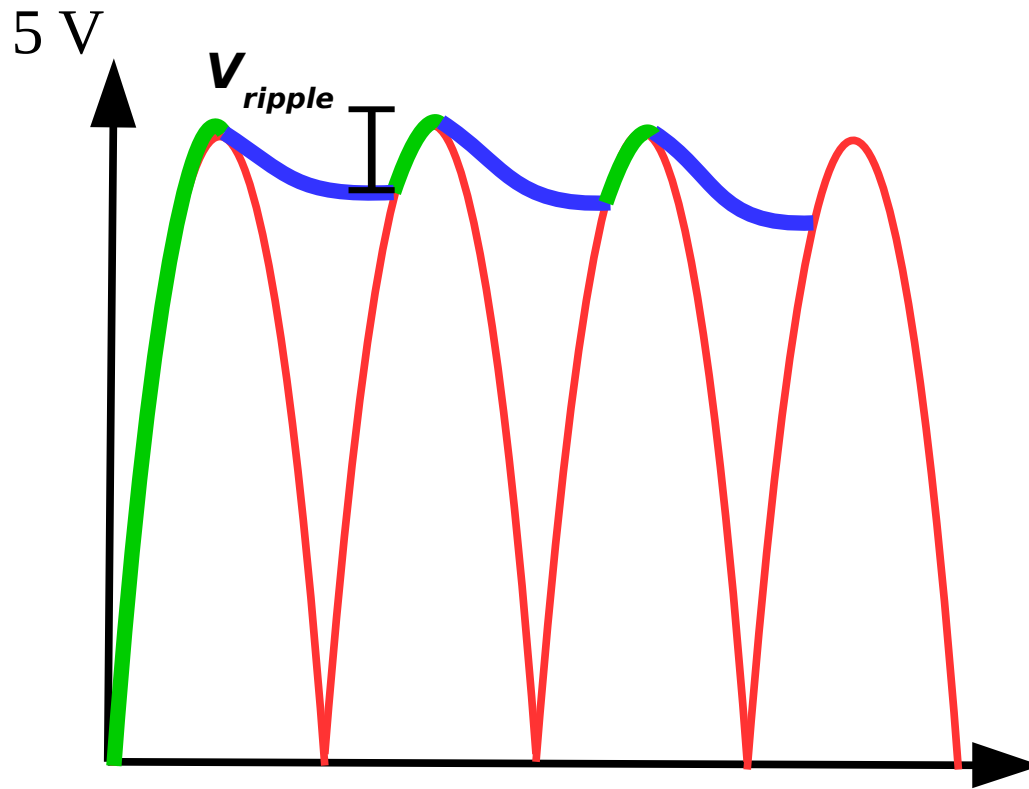

$$V_{\text{ripple}} = \frac{I}{fC}$$

Where  $V_{\text{ripple}}$  is the ripple voltage,  $f$  is the frequency,  $C$  is the capacitance and  $I$  is the current being drawn.

$$V_{\text{ripple}} = \frac{I}{fC}$$

You are designing a 5V DC power supply to deliver 10 mA, from a 50 Hz supply. You pick a  $100 \times 10^{-6}$  F capacitor.

What ripple voltage would the power supply have? Is this reasonable?

What value of capacitor would you need to have a ripple voltage of 0.2 V.

# Exam question




**A: 2V**

**A: No.**

**A:  $1000 \times 10^{-6}$  F**

## Getting rid of ripple


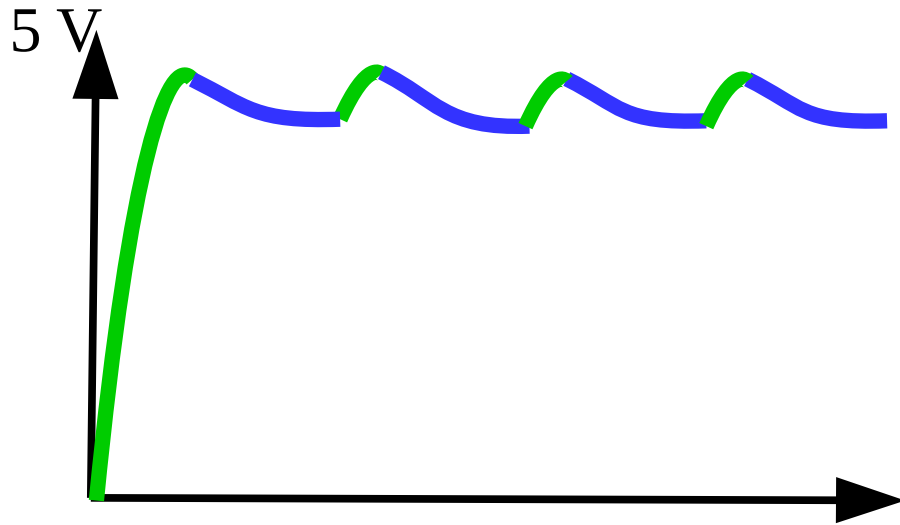


However, in reality no matter what you do to the size of the load or the capacitance of the supply **you will always get ripple.**


- Sometimes this does not matter – **driving a DC motor – simple digital circuits** (may be).
- Sometimes this matters a lot, **powering complex digital circuits, computers and audio amplifiers.**



# Perfect DC - the voltage regulator

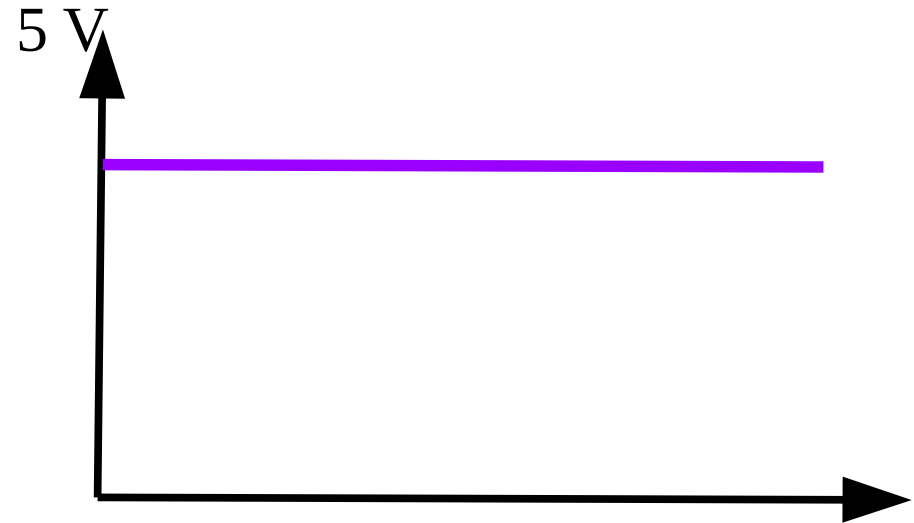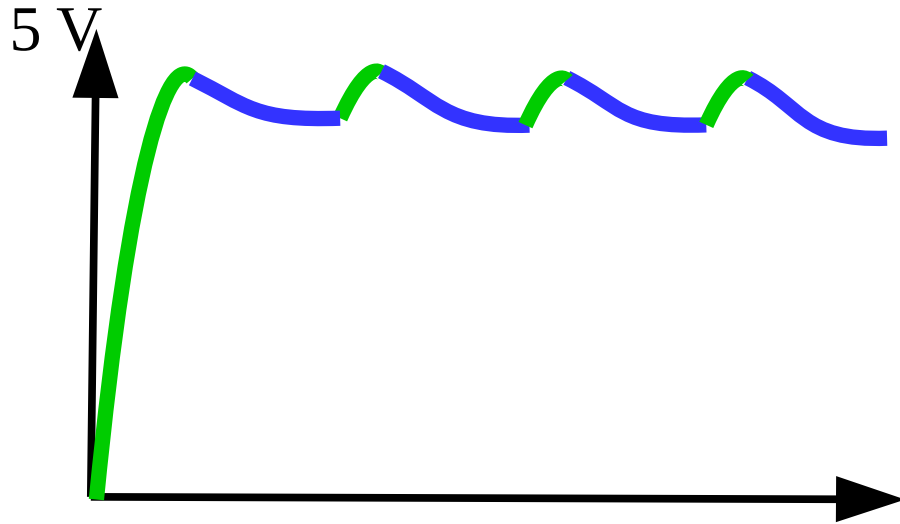


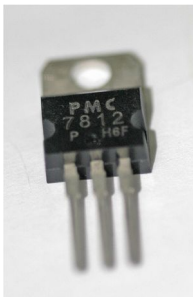
•If you want a perfect DC voltage source you have to use a voltage regulator which looks like this:



Mataresephotos
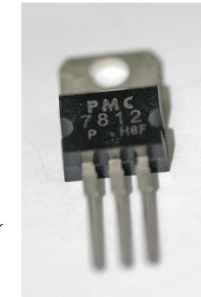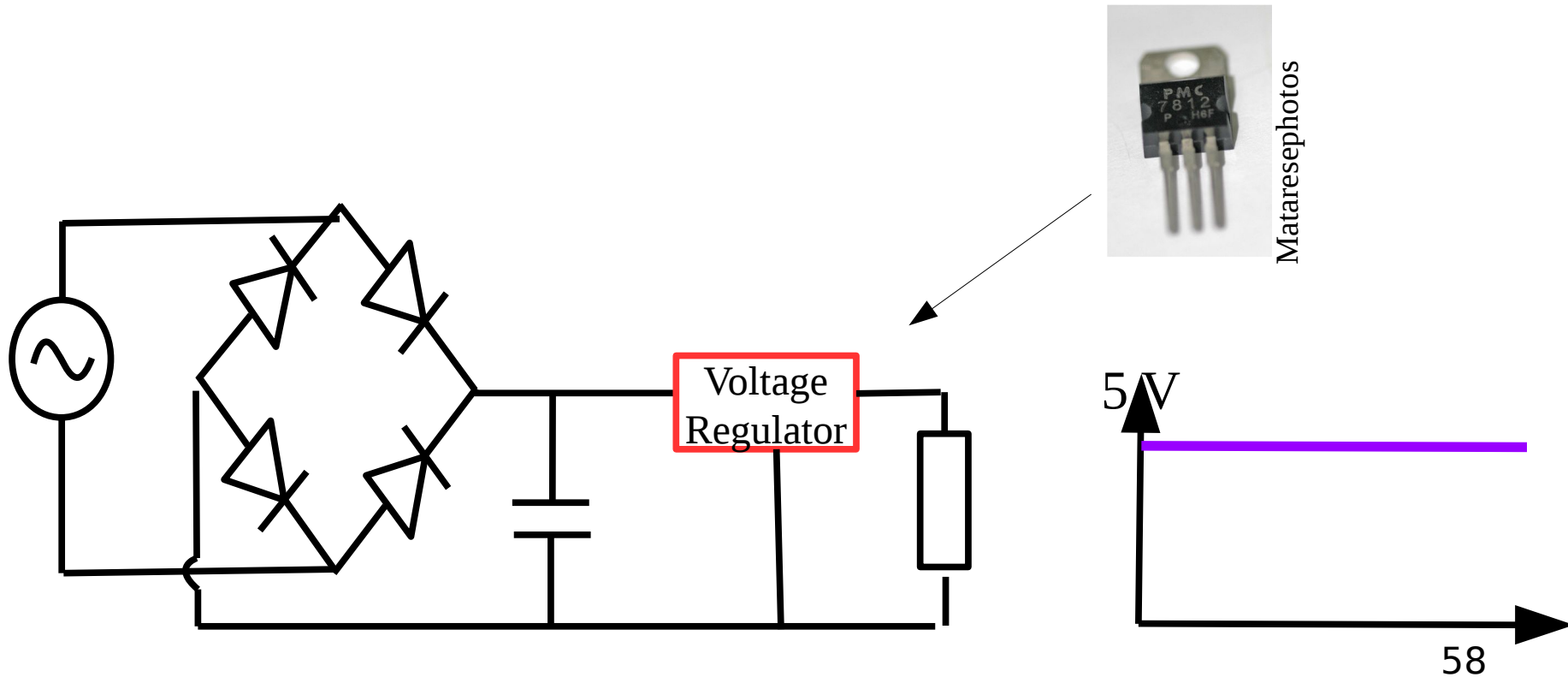
# Voltage regulator

- You stick it on the output to your capacitor and you get nice DC out.





Mataresephotos

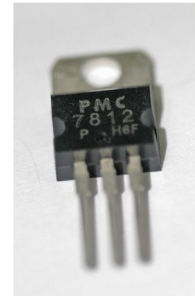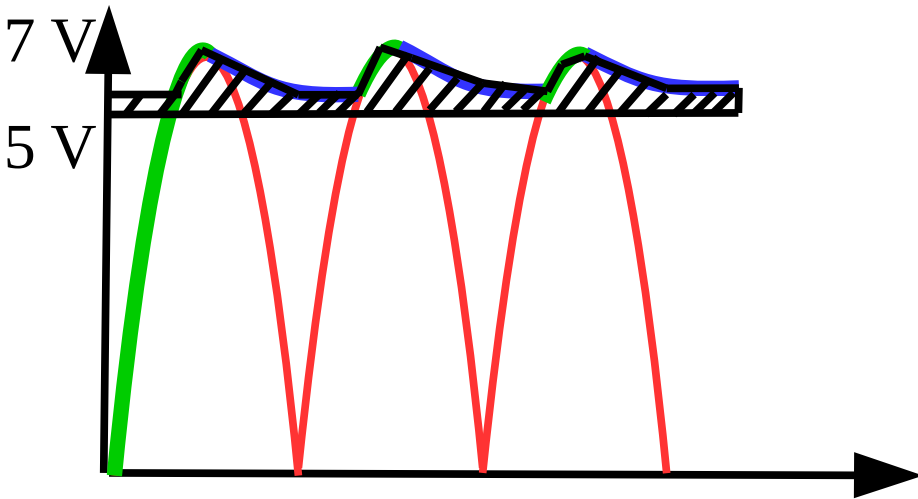
# How does the voltage regulator work?



- In simple terms, it's got a smart resistor in it that absorbs any excess voltage.



Matarsephotos

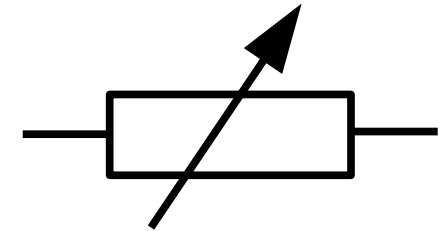

- This means it will waste quite a lot of power and get hot! So bolt it to a heat sink to it.




# How does the voltage regulator work?



- Recap of last lecture
- Introduction to diodes.
- Power diodes – the basics.
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode**
- Other kinds of diodes including Solar cells
- Summary

# Recap: The ideal diode


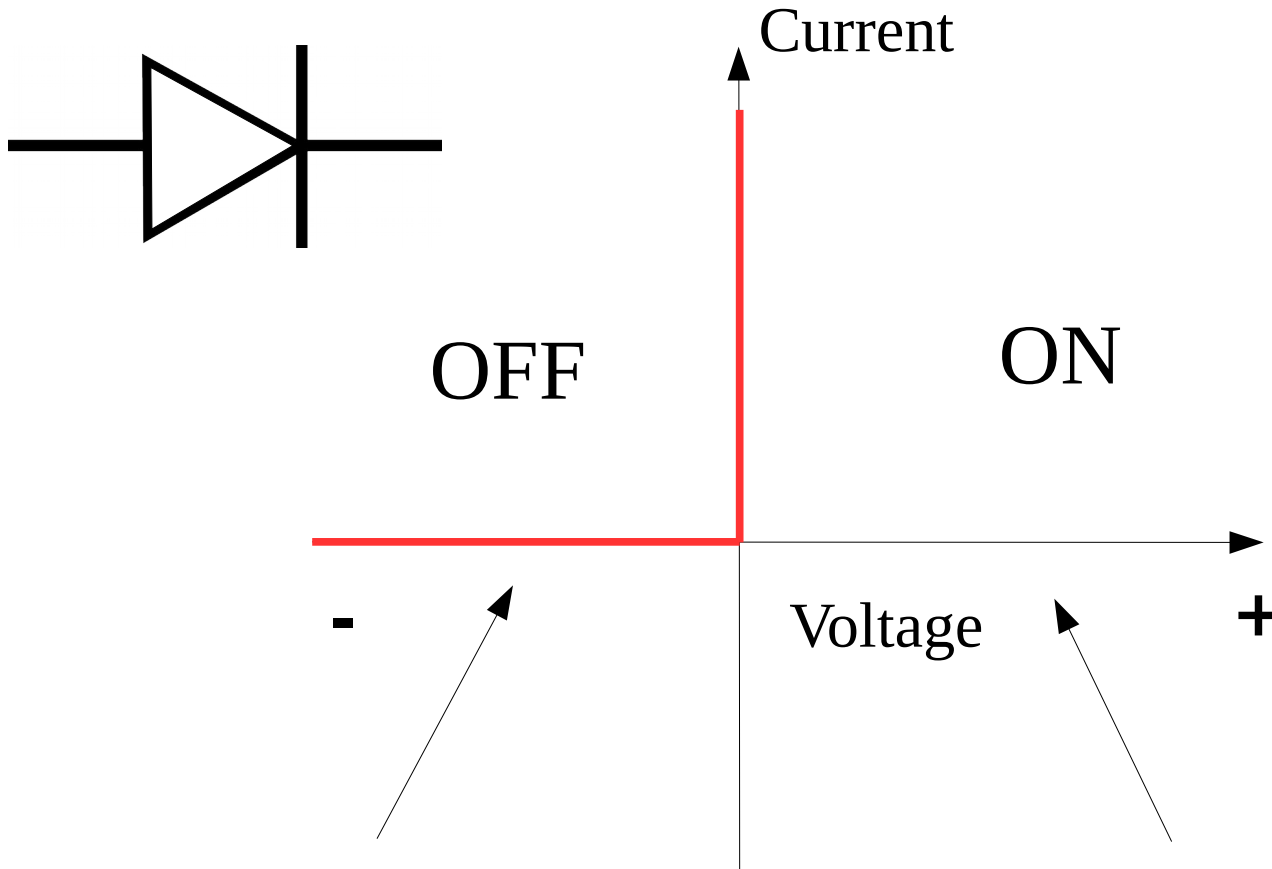


At negative voltages it blocks current

At positive voltages any amount of current can flow


# A less ideal diode

Morcheeba at en.wikipedia

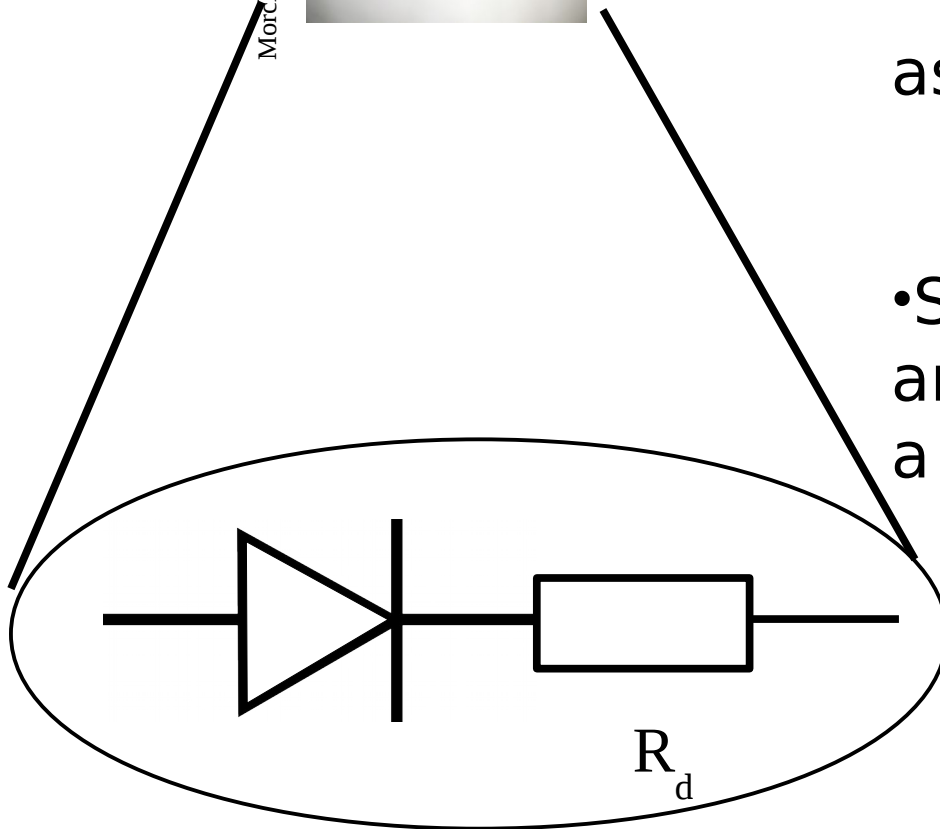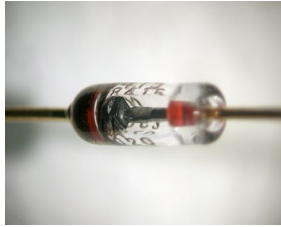

- However real diodes are like any other device they have a resistance  $R_d$  associated with them.
- So you can think of them as an ideal diode in series with a resistor.

# A less ideal diode

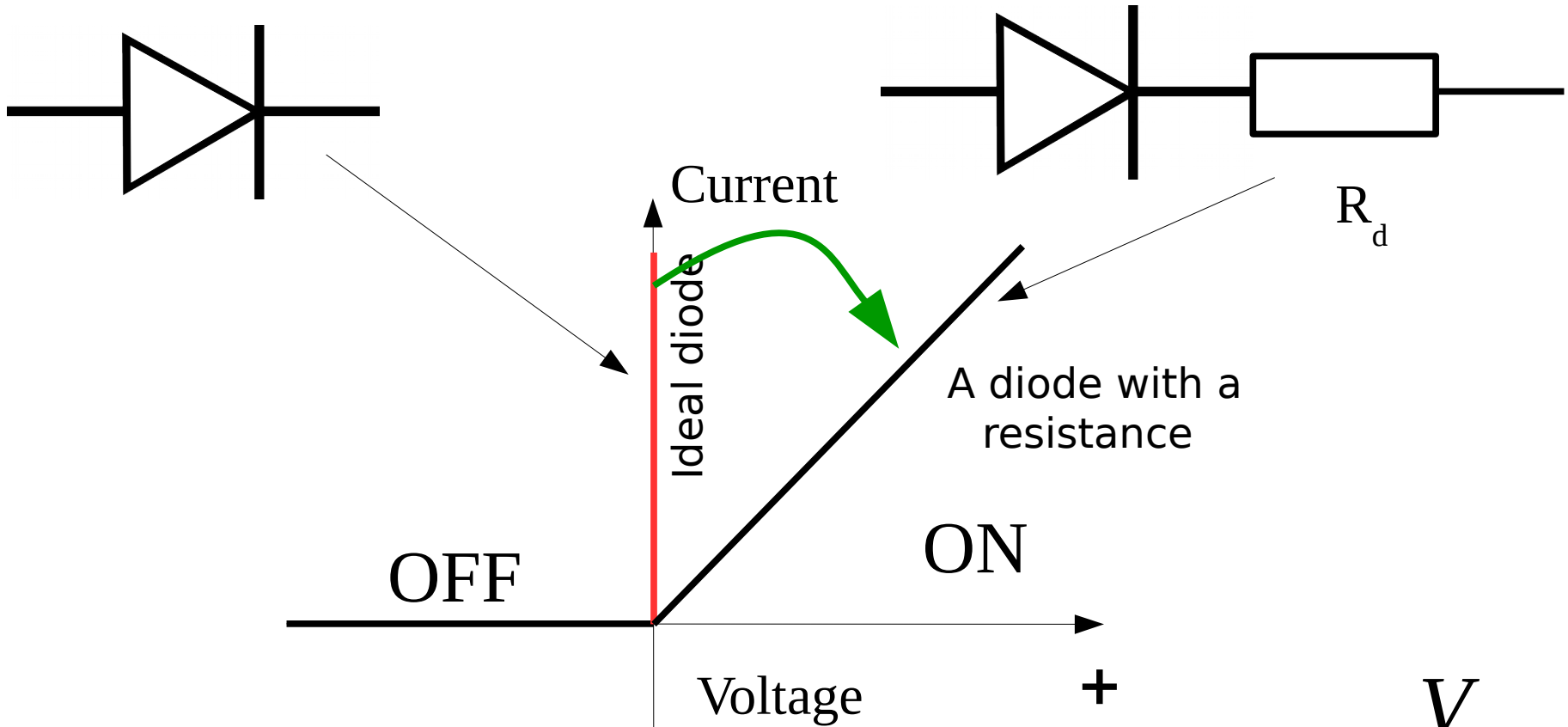


$$R_d = \frac{V}{I}$$

- This means there will be some resistive power loss over a diode.
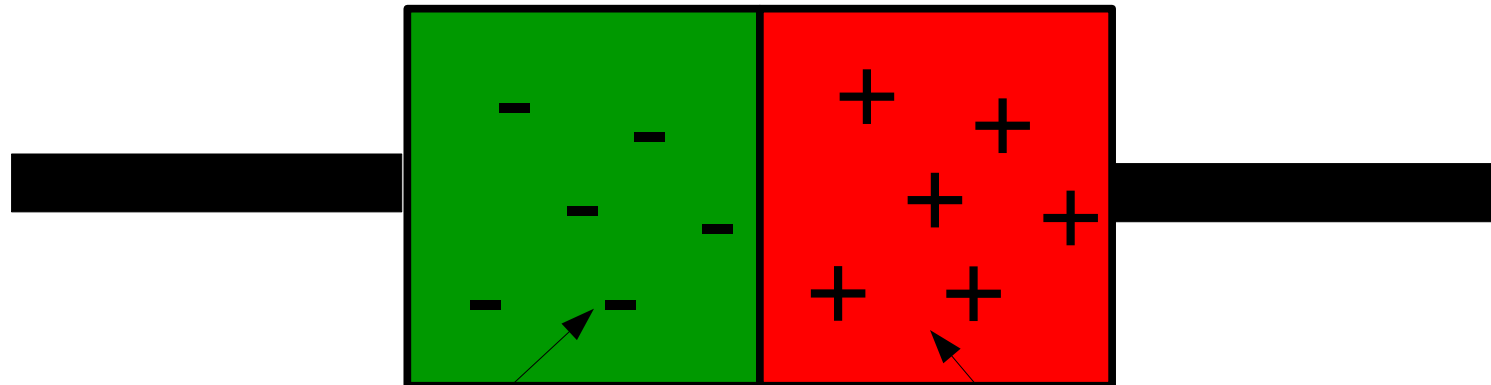
## Furthermore.....

- Diodes are made of two materials, one with lots of negative charges and one with lots of positive charges




Negative charges  
called an **n-type**  
material

Positive charges  
called a **p-type**  
material



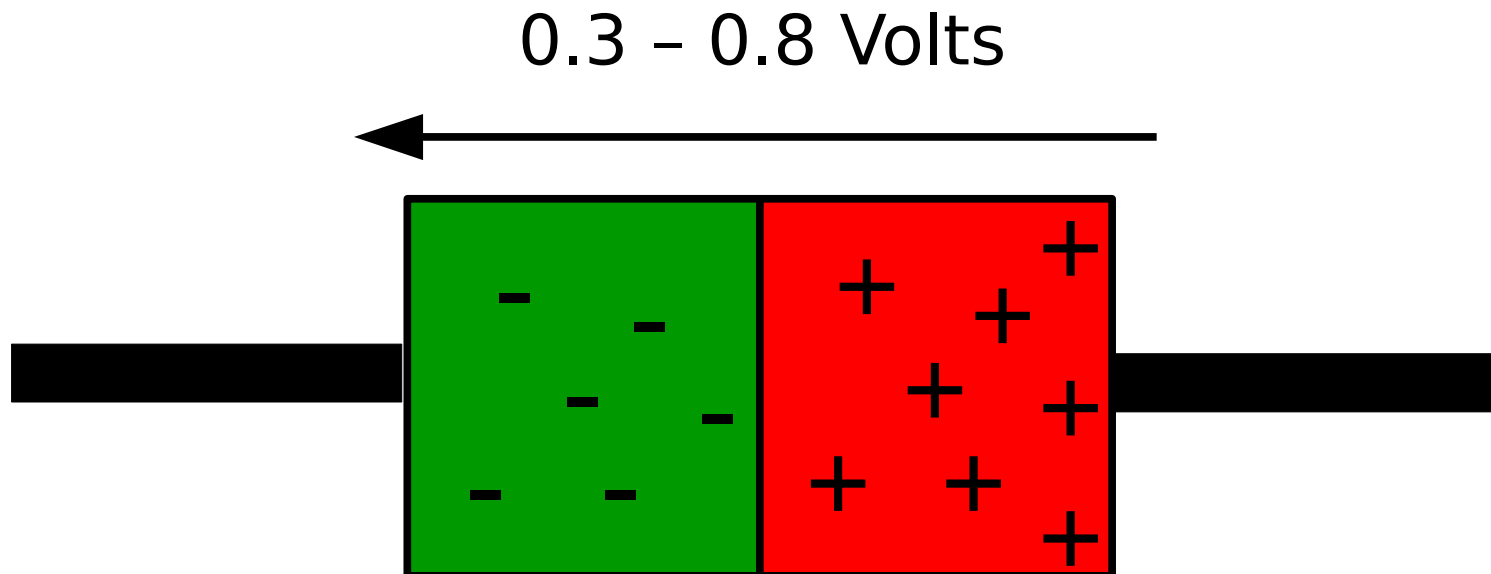
## Positive and negative charges

- This charge build in the device means that every diode produces a voltage of between 0.3 V to 0.8 V.
- This is called the built in potential.




- In some applications this built in potential is a pain, in others it is really useful

# A diode with a built in potential

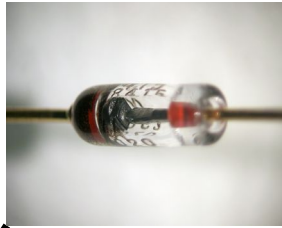

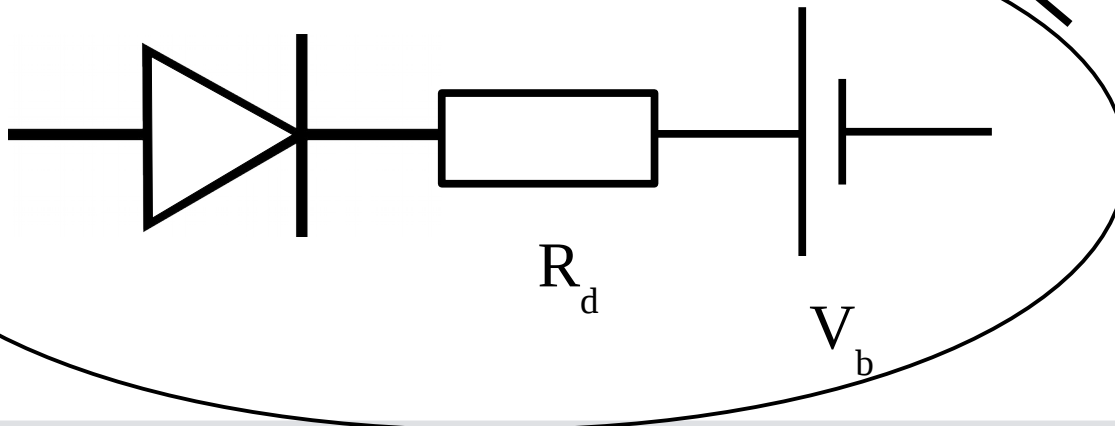- Because of this built in charge you can actually think of a diode as having a small (0.3 V-0.8 V) battery in series with it.





# The built in potential



- This means you need to apply 0.3-0.6 V to a diode to turn it on.


Morcheeba at en.wikipedia

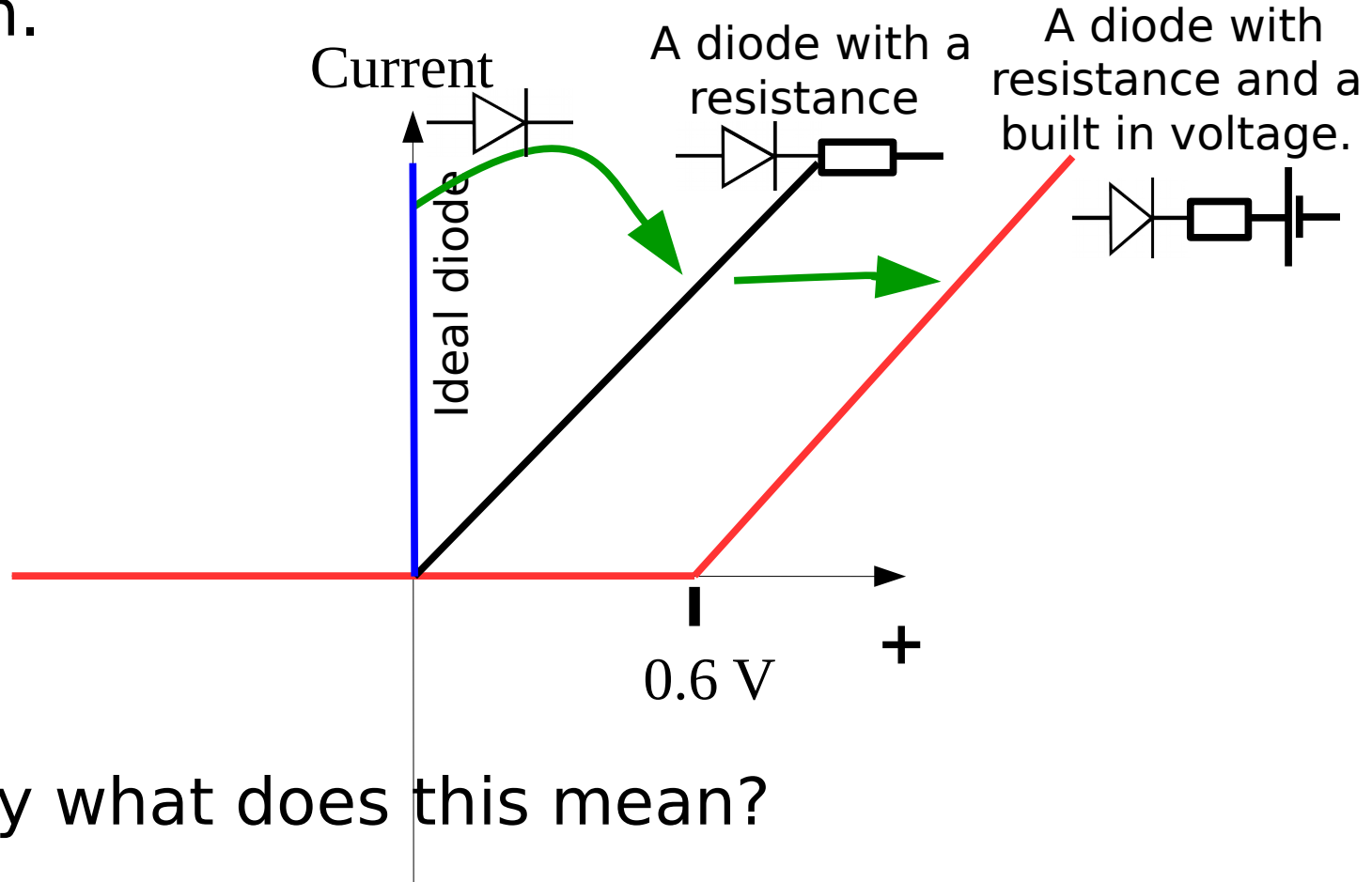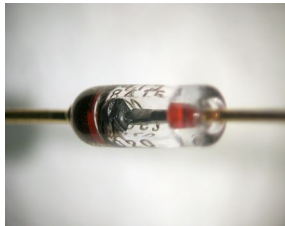

- Practically what does this mean?
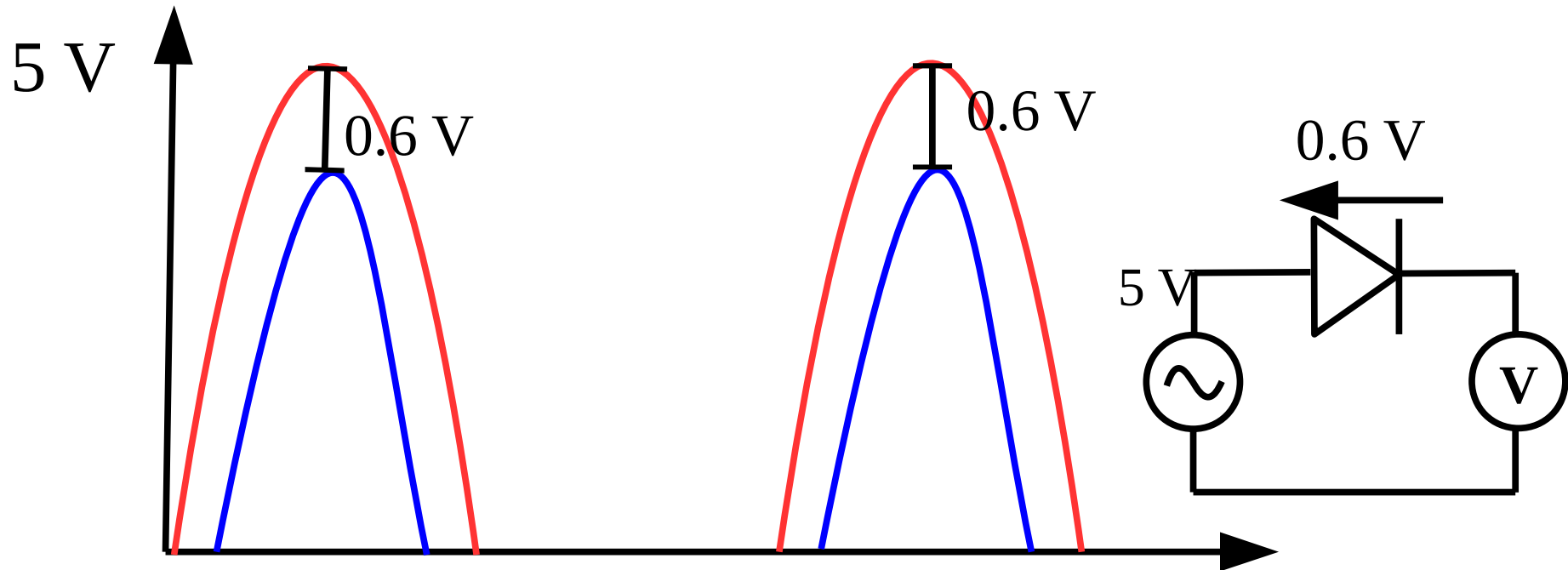
## What does this built in voltage mean in practical terms.

- We will always get 0.3-0.8 V lost when we use a diode.




- So when ordering a transformer for a 5V chip – make sure it provides at least 6V.

# How does the voltage regulator work?



- Recap of last lecture
- Introduction to diodes.
- Power diodes – the basics.
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode
- Other kinds of diodes including Solar cells**
- Summary

# Different types of diodes

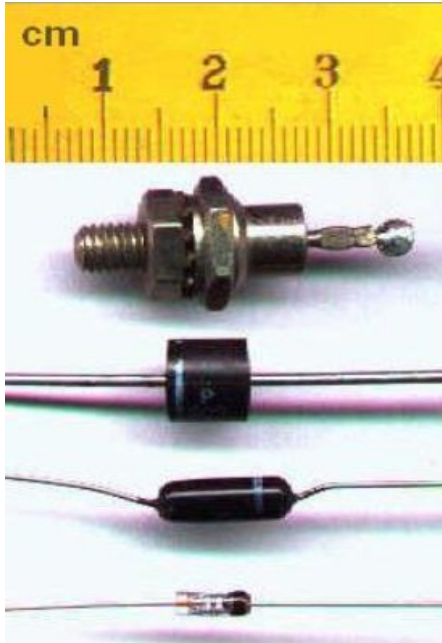

The diodes we have talked about up to now look like this and are made of silicon.




**Silicon (Si)**

- However if you change the material from which a diode is made it can do far more than just block current.
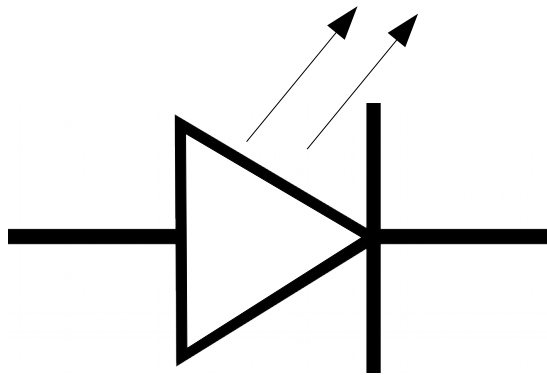
# Or Light Emitting Diodes

- If you make the diode of **gallium (Ga)** and **arsenic (As)** the diode will generate light.
- And you get an Light emitting diode (LED)




PiccoloNamek



**Gallium (Ga)** 71
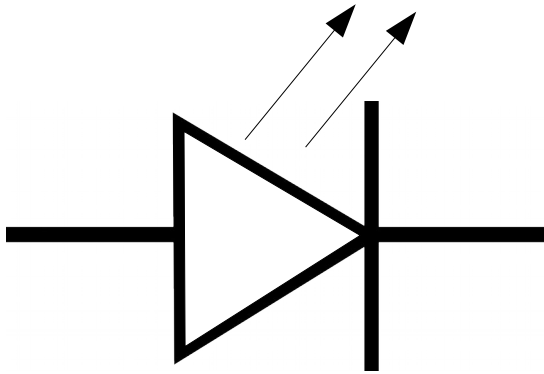
# Lasers

- If you focus the light coming out of a LED structure you can get a laser.



Bành Gia Kiệt



**Gallium (Ga)** 72



- Recap of last lecture
- Introduction to diodes.
- Power diodes – the basics.
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode
- From a diode to a solar cell**
- Summary

# Why learn about solar cells?





Dwernertl


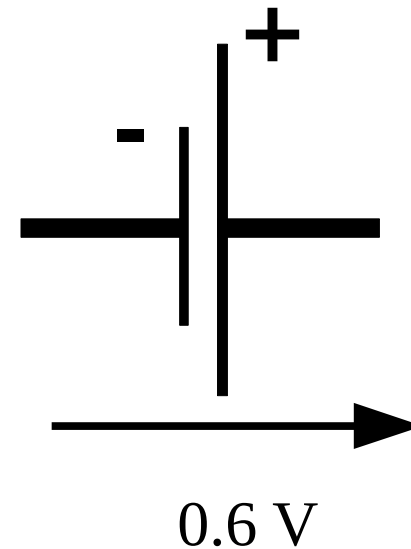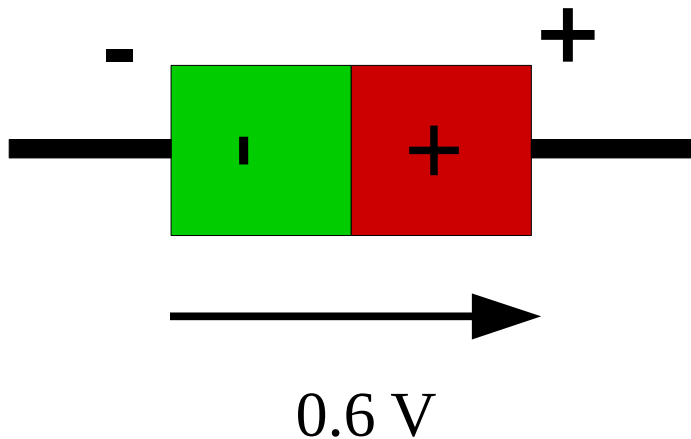
# From a diode to a solar cell..



- I said previously that a diode is made of two types of material and **n-type** material and a **p-type** material.
- Because of this a diode always has a voltage across it a **bit like a battery**.




- Let's draw this a bit bigger....


# From a diode to a solar cell..



- Here is our diode again.



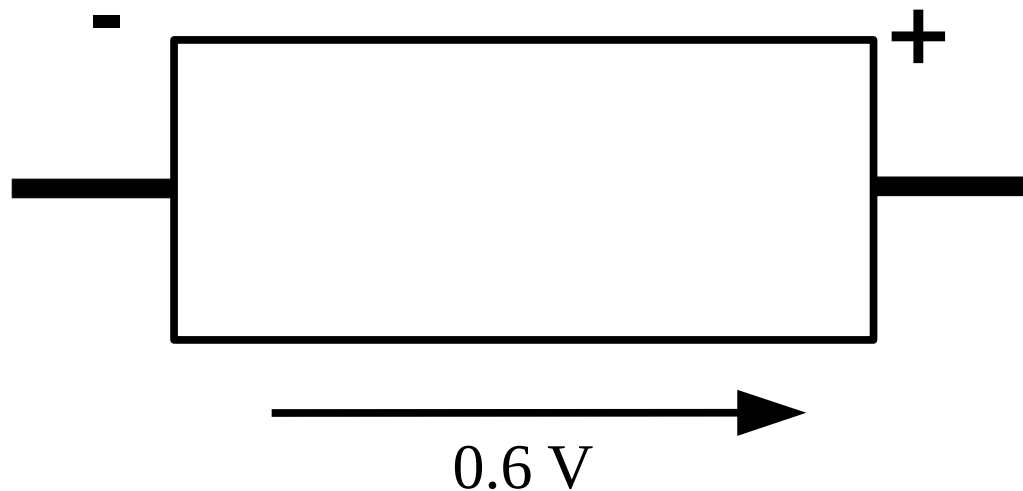


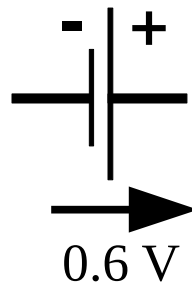- Now let's change the material so it absorbs light.



# A light adsorbing diode...

- Light adsorbing material.

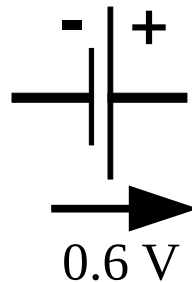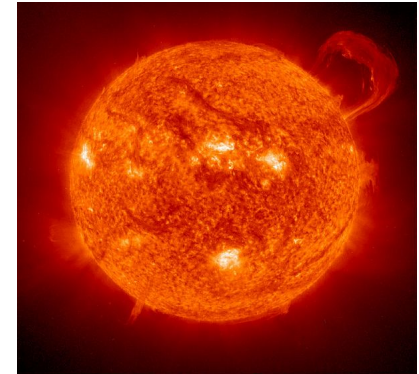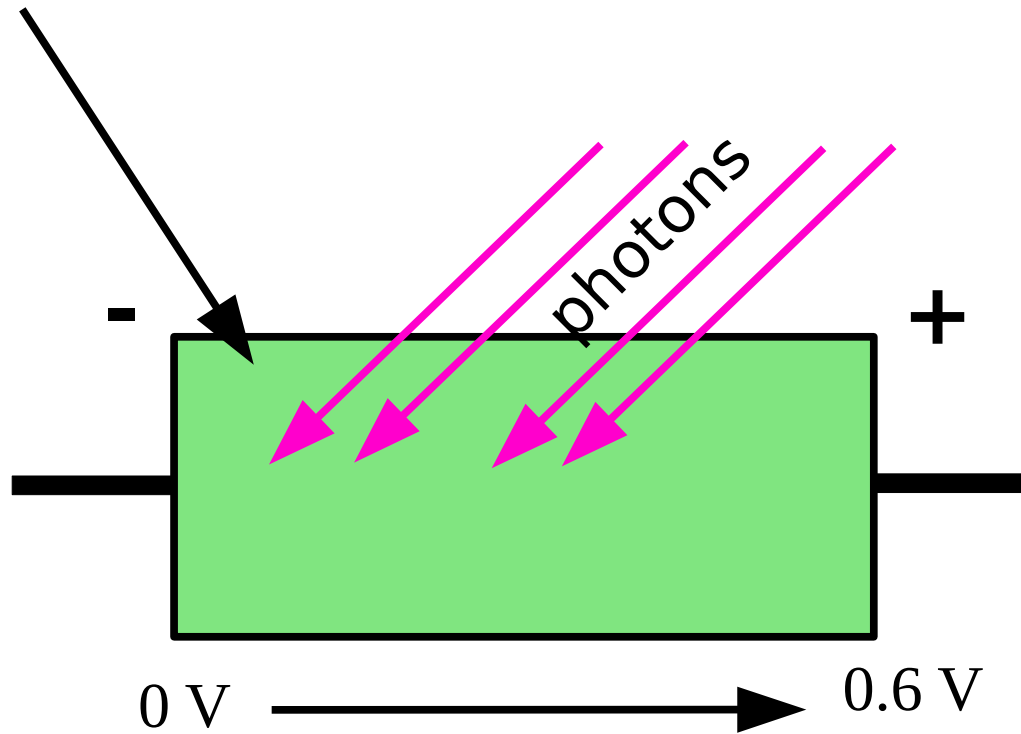


7
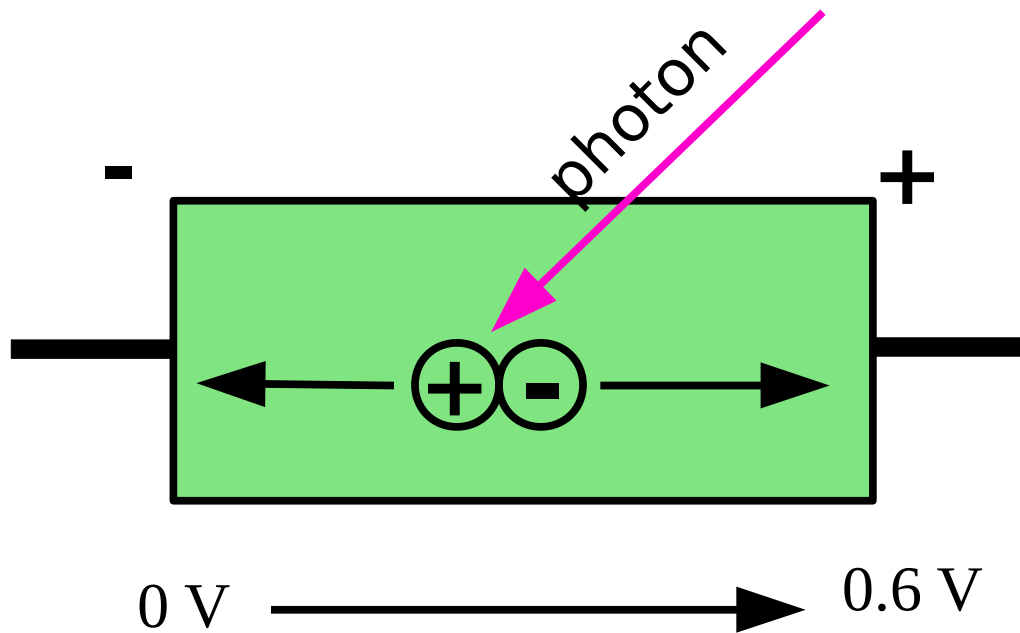
# Generation of charge...



- When a **photon** is adsorbed, it generates an positive and a negative charge...




- The field forces these charges to move towards the contacts.

0.6 V
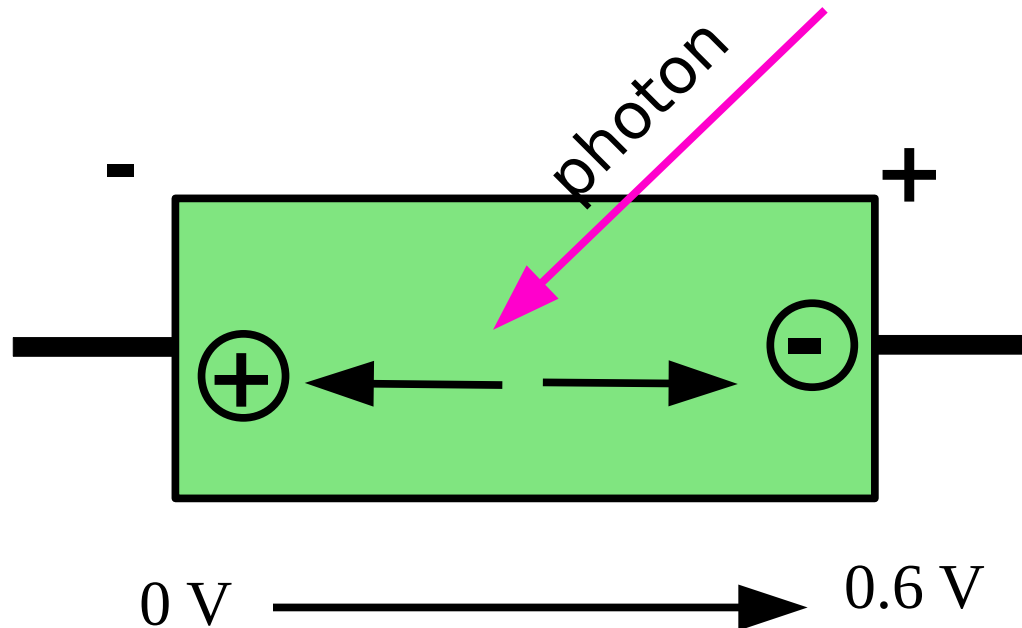
# When a photon is adsorbed in a material.....




- The positive charge goes to the negative contact and the negative charge goes to the positive contact.


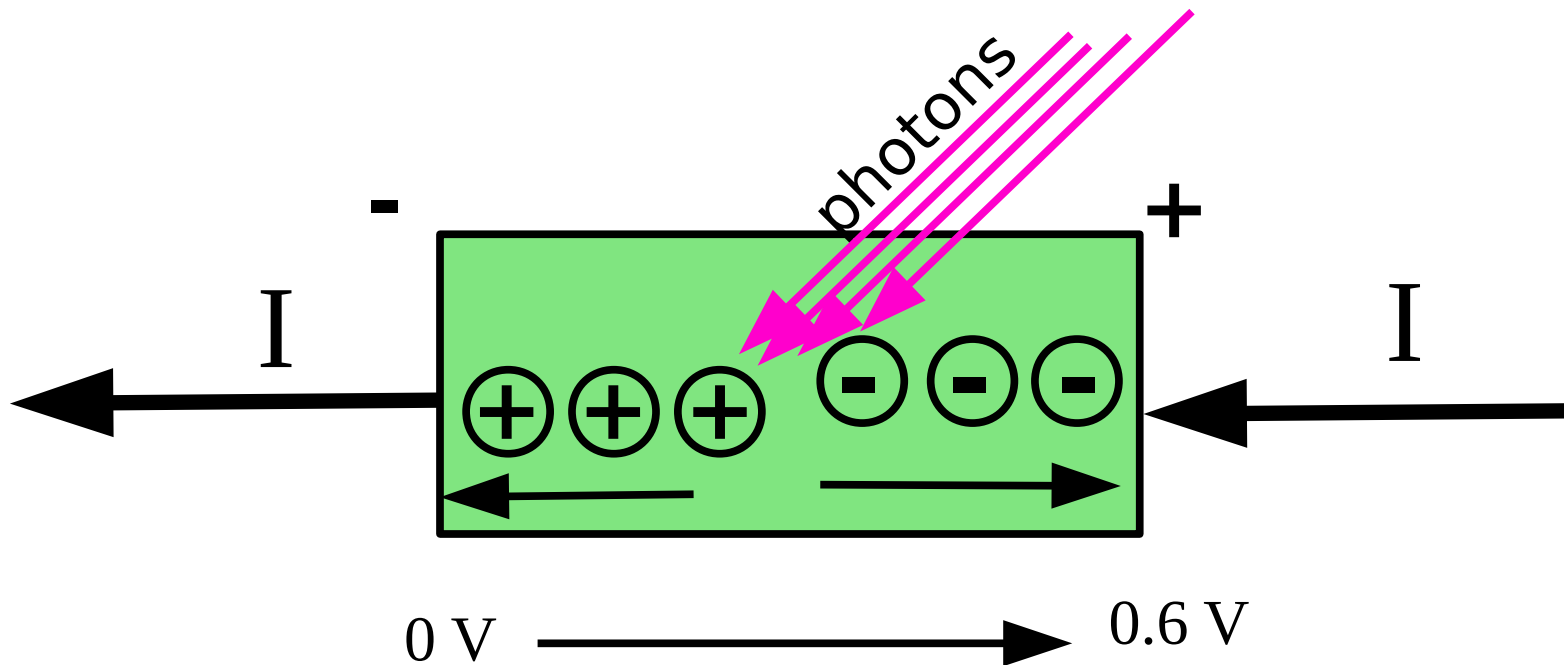
# When a photon is adsorbed in a material.....




- If lots of photons hit the diode lots of positive and negative charges move to the contacts and we get current in the external circuit.





# Power generation.....

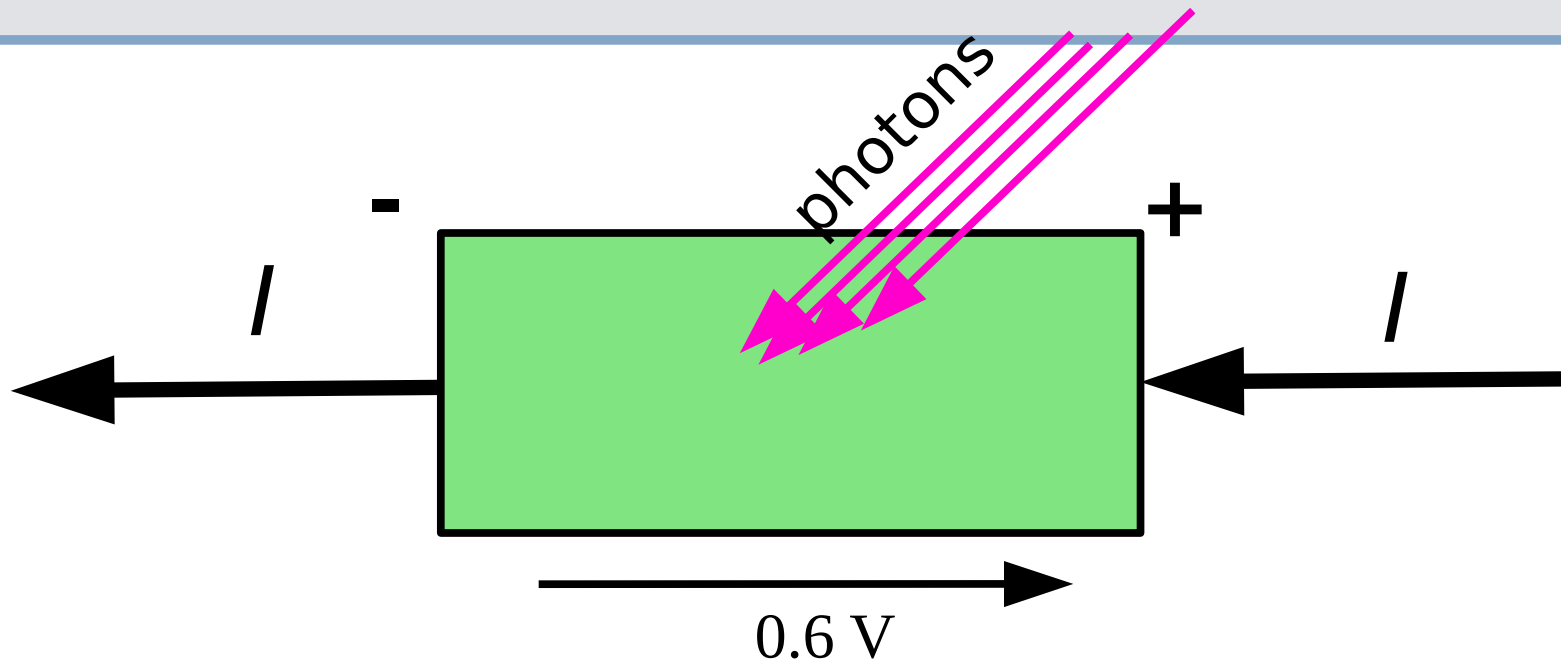

$$\text{Power} = I * V$$

N = Number of photons adsorbed per second per unit area.

A = Area of solar cell.

$$\text{Power} = A * N * q * V$$

**And we have a solar cell!!**

81

# Exam question



a) A  **$0.01 \text{ m}^2$**  solar cell produces a voltage of  **$0.6 \text{ V}$** , it adsorbs  **$1 \times 10^{20} \text{ m}^{-2}$**  photons per **second** if the charge on an electron is  **$1.6 \times 10^{-19} \text{ coulombs}$**  how much power will it produce.

$$\text{Power} = A * N * q * V$$

Power produced by cell = ???

b) How many pink **500 Watt** 'Hello Kitty' toasters would that run??



Janine from Mililani

# Exam question



A  $0.01 \text{ m}^2$  solar cell produces a voltage of  $0.6 \text{ V}$ , it adsorbs  $1 \times 10^{12} \text{ m}^{-2}$  photons per second if the charge on an electron is  $1.6 \times 10^{-19}$  coulombs how much power will it produce.


$$\text{Power} = A * N * q * V$$

$$\text{Therefore Power} = 0.06 \text{ W}$$

That's not enough to run anything - let alone a toaster...

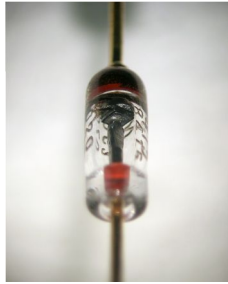
# Power generation.....

- So what we do is firstly make the diode (solar cell) as big as possible




↑  
$$\text{Power} = A * N * q * V$$

- So we just make it wider...

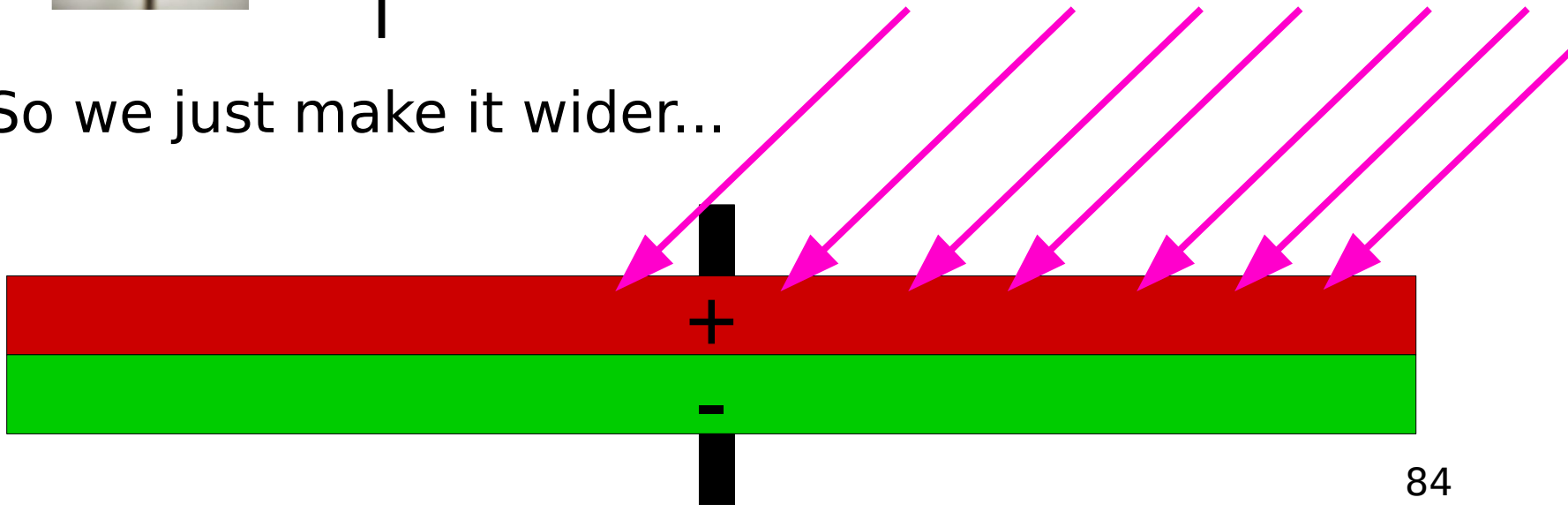

# And then we stack lots together

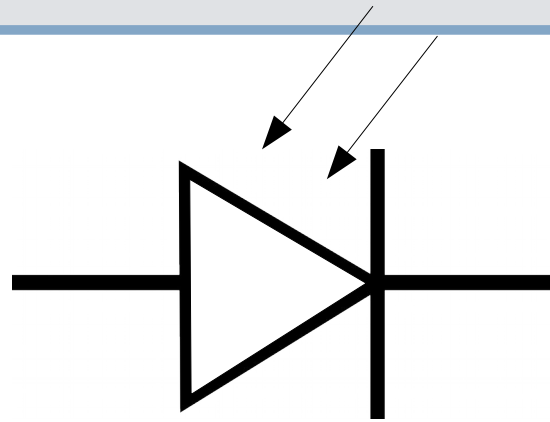


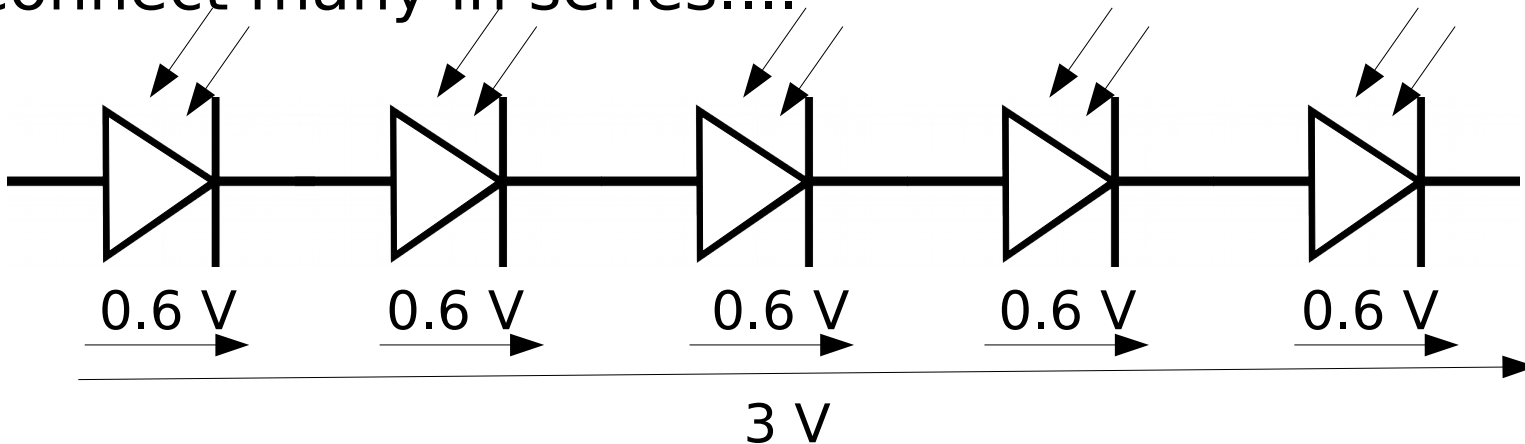0.6 Volts


$$\text{Power} = A * N * q * V$$



- However 0.6 V is not very much voltage, so we connect many in series....





# To make a solar module

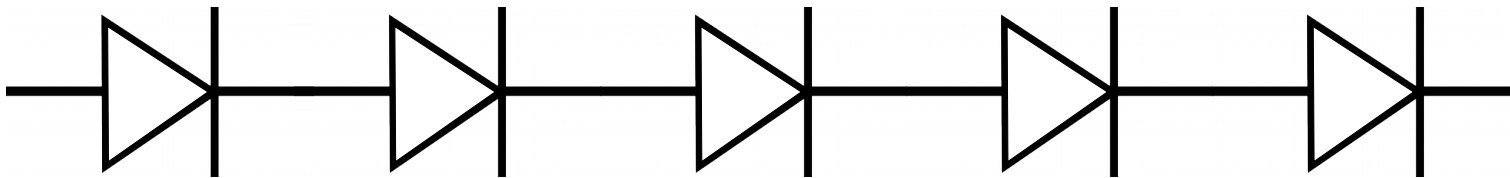


# Powering your device

- Now you can power your device

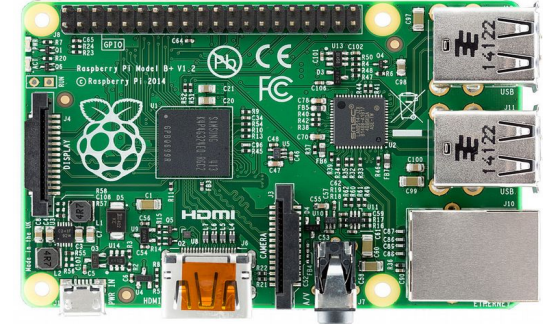 

Lucasbosch

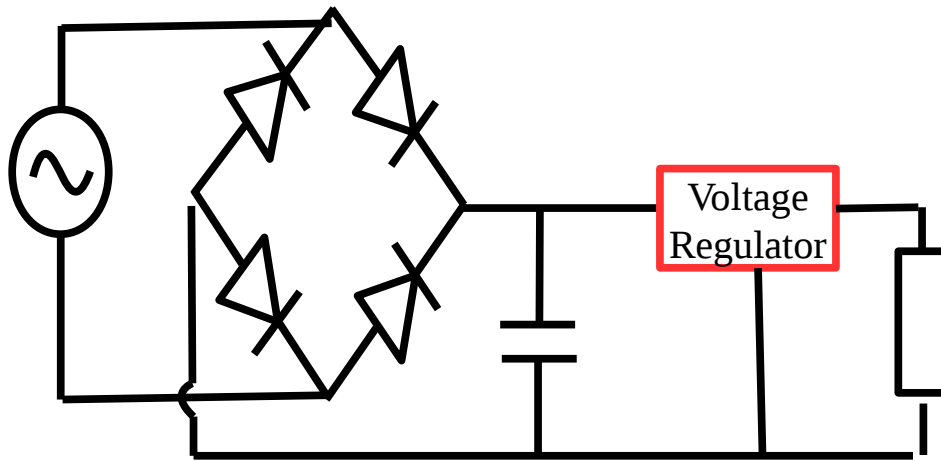

- From the mains



- And from the sun

- Recap of last lecture
- Introduction to diodes.
- Power diodes – the basics.
- Designing a power supply
  - Diodes the bridge between AC and DC
- The less ideal diode
- Solar cells
- Summary