

# **Electromechanical devices MM2EMD**

## **Lecture 7 - Transistors - Switching high voltage things on with a low voltage**

**Dr. Roderick MacKenzie**

**roderick.mackenzie@nottingham.ac.uk**

**Summer 2015**



**@rcimackenzie**

Released under  **creative  
commons**

- **No recap of last lecture :)**
- Transistor basics
  - Relays (Mechanical transistor)
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- One last thing
- Summary



# Outline of the lecture

- No recap of last lecture :)
- **Transistor basics**
  - Relays (Mechanical transistor)
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- One last thing
- Summary

Think back to lecture 1.



## Smart Electronic Circuits (low voltage)



Dave Jones



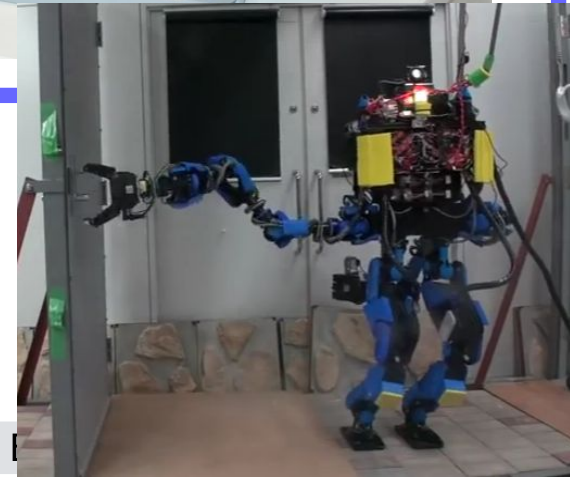
## Simple Electrical Circuits (high voltage)



S.J. de Waard


- This lecture is making low voltage electronics control high voltage electrical devices such as motors.




# Think about an AND gate chip



And gate

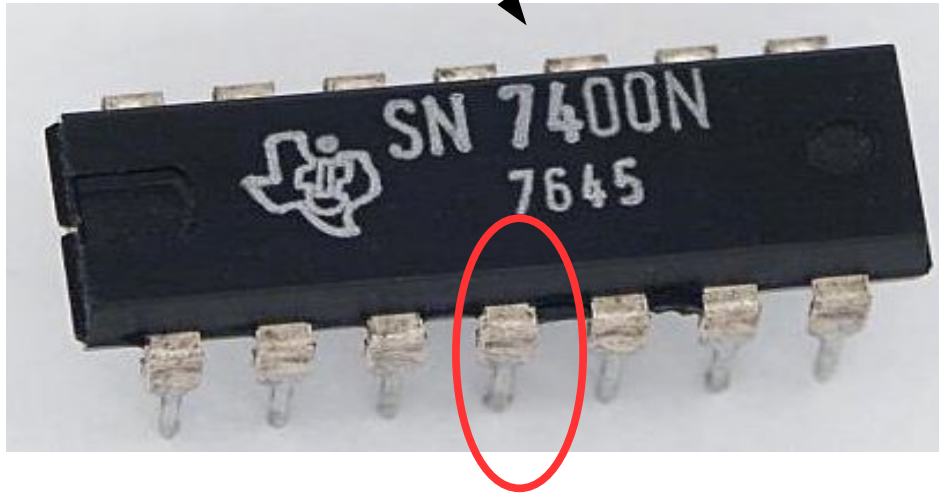


Biro

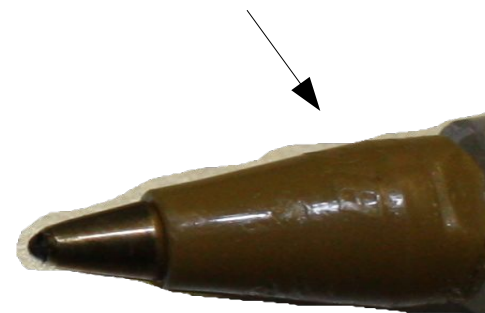

- Look at the tiny thin pins which are used to carry current in and out of the chip.
- These pins can supply **25 mA @ 5V** at the most.

# But why is this?

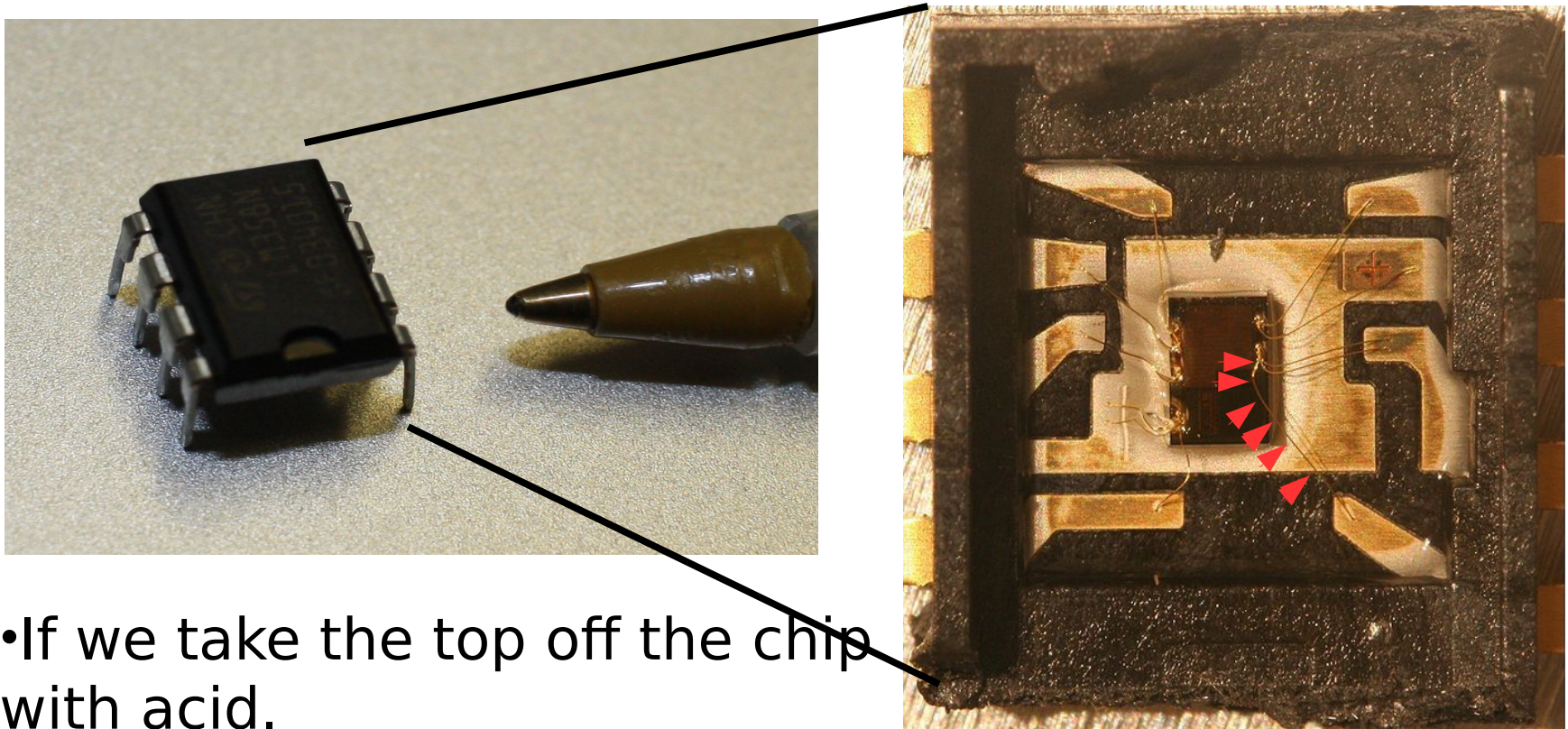

- If we take the top off the chip with acid.

- Look how much small the actual chip is and look at the tiny bond wires (**25 mA @ 5V max!!!**)

Gopfi


# Now think about this motor.



- It needs **10 Amps** at **500 V** to run.



CMBJ

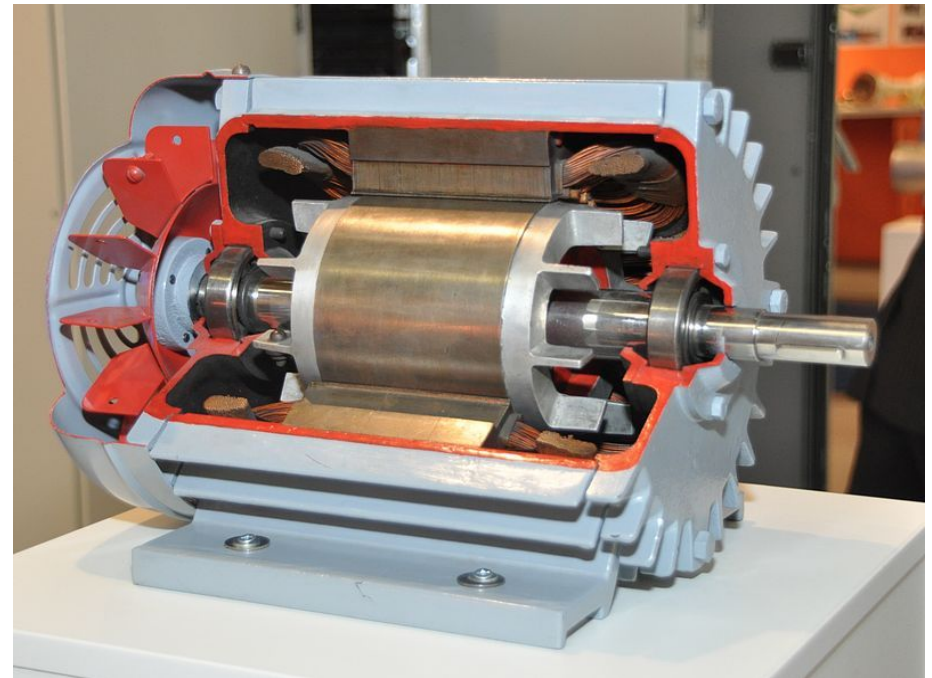


S.J. de Waard

- It will also need cable as thick as my finger to carry the current.
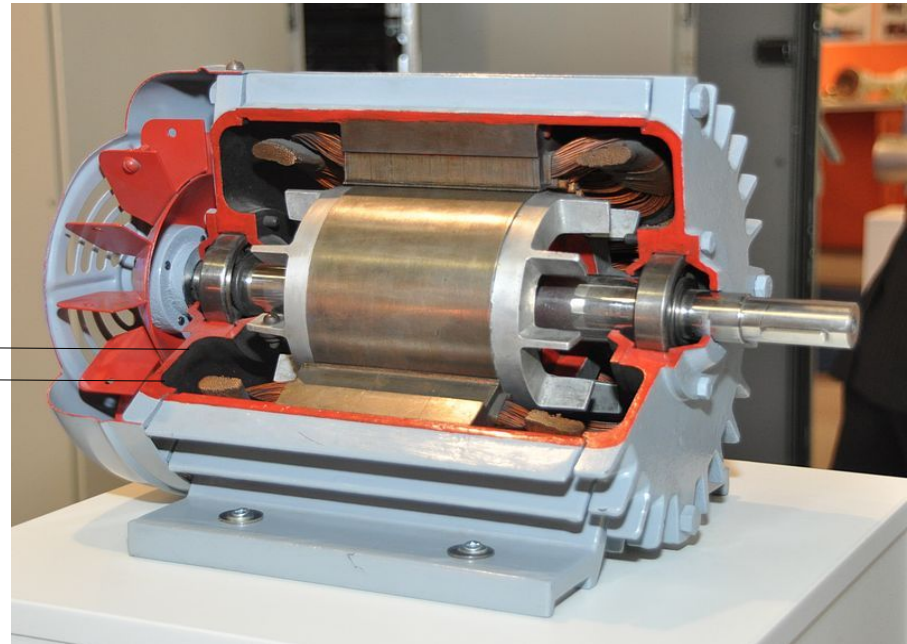
# Using chips to run large voltage/current loads.



- Now imagine trying to run this motor which needs **500V @ 10 Amps** from this tiny chip that can only deliver **5V @ 25 mA**.





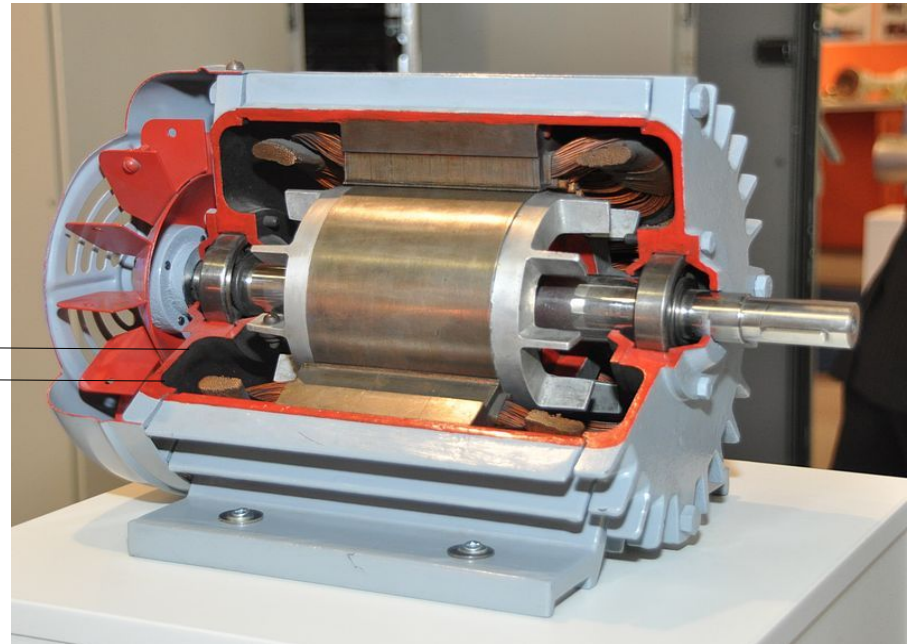
# Using chips to run large voltage/current loads.



- It would not work – the chip would just get hot and melt because it can not deliver enough voltage/current.




# Voltage/current amplifier



- So if we want to use our chip to run a motor, we need some type of voltage/current **amplifier component**.





5V/25 mA

 

**Amplifier**

500V/10 A

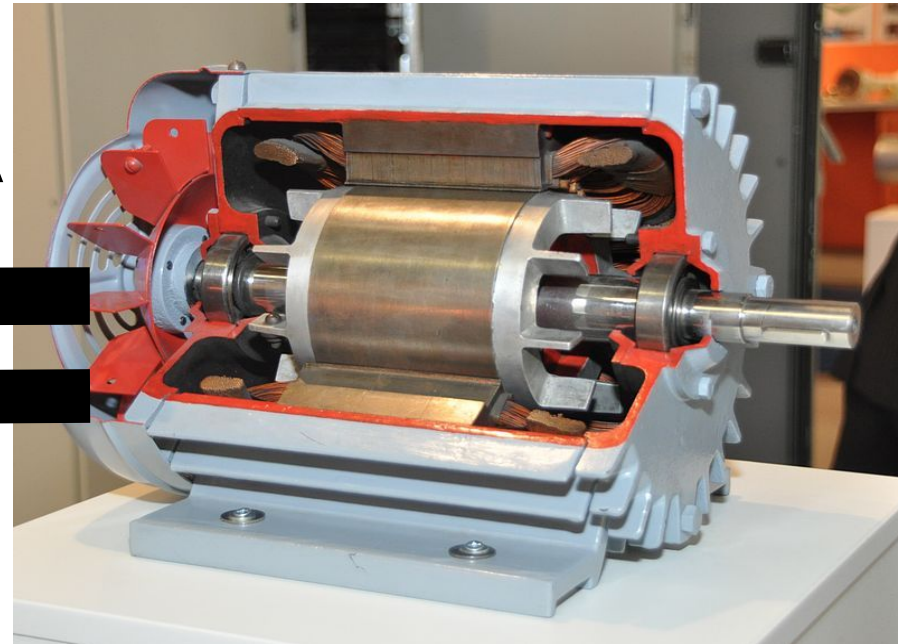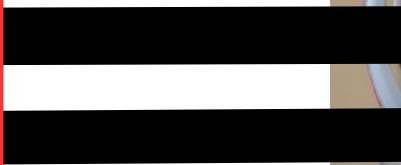

(Notice this is different from a transformer)




# Outline of the lecture

- No recap of last lecture :)
- Transistor basics
  - **Relays (Mechanical transistor)**
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- One last thing
- Summary

One such component is the **relay**





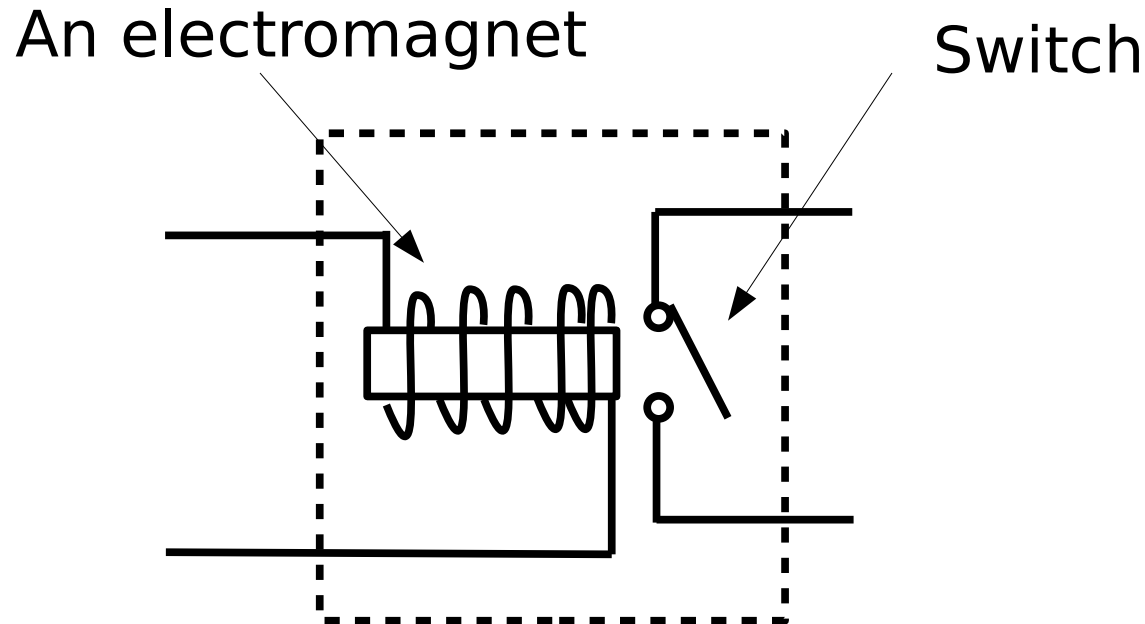- A relay is a an **electromechanical switch**




- And this is how it works.....

# Relay example

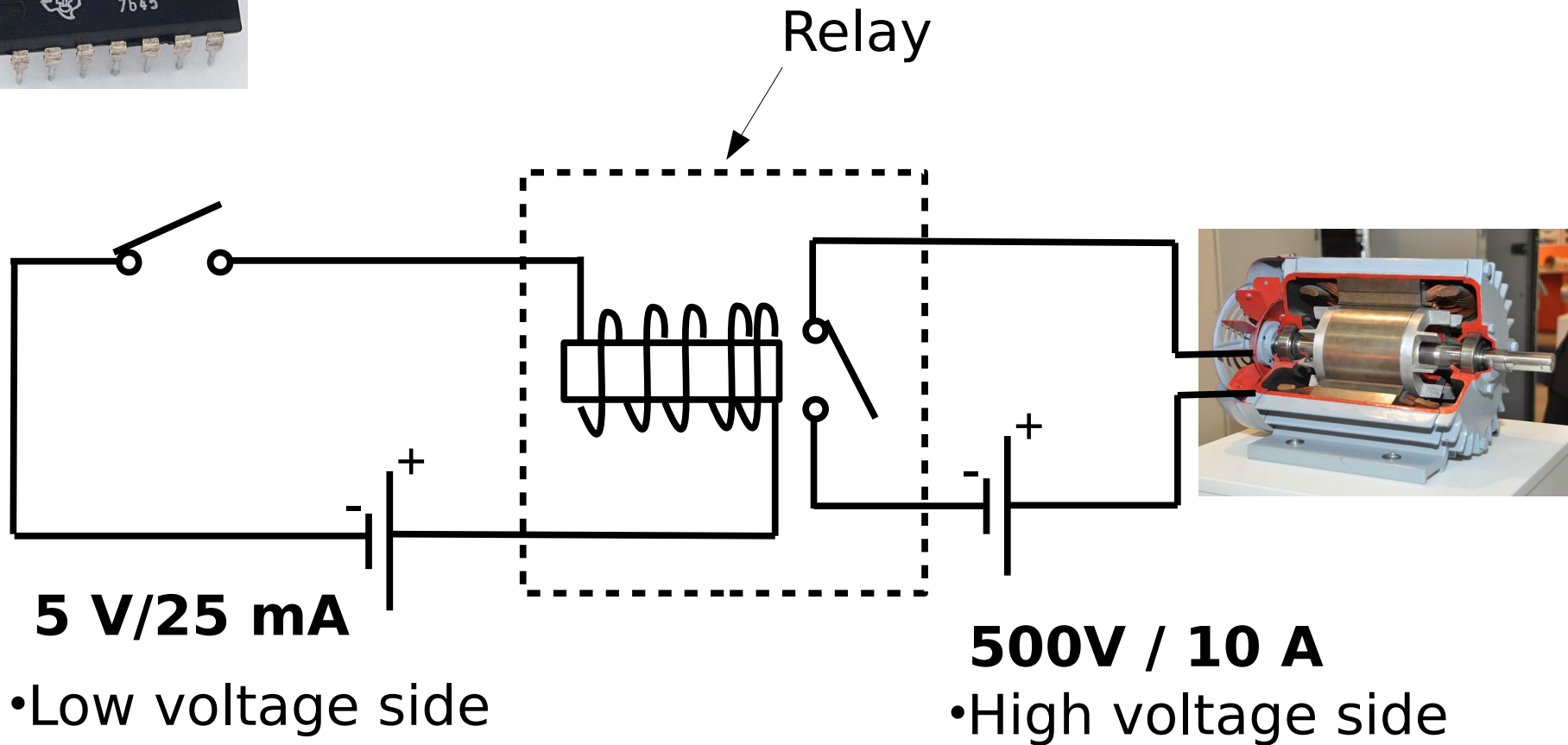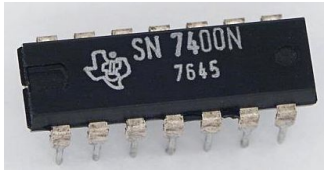

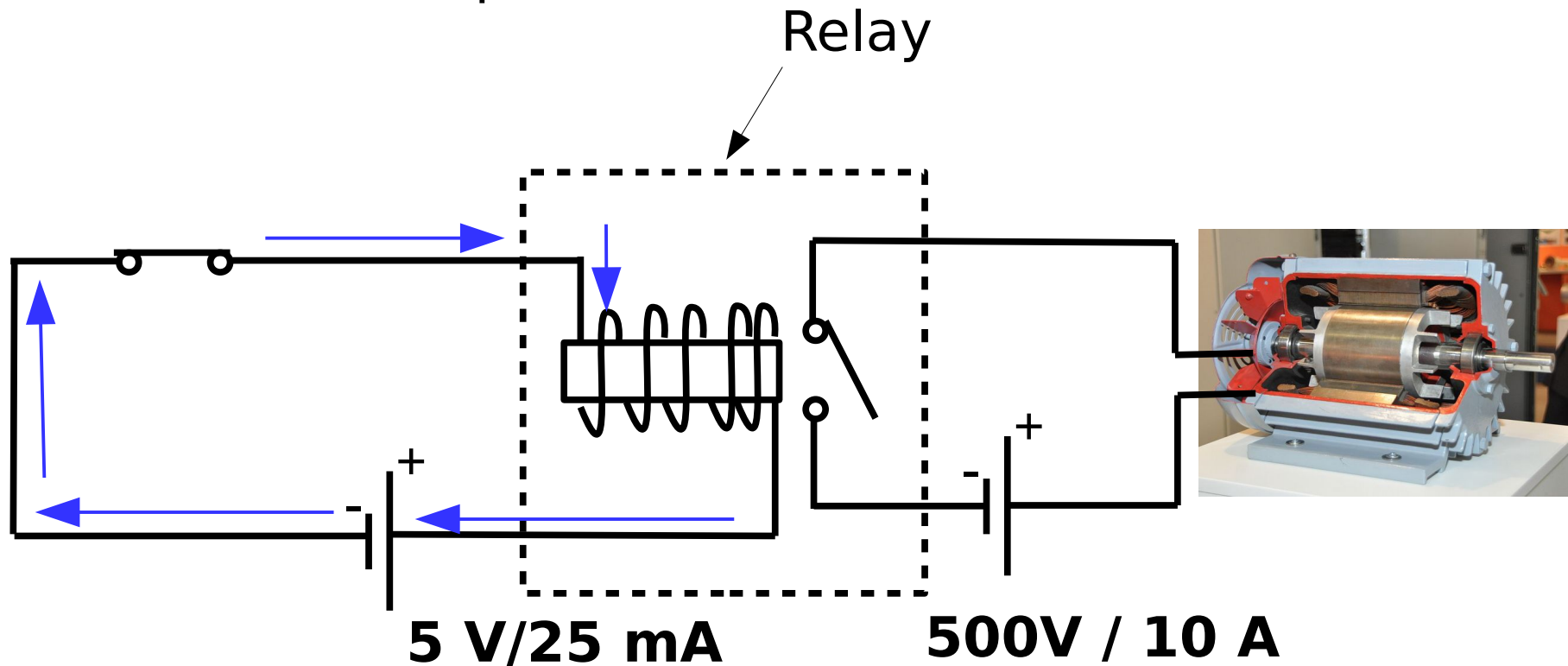
# Relay example

- When the **5 V** supply is turned on current flows in the low voltage side of the relay. This current *could* come from a chip.




# Relay example

- The electromagnet becomes energized

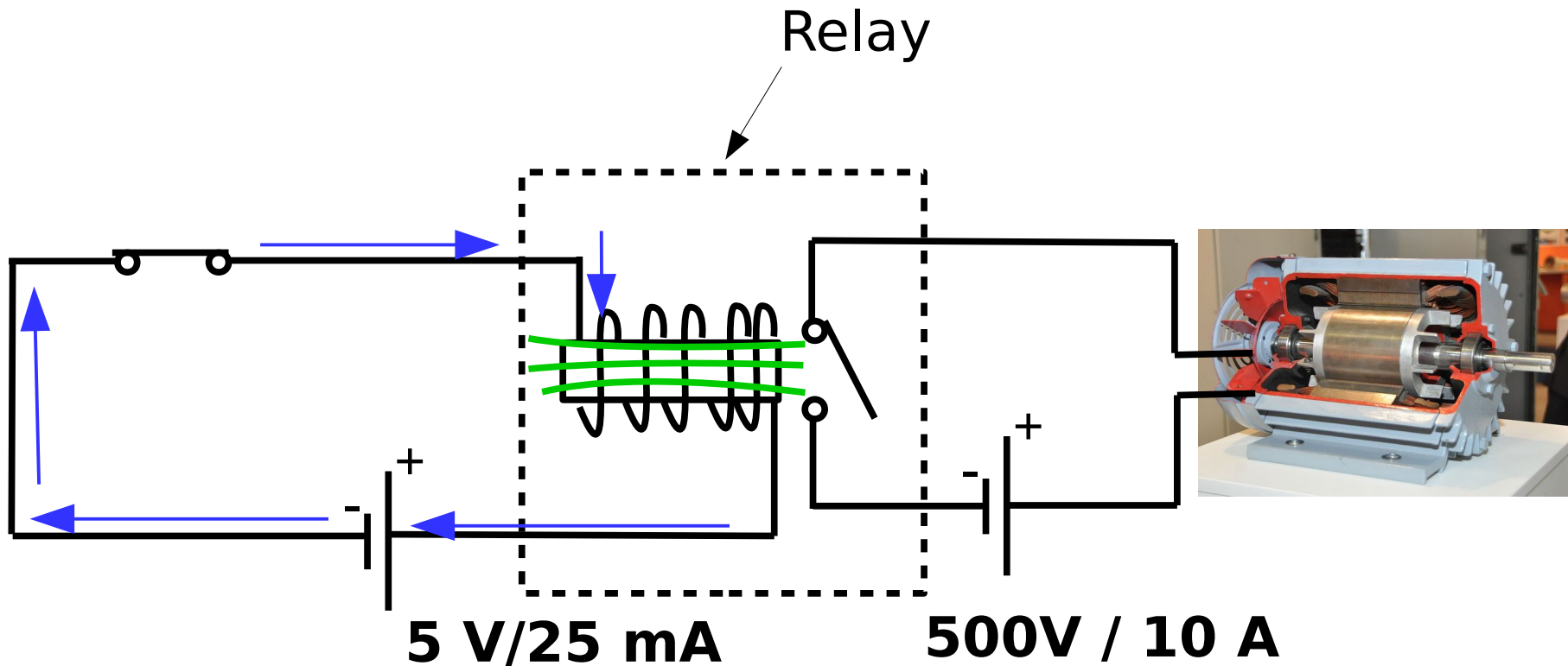
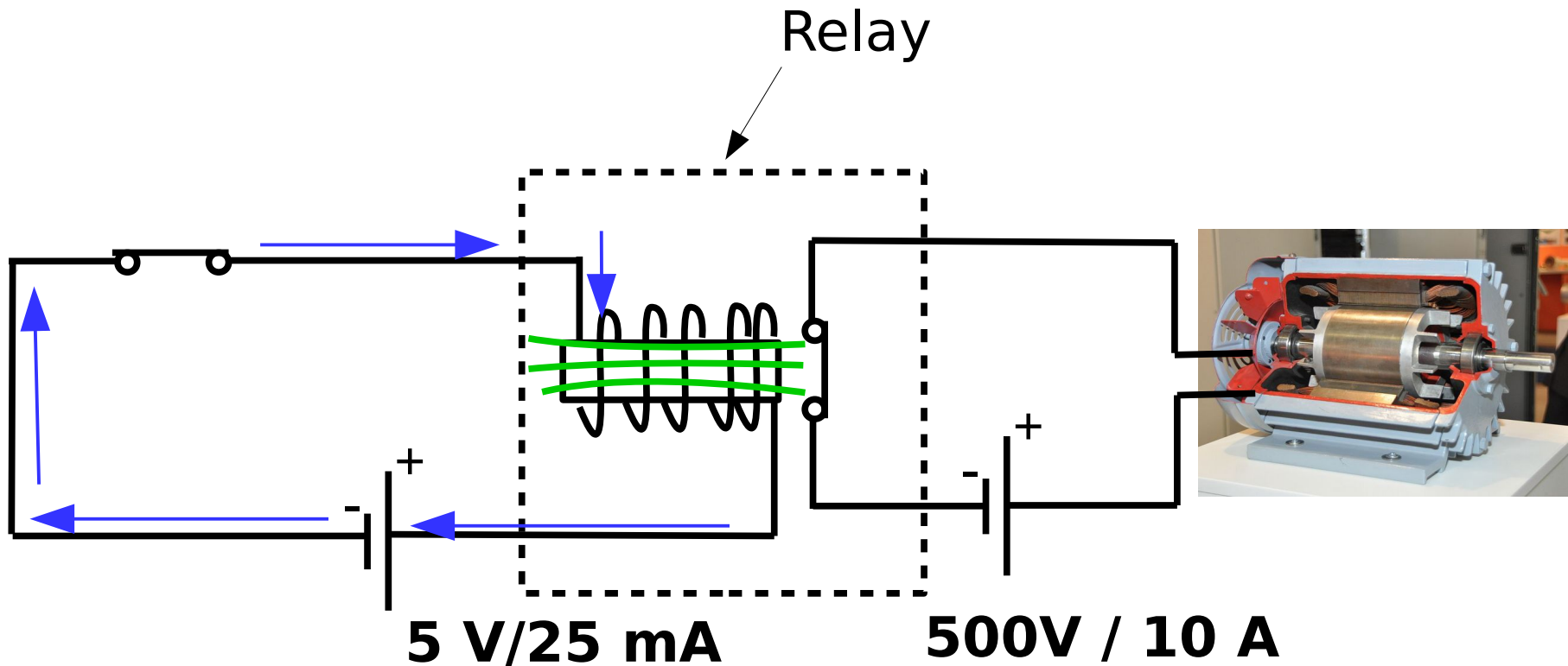
# Relay example


- The magnetic field pulls the switch shut.





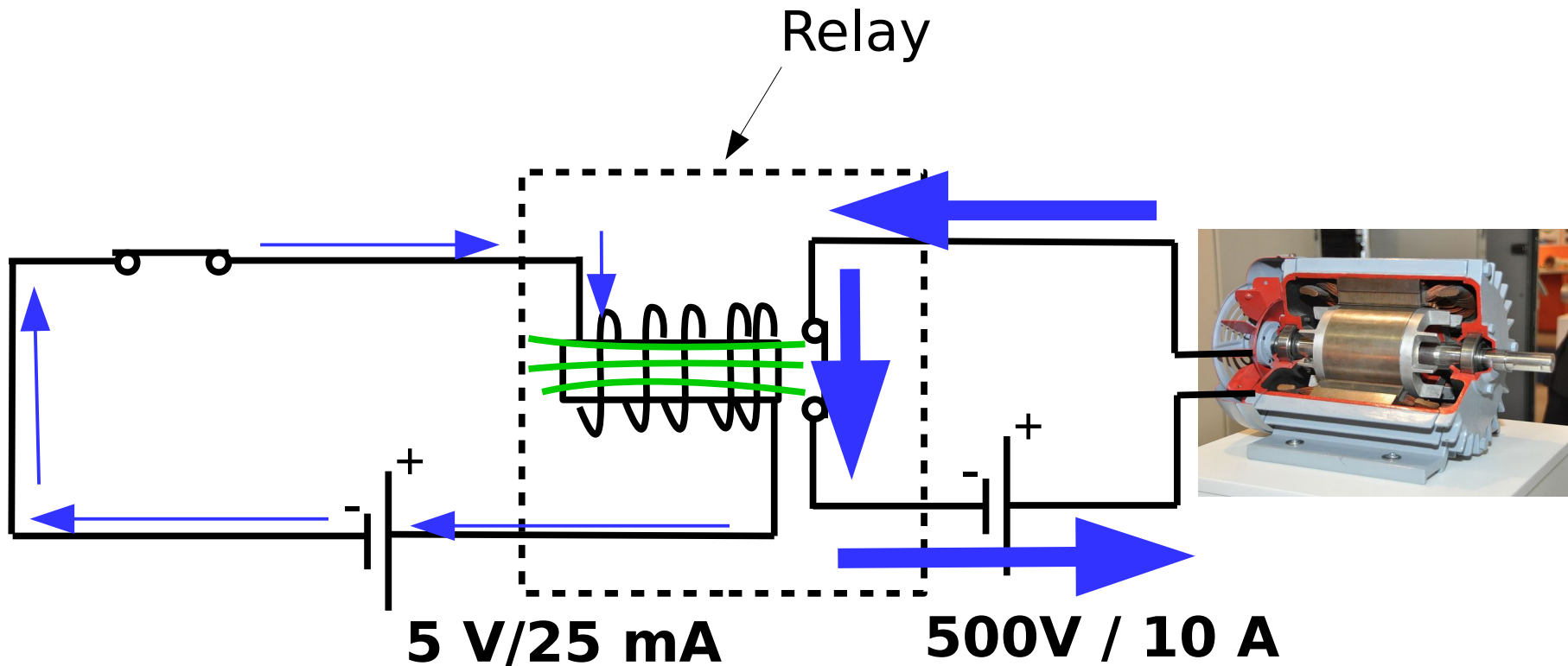
# Relay example

- Current flows in the high voltage circuit.




# Relay example

- And the motor turns

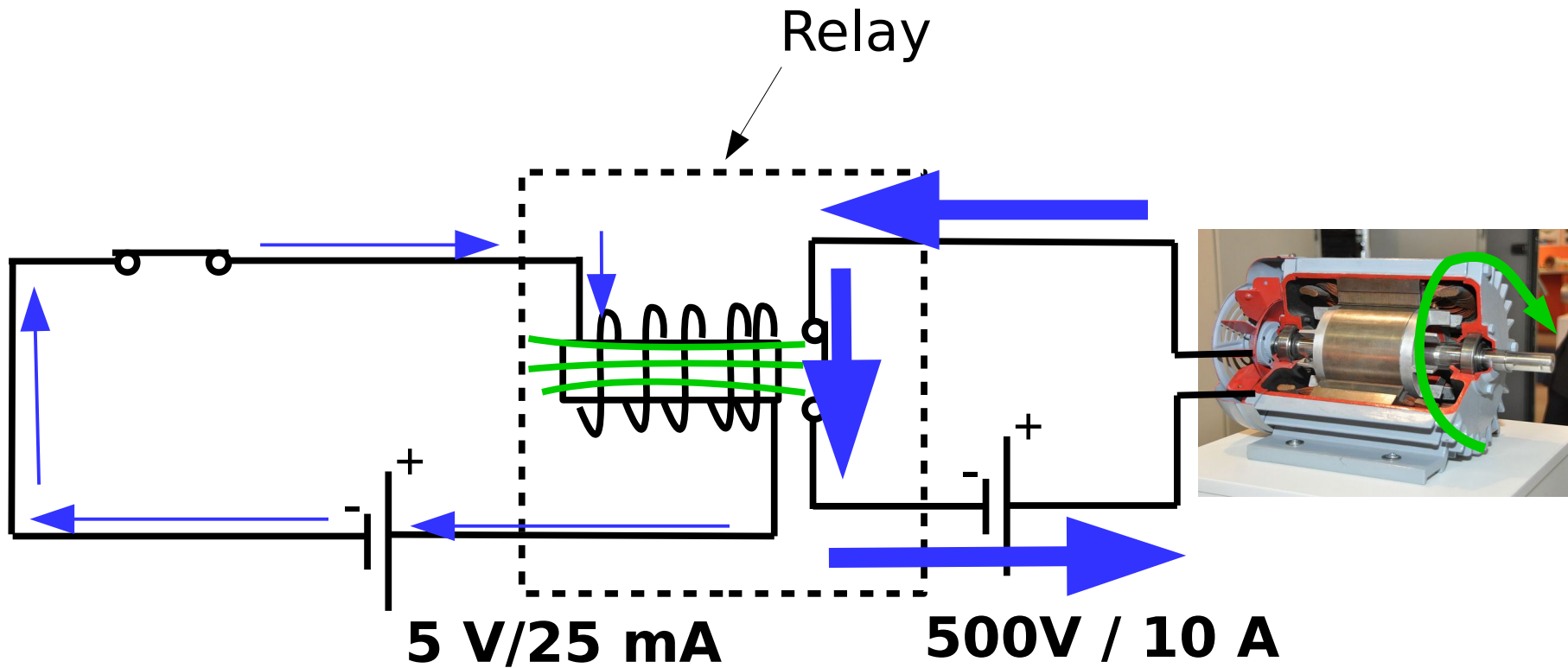


# Relay example

- When the 5V supply is turned off...

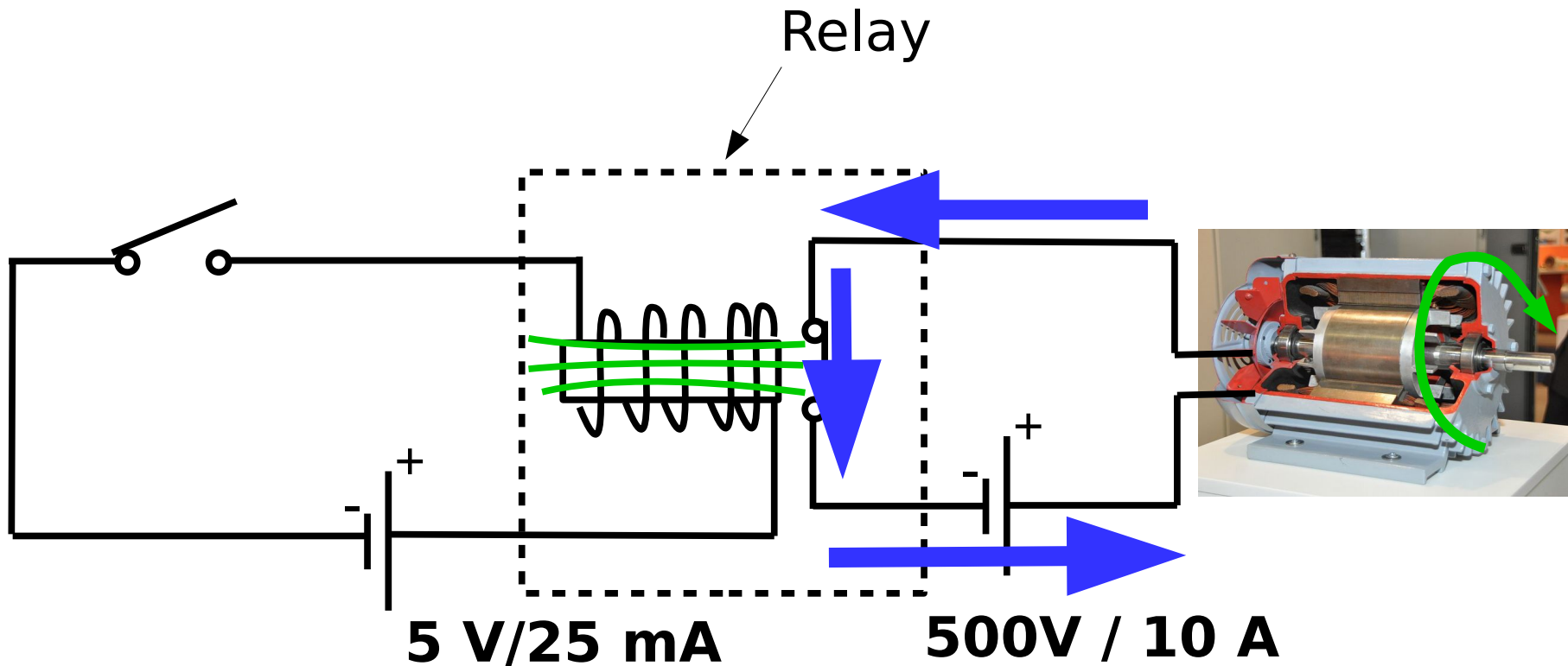


# Relay example

- When the 5V supply is turned off...

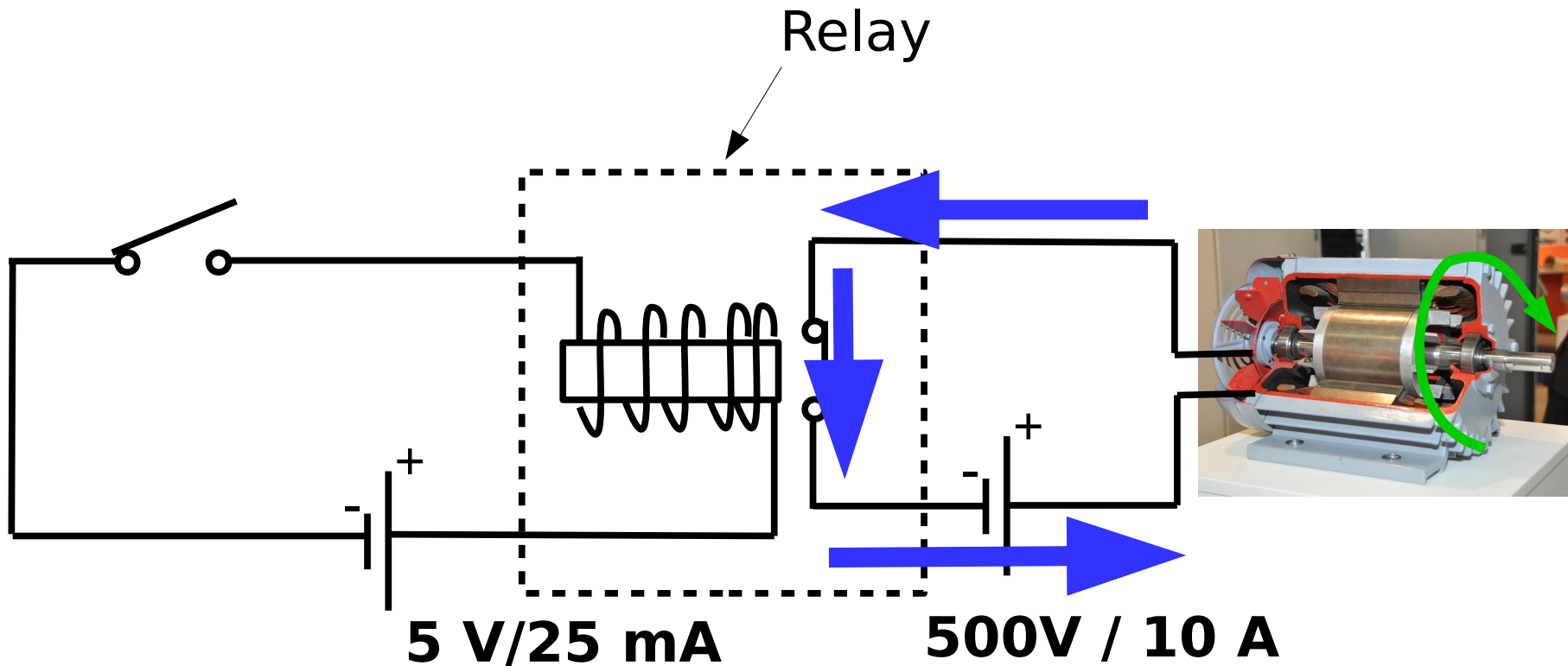
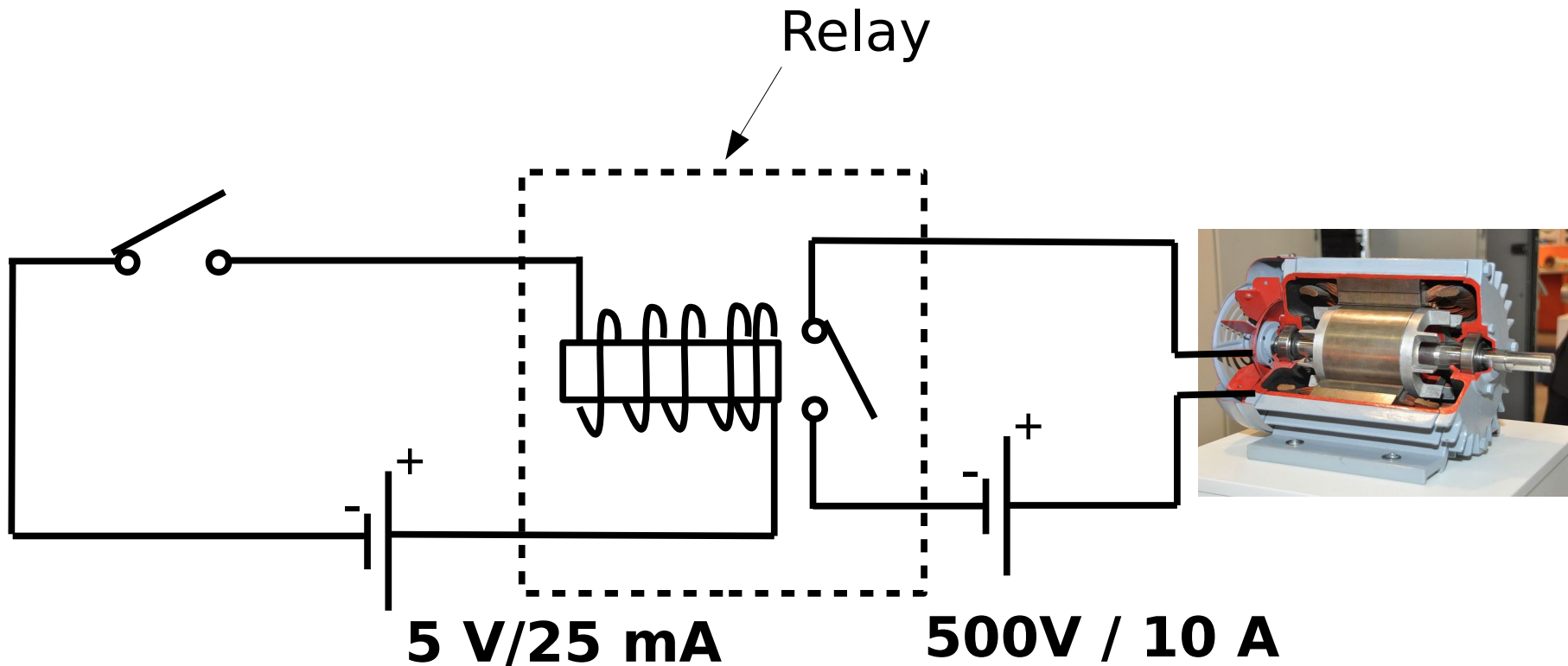
# Relay example




- The magnetic field disappears and the motor turns off.



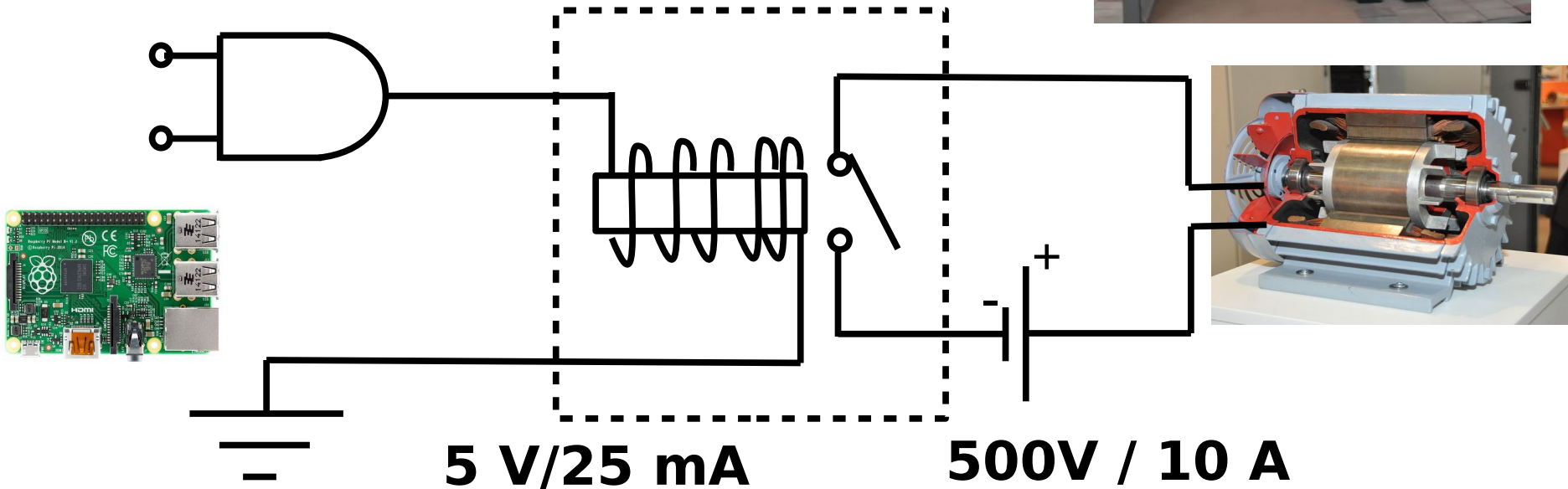
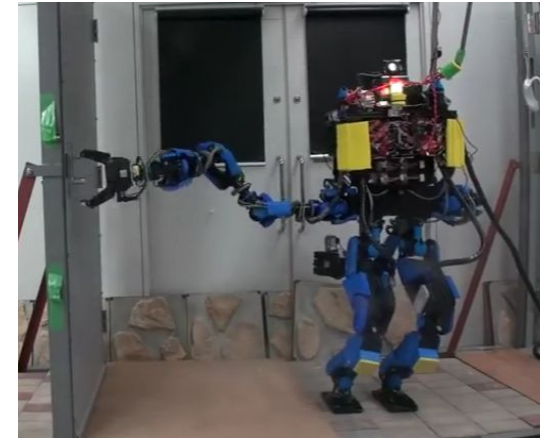
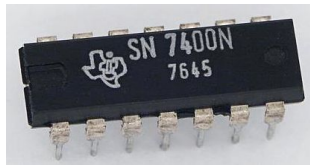
# Relay example



- The magnetic field disappears and the motor turns off.




# A real relay looks like this:

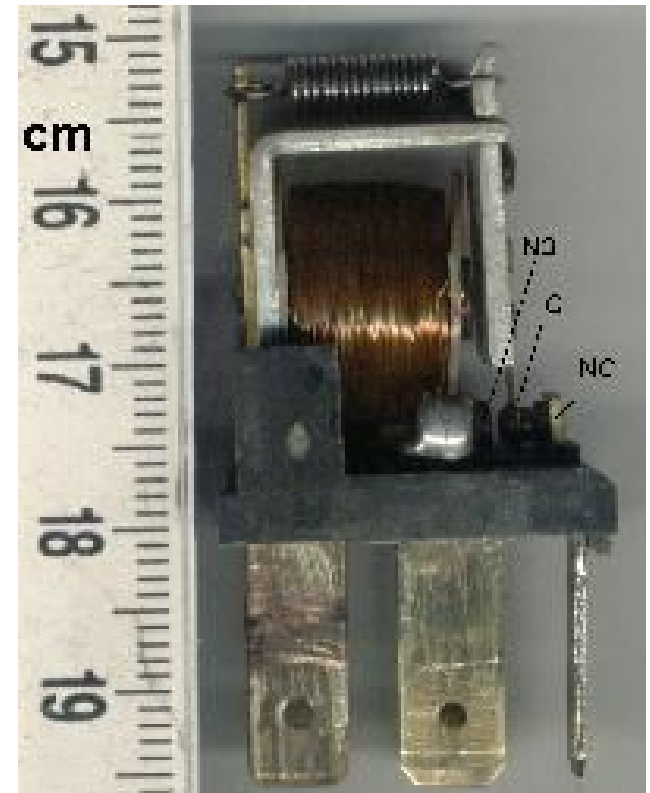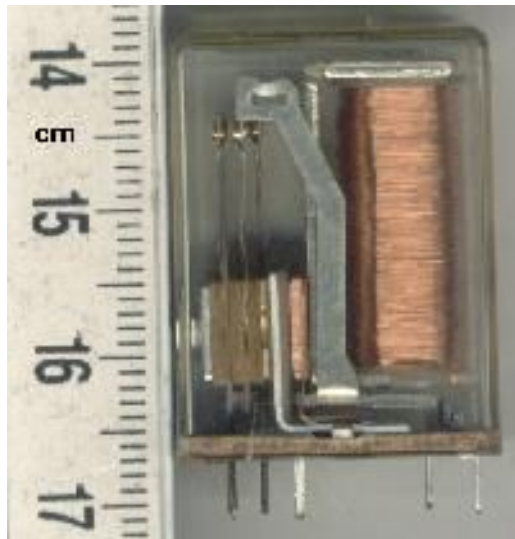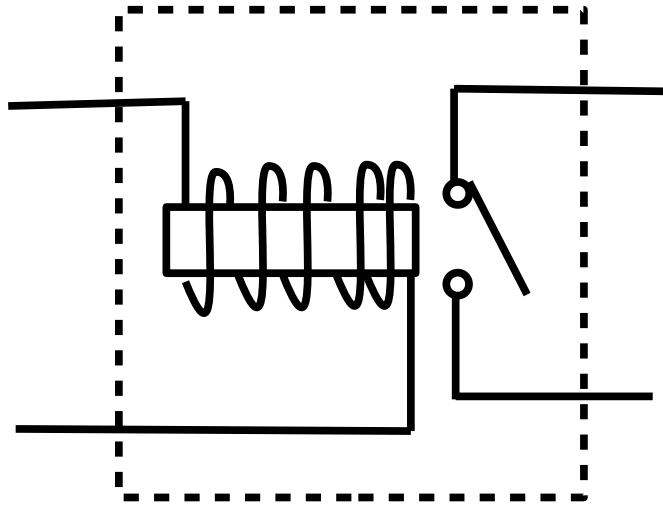
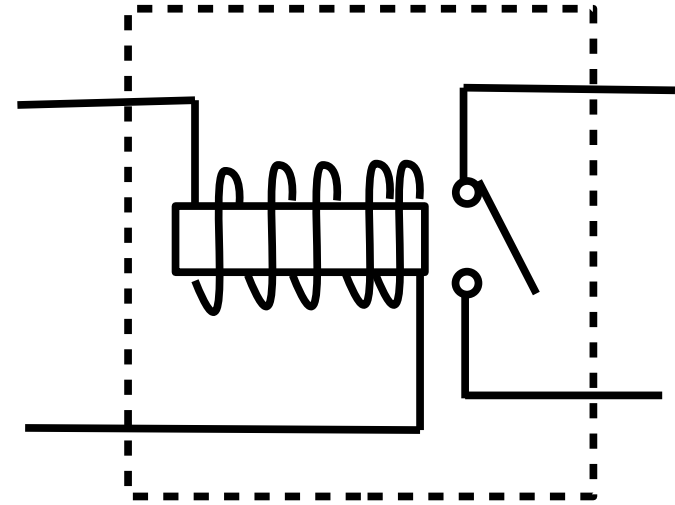
# Advantages of using relays for switching things on and off



- You get physical isolation of both circuits. Important when you are dealing with very high voltages.



- Relays were the primary way to turn high voltages on/off before the advent of the transistor in the 1960s – they not so bad at this.






# The drawbacks of using relays for switching



- You have to keep that coil **energized if you want to keep your device on.**



- **This uses a lot of power.**

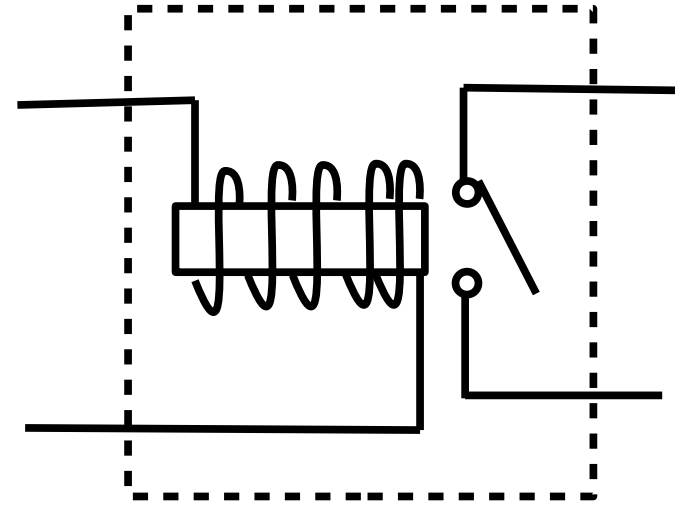

- They are **mechanical devices** and therefore slow.



- They are **full of copper and cost a lot (a few pounds.)**




- **They are big.**




- **No recap of last lecture :)**
- Transistor basics
  - Relays (Mechanical transistor)
  - **NPN Bipolar Junction Transistors**
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- One last thing
- Summary

- You can think of a transistor as being just like a relay except they have only one control wire.


## Relay

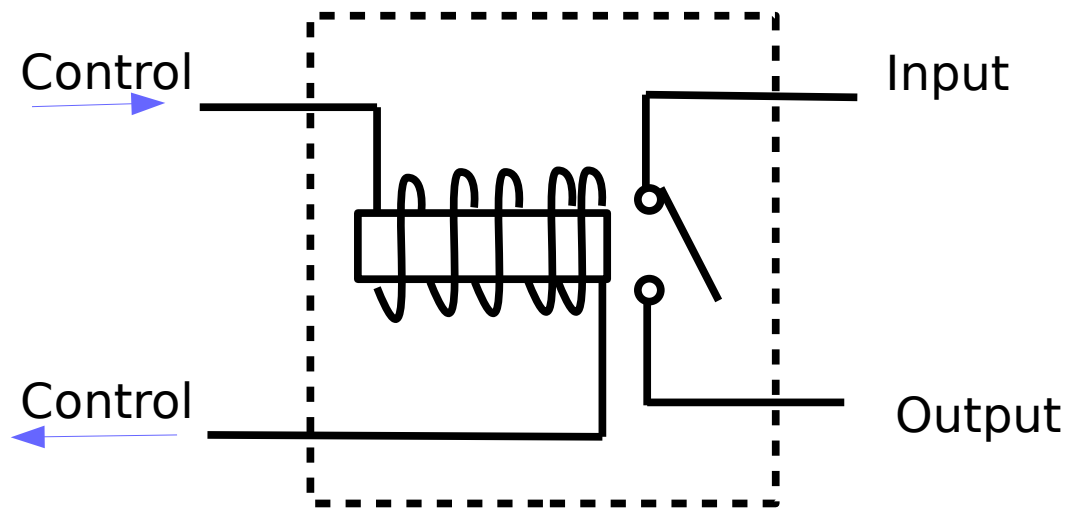

## Transistor

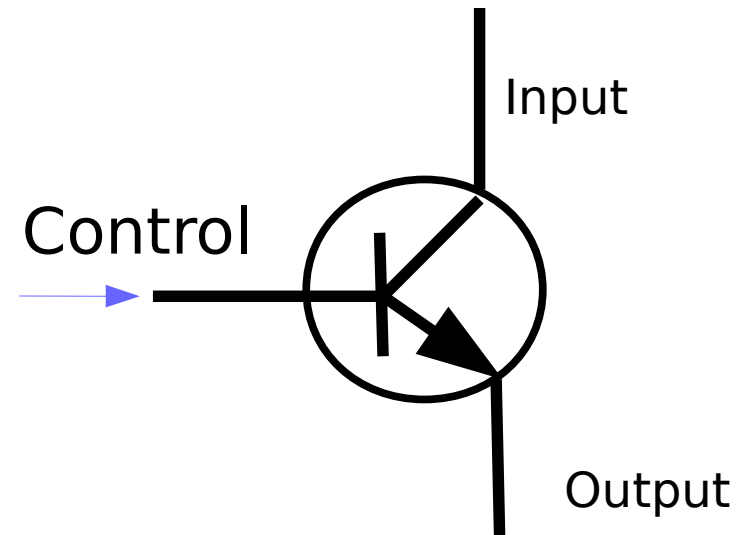
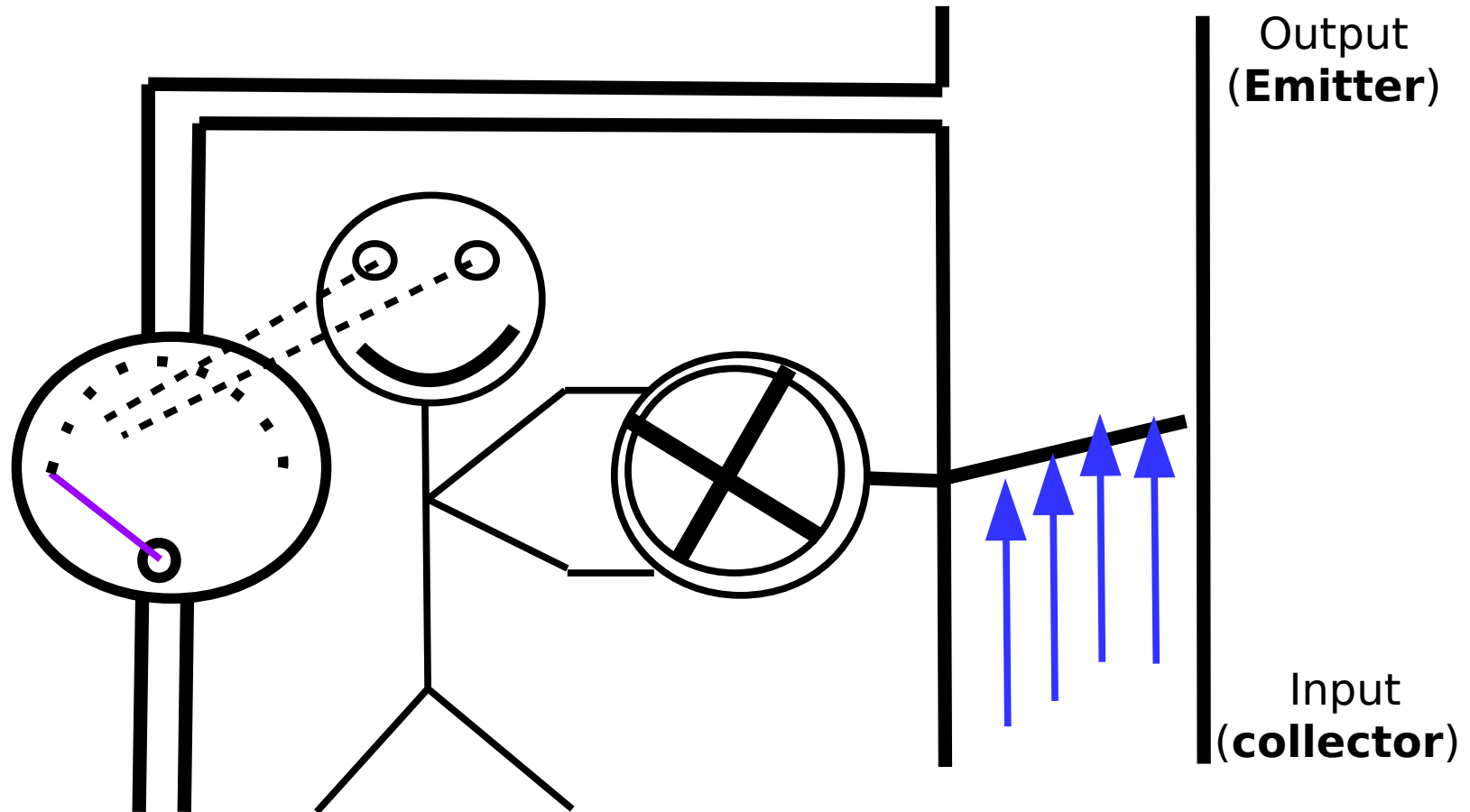
# You can think of a transistor like this.... The Transistor Man




Control  
(**base**)

*After Horowitz and Hill*

28

# Transistors - The Transistor Man

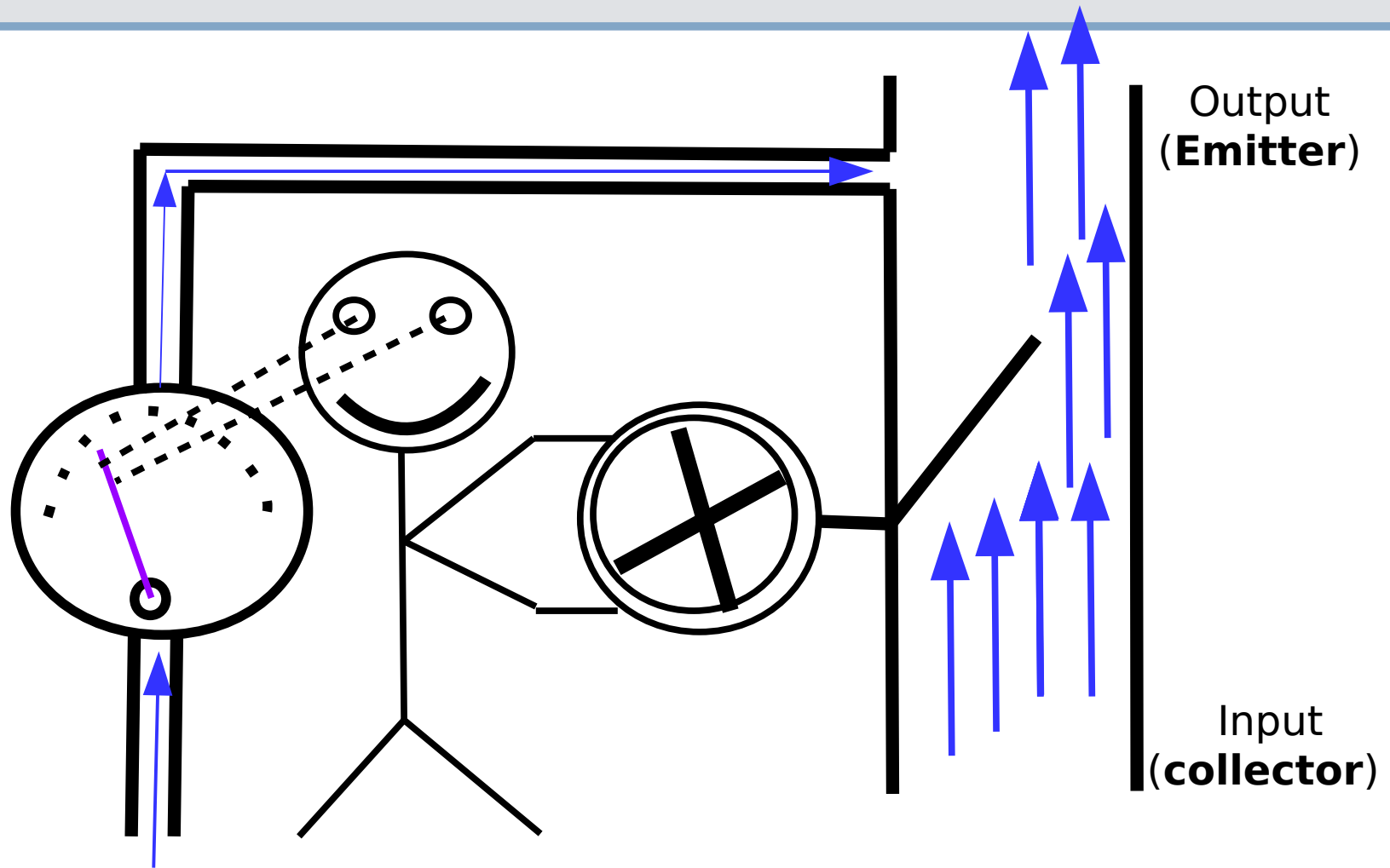


Control  
(**base**)

After Horowitz and Hill


Input  
(**collector**)

Output  
(**Emitter**)

# Transistors - The Transistor Man

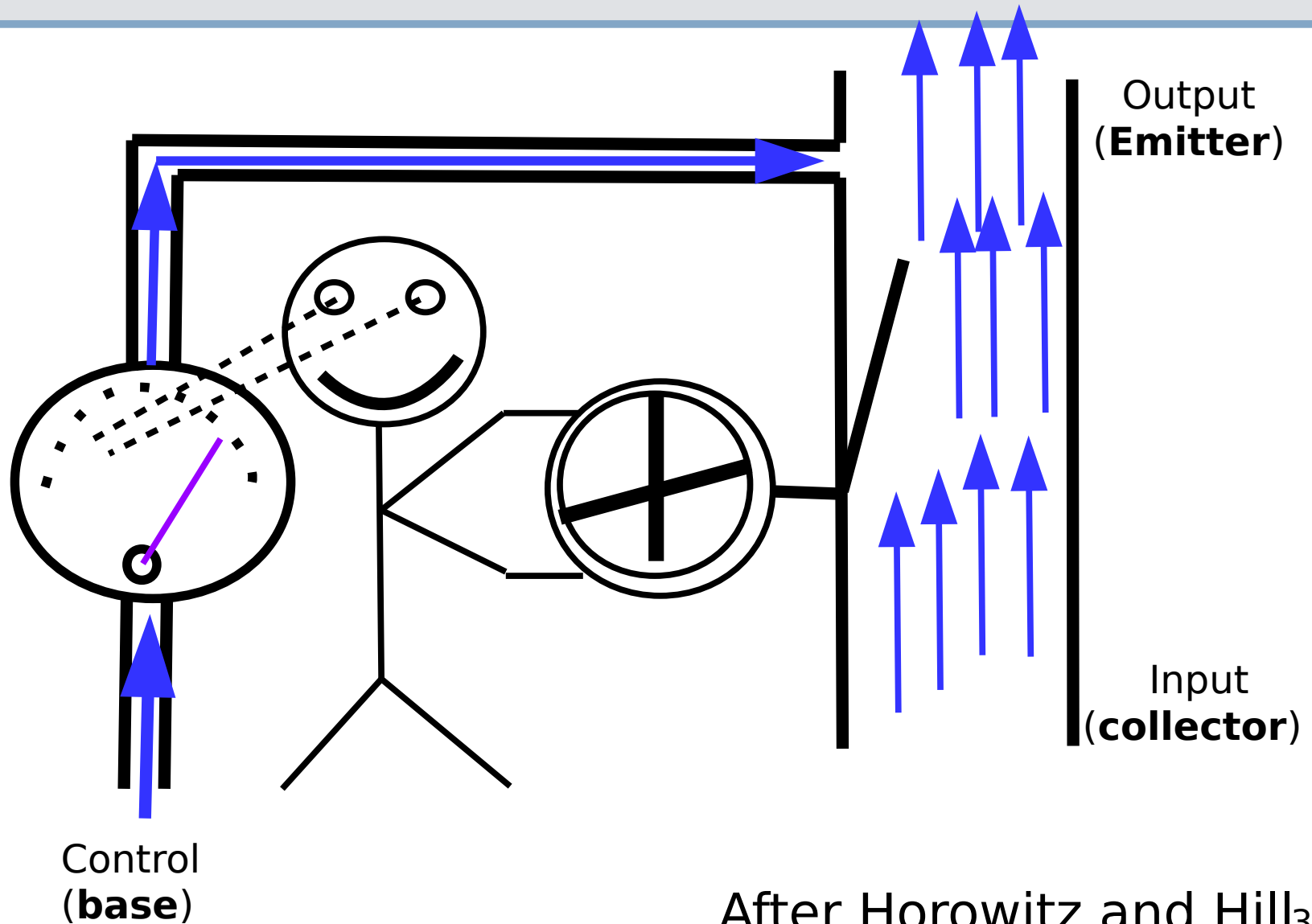

After Horowitz and Hill<sub>30</sub>

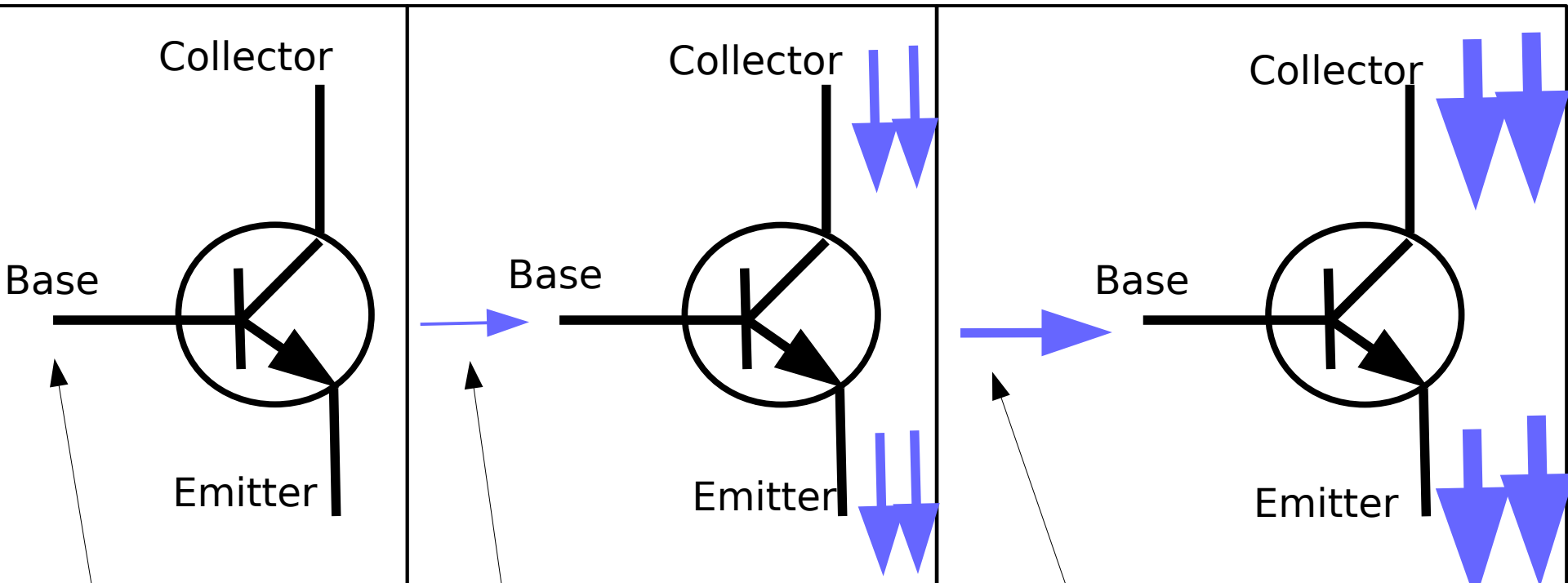

1. No base current - **no output current**

2. Small base current - **small output current**

3. Big base current - **big output current**

# Transistors

- Transistors look like this →
- Little black beads (although sometimes silver boxes)
- They always have three legs.
- Invented in June 30<sup>th</sup> 1948



John Bardeen, William Shockley and Walter Brattain



Transisto



# Advantages of Transistors

- No moving parts so they won't break - very long lifetime.



- Don't need as much control current to operate as a relay.




- Cheap as chips!




Transisto
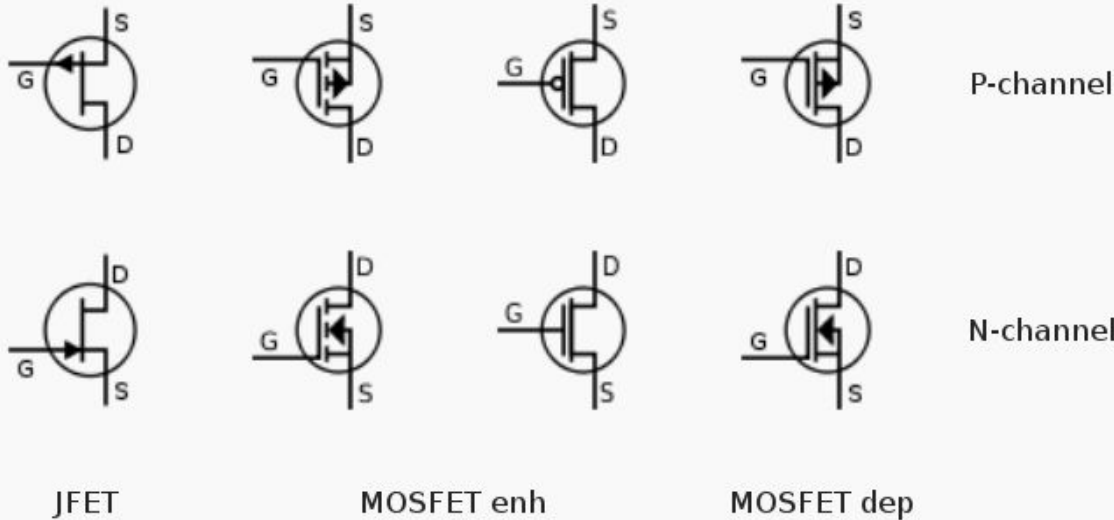
# Transistors – Different types of transistors




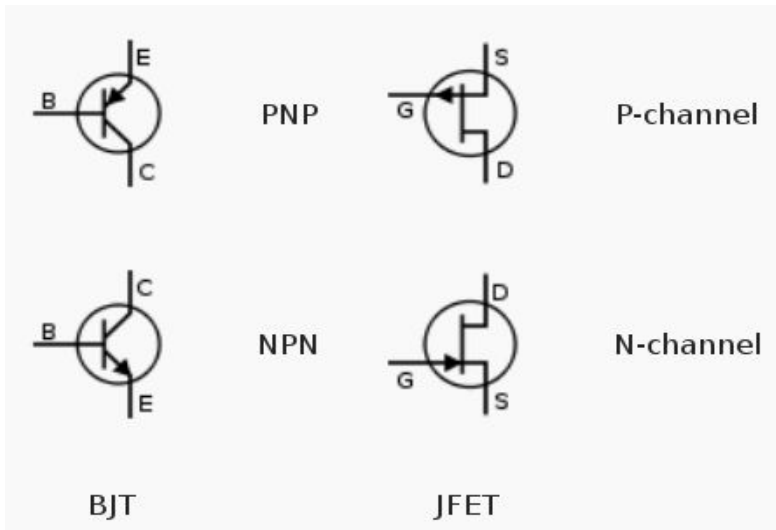• There are lots of different types of transistors – too many to learn about in this course.




• I have decided to teach you about the three of the most useful ones.
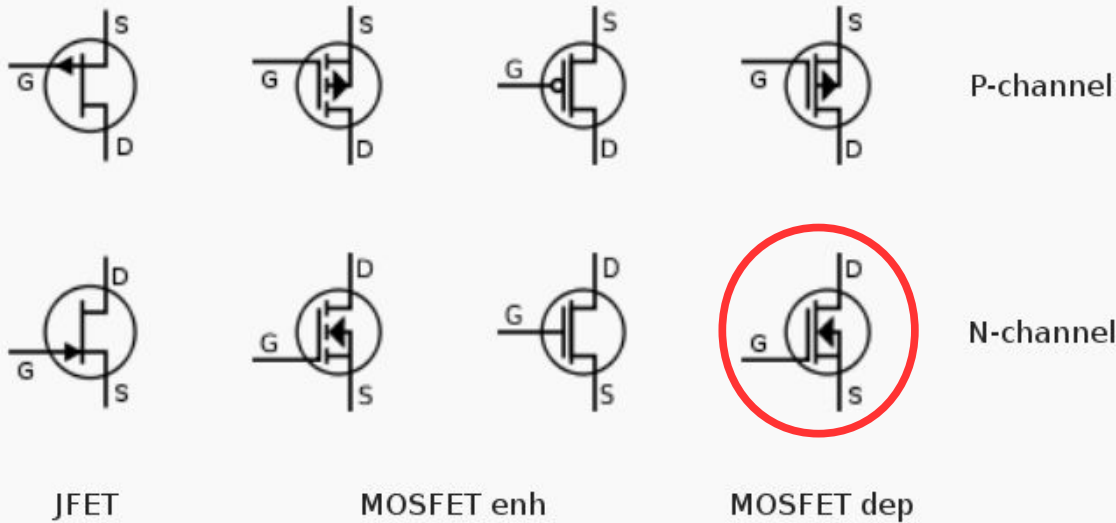
# Transistors – Different types of transistors



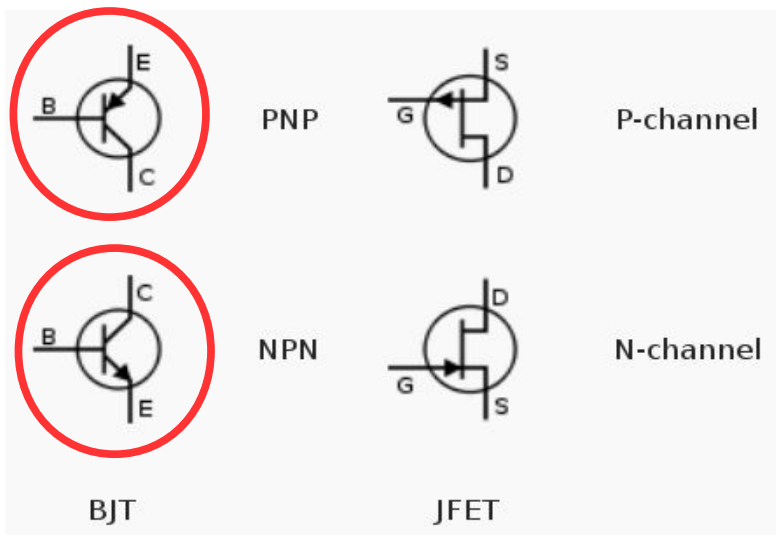• There are lots of different types of transistors – too many to learn about in this course.





• I have decided to teach you about the three of the most useful ones.

- **No recap of last lecture :)**
- Transistor basics
  - Relays (Mechanical transistor)
  - **NPN Bipolar Junction Transistors**
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- One last thing
- Summary
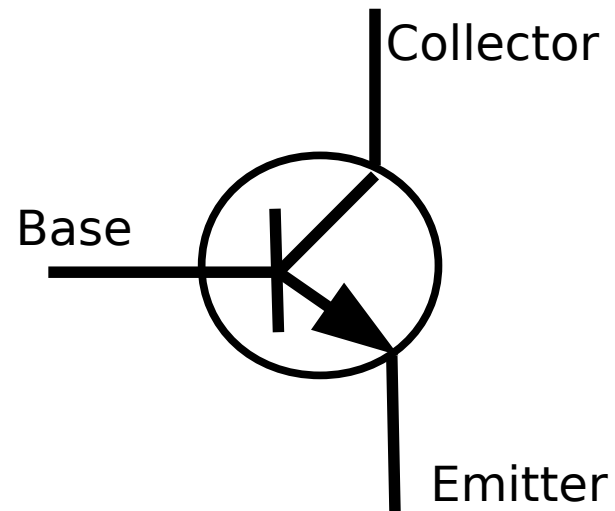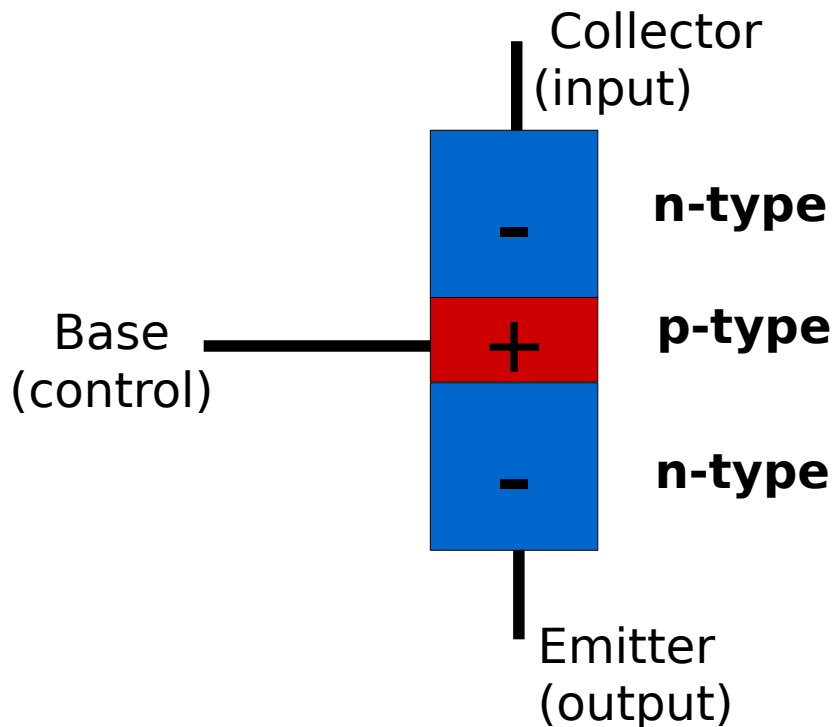
# Transistors – The NPN Bipolar Junction Transistor (**BJT**)




- It's called an **NPN** transistor because it's made of three layers of material, one with **n**egative charge, one with **p**ositive charge and one with **n**egative charge.


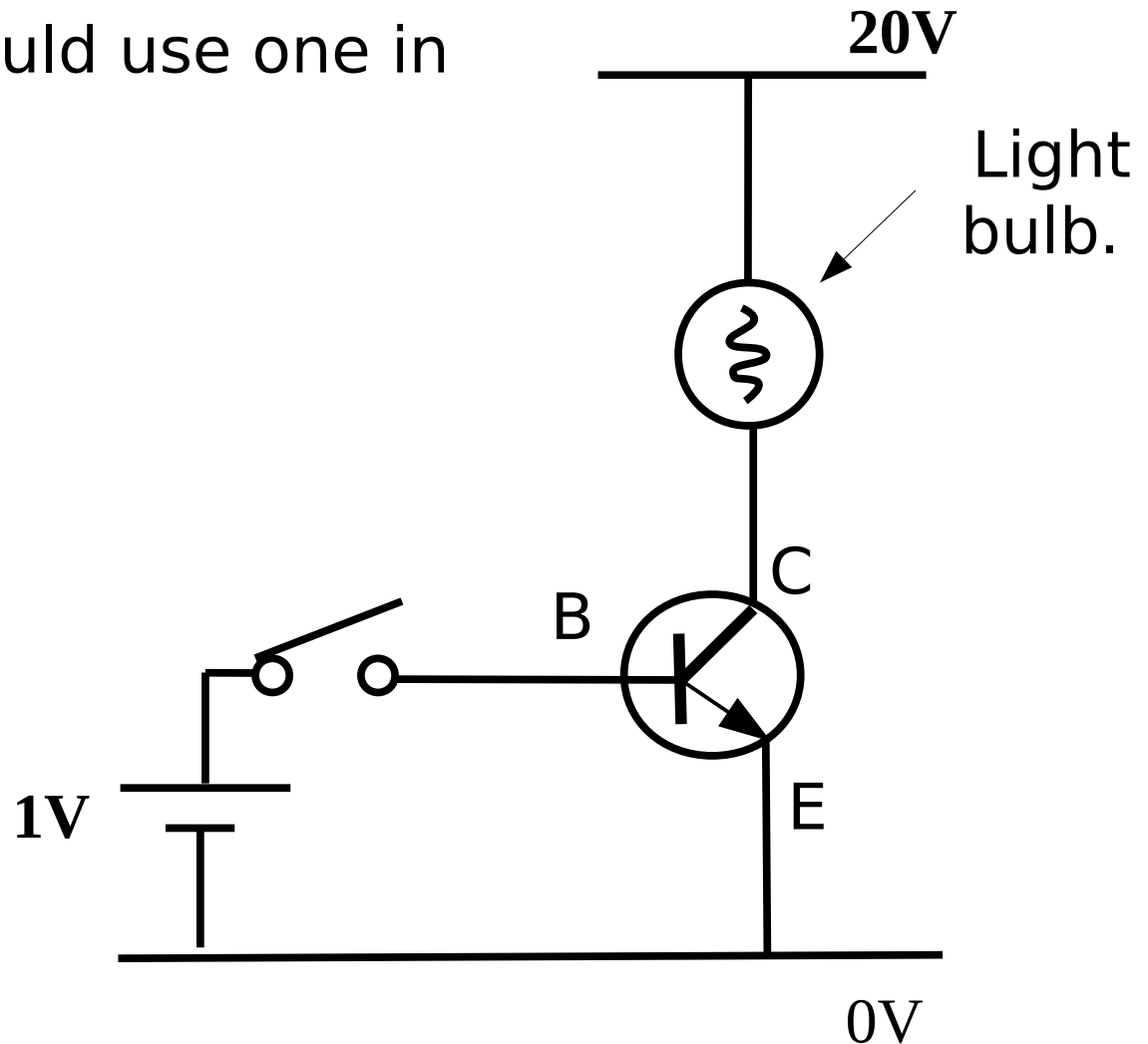
# Transistors – The NPN Bipolar Junction Transistor (**BJT**)


- This is how you would use one in a circuit.....



# Transistors – The NPN Bipolar Junction Transistor (BJT)




- Put a small current into the **B**ase.

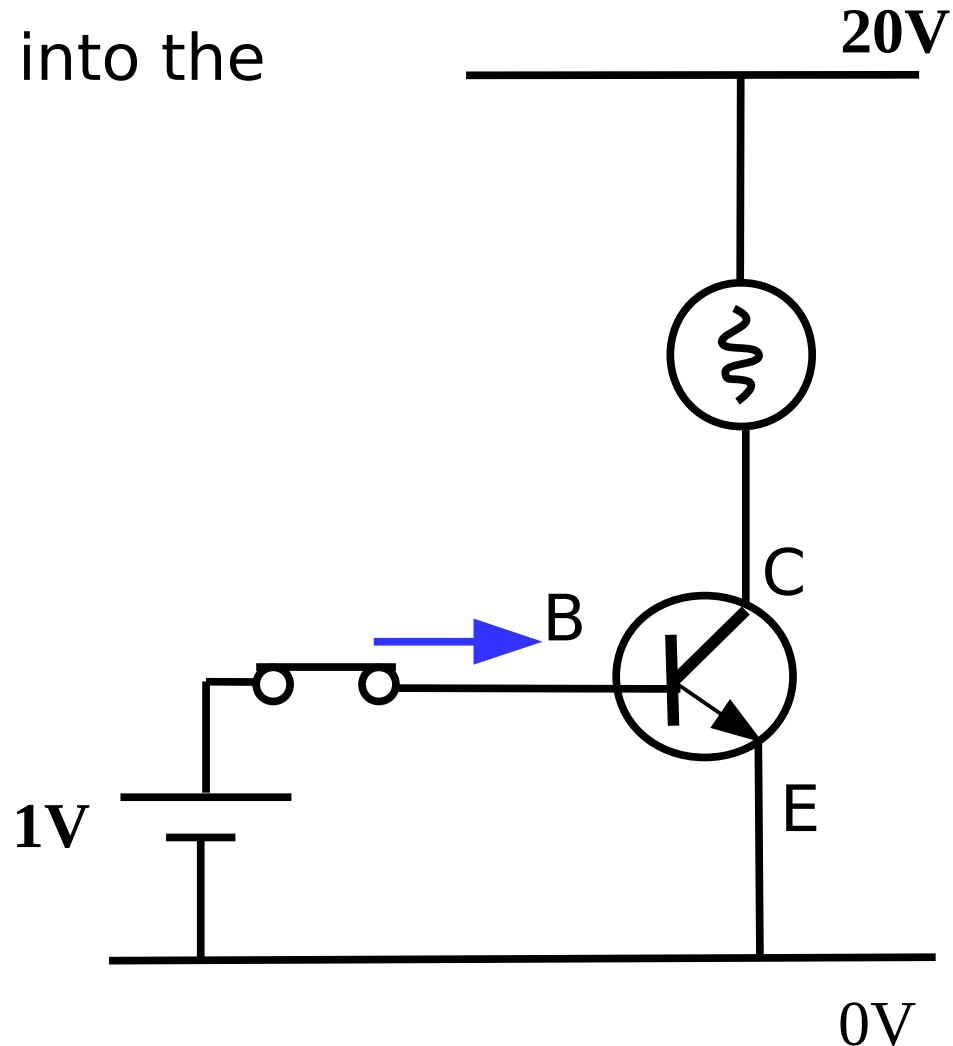

# Transistors – The NPN Bipolar Junction Transistor (BJT)




- The transistor switches on

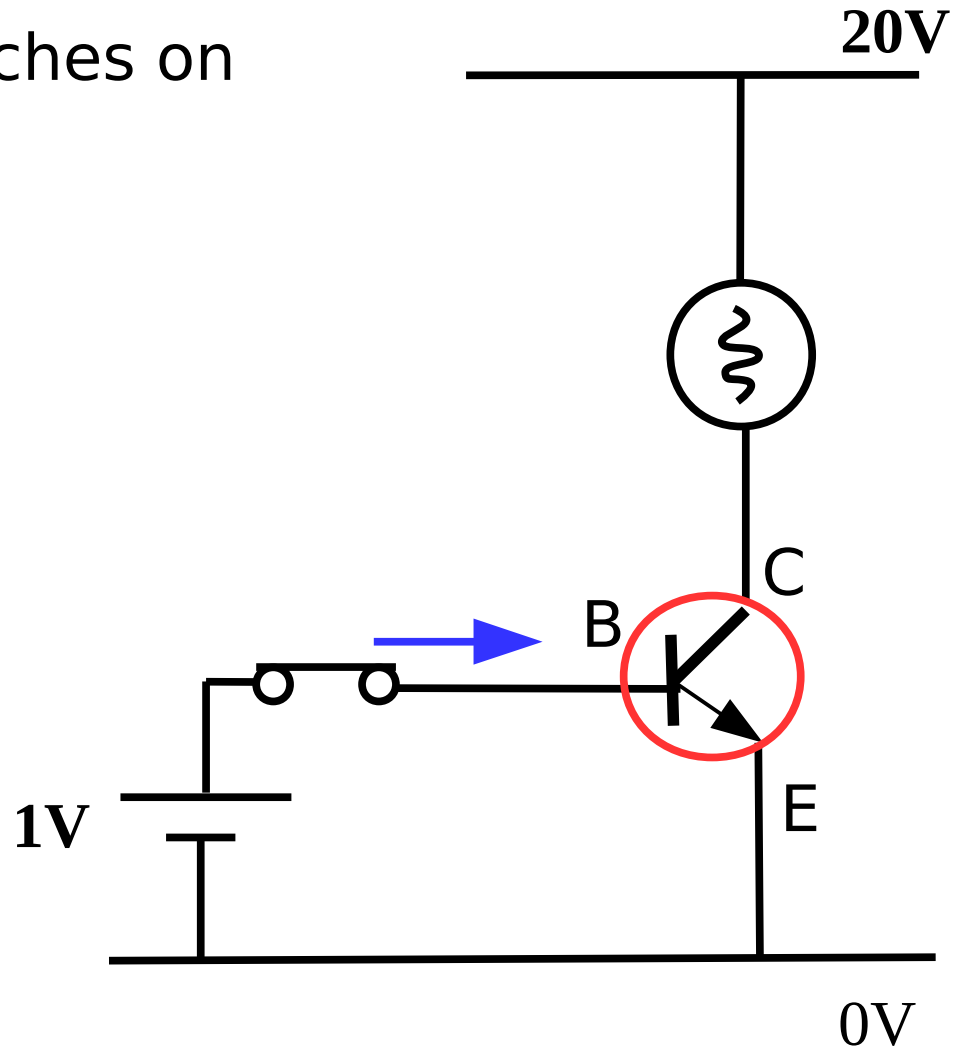


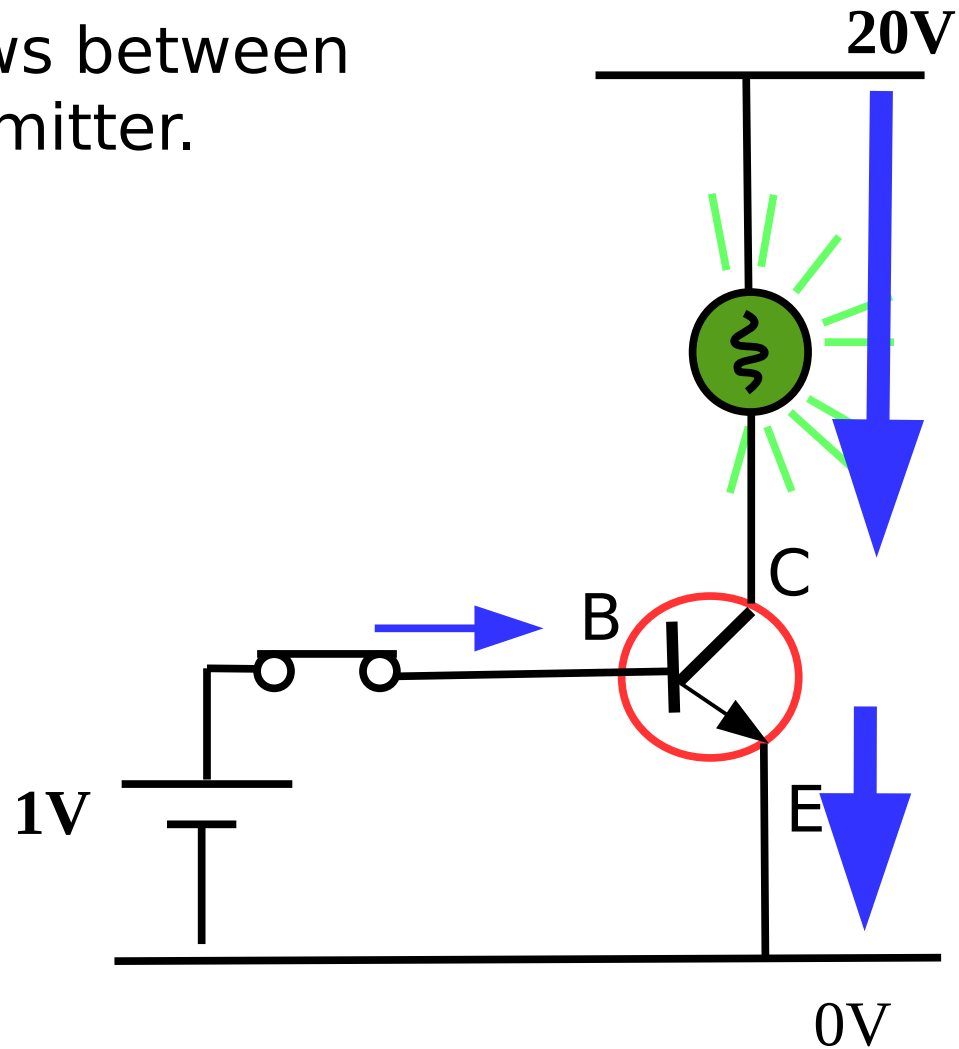
# Transistors – The NPN Bipolar Junction Transistor (BJT)


- A large current flows between the **C**ollector and **E**mitter.


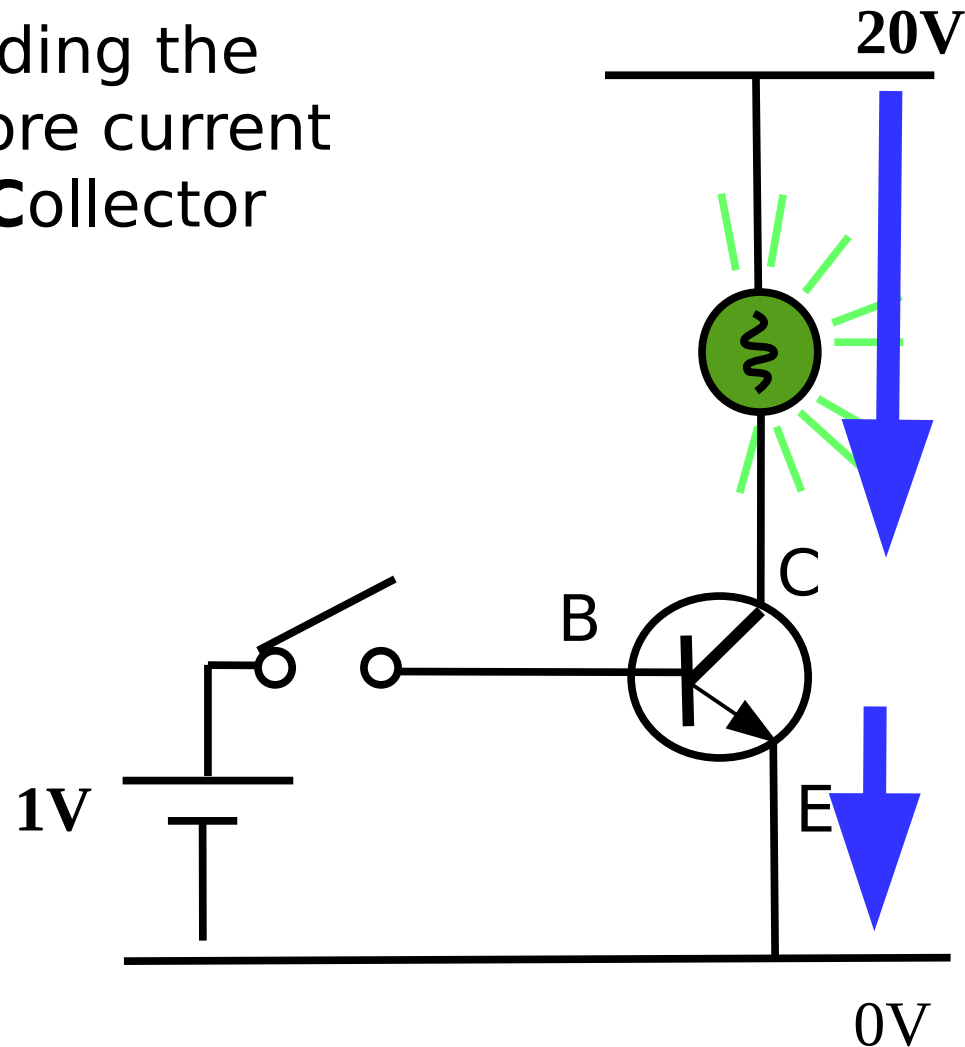
# Transistors – The NPN Bipolar Junction Transistor (BJT)




- When you stop feeding the base current, no more current flows between the **C**ollector and the **E**mitter.



# Transistors – The NPN Bipolar Junction Transistor (BJT)






- And the light bulb will turn off.

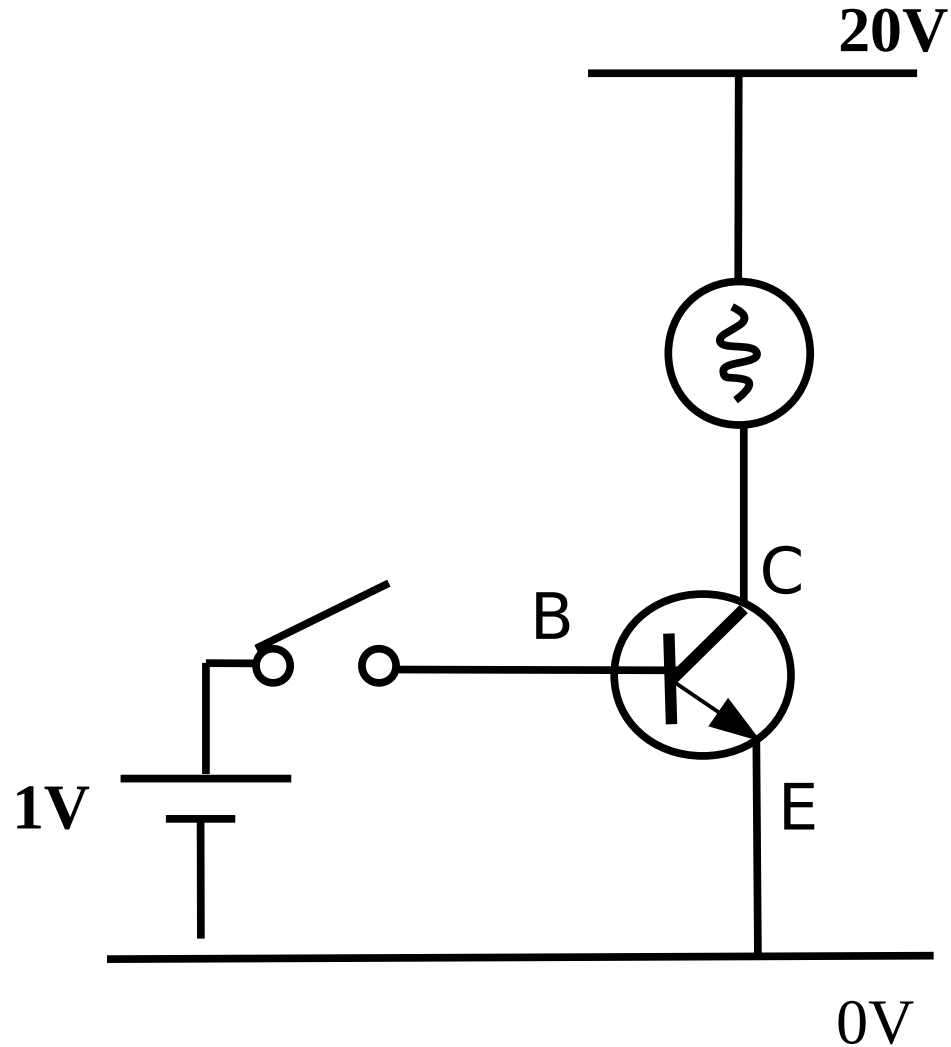
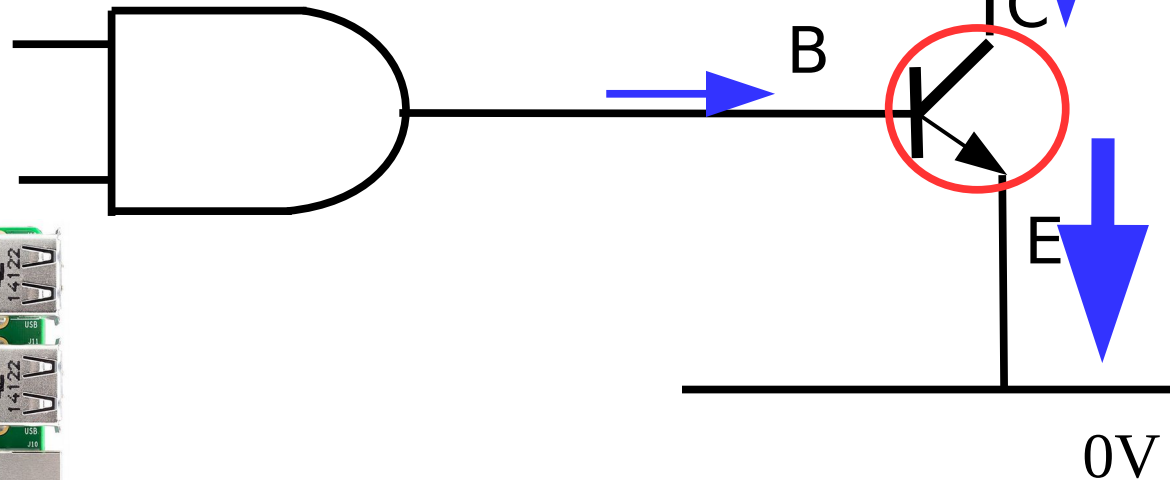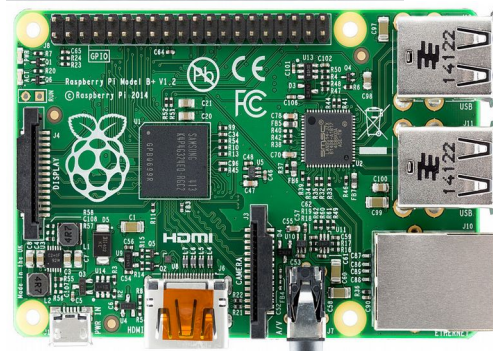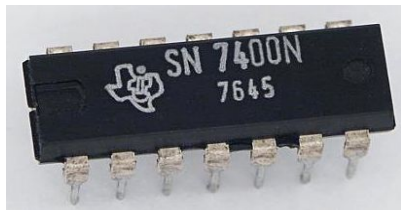
# Transistors – The NPN Bipolar Junction Transistor (BJT)



- The base current could come from a chip!
- Now we can power any sized device using a decision made from a tiny chip we want.



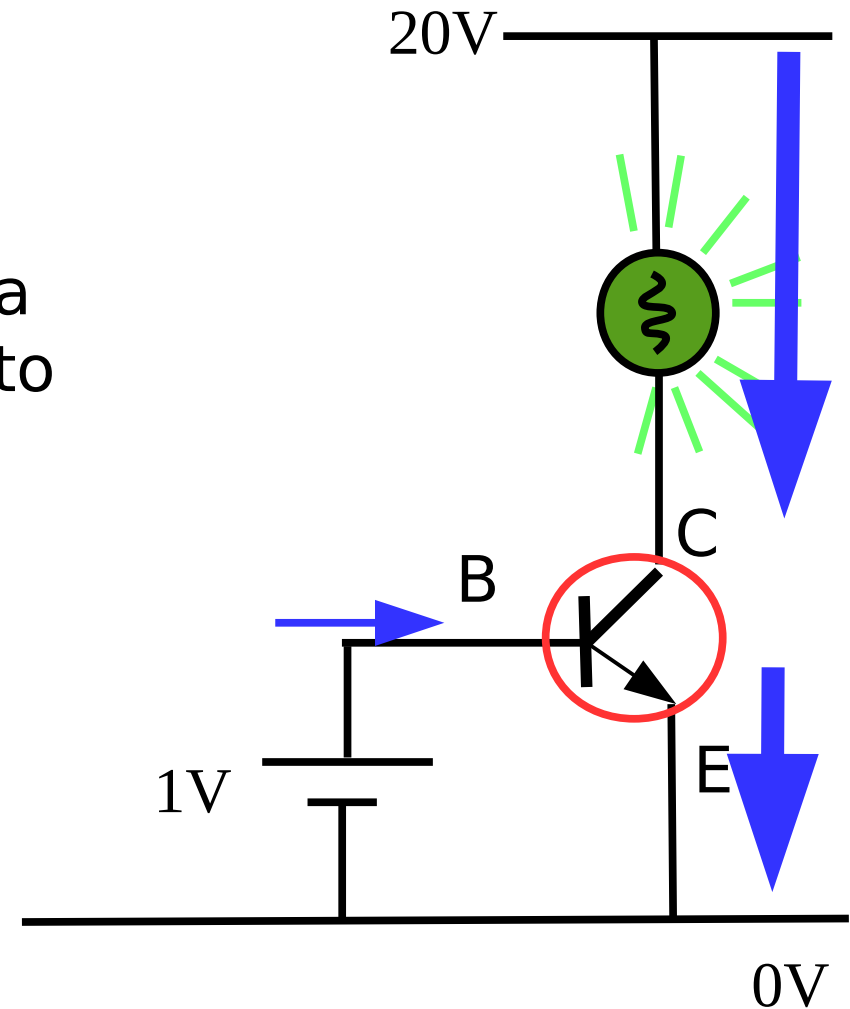
# Transistors – The NPN Bipolar Junction Transistor (BJT)





- In summary:

The **NPN** Bipolar Junction Transistor will turn **ON** when a **positive** voltage is supplied to the **Base**.



- **No recap of last lecture :)**
- Transistor basics
  - Relays (Mechanical transistor)
  - NPN Bipolar Junction Transistors
  - **PNP Bipolar Junction Transistors**
  - MOSFETs
- Push pull pairs to drive MOSFETs
- One last thing
- Summary

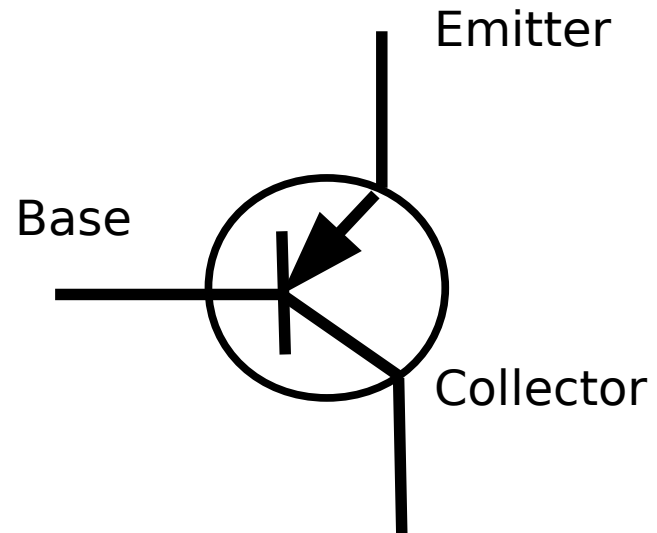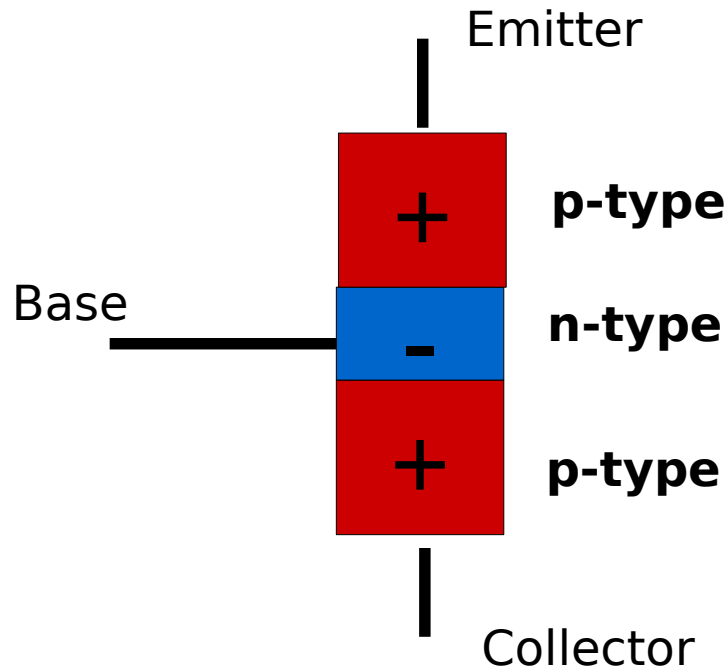
# Transistors – The PNP Bipolar Junction Transistor (BJT)


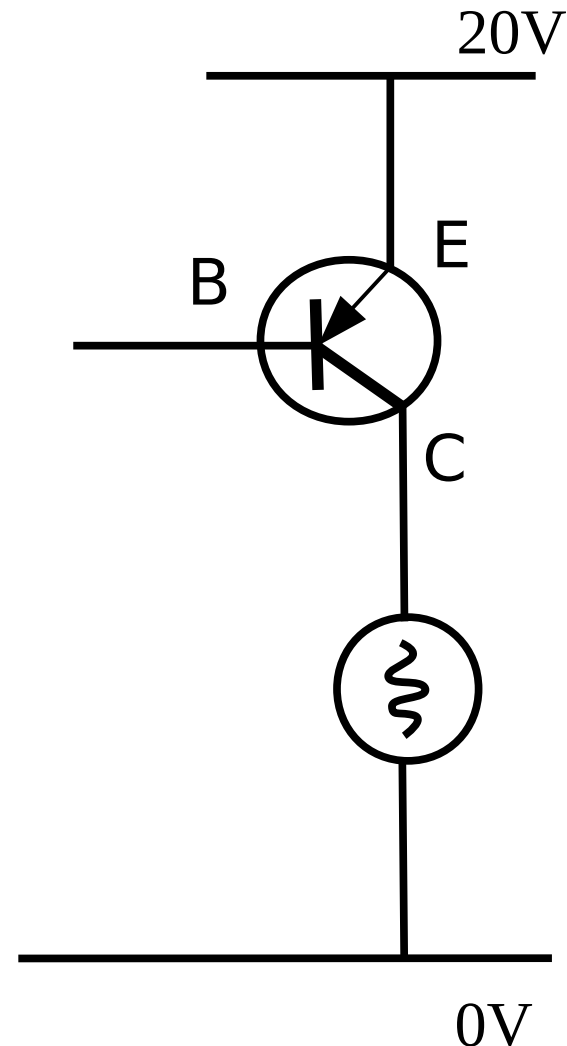
# Transistors – The PNP Bipolar Junction Transistor (BJT)



- The **PNP** transistor is just like the **NPN** transistor.
- Except it turns ON when the input is switched OFF by connecting it to 0V.**
- And switched OFF when the input is connected to a positive voltage.**





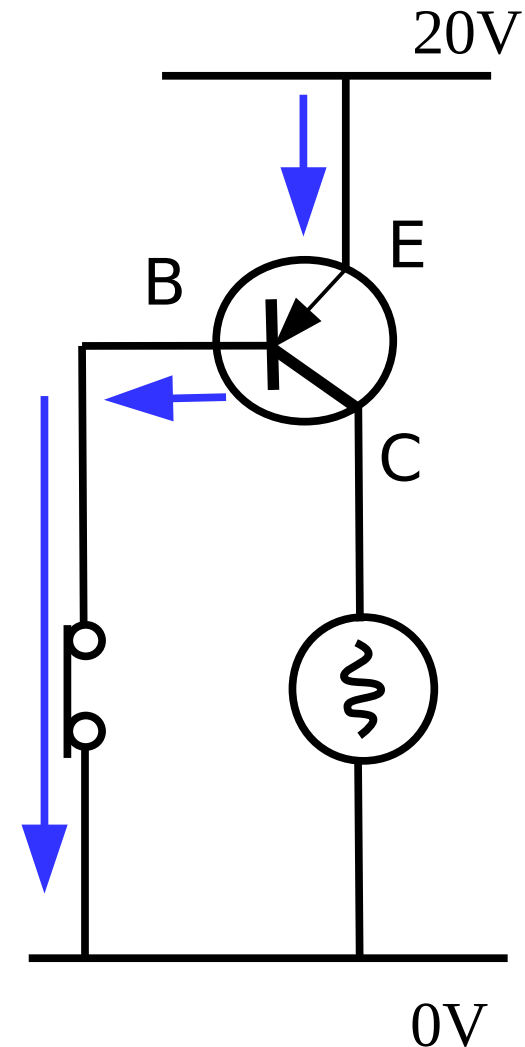
# Transistors – The PNP Bipolar Junction Transistor (BJT)




- If you connect the base to 0V allowing a small current to flow out of the transistor.



# Transistors – The PNP Bipolar Junction Transistor (BJT)




- This turns the transistor on

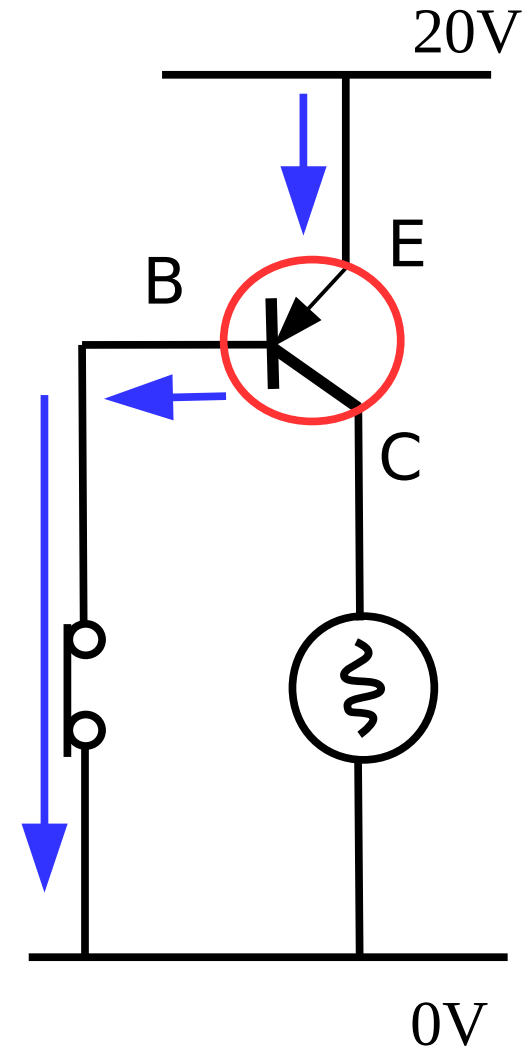
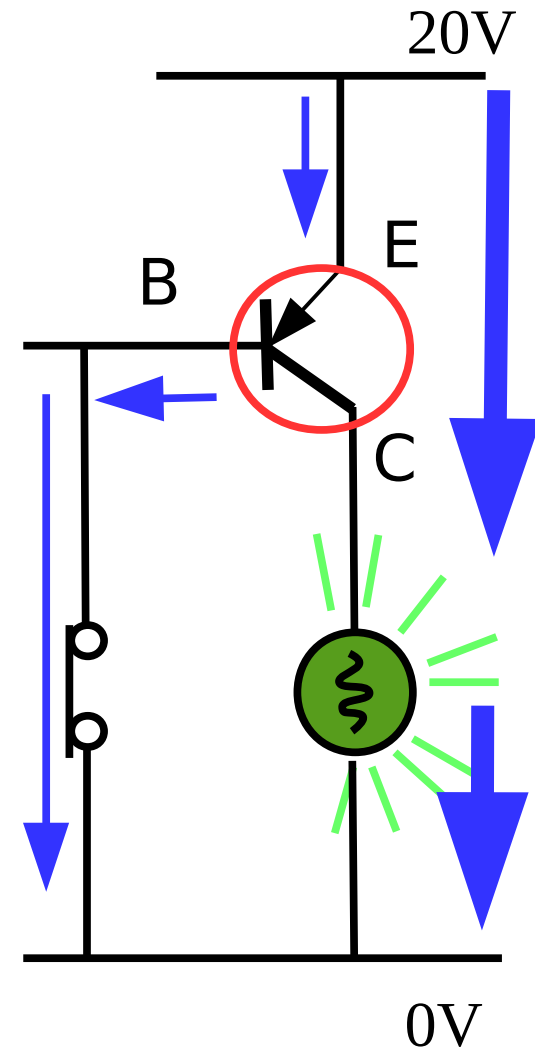
# Transistors – The PNP Bipolar Junction Transistor (BJT)




- Then a large current is turned on between the emitter and collector.
- Thus your light bulb will turn on.




# Transistors – The PNP Bipolar Junction Transistor (BJT)

- When the switch is opened...

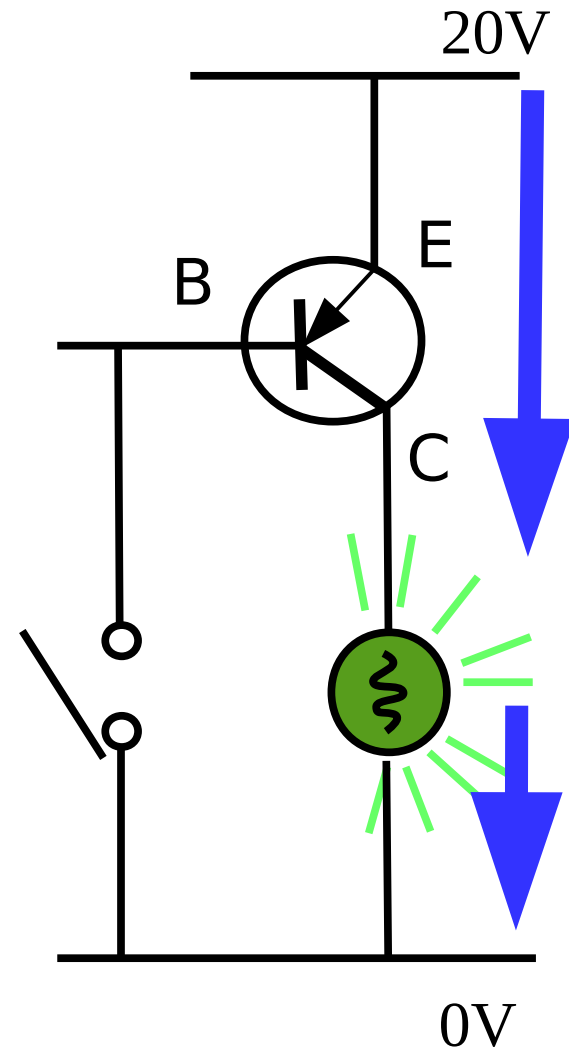
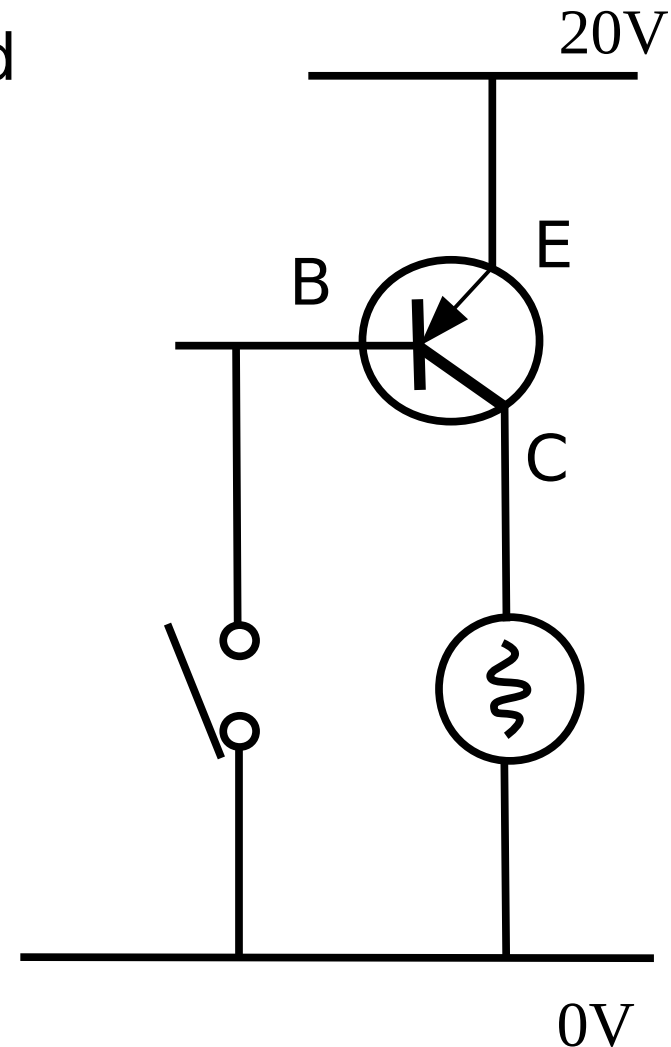
# Transistors – The PNP Bipolar Junction Transistor (BJT)


- Remove the base current and the transistor will turn off.


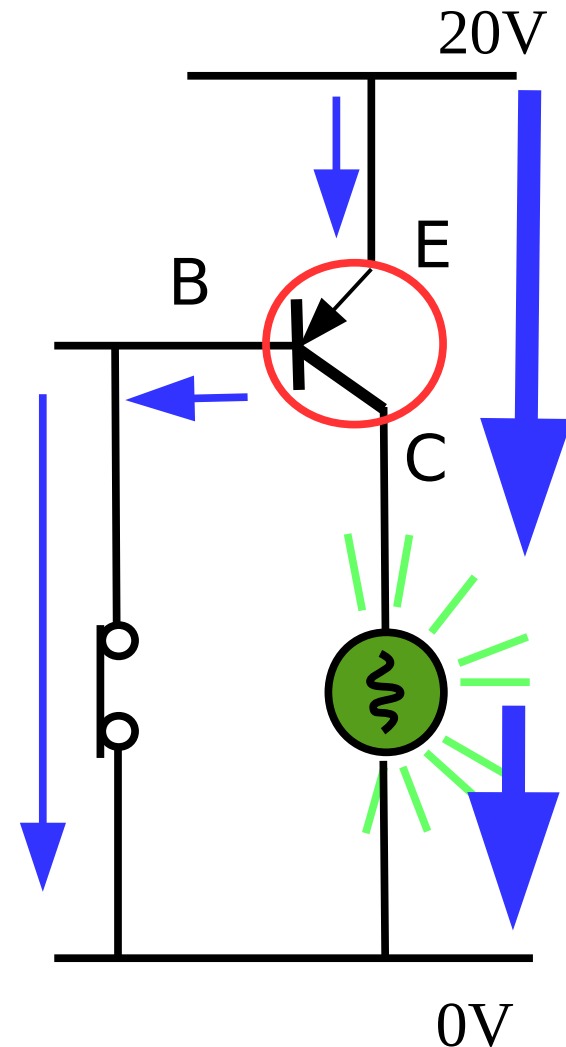
# Transistors – The PNP Bipolar Junction Transistor (BJT)





- In summary the the **PNP** transistor will turn **ON** when 0V is applied to the input.
- Which is the **opposite** of how the **NPN** transistor works.


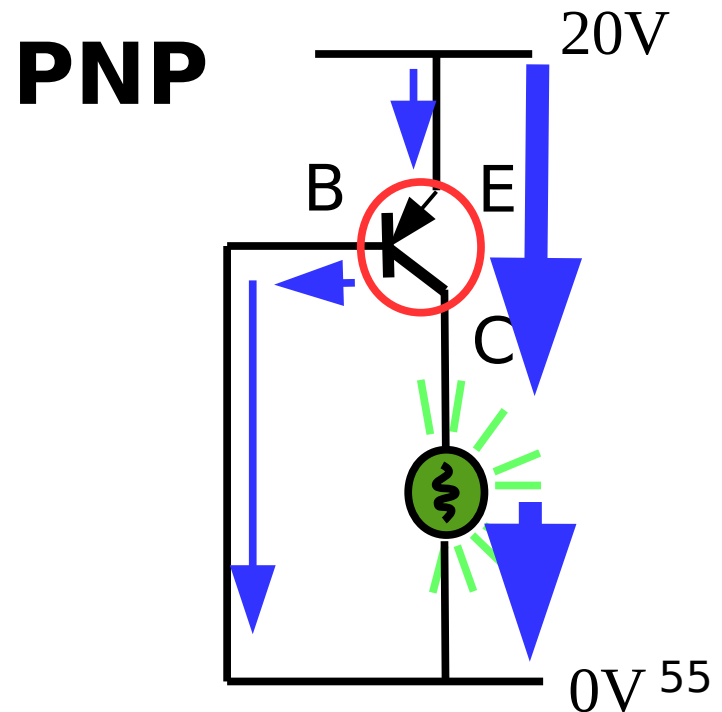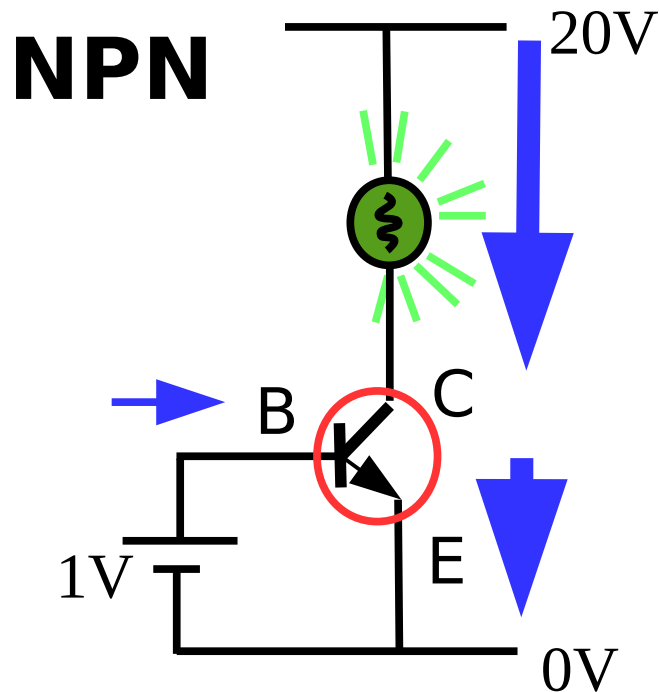
# NPN/PNP Bipolar Junction Transistors summary



- We have two transistors the **NPN** that turns **ON** when a positive voltage is applied
- And then **PNP** which turns **ON** when 0V is applied.



# Advantages and disadvantages of BJT transistors



## •Advantages

•**They can turn on and off very quickly** – good ✓  
for audio amplifiers and (Radio Frequency) RF.

•Low cost. ✓

## •Disadvantages

•They continually need a **base** current to keep them turned on. ✗

•**Not** so good for switching high currents i.e. running motors. ✗






- **No recap of last lecture :)**
- Transistor basics
  - Relays (Mechanical transistor)
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - **MOSFETs**
- Push pull pairs to drive MOSFETs
- One last thing
- Summary



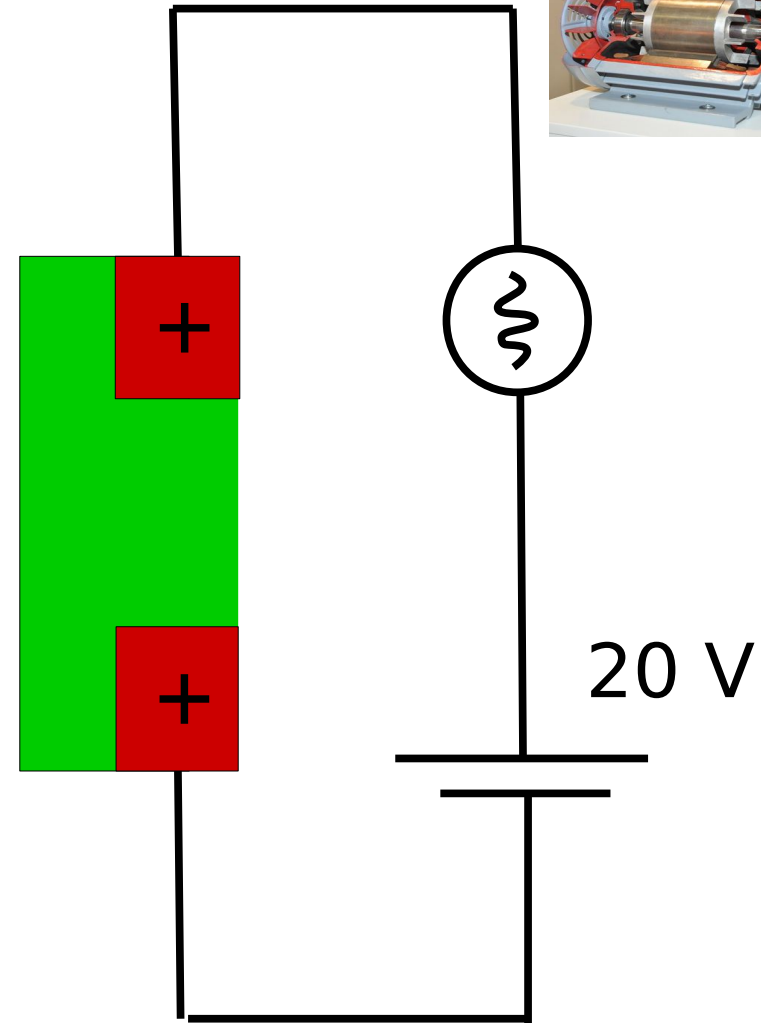
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)

- Good for **high currents** i.e. running motors.
- MOSFETs consists of two contacts which are made of a material with a positive charge.
- Between these two contacts is an insulator - **no charge can flow through this layer.**


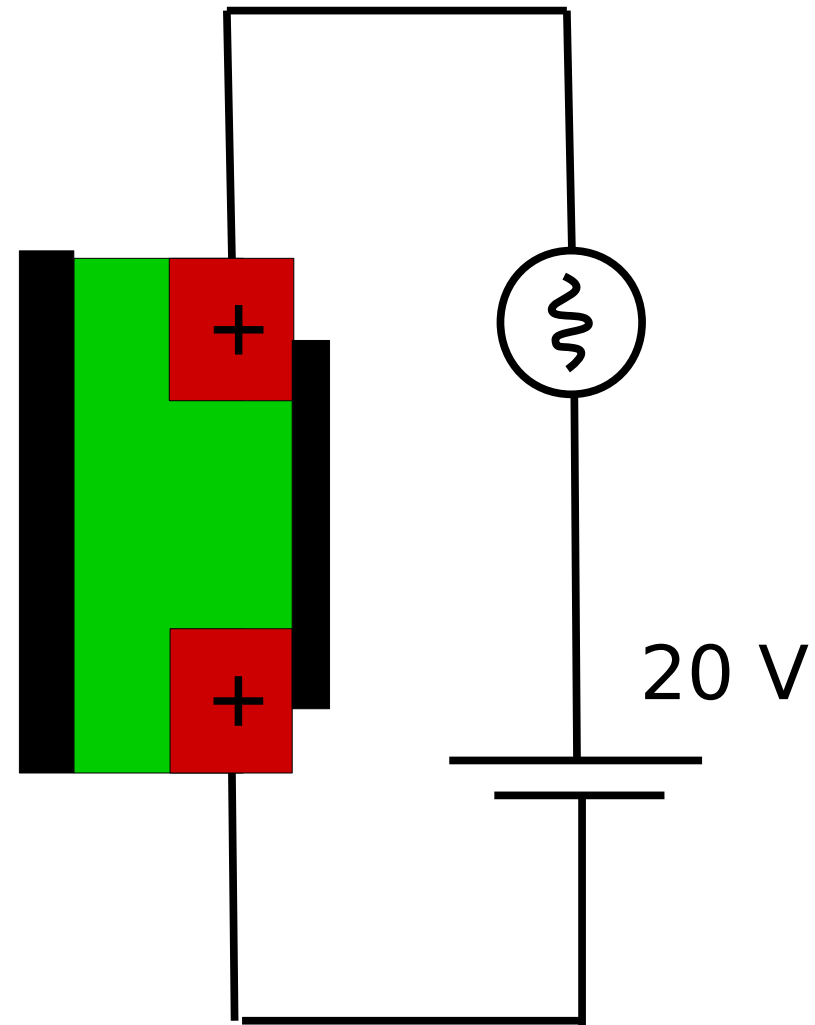
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)


- On the edge of our MOSFET we attach two metal plates.
- These act like a capacitor.




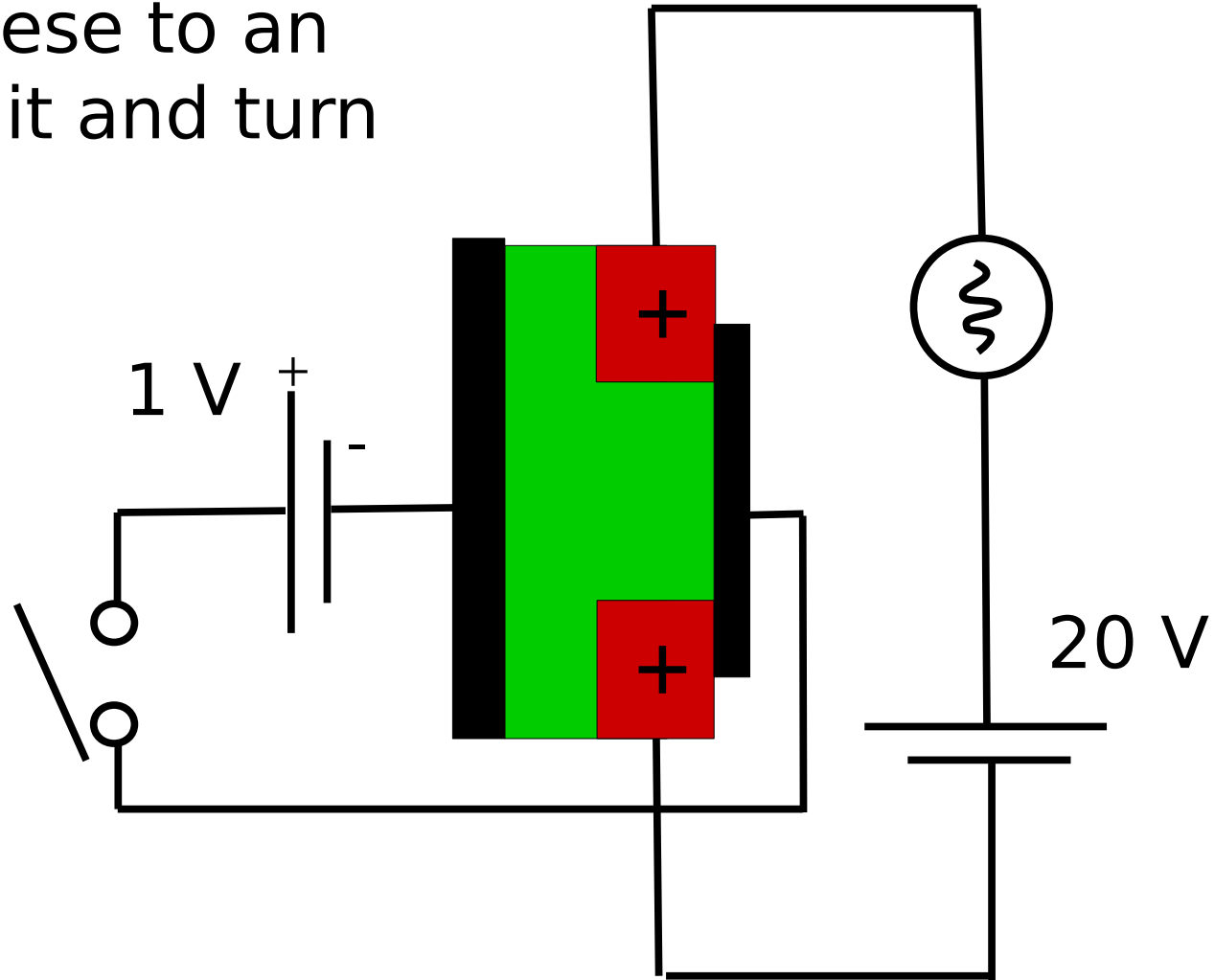
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)


- We attach these to an external circuit and turn it on....




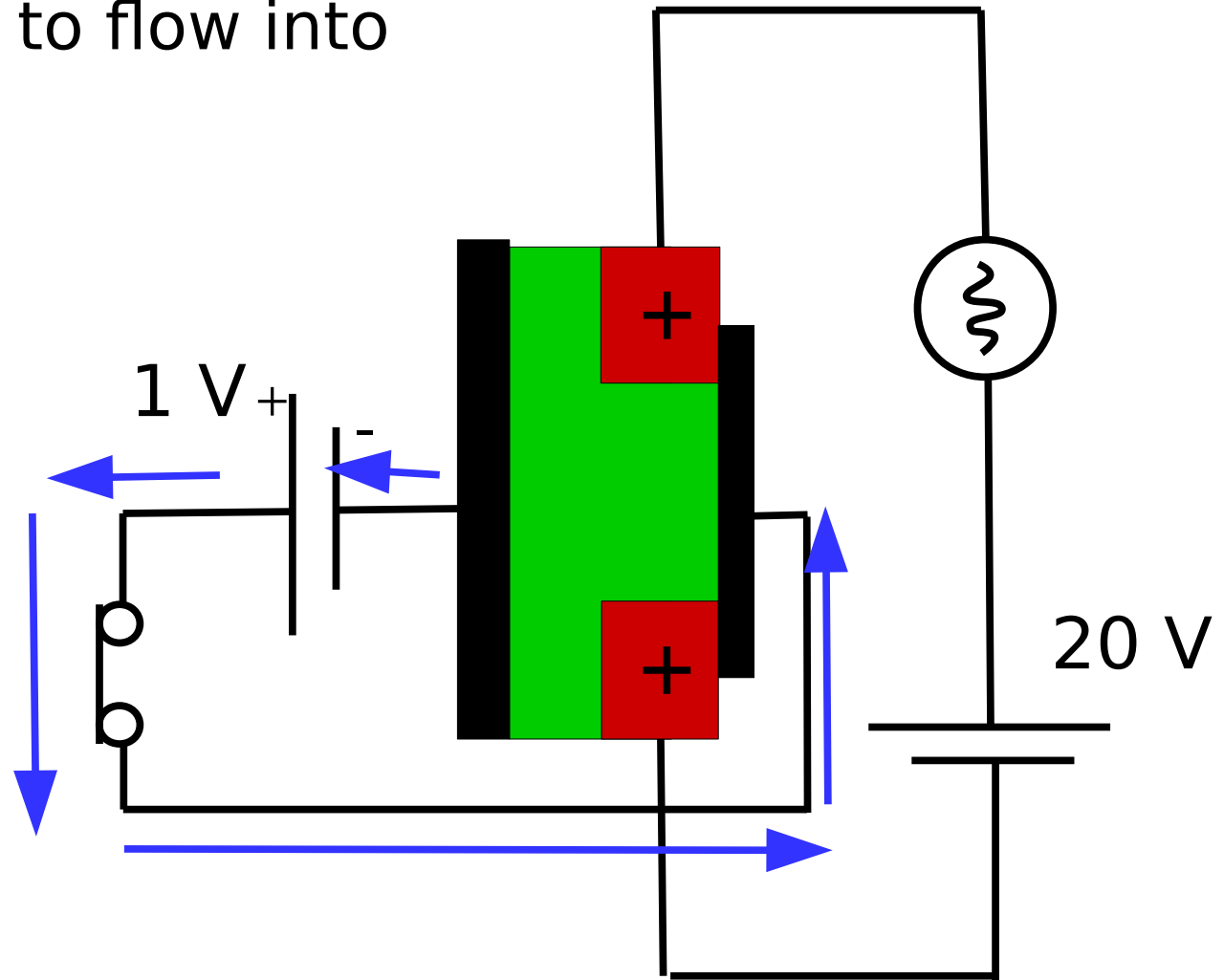
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)


- Charge starts to flow into the capacitor.






# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)

- The plates charge up.....

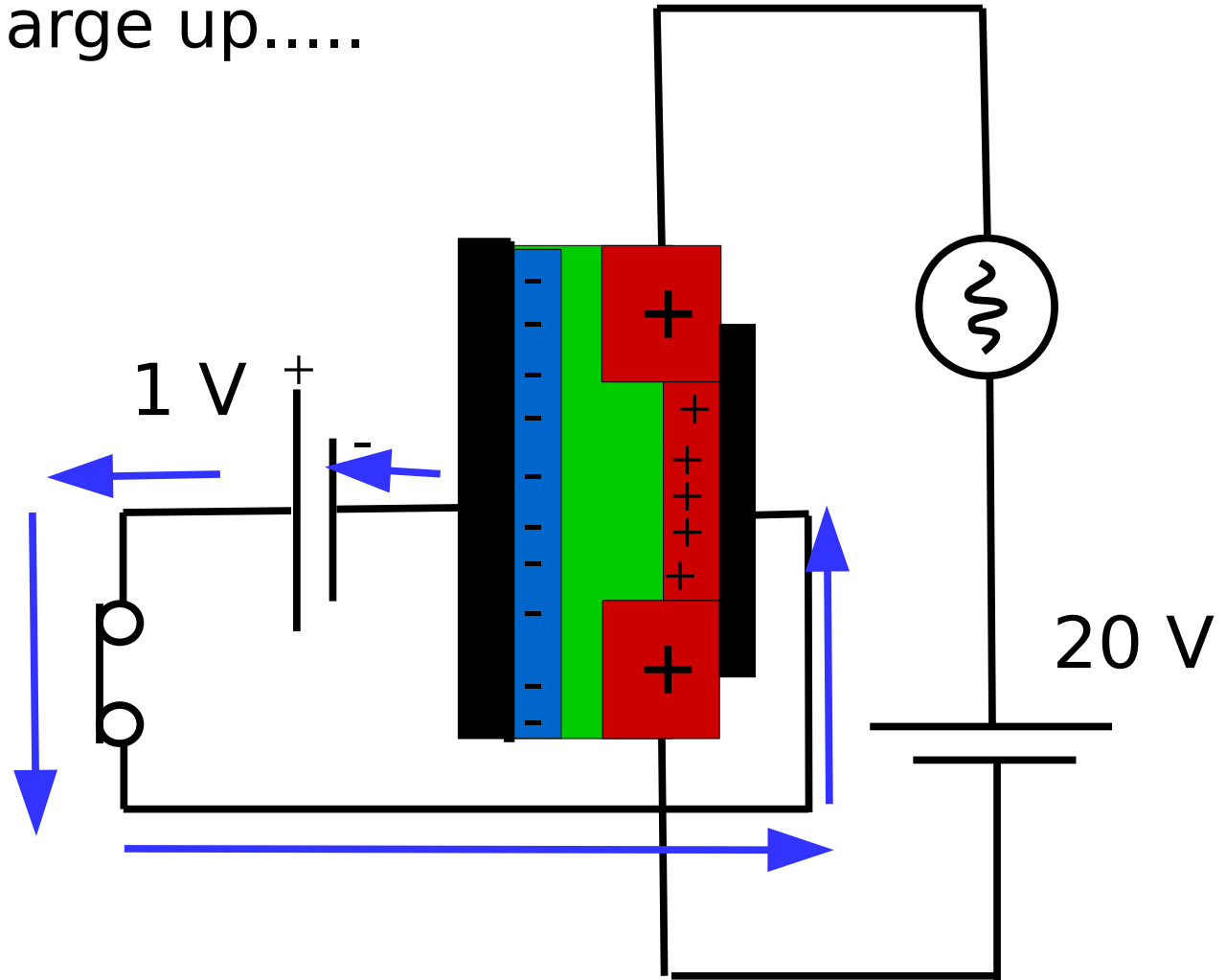

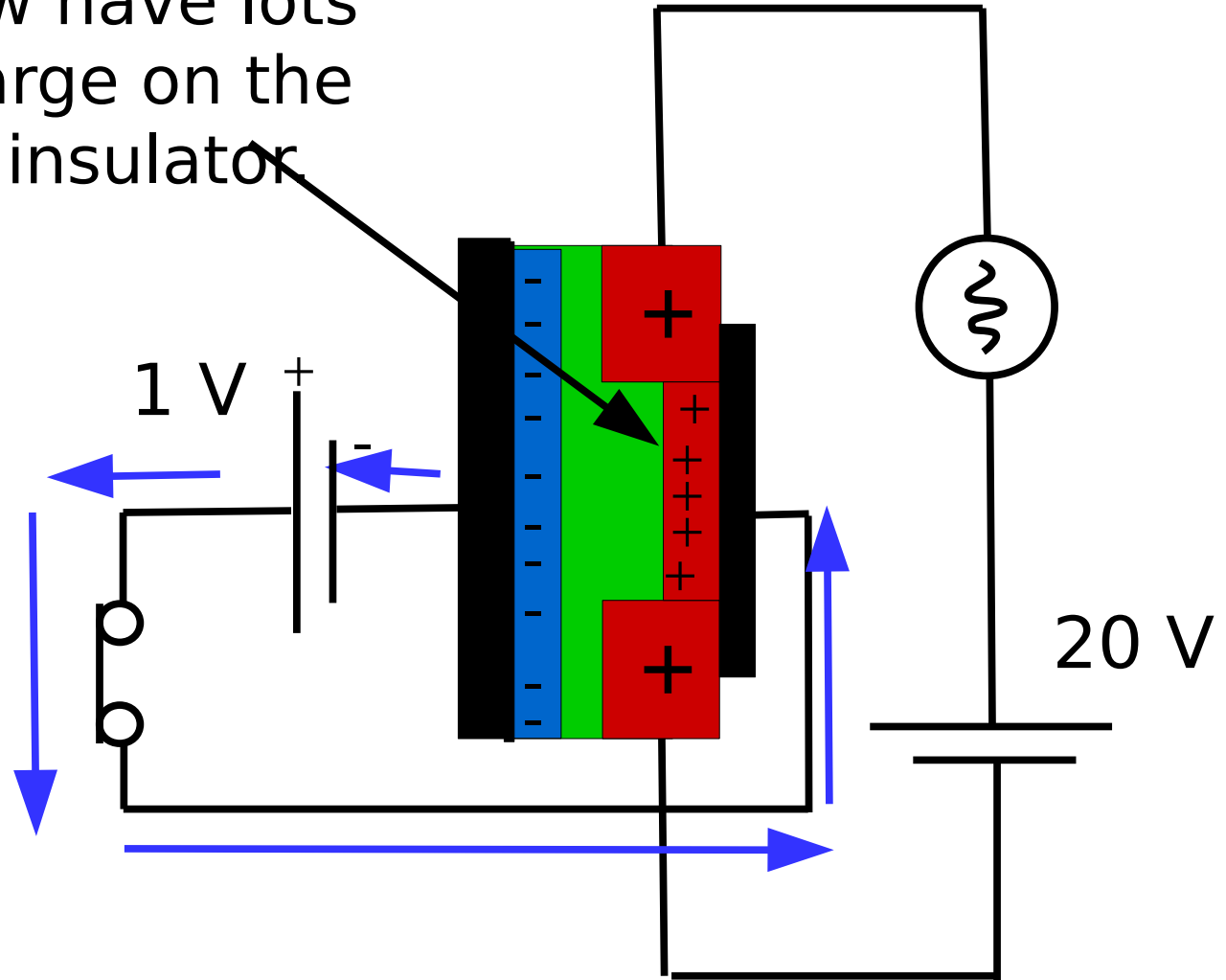
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)

- Notice we now have lots of positive charge on the surface of the insulator



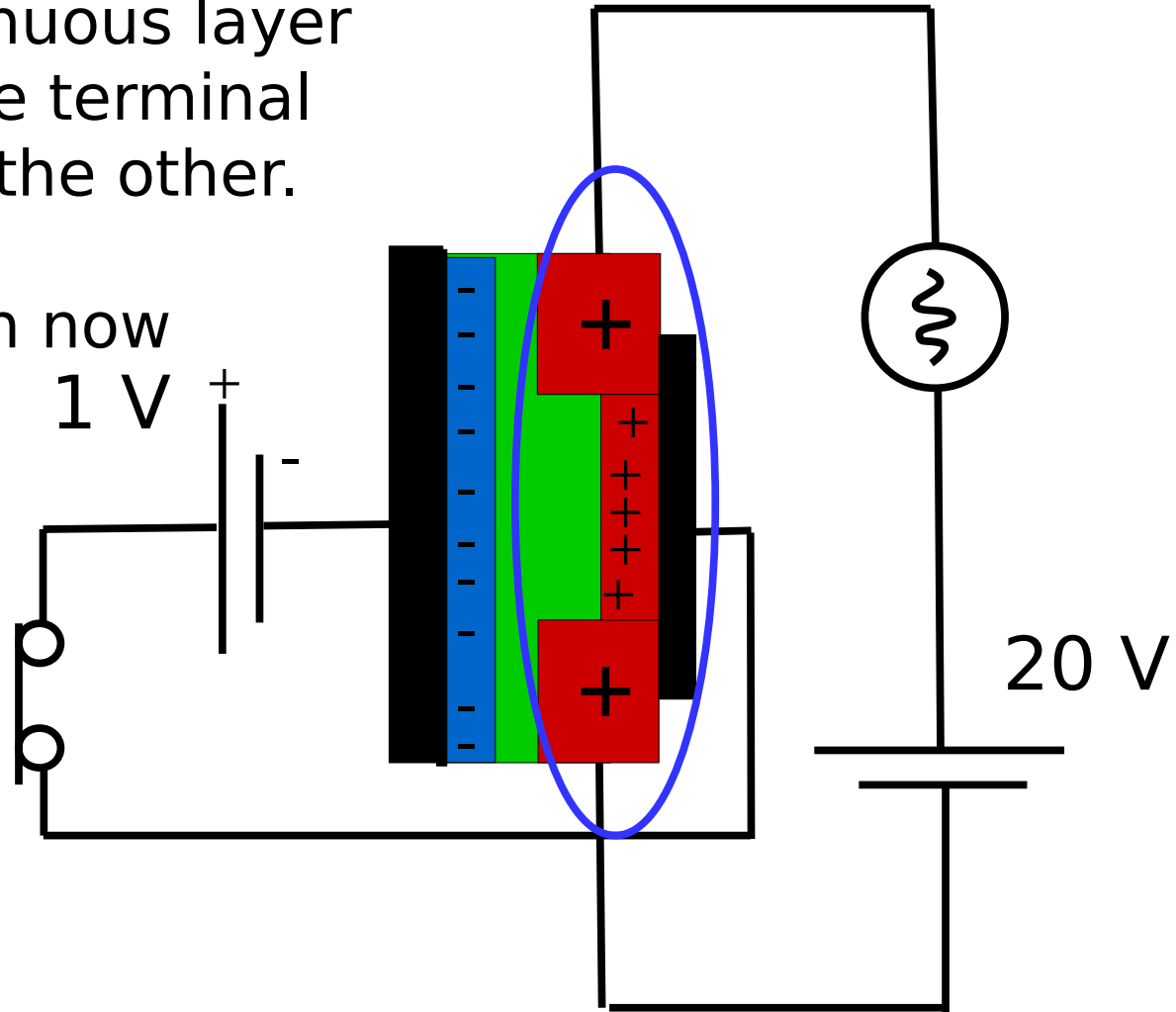
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)

- And have a continuous layer of charge from one terminal of the MOSFET to the other.
- The transistor can now conduct current.





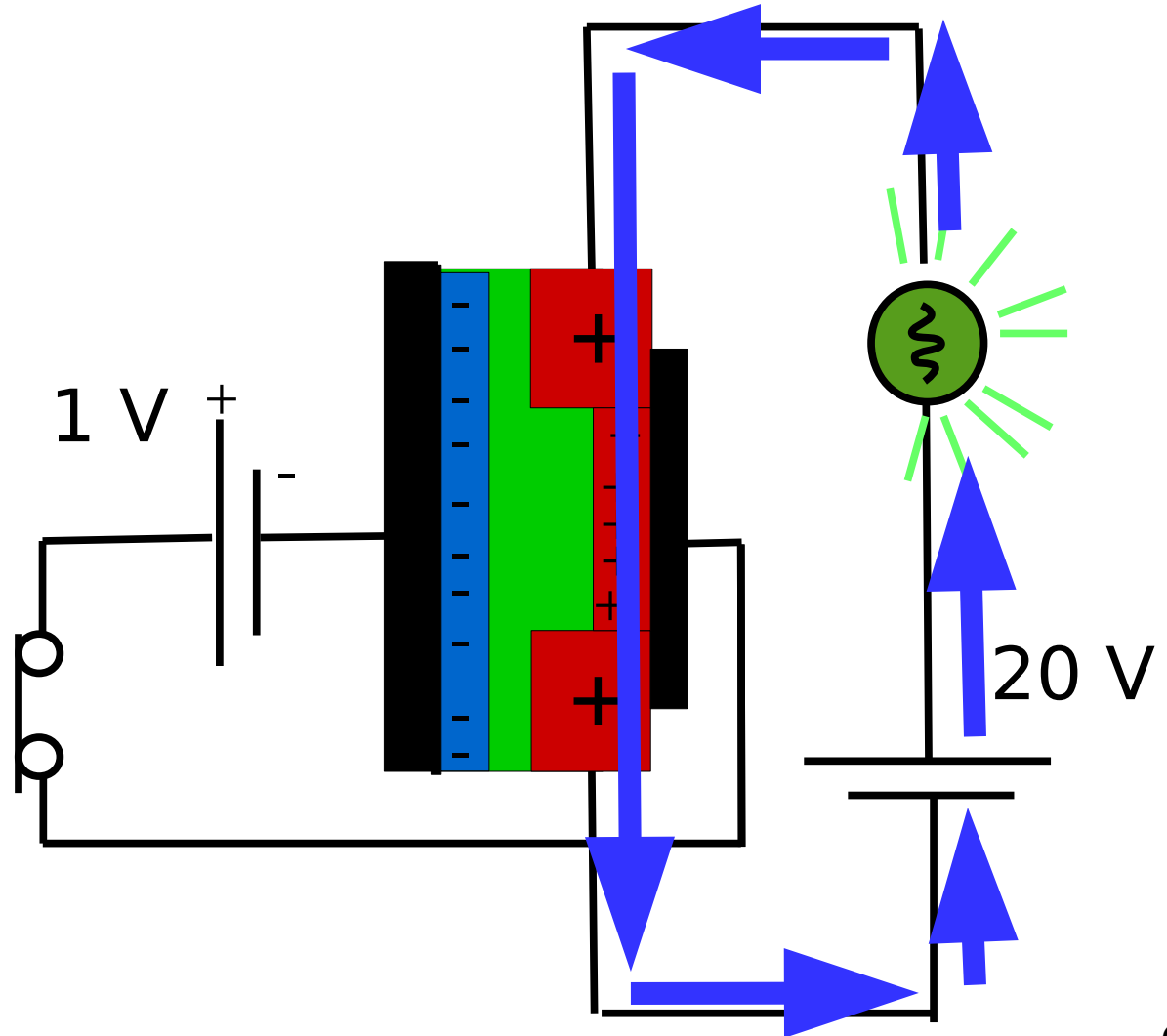
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)


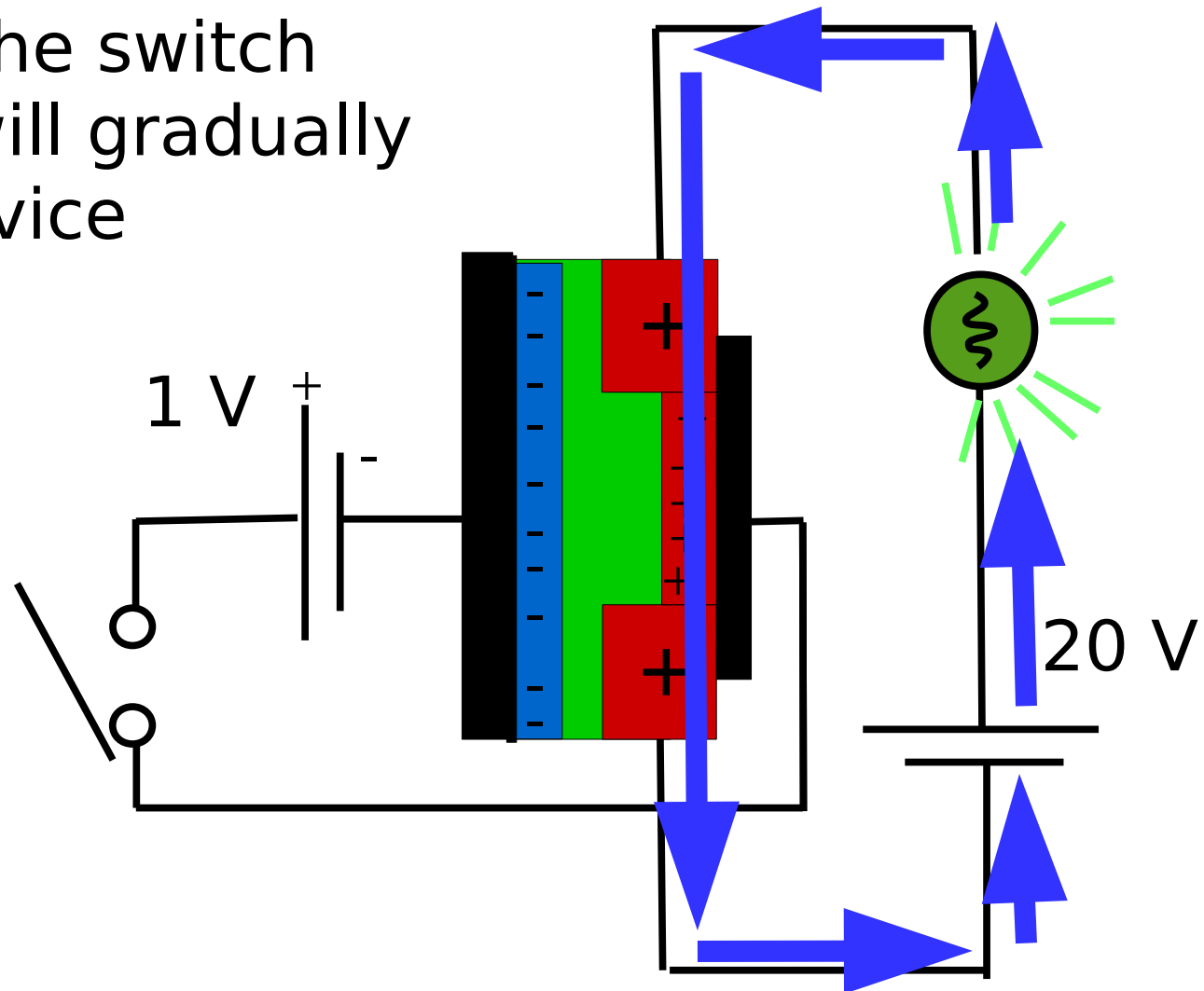
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)


- If we open the switch the charge will gradually leave the device (eventually).




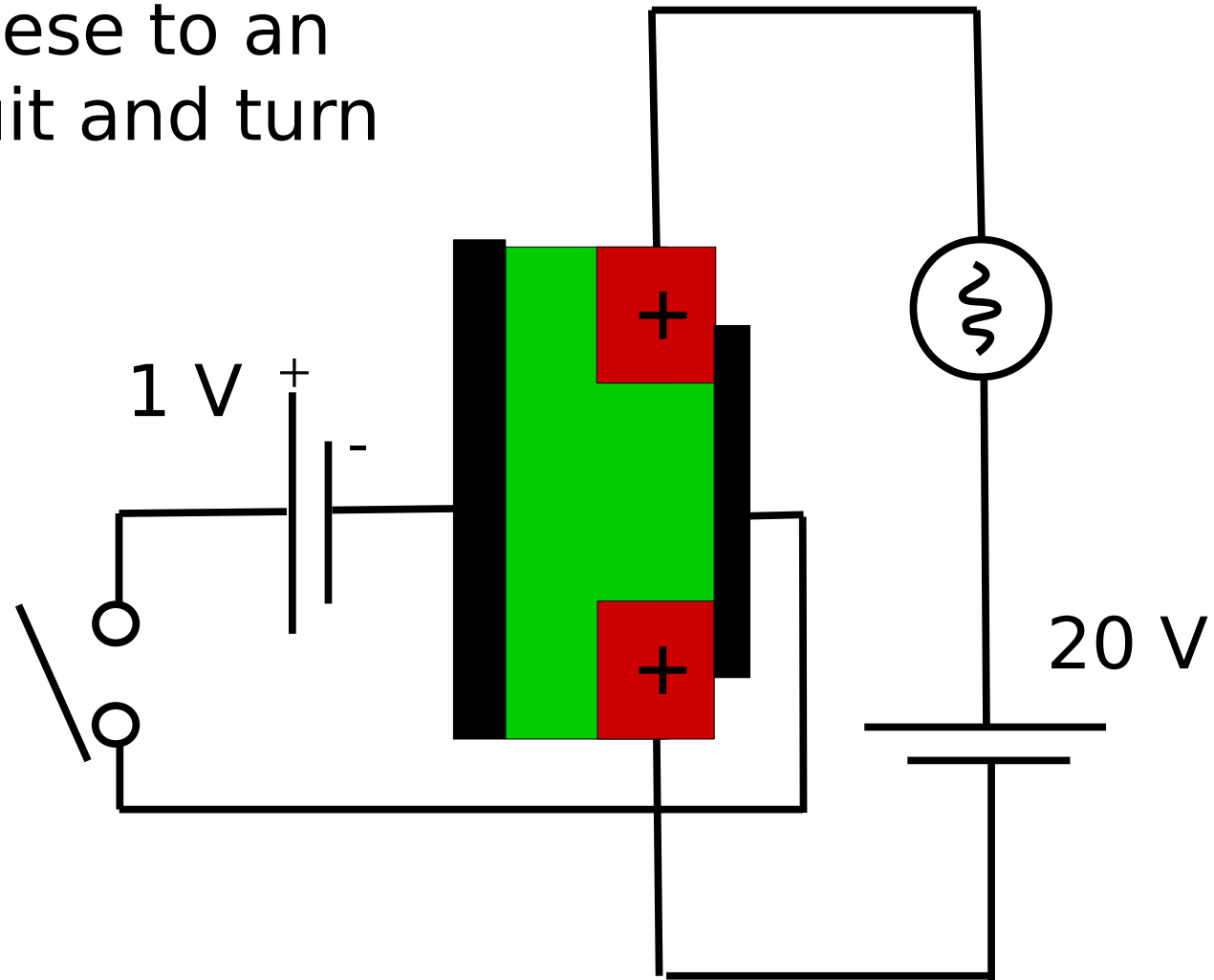
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)



- We attach these to an external circuit and turn it on....





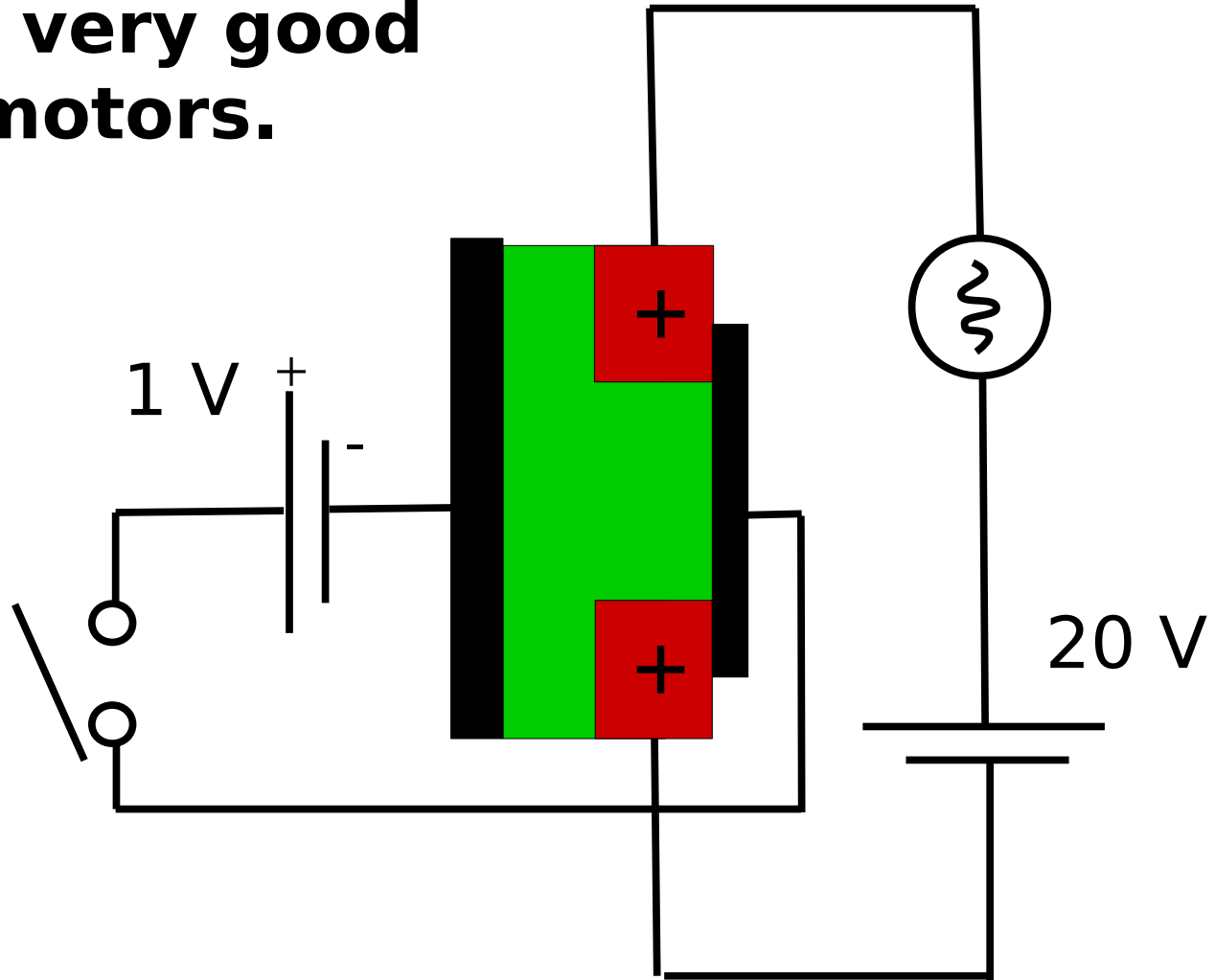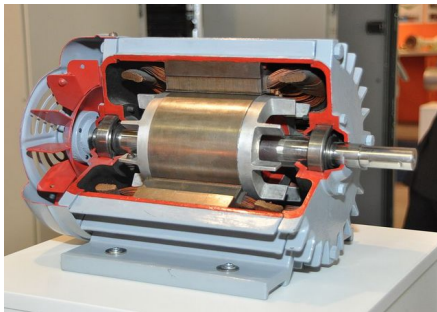
# MOSFET (Metal Oxide Semiconductor Field Effect Transistor)

- MOSFETs are **very good for driving motors.**



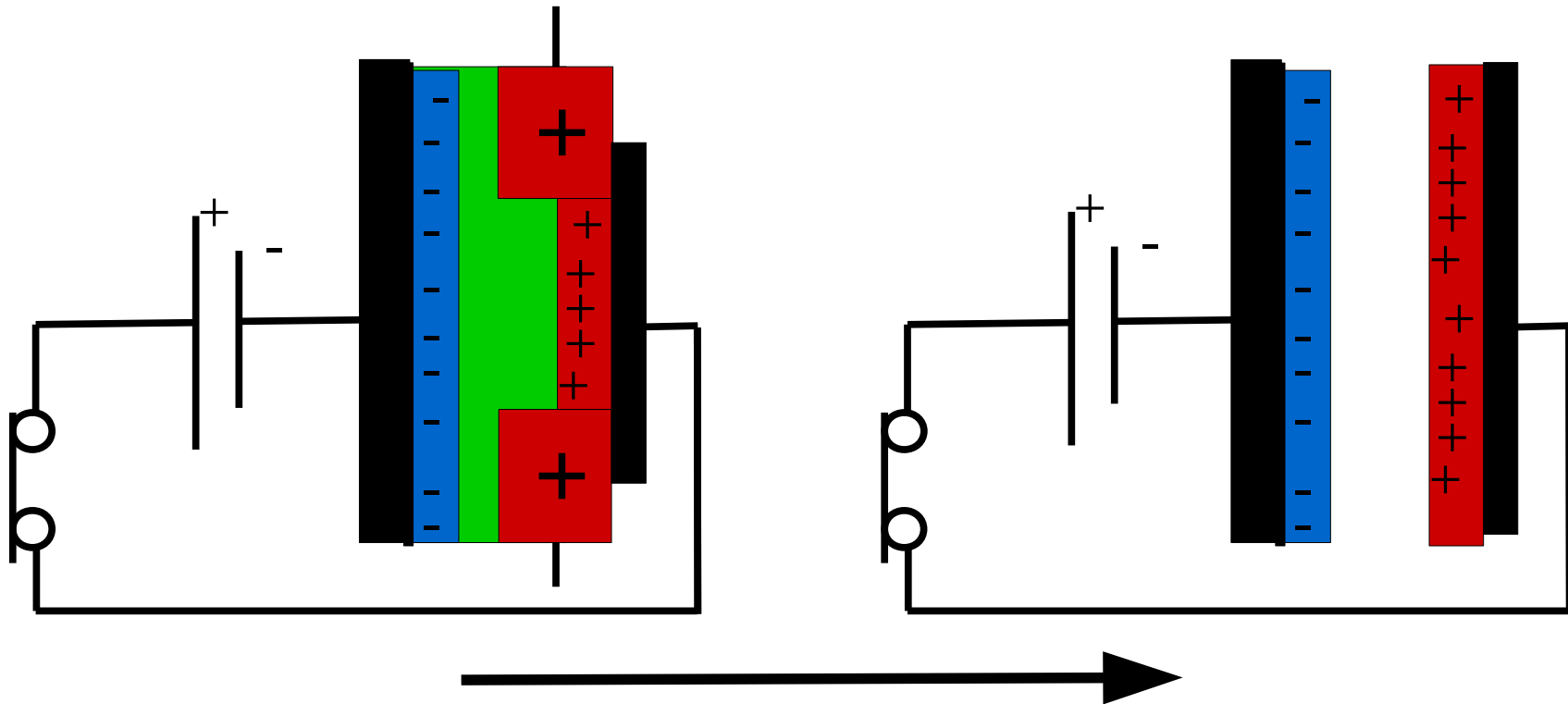
# The problem with MOSFETs

- The problem with MOSFETs is that they are in effect a capacitor


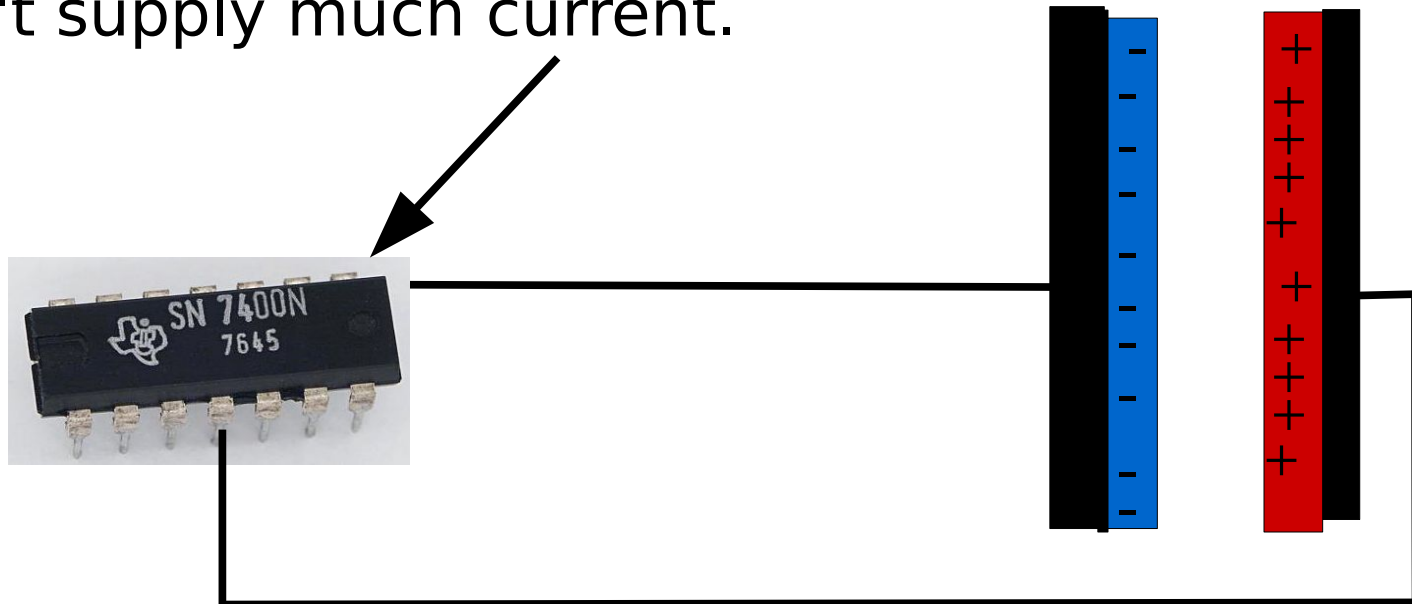
# The problem with MOSFETs


- And capacitors take a long time to charge up.
- Especially if you are driving it from a tiny chip that can't supply much current.



- This means they will **turn off and on really really slowly in fact too slowly to do anything useful.....**

# Circuit symbol for a MOSFET

- Notice it looks a bit like a capacitor

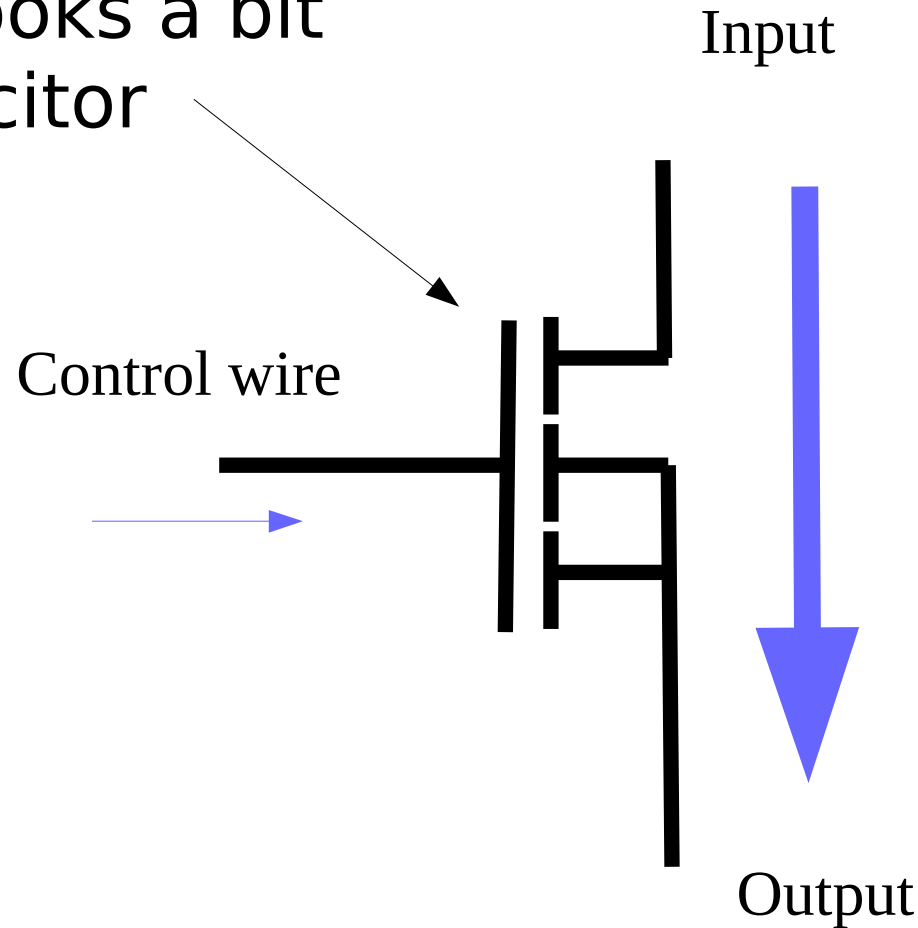



# Outline of the lecture

- No recap of last lecture :)
- Turning things on and off
  - Relays
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - MOSFETs
- **Push pull pairs to drive MOSFETs**
- One last thing
- Summary



# Question:



•Q: What type of transistors turn on and off very quickly??

## Question:






- Q: What type of transistors turn on and off very quickly??
- A: Bipolar Junction transistor
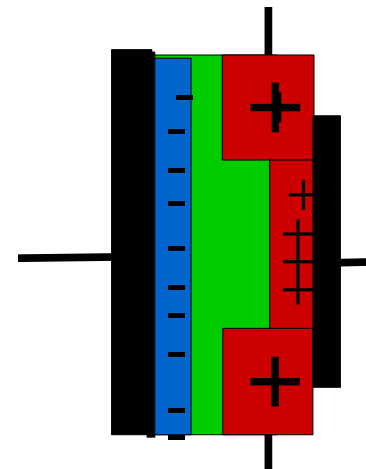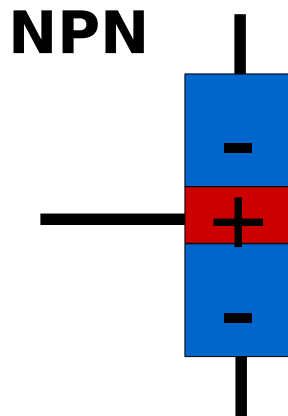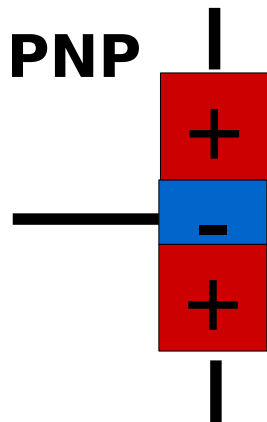
# Two types of transistor




**Bipolar Junction  
transistors: Fast / not very  
good for high currents**

**MOSFET: Slow to turn on  
and off/ But good for  
motors.**



- May be we can combine these transistors to make an optimum circuit to switch high current devices on and off.....

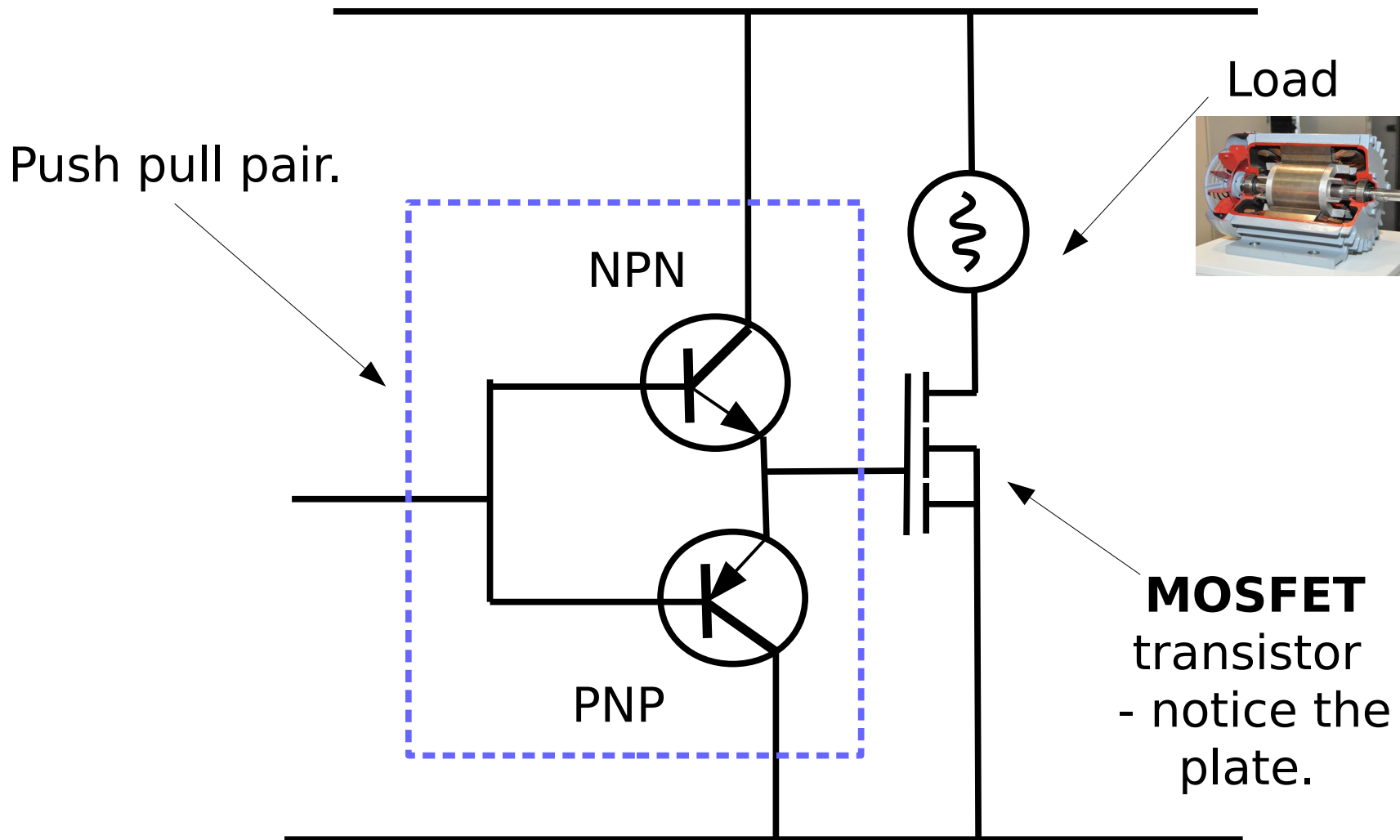
Yes, we can and the circuit looks like this.... a push pull pair circuit...


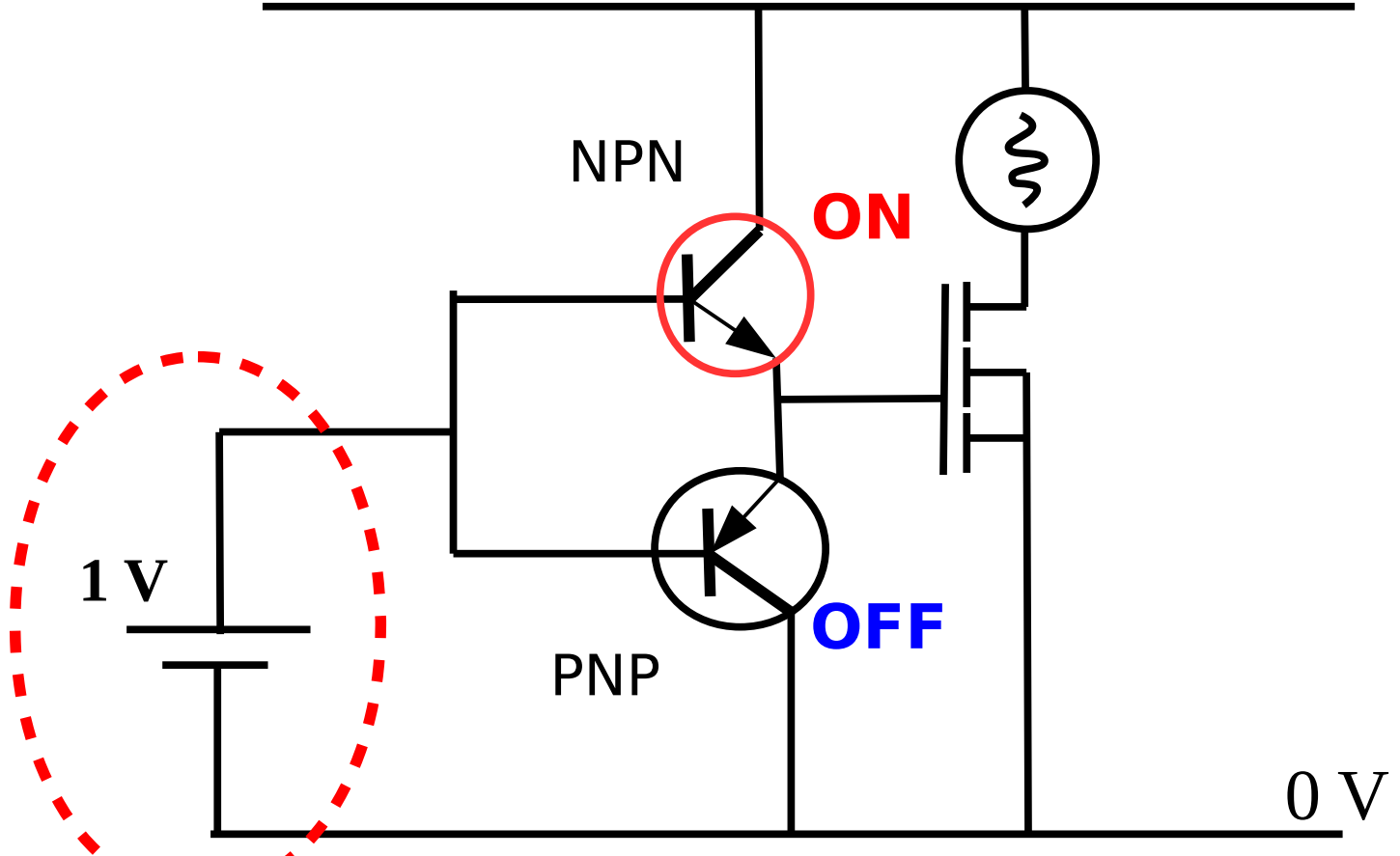
# Push pull pair – turning the MOSFET ON


- If we attach a **positive voltage** to the base of an **NPN** transistor it will turn **ON**.

- If we attach a **positive voltage** to the base of a **PNP** transistor it will turn **OFF**.



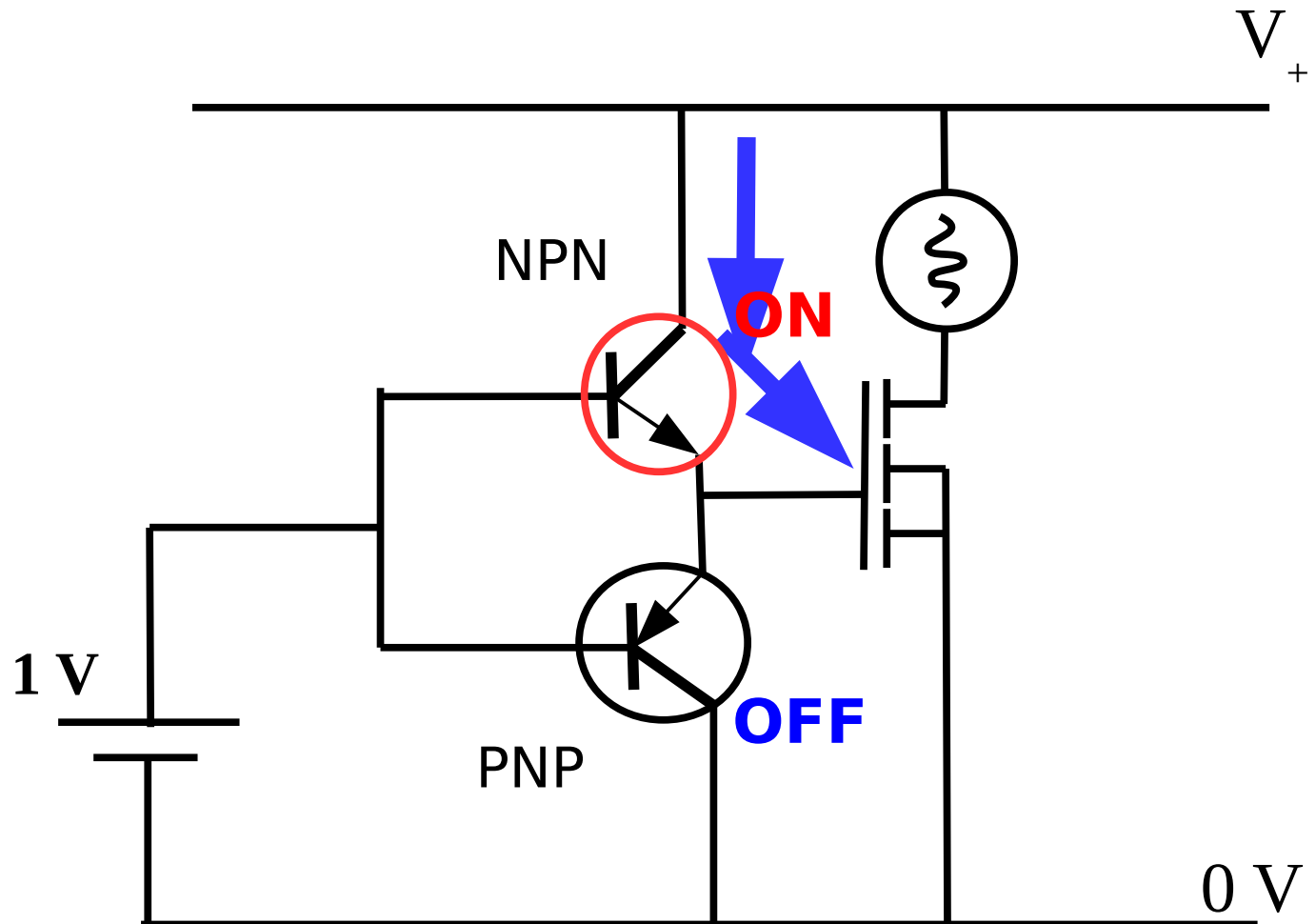
# Push pull pair – turning the MOSFET ON

- This will allow charge to flow through the NPN transistor, to the gate of the MOSFET




# Push pull pair – turning the MOSFET ON

- And the MOSFET will turn ON!

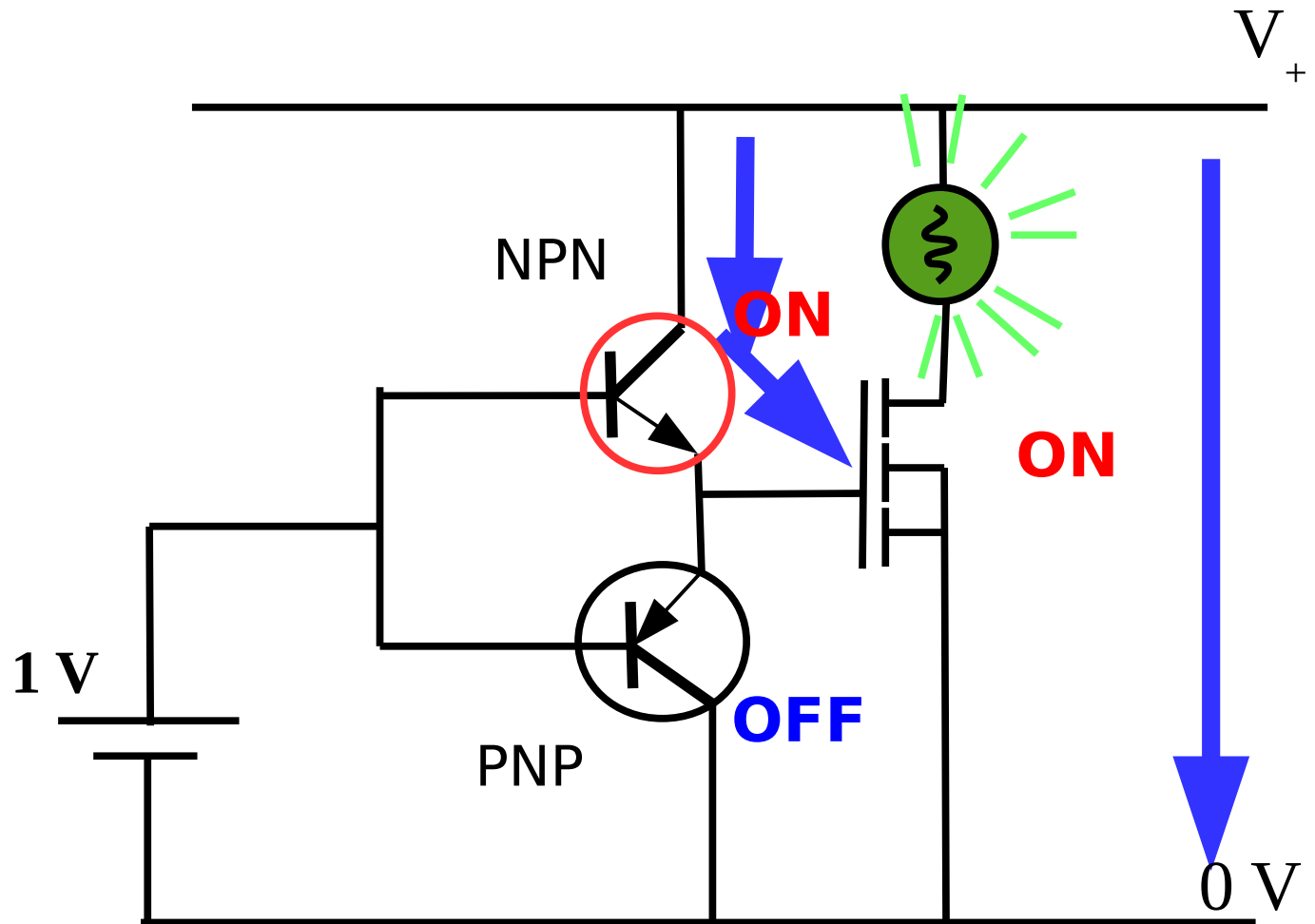

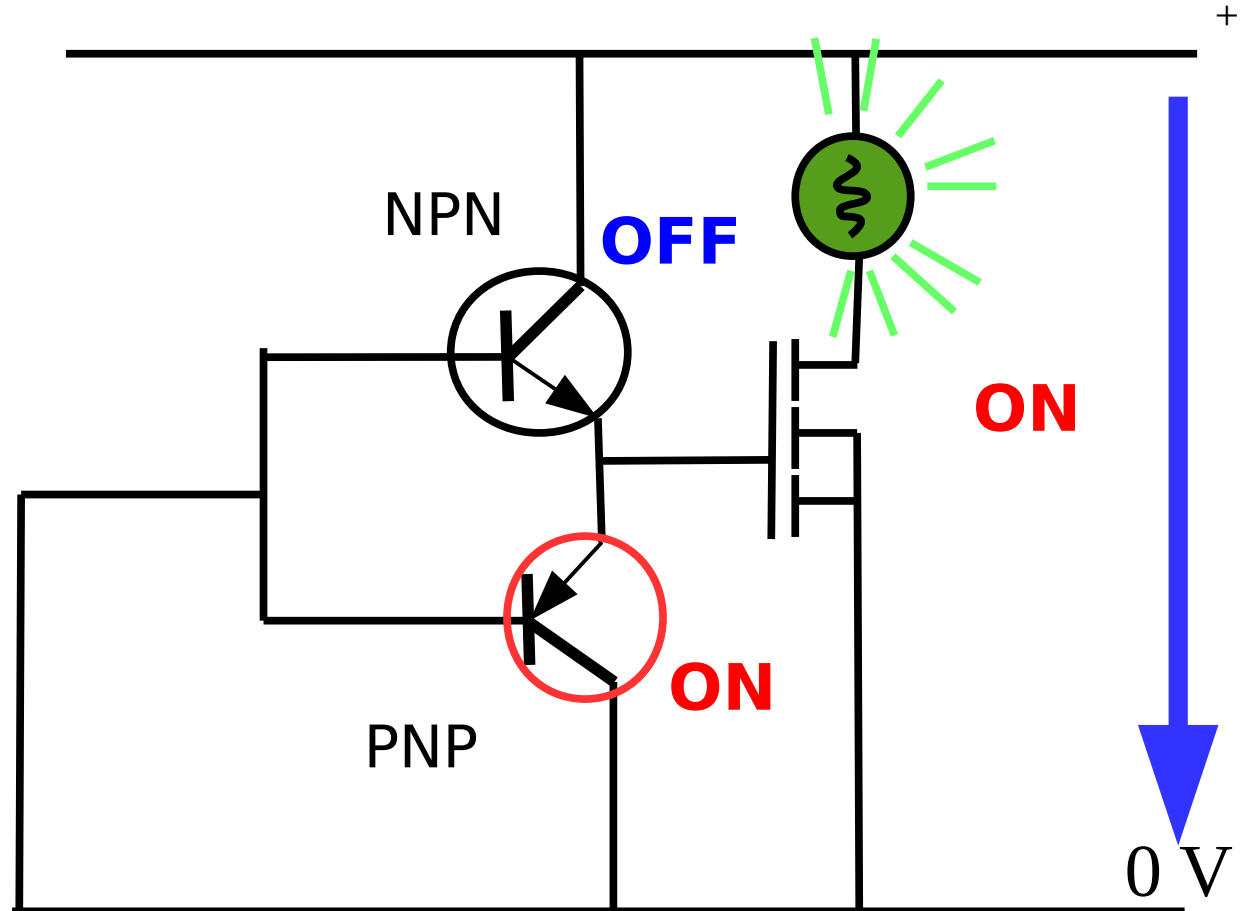
# Push pull pair – turning the MOSFET OFF

- If we attach a **0 Volts** to an **NPN** transistor it will turn **OFF**.
- If we attach **0 Volts** to a **PNP** transistor it will turn **ON**.





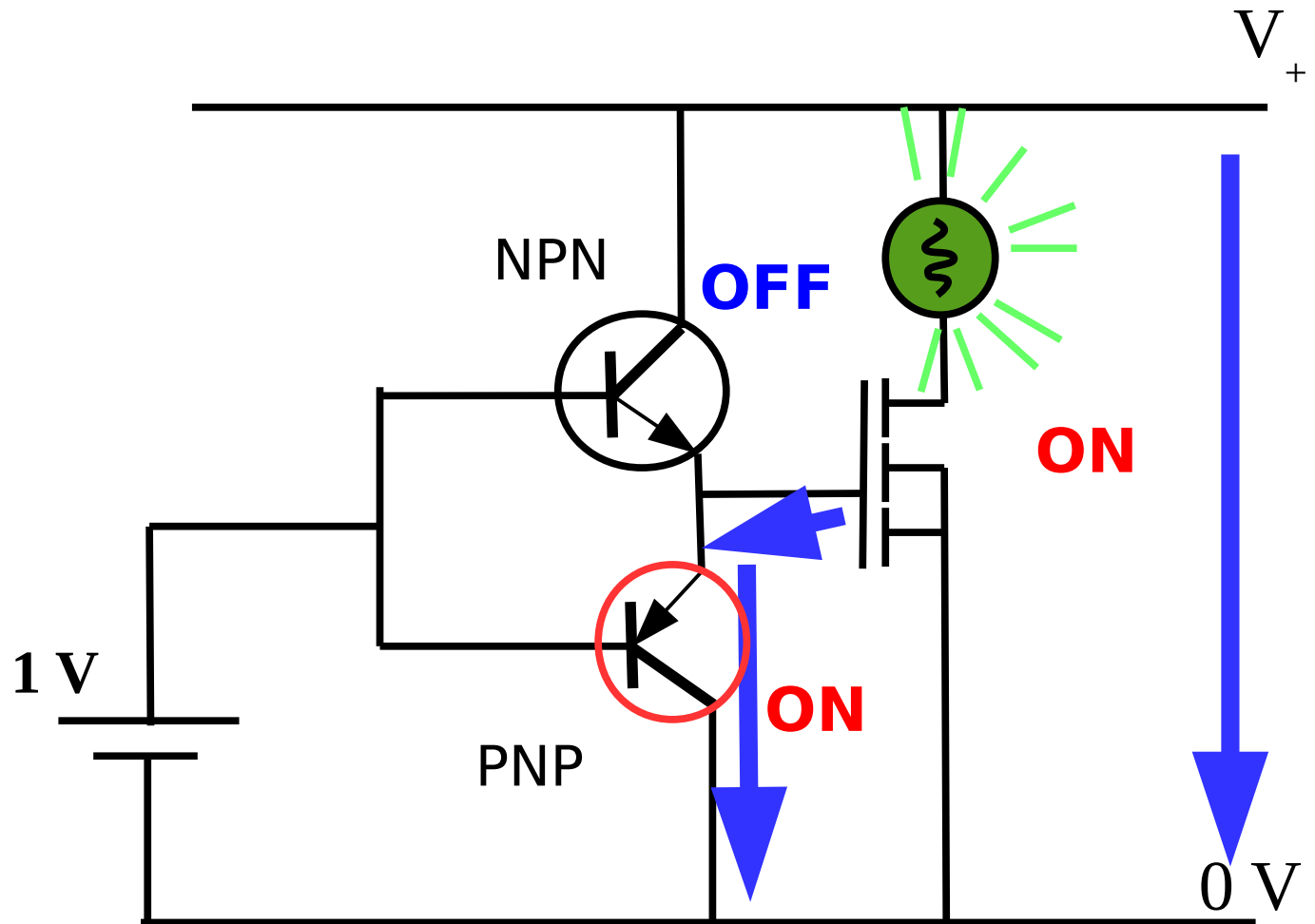
# Push pull pair – turning the MOSFET OFF




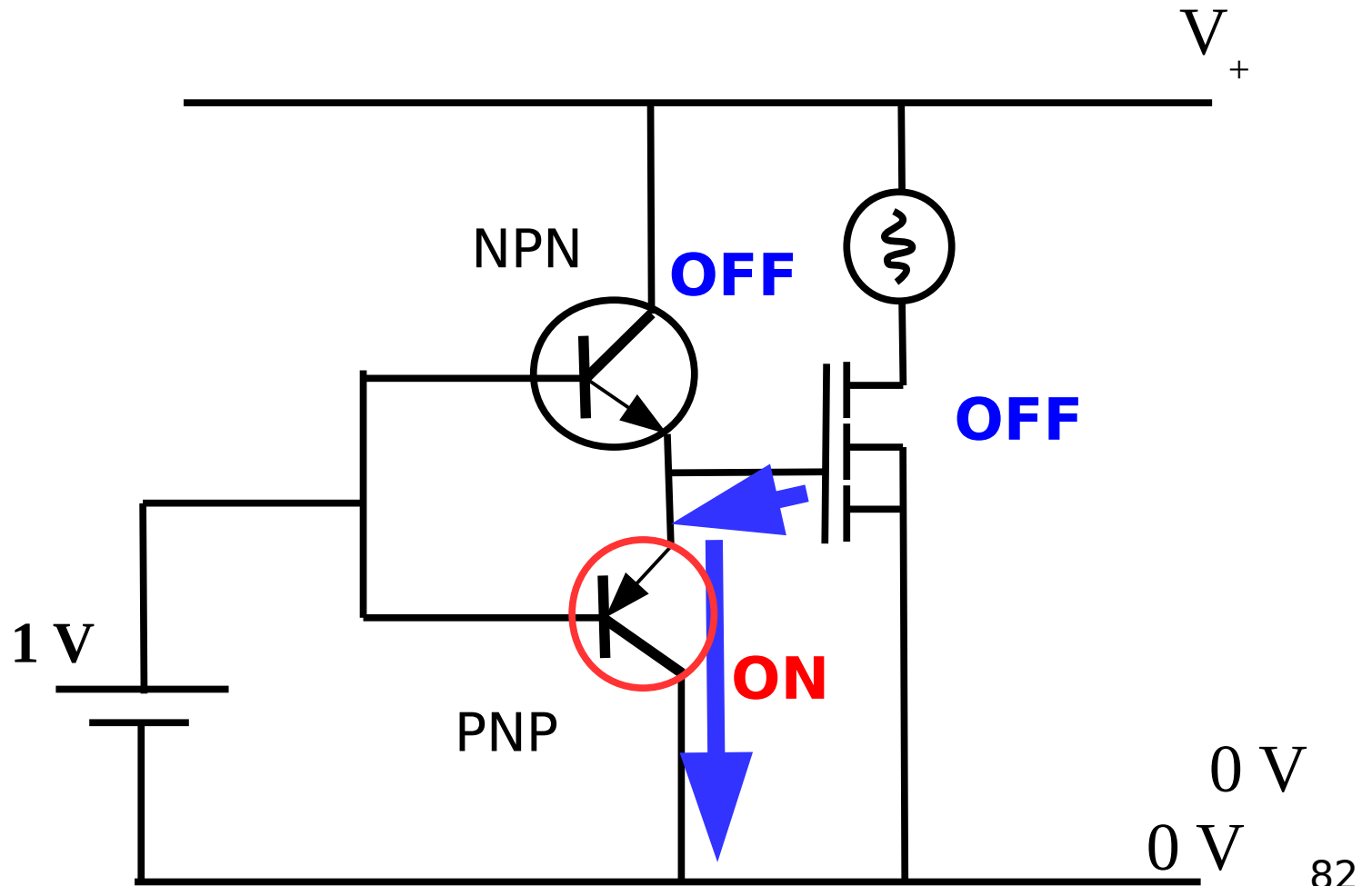
# Push pull pair - turning the MOSFET OFF


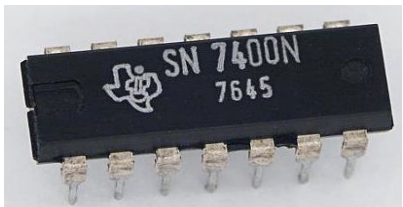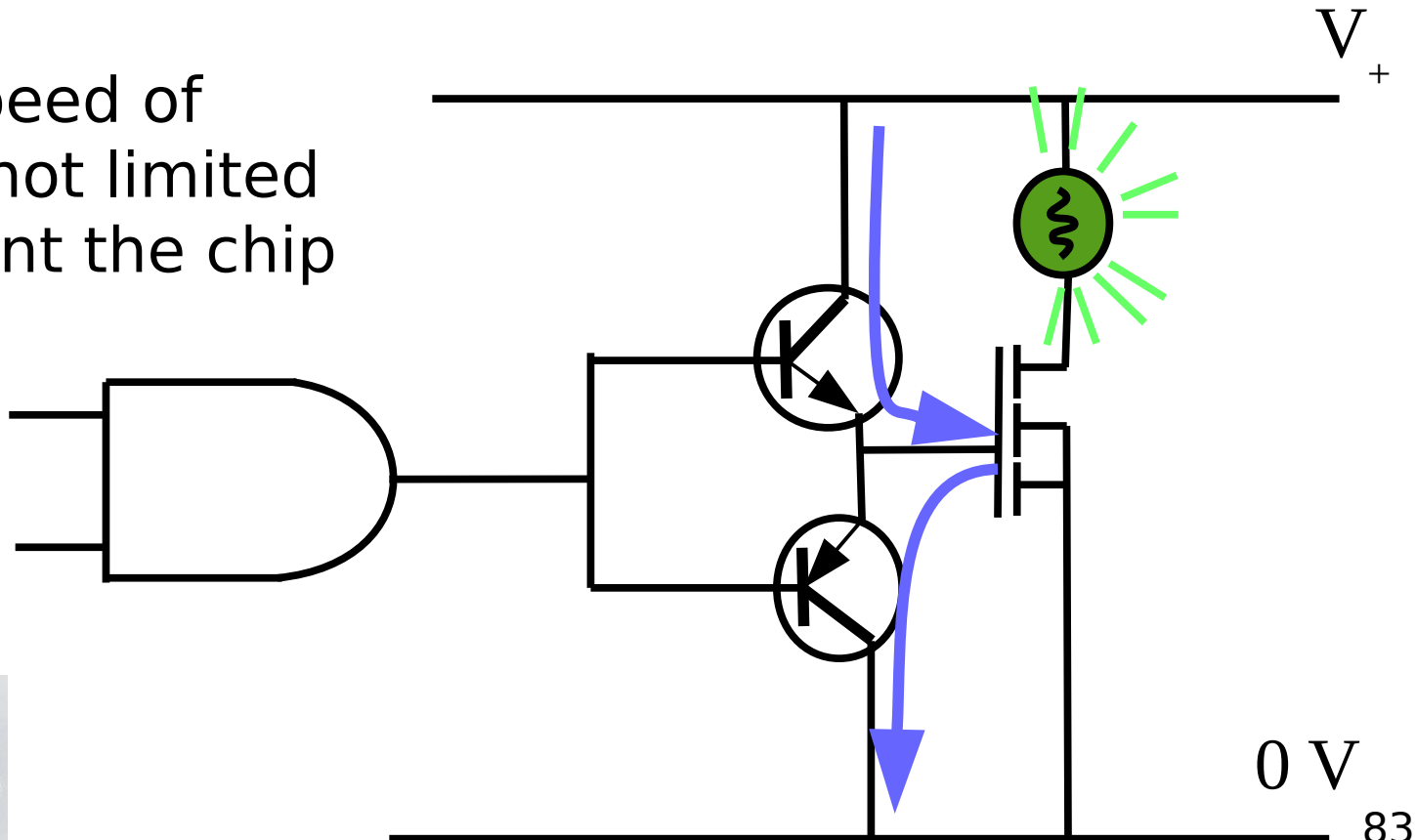
## Notice...


- The current to charge and discharge our MOSFET does not come from the chip it comes directly from the power supply.

- Thus the speed of charging is not limited by the current the chip can supply.



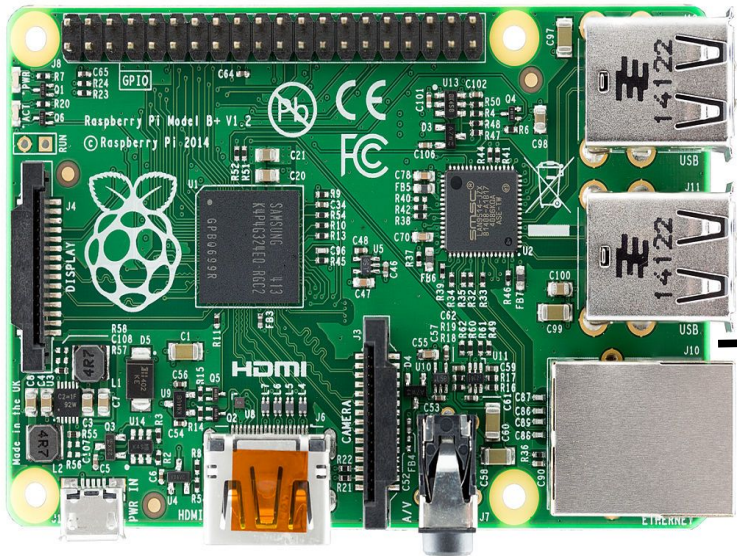
# Push-pull pair

- This now means that we can now use any digital circuit such as a microcomputer to turn of big loads such as a motor **FAST**.



Lucasbosch

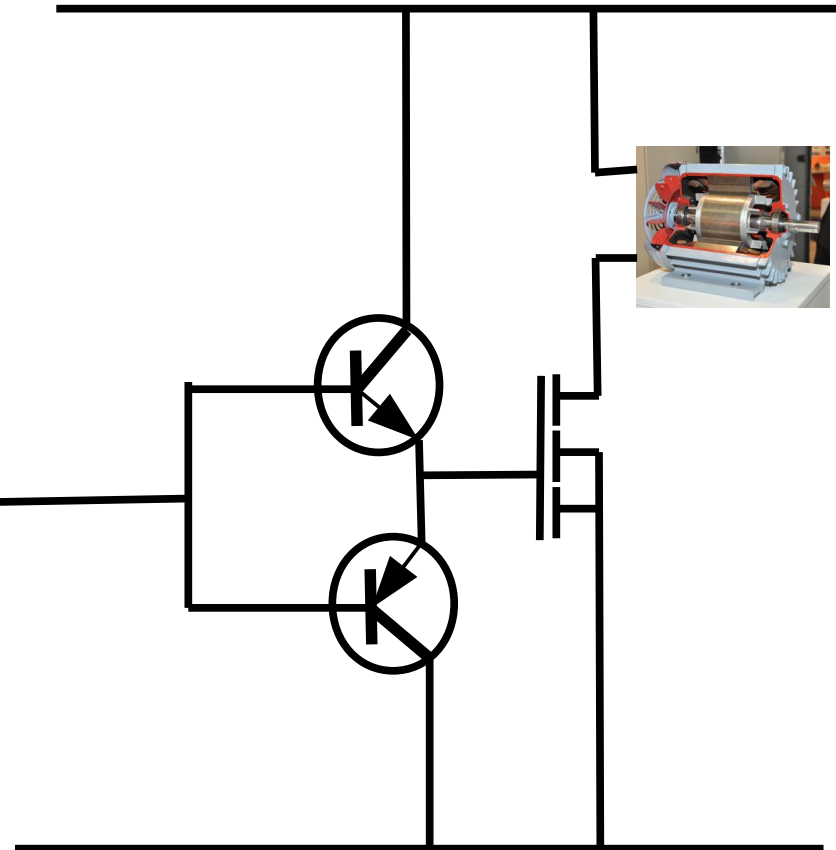



# Outline of the lecture

- No recap of last lecture :)
- Transistor basics
  - Relays (Mechanical transistor)
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- **One last thing**
- Summary



# Outline of the lecture

- No recap of last lecture :)
- Transistor basics
  - Relays (Mechanical transistor)
  - NPN Bipolar Junction Transistors
  - PNP Bipolar Junction Transistors
  - MOSFETs
- Push pull pairs to drive MOSFETs
- **One last thing**
- **Summary**